

**NEW IMPROVED**

APRIL 1984 85p

**SOR**

AUSTRALIA  
HOLLAND  
NEW ZEALAND \$2.20  
NORTH AMERICA \$2.95  
D71699

# Radio & Electronics World

The communications, electronics & computers magazine

**Simply  
the  
Best**

**ONE NIGHTS WORK -  
A USEFUL IF OSCILLATOR  
FOR RX ALIGNMENT**

**CONSTRUCTING A 200 WATT  
LINEAR AMPLIFIER**

**UPGRADE THE BEEB  
COMPUTER FOR SPEECH**


**EASY TO BUILD KEYER**

**BUILDING A 2 METRE ANTENNA -  
THE 9dB PLUS 'TIGER'**

**THE HALL EFFECT AND  
DEVICES THAT UTILISE IT**

**PAGES OF SURPLUS  
GEAR FOR SALE**

**EXTRA  
PAGES**

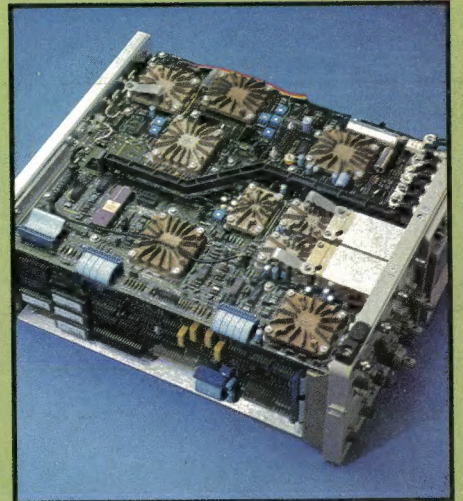

**FOR MORE  
SUCCESSFUL PRACTICAL  
AMATEUR RADIO**



# AMTRONICS (TONBRIDGE) G4 SYZ

## THE AMATEUR RADIO SPECIALISTS IN KENT

CLOSED MONDAYS: 9 TO 5.30 TUES TO SAT



### FDK

750XX.....	£329.00
725X .....	£219.00
70cm EXP.....	£249.00

### FORTOP <sup>A</sup><sub>T</sub><sub>V</sub>

Converter.....	£26.95
70cm TX.....	£149.00
70cm TX/RX.....	£169.00
24cm TX.....	£199.00

### B.N.O.S.

1-100 Linear..	£172.50
3-100 Linear..	£172.50
10-100 Linear..	£149.50
25 amp PSU ....	£125.45

### ADONIS

Safety Mic .....	£39.95
Safety Mic .....	£26.50
503 Mic .....	£42.50
303 Mic .....	£29.00

FT690R Multimode Transceiver 6m.....	£249.00
FT290R Multimode Transceiver 2m.....	£269.00
FT790R Multimode Transceiver 70cm.....	£249.00
SMC 2.2C 2.2Ah Nicads 'C' size, per set.....	£21.60
SMC 8C 220mA Charger (13A Style).....	£8.80
MMB11 Mobile mount.....	£26.85
CSC1A Carrying case.....	£4.20
FL2010 2m 10w Amplifier.....	£63.25
FL7010 70cm 10w Amplifier.....	£91.00
FT203R New 2m Handy.....	£169.00
FT230R 2m Transceiver 25w.....	£259.00
FT730R 70cm Transceiver 10w.....	£229.00
FT208R 2m Handheld 2.5w.....	£199.00
FT708R 70cm Handheld 1w.....	£179.00
SMC8.9AA Compact charger (13A Style).....	£8.05
NC7 Base charger.....	£32.95
NC8 Base quick charger & psu.....	£54.05
PA3 DC Adaptor and charger.....	£15.35
FT77 8 Band RX/TX 100w output.....	£459.00
FT77S 8 Band RX/TX output.....	£425.00
FP700 Matching AC PSU.....	£135.00
FC700 Matching Antenna Tuner.....	£98.90
FV700DM Digital VFD Unit.....	£200.00
MKT77 Marker Unit.....	£10.35
FMUT77 FM Unit.....	£27.20

package deal  
FT790R +  
FL7010 amp  
bought together  
**£299.00 inc**

FT57GX All Modes and Filters Fitted.....	£685.00
FP757 GX Switched Model PSU.....	50% duty £149.40
FP757HD Heavy Duty PSU.....	100% duty £162.50
FC757AT Automatic Antenna tuner.....	£231.50

### JAYBEAM — Full range in stock

5XY/2m 7.8DB	MBM 28 70cm 11-5DB	LW 5 2m 7.8DB
8XY/2m 9.5DB	MBM 48 70cm 14.00DB	LW 8 2m 9.5DB
10XY/2m 10.8DB	MBM 88 70cm 16.30DB	LW10 2m 10.5 DB
		LW16 2m 13.4DB

Phasing Harness	C5 Colinear 2m 4.8 DB
PMH 2/2m 2 way 2v	LR1 Colinear 2m 4.3 DB
PMH 4/2m 4 way	UGP/2m Ground Plane 0-0DB
PMH 2/70cm 2 way	C8 70cm Colinear 6-1 DB
PMH 4/70cm 4 way	

**ALSO:** Poles, Masts, Rotors, Brackets  
Clamps, Plugs, Sockets, Cable,  
Tape etc in stock.

### WE ALSO SELL:

Met: Welz: KDK: Azden: Drae: Datong: Diamond:  
Sagant: Amtron kits: DK Tronics ZX software.

SEND LARGE SAE for details on any of the above  
equipment.



**INSTANT CREDIT AT VERY COMPETITIVE RATES FOR THAT  
NEW RIG CAN BE AVAILABLE TO YOU. ASK FOR DETAILS  
WHEN YOU CALL OR WRITE FOR A QUOTE.**



## SPECIAL OFFERS

**YAMATO ROTATOR** takes up to 8 element 2  
metre beam. Uses 3 core cable, in line and  
neat controller ..... **£40.00**

**ALINCO EMR 400 ROTATOR** similar spec to  
KR400. Takes large 2 metre beam etc.  
**£79.00**, lower bracket ..... **£14.00**

**GLOBAL MINI CLOCK** Rotate the  
Globe: London and Country zone time.  
Special price ..... **£45.00**

### FAST MAIL ORDER:

Access, Visa, Postal Order or Cheque.  
Instant HP with Call sign for callers at the  
shop.



**8 TOLLGATE BUILDINGS, HADLOW RD, TONBRIDGE.**

**TEL: (0732) 361850**



# Radio & Electronics

The communications, electronics & computers magazine

## World

## CONTENTS

### DESIGNS

- 16 **One Night's Work** – A useful little IF oscillator
- 19 **HF Linear Amplifier** – A 200W amplifier that will provide excellent linearity
- 55 **The Piano Keyer** – For around a fiver you too can play perfect Morse
- 61 **Data Brief** – The TDA 2002A, one of the great standards in linear ICs
- 64 **A Peak-Reading LED RF Wattmeter** – A useful addition to your test gear
- 66 **Speech and the Computer** – Making the Beeb computer talk
- 74 **A 2 metre Tiger Antenna** – A 6-element Yagi costing under ten pounds

### FEATURES

- 27 **Hall Effect Devices** – Exploiting magnetisms' effect on conductors
- 37 **Data File** – CMOS bilateral switches and multiplexer/demultiplexer ICs

### REGULAR FEATURES

- 4 **Product News**
- 12 **News**
- 34 **Amateur Radio World**
- 49 **Latest Literature**
- 63 **Notes from the Past**
- 69 **Contact Point**
- 72 **Back Issues Order Form**
- 80 **DX-TV Reports**
- 82 **Newsagents Order Form**
- 83 **Dates for your Diary**
- 84 **Short Wave News**
- 87 **Letters to the Editor**
- 88 **ATV on the Air**
- 89 **Corrections and Mods**
- 90 **Next Month in R&EW**
- 92 **Subscription Order Form**
- 93 **Club News**
- 96 **Free Readers Small Ads**
- 100 **Small Ads**
- 102 **Advertisers Index**
- 102 **Advertising Rates and Information**

Editor ..... DENNISH HAYES

Advertisement Sales

A-O ..... ANNE BRADY  
P-Z ..... NICOLA DYER

Subscriptions ..... 01-684 3157

Accounts ..... CLARE BRINKMAN

Publisher ..... PETER WILLIAMS  
General Manager ..... ALAN GOLBOURN

ON SALE: Second Friday of the month preceding cover date

NEXT ISSUE: Cover date May 1984 on sale 13 April 1984

PUBLISHED BY: Radio & Electronics World Magazines, Sovereign House, Brentwood, Essex CM14 4SE, England (0277) 219876

PRINTED: In England

ISSN: 0262-2572



NEWS TRADE SALES BY: Seymour Press Ltd, 334 Brixton Road, London SW9 7AG Tel: 01-733 4444

### SAFETY IN THE SHACK

Some of the constructional projects described in **R&EW** and other magazines refer to additions or modifications to television receivers, communication equipment and other items that may be under guarantee by the manufacturer. Please remember that any alterations or addition to the circuit may invalidate the guarantee.

We prefer that each constructional project contains its own power supply or battery. A constructional project will occasionally describe how the power supplies of any equipment may be used to supply the circuit of that project. In these circumstances, please ensure that the power unit in the equipment is adequate to provide the additional load current that will be necessary and, in all cases, check that the equipment mains fuse is correctly rated to protect the apparatus from damage.

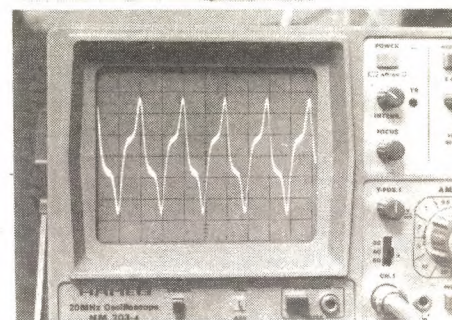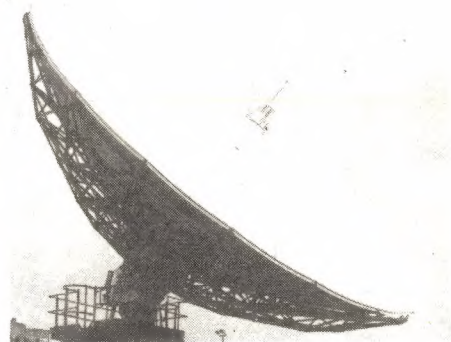Safety in the shack, please, at all times. Use good practice in your constructional work as we want you to be around to enjoy **R&EW** in the future! Thank you for reading this caution, now go ahead and build one of your projects



1 Top left – Valves (MO Valve Co) 2 Top right – Spectrum analyser (Tektronix) 3 Antenna (Ant Products) 4 D/T Oscilloscope (Bridge Scientific Inst) 5 CSO 4 Amplifier (Nore Microwave)

Whilst every care is taken when accepting advertisements we cannot accept responsibility for unsatisfactory transactions. We will, however, thoroughly investigate any complaints.

The views expressed by contributors are not necessarily those of the publishers.

Every care is also taken to ensure that the contents of **Radio & Electronics World** are accurate, we assume no responsibility for any effect from errors or omissions.

Audit Bureau of Circulations  
membership approved pending first audit  
© Copyright 1984  
Radio & Electronics World Magazines



# PRODUCT NEWS

Featured on these pages are details of the latest products in communications, electronics and computers. Manufacturers, distributors and dealers are invited to supply information on new products for inclusion in Product News. Readers, don't forget to mention **Radio & Electronics World** when making enquiries

## BRITISH MADE FREQUENCY COUNTERS

The competitively priced Meteor Series of Frequency Counters, designed and manufactured in Britain by Black Star, is now available fitted with a Temperature Compensated Crystal Oscillator (TCXO) for extra accuracy and temperature stability.

The Meteor 1000X which measures typically from 2Hz to 1.2GHz, with <50mV sensitivity at 1GHz, features a temperature stability of  $\pm 0.5\text{ppm}$  from  $-10^\circ\text{C}$  to  $+40^\circ\text{C}$ , an aging rate of  $\pm 1\text{ppm}$  per year, and setability of  $< \pm 0.2\text{ppm}$ .

The other models in the range, the Meteor 100X (2Hz-100MHz) and the Meteor 600X (2Hz-600MHz) are available with the same TCXO. All models are battery or mains powered and are fitted with a Trigger Level Control, a Low Pass Filter and offer three Gate Times (0.1 sec, 1 sec and 10 sec).

The Meteor 'X' series of Counters are complete with mains adaptor/charger, a comprehensive instruction manual, and a year's guarantee.

A wide range of optional accessories is available.

**Black Star Limited,**  
9A Crown Street, St Ives,  
Huntingdon, Cambs. PE17  
4EB. Tel: (0480) 62440.

## IC SOCKETS

Thomas & Betts Ltd, announces a new range of IC sockets designed especially for laboratory and small prototype series use. Known as the CDF 400 series, the new sockets are available with 6 to 64 contacts and are designed so that they can be soldered above and below the PCB allowing their use with double-sided printed circuits that

have no through-plated holes. Also the cut-away moulded frame allows test probe access from both sides of the PCB. The contact material is brass plated gold on nickel.

**Thomas & Betts Limited,**  
Sedgwick Road, Luton, Beds.  
LU4 9DT. Tel: 0582 597271.

## PROM REMOVAL TOOL

A new tool manufactured by the Swedish Company Owoco AB, who are already well known for the quality DIP-IN range of IC Inserters, is announced.

The PROM-OUT makes light work of removing 24 and 40 pin ICs from Proms fitted in sockets (as distinct from soldered to the PC board). Structural damage to the PC board or IC is avoided by the design of the PROM-OUT. The force is restricted to the top of the base of the socket avoiding damage by pressure to the board and IC.

Two models are available ex stock, No. 2428 PROM-OUT for 24 and 28 Pin IC and No. 3640 PROM-OUT for 36 and 40 Pin IC.

**Welwyn Tool Co. Ltd,** 4 Black Fan Road, Welwyn Garden City, Herts. AL7 1EH. Tel: (07073) 31111.



sions to be displayed.


The BBC computer was chosen because of the high level of ownership in ham radio and short wave circles and the new unit is complete with software.

Many transmissions can be copied from all over the world using this system which has facility within the software to receive pictures from both 50Hz and 60Hz countries.

The rear of the hardware has a 20pin IDC connector which mates directly with the BBC computers I/O port. This cable carries all digital and power rails to and from the computer. The tape containing the program also has SSTV video pictures and test signals recorded on the reverse side. This facilitates setting up the converter as well as allowing the owner to become familiar in using the equipment.

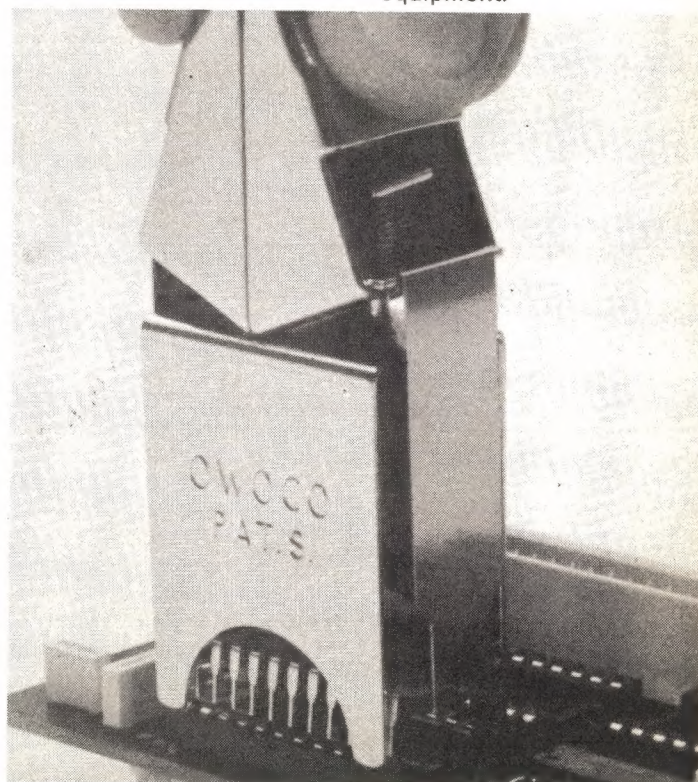
## SLOW SCAN TV

There is now a great interest in ham radio circles towards the reception of Slow Scan Television using computers and G3LIV and G8VEE have jointly designed a new add-on for the BBC computer which allows reception of ham radio video transmis-





# SPRING HAS SPRUNG!

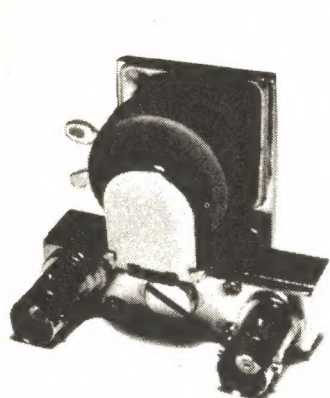

Ambit's Spring '84 catalogue brings all the parts you need for electronics, radio, audio and computing to your front door.



There's details about an exciting new range of kits and modules being launched into the UK in conjunction with the leading German hobby supplier; full information on our two new regional sales counters in Portsmouth and Broxbourne; new low cost instruments from Black Star - plus all your old favourites:

NiCads, chargers, TOKO coils, filters, and communications ICs, crystal filters, Audio and RF semiconductors - including the biggest range of low cost varicap diodes for all types of electronic tuning.



Available from all good newsagents, or direct from ambit  
Order as Stock Number:  
02-00009

More than ever, Ambit's concise 'price on the page' Spring catalogue is the one that you cannot afford to be without. It's fully indexed, precise and up to the minute - get a copy now!

We operate a fully on-line telesales service between 9am and 5.30pm (Visa, Access, Amex)



# ambit international

all mail order to:

200 North Service Road, Brentwood, Essex  
telephone (0277) 230909

Sales counters at:


Park Lane, Broxbourne, Herts  
Burrfields Road, Portsmouth





# HART

## 'PRINTER BARGAIN'

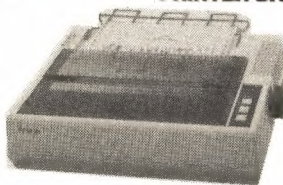

EPSON RX80F/T. Very latest Model with Friction and Tractor feed to take plain or sprocketed paper up to 10" wide. 100 cps, 9x9 Matrix. Bi-Directional. Logic Seeking. Prints normal, Italic, condensed and double width characters, dot addressable graphics capability. Centronics parallel standard input, connects straight to the BBC 'B' and many other computers. Other printers and a wide range of interfaces for other machines is available, see our lists.

OUR PRICE ONLY £274

RX80 as above but Tractor feed only £244 Both Plus Vat. Carr £7

## SOLENOID CONTROLLED HI FI/DIGITAL CASSETTE MECHANISM



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

## LINSLEY-HOOD 100 WATT POWER AMPLIFIER

Our complete kit for this brilliant new design is the same size as our Linsley-Hood Cassette Recorded 2. Kit includes all parts for two power amplifiers with large heatsink area, huge power supply and speaker protection circuit. Total cost of all parts is £114.46 but our special introductory price for all parts bought together is only £105.50.

### DOLBY 'B' NOISE REDUCTION IC LM1011

Marvellous opportunity for home experimenters, build your own noise reduction system. Supplied complete with circuit showing typical application. **Absolute knockout price only £3.50 for two inc. VAT and post**

### COMPLETE STEREO CASSETTE DECK

Brand new high quality top-loading Cassette Deck complete with Record/Play electronics. Supplied with connection data and circuit diagram. Automatic chrome/ferric switching. Only needs 9v DC supply. **Total price only £18.34 inc. VAT and post**

### COMPLETE STEREO TUNER MODULE

Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. **Price only £7.99 inc. VAT and post.**


### HALF HEIGHT 5 1/4" FLOPPY DISK

Incredible Offer on latest MPU controlled 80 Track Drives, 100% compatible with BBC Micro. Support single or double density according to control chip in use. Fully compatible with Teac, Shugart and many other full and half height drives.

80 Track, Single Side £179

80 Track, Double Side £225

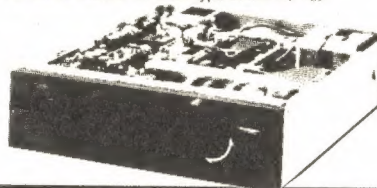full works Manual for each type £14.50 No Vat.



## HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

**HC20 Permalloy Stereo Head.** This is the standard head fitted as original equipment on most decks. £4.25

**HM90 High Beta Permalloy Head.** A hard-wearing, higher performance head with metal capability. £6.20

**HS16 Sandust Alloy Super Head.** The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response. £3.20

**HQ551 4-Track Head** for auto-reverse or quadrophonic use. Full specification record and playback head. £7.40

Please consult our list for technical data on these and other Special Purpose Heads.

## HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £3.80 plus VAT and 50p postage.

**Tape Head De-magnetiser.** Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback. £3.68

Full details of the entire range of HART products is contained in our illustrated lists.

Ask for your FREE copy NOW.

Enquiries for lists are also welcome from overseas but please let us have three IRCs to cover the cost of surface post or 5 IRCs for airmail.

In a hurry? A telephone order with credit card number placed before 3pm will be despatched THAT DAY!

Please add part cost of post, packing and insurance as follows:

**INLAND**  
Orders up to £10 — 50p  
Orders £10 to £49 — £1  
Orders over £50 — £1.50

**OVERSEAS**  
Postage at cost plus £2  
documentation and handling

**PLEASE ADD VAT TO ALL PRICES**

Please Note: New Phone Number: (0691) 652894  
Personal callers are always very welcome but please note that we are closed all day Saturday

**HART**  
ELECTRONIC KITS LTD  
PENYLAN MILL  
OSWESTRY, SHROPSHIRE  
SY10 9AF

# SPRING SALE!

## DIGITAL MULTIMETER KITS

These 3 1/2 digit handheld DMM's are fully complete with all components (except PP3 battery) and test leads. We are using up all stocks of the DP2010K prior to launch of a new range of meters. The Kits will be sold on a 'first come first served' basis, and are fully guaranteed. A trouble-shooting and calibration service will be maintained. This is a once-only opportunity to make a DMM at an incredibly low price. Supplied with a comprehensive description of operation and full constructional data. After selling over three thousand kits in the last 4 months we now have only 500 left — so hurry.


### TYPICAL SPECIFICATION

Function	PSD	Accuracy	Function	FSD	Accuracy
Volts (d.c.)	2V	1.5% ±1 digit	Current (a.c.)	2mA	2% ±5 digit
	20V			20mA	2% ±5 digit
	200V			200mA	4% ±5 digit
	500V			2000mA	12% ±5 digit
Current (d.c.)	2mA	1% ±1 digit	Resistance	2k	1% ±1 digit
	20mA	1% ±1 digit		20k	1% ±1 digit
	200mA	3% ±1 digit		200k	1% ±1 digit
	2000mA	10% ±1 digit		2000k	1% ±1 digit
Volts (a.c.)	2V	2% ±5 digit	Diode Test	2V	1% ±1 digit
	20V				
	200V				
	500V				

Please allow 28 days for delivery.

**LASCAR ELECTRONICS LIMITED**  
Module House, Whiteparish, Salisbury, Wilts. Tel. 07948-567

ONLY  
**£9.95 ea**  
PLUS P&P  
& VAT

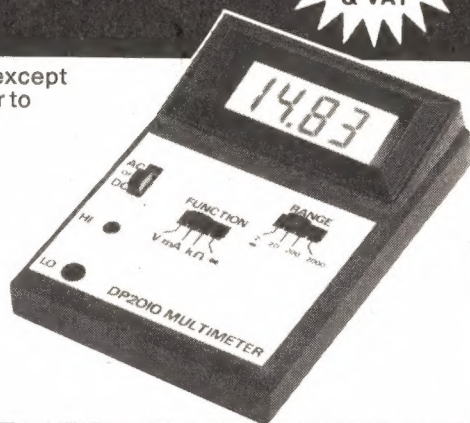

**LASCAR ELECTRONICS LIMITED**  
Module House, Whiteparish, Salisbury, Wilts.  
Tel. 07948-567

PLEASE SEND ME.....kits at £12.59 each

I enclose cheque/P.O./Access no. ....

Amount .....

NAME .....

ADDRESS .....

.....

Export Orders please add £5 for airmail despatch.



## PRODUCT NEWS

Until this unit was designed SSTV was only possible with the use of very expensive scan converters costing many hundreds of pounds, or by using the old fashioned long persistence crt design.

Please send sae for information.

*John Melvin (G3LIV), 2 Sallerters Court, Gosforth, Newcastle, Tyne & Wear. Tel: 0632 843028.*

### COMPACT POWER SUPPLIES

A new range of modular mains switching power supplies from Gresham Powerdyne Ltd are available in output levels up to 500W, but are unusually compact and extremely efficient for their size. The range includes multiple output types. They employ direct-off-line switching techniques to reduce physical dimensions to a minimum and keep efficiencies around 70%. At each of the output power levels, 50, 100, 200, 300 and 500W, the units are available with various combinations of output voltage (5, 12, 15, 24V) and equivalent maximum current ratings.

The two triple output versions provide a principal 5V rail (either 20 or 60 amps), with two further secondary outputs of either 12 or 15V. Units are tested to 2.5kV isolation between input and output and comply with both BS800 and VDE0875. Output voltages are adjustable to  $\pm 5\%$  of nominal by means of screwdriver adjustments on the front panel. Facilities are also provided for local or remote sensing and for voltage programming by means of an externally connected resistor. All units are provided with constant current protection against overloads or short circuits, also with overvoltage protection by means of automatic control circuit shut-down. For single output models, voltage regulation is better than 0.1% for a worst case combination of 0-100% load change and a  $\pm 10\%$  line change within the rated input voltage. Ripple and noise is better than 10mV rms in all cases and operating temperature coefficient is less than 0.01%/°C. Over voltage protection is standard on all units.

*Gresham Powerdyne Ltd. Tel: (025672) 4246/7/8.*

### OPTICAL ENCODERS

Litton Precision Products has introduced a new family of rotary shaft optical encoders, the G61S and G61M family, which features a frequency range of 0 to 100kHz, a long life LED light source, supply voltage requirements of 5V and 8-15V and operating temperature range of 0 to 70°C.

With optional radial or axial cable output, these devices can easily be fitted to a shaft in place of an existing potentiometer to give a digital instead of an analogue output signal. Variants within the range include the TL (TTL - compatible) OC (open collector), PP (push-pull), PS (push-pull with short circuit

protection) and LD (line driver). The G61 series is a family of low-cost encoders with up to 1024 lines.

Applications include digital control motors in computer peripherals such as printers, control of tensile testing machines and cut-to-length machines.

G61M models are supplied as a 'kit' for OEM applications. However, Litton offer a fitting service and will fit these encoders on to customers' shafts for them.

The G61S models are supplied complete with housing.

A hand-operated dial with mechanical indent is an option available for both models and has been designed specifically for applications

where operator hand control of, say, CNC machines is required.

An additional feature of these encoders is that two output channels are provided so that both clockwise and anti-clockwise direction of rotation can be sensed.

*Litton Precision Products International Inc, 95 High Street, Slough, Berks. SL1 1DH. Tel: 0753 77788.*

### SOCKETS & TERMINAL STRIPS

Robinson Nugent Ltd, announces a new range of strip sockets and mating terminal strips. Known as the SBQ series, the sockets are for .025in square terminals, feature beryllium copper contacts and are ideal for mother-/daughter module connectors.

The WTS .025in square terminal strips are for use with the new SBQ sockets. Standard size is 36-pin with notching to break for desired size. Mounting is straight or right angle.

*Robinson Nugent Ltd, 74 London Road, Riverhead, Sevenoaks, Kent. Tel: (0732) 460033.*


### INSTRUMENT KNOBS

The Mentor range of top-quality instrument knobs, supplied by West Hyde, has now been extended to include three new products.

The first is a series of plastic collet knobs, featuring a raised, knurled band to ensure a slip-free grip and is available in black or grey in seven sizes from 10 to 50mm diameter. Collet knobs are now available with a black anodised finish in addition to the original silver version. They are machined from aluminium alloy and are suitable for use under the most arduous conditions. Both colours are available in seven sizes from 9 to 36mm diameter. These can be fitted with caps, dials, pointers and other accessories from the existing wide range.

Where a variety of accessories is unnecessary, an 'Economy Series' knob is available at low cost in a matt, textured black or grey finish.

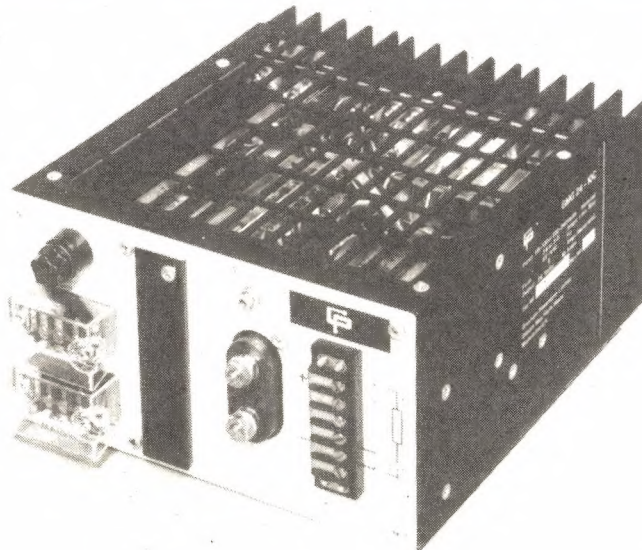Four sizes from 12 to 28mm diameter can be supplied, with or without a nut cover. Caps in three colours with an



### LOW NOISE GaAs FET

The Mitsubishi MGF 1404 is a super-low noise GaAs FET with a N-channel Schottky gate which is designed for use in S to Ku band amplifiers. Its hermetically-sealed metal-ceramic package assures minimum parasitic losses and has a configuration suitable for microstrip circuits.

Features include typical high maximum frequency of oscillation of 90 GHz, noise figure of 1.6dB at 12GHz, and a gain of 10.5dB at 12GHz.

*Aspen Electronics Limited, 2 Kildare Close, Eastcote, Ruislip, Middlesex HA4 9UR. Tel: 01-868 1188.*

### MINIATURE VCO'S

New ADE products from Nore Microwave include four voltage-controlled oscillators which cover the frequency range 0.1 to 1.6 GHz

and have individual bandwidths of 0.1-0.2, 0.2-0.4, 0.4-0.9 and 0.9-1.6GHz.

Featuring low noise and highly stable operation with good linearity, each of the units has an output power of +10 dBm x dB (in 50ohms), the fm noise (@50KHz) is -70dBc, harmonics - 15dBc and its control voltage range is 0 to +10 volts. The frequency drift related to variations in supply voltage, temperature and VSWR is 1MHz/V, 150KHz/°C and 1MHz (VSWR 2:1). The units operate with power supplies of +15 V and are ideal for use in applications where space is restricted, the overall case dimensions (in millimetres) of each device being only 24.5 x 12.5 x 9.0 (excluding terminations).


*Nore Microwave Limited, 56 Towerfield Road, Shoeburyness, Essex. SS3 9SH.*


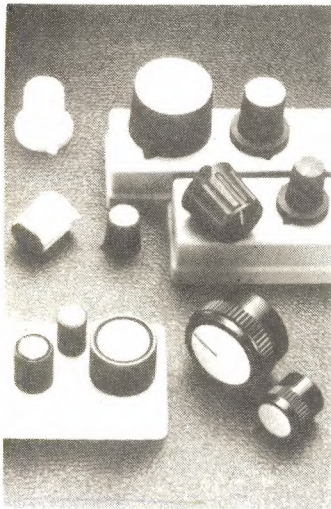
## PRODUCT NEWS

optional indicator line are also available to fit these knobs.

Knobs can be chosen to suit a wide variety of spindle sizes and feature a precision brass collet which ensures the maximum grip on the spindle.



West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks. HP20 1ET. Tel: Aylesbury (0296) 20441.

### WEIR SMM 100S POWER SUPPLIES

The Weir Electronics SMM 100S switched-mode power supply units are the latest in the SMM series to receive British Telecom approval to TG2 and TG26 specifications. This approval allows the use of these oem units in equipment which is connected to BT voice or data networks.

SMM 100S series are compact, high-efficiency, switched-mode power supply units, capable of delivering up to 100 W continuous power output. They are multi-rail units with output voltages particularly suitable for micro-computers, intelligent terminals, disc drives, tape-cartridge units, modems and other equipment employing TTL and CMOS technology.

This type of equipment is frequently connected directly or indirectly to BT lines, so that power supply approval is an important factor. SMM 100S power supplies are also designed to meet all relevant BS, IEC, VDE and ECMA safety requirements.

Basic models of the range combine a 5V, 10-amp main output with 12V 3-amp and 12V 1-amp outputs and a 5V 1-amp negative bias rail. The 12V 3-amp output can provide surge

currents up to 5 amps for DC motor starting. Five-output variants of these models include either an additional 12V or 24V output with peak current capability up to 2 amps.

WEIR ELECTRONICS LTD,  
Durban Road, BOGNOR  
REGIS, Sussex, PO22 9RW.  
Tel: (0243) 865991.

### EUROCARD DC/DC CONVERTER

For systems designers the versatility of a plug-in DC/DC converter for standard Eurorack offers ease and simplicity of use. Available from Powerline the SW range of single output PWM switchmode converters is manufactured in Europe by Fabrimex.

The range includes 9 models with output powers of between 25W and 96W with guaranteed minimum efficiencies of 65% to 85% depending on model. Five output voltages of 5V, 12V, 15V, 24V and 48V are available with currents of between 12A for the 5V output and 2A for the 48V output.

With a wide input voltage range of 20V to 60V these units are suitable for many applications. No additional cooling or derating is required across the operating temperature range of 0-50°C.


All models feature short circuit and overvoltage protection, together with input/output isolation of 500V. TTL-compatible inhibit is standard and all outputs are adjustable by  $\pm 10\%$ .

The units are standard Eurocard size of 160mm by 100mm with two heights of either 24mm or 60mm.

Powerline Electronics Ltd, 5 Nimrod Way, Elgar Road, Reading, RG2 0EB. Tel: Reading (0734) 868567/9.
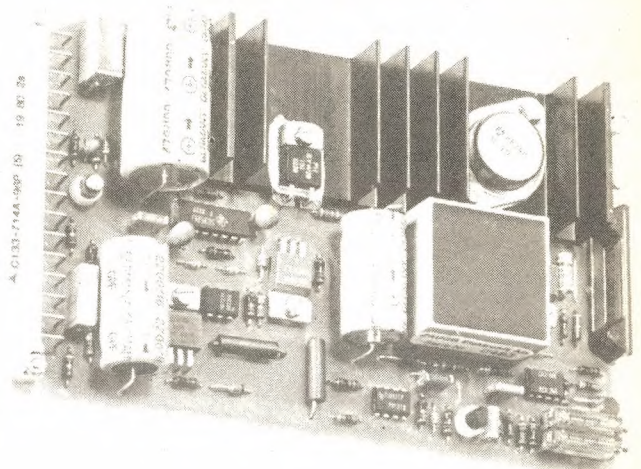
### A PRECISION ENGINEERED KEY

The Alpha Key is designed and engineered for the operator who wants only the best. Each is made and finished to a high standard. Two types are available - cast aluminium or cast iron. Both with a large base area for stability. The paddle is pivoted on ball bearings for a very smooth movement and when adjusted correctly there is no vertical movement. Both sets of contact points are silvered for good



electrical contact and long life.

For the return pulling power, polymer-bonded rear earth magnets are used. These offer a high power and good properties against demagnetization.

The Alpha Key has a very stable design that does not alter with temperature. The aluminium base is finished in black and a personalised base can be supplied with your own call sign on it. The cast iron base is a heavy base finished in black or chrome.

P Sergeant (G4 ONF), 6 Gurney Close, Costessey, Norwich, NR5 0HB. Tel: (0603) 747782.

### G2DYM SUPER-Q TRAPS

G2DYM SUPER-Q TRAPS are actually parallel coil-condenser combinations designed to resonate in the various Amateur bands. The condensers are 16kV ceramics completely epoxy-potted against moisture. Traps are wound with 1.5mm lacquered copper wire on threaded formers. Ratio of length to diameter plus low loss material results in Super-

Q Traps. Because of the high Q and impedance at resonance the traps act as effective insulators in the band in which they are resonant.


By adding three additional sets of traps resonant at 10-15 and 20 metres, it is possible to have a perfect dipole on each band. It is not necessary of course to use four sets of traps. For example, if you do not care to operate 10 metres, the DYM-10 traps may be left out and the centre section cut for 15 metres.

Another example: if operation on 80 is not required, insulators may be used in place of the DYM-40 traps, in which case the aerial will provide dipoles for 10-15-20 and 40 metres.

G2DYM Aerials, 'Cobharnden Castle', Upplowman, Nr Tiverton, Devon.
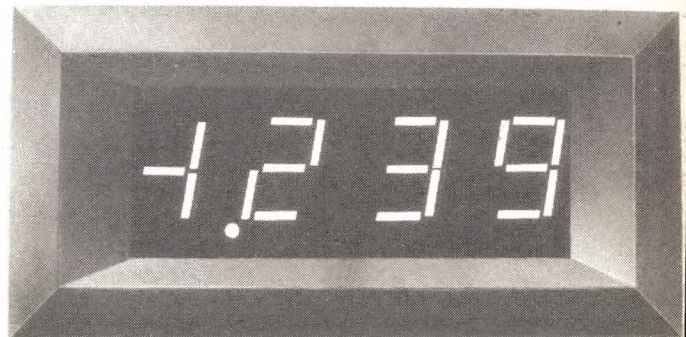
### LED DPM

A recently introduced LED DPM is claimed by its manufacturers to be the smallest available DPM with standard 11mm high efficiency digits. Auto-polarity, Auto-zero, 200mV fsd programmable





## PRODUCT NEWS

decimal points, polarised filter and a single 5V supply are all standard features. The meter can be used in single-ended, differential or 'floating' modes, and can be easily adjusted by the user to read volts, amps or other units.

The compact size and low-cost of the DPM40 makes it very suitable for high volume OEM applications such as bench power supplies and battery chargers.

*Lascar Electronics Limited, Module House, Whiteparish, Salisbury, Wiltshire, SP5 2SJ. Tel: Whiteparish (07948)567*

### INTERFACE FOR ZX81 AND SPECTRUM

Velleman are pleased to announce the introduction of their interface system consisting of a specific motherboard for each type of computer and interface cards that can be plugged onto the motherboards.

In this way, it is possible to add to each system the following features: K2609: eight (8) open collector outputs (25V/50mA), K2610: A/D conversion, 8 bit precision, 5.1V full scale, K2611: eight (8) optocoupler inputs, K2614: Centronics parallel printer interface, K2618: D/A conversion, 8 bit precision 1.02V full scale. Several other cards are also being developed.

The motherboards for the ZX81 and the ZX Spectrum are now available, both offering space for for interface cards. They are provided with a 23

pole edge connector at the back, giving the facility to connect the ZX printer or to stack more motherboards one after the other.

Power is taken from the computers' 9V DC supply or from an external unregulated 9-12V DC power supply, depending on the consumption and the number of interface cards that are used.

*Velleman (UK) Limited, P O Box 30, St. Leonards on Sea, East Sussex. TN37 7NL.*

*Tel: 0424 753246.*


### INTERCONNECTION SYSTEM

A full colour, 20-page catalogue is now available from BICC - Vero Electronics Ltd detailing their M50 flat cable interconnection system.

The catalogue provides full details on the fifteen connector types which go together to make the comprehensive M50 system, plus information on application tooling and data on both M50 and M50E flat cable.

Connector types within the range include sockets; fully shrouded, unshrouded and low profile headers; 'D' sub-miniature connectors; crimp sockets; transition connectors; DIP connectors; pcb-mounted plugs and associated sockets; plus card edge connectors.

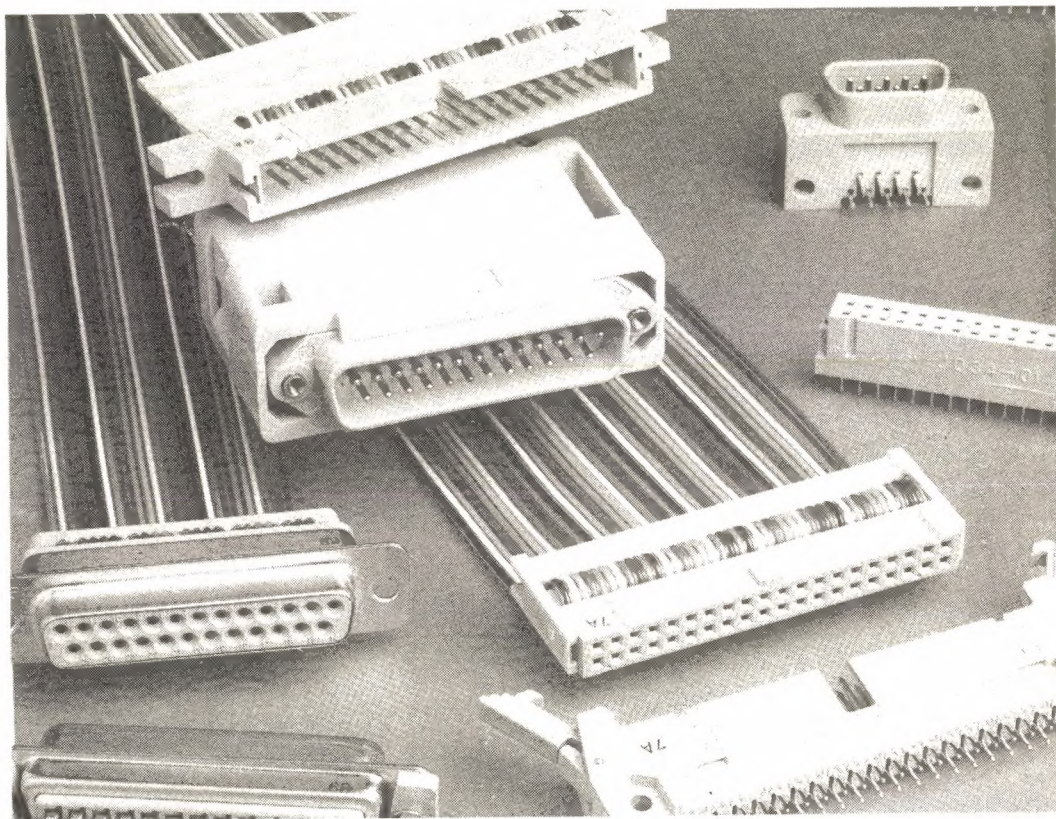*BICC-Vero Electronics Ltd., Hedge End Industrial Estate, Flanders Road, Hedge End, Southampton, SO3 3LG Tel: (04892) 81424/5.*





# We don't sell our sets until we know them inside

## The new IC-02E Push-button Perfection



ICOM introduces the new top-of-the-line IC-02E to compliment its existing line of popular handheld transceivers and accessories. The new direct entry microprocessor controlled IC-02E is a 2 meter handheld jam packed with excellent features.

Some of these features include: scanning, 10 memories, duplex offset storage in memory & odd offsets also stored in memory. Internal Lithium battery backup and repeater tone are of course included.

Keyboard entry is made through the 16 button pad allowing easy access to frequencies, duplex, memories, memory scan and priority. The IC-02E has an easy to read custom LCD readout indicating frequency, memory channel, signal strength, transmitter output and scanning functions.

A battery lock, frequency lock and lamp on/off switch are also featured, as is an aluminium case-back, providing superior heat sinking.

A variety of batteries will be available for the IC-02E, including new long-life 8.4 volt and 13.2 volt packs. Top panel connector for 13.8 volts which will power transceiver operation.

The IC-02E continues to be available, and its complete range of accessories work with the new IC-02E.

The IC-02E comes with the BP3 Nicad battery pack, BC25E wall charger, flexible antenna, wrist strap and belt clip as standard equipment. A truly excellent product destined to a great future.

We do not sell any sets until we know them inside out. A bold claim, but true. Our engineers have been trained by ICOM in Japan, and can guarantee the best after-sales maintenance service available.

As well as the 02E, 751, 745, 271, 471, R70, 290D, 490E, 25H, 45E, 2KL, AT100, AT500, 120, 2E, 4E in the ICOM range we also stock such famous names as Tono, Telereader, Cue Dee, Versatower, Yaesu, Jaybeam, Datong, Welz, G-Whip, Western TAL, Bearcat and RSGB Publications. Thanet Electronics can offer you the most comprehensive and thorough service.

**Thanet ICOM** **Thanet ICOM** **Thanet ICOM** **Thanet ICOM** **Thanet ICOM** **Thanet ICOM** **Thanet ICOM**



The IC745 is another superlative set in the ICOM range, see it in our retail shop at 95 Mortimer Street, Herne Bay Kent, or contact our Reculver Road address for more information. Your own local ICOM dealer will be able to help you too.

The price has not yet been announced but give us a call for this and other information.

Gordon G3LEQ Tel: Knutsford (0565) 4040

**net**  
**ICOM**

**Thanet**  
**ICOM**

**Thanet**  
**ICOM**

**Thanet**  
**ICOM**

**Thanet**  
**ICOM**

**Thanet**  
**ICOM**

**Electron**


143 Reculver Road, Herne  
Tel: (02273) 63859/6385

**BARCLAYCARD**  
**VISA**

  
See it with Xerox



# NEWS

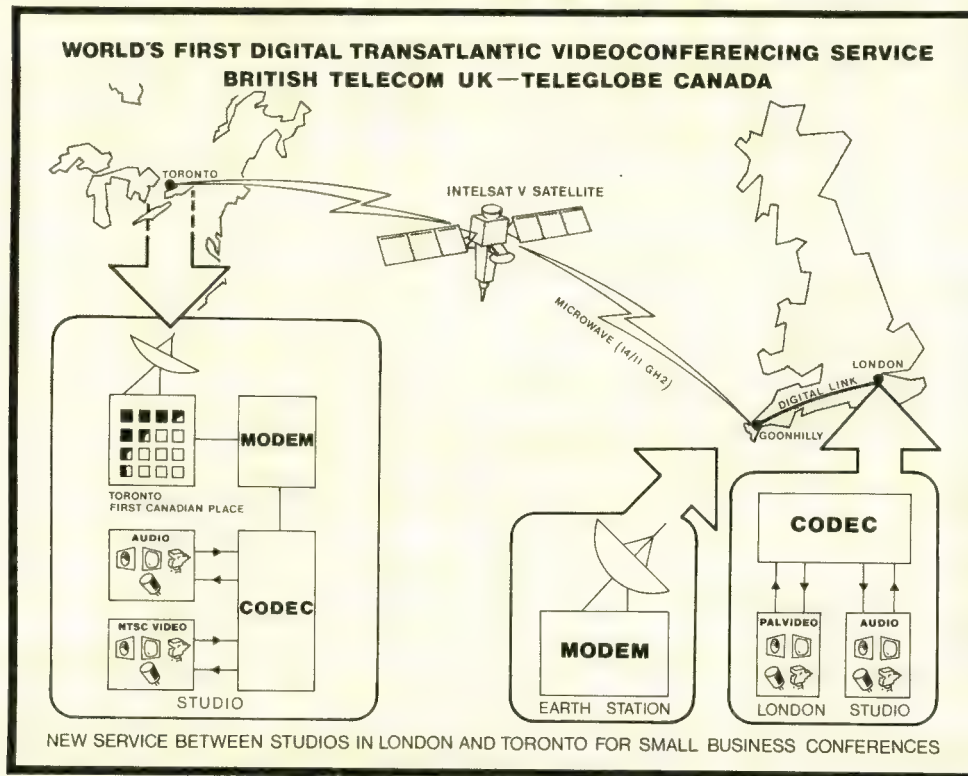

## First of its kind

A new generation of small dish aerials, with an improved performance that will enable more countries to use satellites for communications, has been successfully developed and brought into operation by British Telecom International

(BTI). It is the first of its kind in the world to go into commercial service.

It will soon be used to launch the world's first satellite based end-to-end digital transmission service across the Atlantic. To be called SatStream North America,

this service is now being set up by BTI and Teleglobe Canada.

The new aerial was developed jointly by BTI and British Telecom's research laboratories at Martlesham Heath, near Ipswich.

It has a 5.5m (18ft) diameter

dish and is known as an offset Gregorian antenna.

The first has been installed on the roof of a Telecom building in Ealing, West London.

It will work to an Atlantic Ocean Intelsat V Satellite.

## Plessey reorganisation

As part of a programme of major investment and the reorganisation of its manufacturing facilities for telephone exchange and related equipment, Plessey Telecommunications Limited has announced a rationalisation programme at five of its plants in the North of England.

At three factories, programmes to accelerate System X and to progressively introduce other new product ranges will take place. These sites are at Edge Lane, Liverpool; Chorley, Lancashire; and Huyton, Merseyside.

At South Shields, where some 600 people are employed, the manufacture of exchange equipment will cease by the end of August 1984. Plessey Circuits Limited, employing 290 people and producing printed circuit boards on the same site, will not be affected.

Plessey's Lamberhead, Wigan factory where 240 people are employed will close by May, 1984.

## The GIOTTO spacecraft

Further to all the information given about GIOTTO in last month's News columns of *R & EW* we now publish the following details from British Aerospace Dynamics Group:

### The Mission

GIOTTO is to be launched by an Ariane 1 from Kourou, French Guyana in the summer of 1985, to intercept Halley's Comet in March 1986, following an 8-month flight. Launch will take place in July 1985. Suitable conditions for the launch exist for 20 minutes or more every day during this period.

Following launch, GIOTTO will be released into an Earth geosynchronous transfer orbit. After a few revolutions in

this orbit, when near perigee, GIOTTO's solid-propellant motor will be ignited and the spacecraft will be propelled into a heliocentre trajectory towards Halley's Comet.

Interception will occur during the night of March 13/14, 1986, about one month after the comet's closest approach to the Sun. GIOTTO is being targeted to pass through the cometary atmosphere (coma) of Halley's Comet within 500km (310 miles) of its nucleus, on the sunward side. Allowing for orbital errors, GIOTTO is expected to penetrate within at least 2000km (1250 miles) of the nucleus.

During the critical final four-hour encounter, phase data will be relayed back to Earth in real time from the experiments carried on board GIOTTO. Completion of the mission occurs 15 minutes after GIOTTO has passed its closest point to the comet.

Ten experiments constitute the scientific payload of GIOTTO.

One of the sensors is a multicolour camera, which will obtain images of the comet's nucleus and the surrounding coma.

The other experiments are concerned with an examination of coma chemistry; analysis and the dynamics of the cometary plasma, and its interaction with the solar wind; and an investigation of mass, distribution and composition of the dust cloud associated with the comet.

GIOTTO will be controlled from the European Space Agency's Operations Centre at Darmstadt, West Germany. Experimental data relayed by GIOTTO during its encounter with Halley's Comet will be received via the 64m dish antenna of the Parkes Radio Telescope in Australia.



# NEWS

## Spacecraft Data

Height almost 3m; Diameter 1.84m; Spin stabilised 15 rpm; Orbit prograde-in same direction as Earth's Satellite fly-by velocity 68 kilometres per second; Data transmission - microwave in X and S bands; Transmitter power 20 watts; Antenna (on-board) 1.5 metre parabolic; Experiments 10; Experiments mass 56 kilograms; Launch - Ariane July 1985; Encounter - March 1986.

Command, control and data signals pass between Giotto and Earth via high gain dish antenna with an effective diameter of 1.47m. The antenna is despun and canted at an angle of 44.2° to Giotto's spin axis to maintain its line-of-sight to Earth during the comet encounter phase. The feed horns are carried on a tripod structure straddling the antenna. Signals will be relayed in either S-band (2.1GHz uplink, 2.3GHz downlink) or X-band (8.4GHz downlink). Antenna pointing accuracy is critical, especially for X-band transmissions (a 3dB loss occurs for 0.8 error in X-band).

## In search of the space shuttle

The March 1984 issue of *73: Amateur Radio's Technical Journal* is devoted to coverage of the historic ninth mission of the Space Shuttle, in which an astronaut/ham radio operator received NASA's permission to operate from space for the first time.

Dr Owen Garriott (callsign W5LFL), on his second shuttle mission, verified ham radio's effectiveness in acting as the ultimate in backup communications systems. On prior missions, the aerospace administration feared that such communications would interfere with the electronics of the spacecraft, and with the astronaut's primary responsibilities. Garriott succeeded in laying those fears to rest and, in post-mission remarks at the Johnson Space Center in Houston, remarked, 'We accomplished everything we set out to do'.

73's 'In Search of the Shuttle: A Ham in Space,' recounts the efforts of twenty-one American ham operators, located from Maine to Hawaii,

who were specially recruited by the magazine on the basis of geographic location to communicate with the shuttle during its mission. The geographically distributed network of operator/reporters, the first such network ever established by an amateur radio journal, was the brainchild of 73's executive editor, Jack Burnett. The project was the most expensive editorial undertaking in the magazine's history.

Both NASA and the ARRL (American Radio Relay League) cooperated in supplying information to Burnett. Since Garriott was only permitted to operate in his spare time, and since the orbital patterns of the shuttle would take it over different areas of the country at different times, the co-operation of NASA and the ARRL was crucial to the success of the project.

Garriott estimates that of the more than 100,000 operators who attempted to make contact, he heard three-hundred operators. Due to the tenacity of the operators' combined efforts and the organisational skills of the 73 staff, it is believed that several 73 reporters succeeded in getting through. Verification will be made after Garriott completes a review of the tape recordings he made onboard which document the contacts.

## Robotics conference 1984

The 1984 ACC Micro-robotics Conference is to be held at Central Hall, Westminster, on 21 April. The venue is in conjunction with the Association of London Computer Clubs' Easter Fair, and many of the stands will have a Robotics flavour.

Subjects planned for the Conference range from hobby interests to commercial applications, with talks and demonstrations by representatives of some of the leading manufacturers. The Micromouse maze will be featured, and a 'friendly' competition has been arranged. Novice constructors are encouraged to see how their mice perform against the old hands. The Robot Arena will also be there, with demonstrations and advice for home constructors.

## Circuit technology conference

LeaRonal (UK) plc will be displaying a comprehensive range of their latest processes and services specially designed for the PCB industry at the forthcoming Circuit Technology Conference to be held at the Kensington Exhibition Centre in London from the 3rd to 5th April 1984.

There are six items that will be of specific interest to Printed Circuit Board manufacturers. These are:- Copper Gleam 125, the new high speed acid copper plating solution; Ronovel N, the latest gold process from LeaRonal with British Telecom M468A approval; Pallamet 30 palladium-nickel process deposit meets the requirements of British Telecom M468A specifications when used in conjunction with a gold flash deposit (0.25 microns); Ronascreen resists and soldermasks, a new range of plating resists, etch resists, soldermasks and legend inks. They are available as thermal cure and UV cure products; the Solderon NF non-fluoborate tin-lead process which provides improved metal distribution, higher current density operating 'window' for given metal concentration and is a more stable alloy over wide current density range.

## Ships at sea and information technology

Ships' crews and passengers can now plug into the world of information technology.

Ships which use British Telecom International's maritime satellite system (Inmarsat), can access a wide range of computers and databases round the world

through BTI's international packet switching service, IPSS.

The new service will provide packet-switched links to the UK's public data network, Packet SwitchStream (PSS), and also to more than 50 similar data networks in over 30 countries. It will enable shipboard users to call up data on a wide range of marine-related subjects, including meteorology, geostrophysics, oceanography, naval records, marine pollution and its control, ports and harbours, seaways and ocean mining.

For computer users, packet switching has several important features: It makes national and international data communications simpler to set up, quicker to connect and more reliable in operation. It provides a flexible and reliable way of linking different computers and terminals and enables terminals working at different speeds to communicate with each other. It automatically re-routes packets along different paths to avoid congestion or route failure.

Shipboard customers will be able to use synchronous character terminals generating data at 300 bit/s. They will connect to IPSS by dialling the London IPSS exchange. Ships in the Atlantic ocean would use BTI's earth station at Goonhilly Downs, Cornwall.

Once connection has been established to the IPSS gateway, the user gives his IPSS 'password' (network user identity) and then the 'address' of the computer to be called.

To gain access to particular databases, users will also need to make the necessary commercial arrangements with their proprietors.

# Company News

## Ambit move

Ambit International, the electronics components supplier to industry and the home electronics market, is to move its headquarters from Brentwood to Broxbourne in Hertfordshire, though it will retain a sales counter in the Essex town.

The move is being made, to

enable the company to maintain the present pattern of growth. Demand for Ambit's services has risen steadily to the point where the Brentwood premises can no longer provide the necessary facilities.

Ambit's new address will be *Ambit International, Park Lane, Broxbourne, Herts.*



# NEWS


EN10 7NQ, the headquarters of its parent company, Cirkitt Holdings PLC and sister company, Broxlea Limited.

## Marconi changes dockland skyline

Engineers from Marconi Communication Systems Ltd, Chelmsford, are working on two projects that will bring the space age to London's dockland. Two separate sites, one on The Isle of Dogs and the other at Woolwich will be nearing the first stages of completion.

On the Isle of Dogs, Marconi is supplying Mercury Communications Ltd with two complete satellite earth stations that will be used to provide international links for leased-line and other switched services. A 13-metre dish will provide service to North America via the INTELSAT V satellite and an 8-metre station will provide services to Europe.

At Woolwich, Marconi is

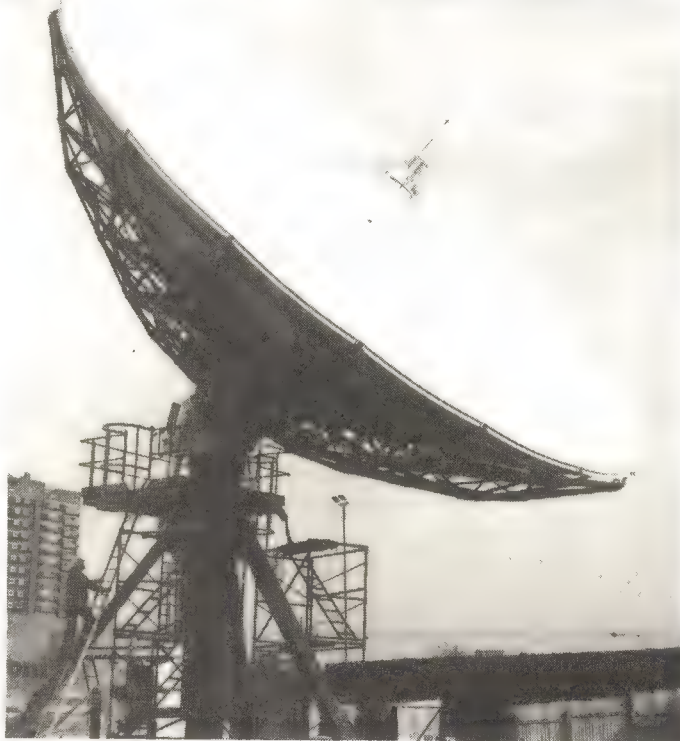

The new London 1 Satellite Earth Station at Woolwich

supplying British Telecom International (BTI) with three 13-metre antennas which will also provide services via INTELSAT V and through the ECS satellite. The system is designed so that, by the substitution of a few components, either terminal may assume the role of one of the others.

Both projects are well in hand. At Woolwich, the first antenna and the container housing the ground communication equipment are in position and work has already started on the second antenna.

A fully duplicated system of ground control equipment is being supplied to both sites.

In addition to the London sites, Marconi has also received from Mercury Communications an order for the supply of a complete earth station for the first terminal to be built at a site near Kidlington, Oxfordshire.



## The magnificent TIGER LY9 antenna

### New from Ant Products

New from Ant Products a superb addition to the range of renowned antennas, the Tiger LY9 for 70cms. A lightweight beam antenna with a heavyweight signal. Offering a high 11dB gain on a 58 inch boom length. Great for vertical or horizontal mounting. Supplied in matched pairs for the ultimate Oscar Station complete with all hardware for mounting with elevation control. Precisely adjustable for angle in order to get the best performance. Also including matching unit for circular polarisation. Right or left hand can be chosen with equal efficiency. Last but not least our famous two year guarantee and full back-up service.

Write now for full details enclosing S.A.E. + 25p in stamps.

**Single Antenna £15.95**  
**Complete Oscar Kit £39.95**

**Ant Products**

All Saints Industrial Estate  
Baghill Lane, Pontefract, West Yorks.  
Telephone Pontefract (0977) 700949

Amateur, Marine, C.B., Aircraft  
and Commercial Aerials supplied

PHILIPS P2000 DAISY WHEEL PRINTER RS232 £375 ea  
SHUGART 801 FLOPPY DISK DRIVES 8" £100 ea  
TRANSTEL DOT MATRIX PRINTER. Compact £35 ea  
Serial Interface 230V With Info. £50 ea  
TELETYPE ASR33 (Printer, Keyboard, Punch and Reader) RS232 £50 ea  
9" MONITOR Cased Non-Standard. With info £20 ea  
12" MONITOR Cased Non-Standard With Info £15 ea  
AZTEC 20" Black & White MONITOR Video in £50 ea  
TV Style 20" MONITOR Black & White Video in £30 ea  
GENERAL ELECTRIC TERMINET Printer with Keyboard Upper/Lower case £125 ea  
ICL Version of above. No Keyboard £95 ea  
QWERTY KEYBOARD. Push to make. Un-cased £15 ea  
P&P £4  
CARRIAGE ALL UNITS £7.

**STEPPING MOTORS**  
Type 1. 200 Steps 4 Phase (5 wire) 12/24V 25oz inch. 2 1/4" dia. £15 ea  
Type 2. 8/12 Steps 3 Phase 12/24V. 1 1/4" dia £2 ea 5 for £7.50  
Type 3. 24 Steps 4 wire 5V 3.3A 0-2500rpm 0-200PPs 2 3/4" dia. £10 ea  
Type 4. 200 Steps 120V (3 wire) 25 oz inch. 2 3/8" dia. £4 ea  
**MOTORS**  
SYNCHRONOUS 2 Phase 9V AC. 375rpm Cap start Will DC step. — 8 steps per rev. £1 ea  
GEARED 117/234V 50HZ. 4" dia £5 ea P&P £2  
GEARED 115/230V 1 rpm 2 3/4" dia £4 ea P&P £2  
MOTOR 12V DC 3" dia £3.50 ea. P&P £3

**TRANSFORMERS**  
TOROIDAL 13.5-0-13.5V 8VA — £1.50 ea 10 off £12  
TOROIDAL 0-12V: 0-12V 10VA per winding £4 ea  
10 off £35 P&P £2  
AUTO 240V Input 115V 1A £1.25 ea  
Sub-Min 12-0-12V 4VA — 75p ea. 10 off £6 P&P £2  
Printed Circuit Mounting 120/240V. Input Sec 15V 0.4A twice £1.50 ea  
Chassis Mounting 120/240V.  
9V 0.33A twice — £1.50 ea; 20V 0.15A twice £1.50 ea;  
5V 0.5A twice — £1.50 ea; 12V 0.96A twice £1.50 ea;  
7.5V 0.34A twice £3 ea  
Sub-Min PULSE TRANSFORMER Centre tapped. Suitable Thyristor triggering — 20p ea. 10 off £1.80  
Many other transformer available — please enquire.

**CAPACITORS**  
Electrolytic 15,000mfd 25V — 20p ea. 10 off £1.80  
Sprague Compulytic 18,000mfd 10V Screw terminal £1 ea  
Electrolytic 900mfd 100V Screw terminal 50p ea. 10 off £4

**OSCILLOSCOPES**  
COSSOR CDU150 Dual Trace 35MHZ Delay Sweep £200  
SE LABS SM111 Dual Trace 20MHZ £200  
TEKTRONIX 585A with 82 Plug-in Dual trace 85MHZ £200  
Dual TB Delay Sweep £200  
TEKTRONIX 545B with CA Plug-in 24MHZ Dual Trace Dual TB £160  
SOLARTRON CD1400 Dual Beam 15MHZ £90  
Ex-Ministry CT438 Dual Beam 6MHZ £30  
ADVANCE Dual Stab DC Power Supply PP3 0-30V. 0-1A twice. Metered. £50  
FARNELL Stab Power Supply TSV30/SEC 30V/5A £60  
AVO TRANSISTOR TESTER TT169. With leads £20  
P&P £2  
CARRIAGE ALL UNITS £7.

Tantalum Bead 0.1mfd 35V. 10 off £1. 100 off £7.50  
De-Coupling — 0.4725V; 0.005 100V; 0.47 12V; 0.001 200V; 33pF. 10 off 30p. 100 off £2

**SWITCHES**  
ILLUMINATED ROCKER 2 pole 250V 8A. Orange-50p ea. 10 off £4  
ROCKER 2 pole c/o — 12p each. 10 off £1.80  
TOGGLE Centre off DPDT — 20p each 10 of £1.80  
SLOTTED OPTO SWITCH with data-50p each 10 off £4  
Min MICROSWITCH V3-Button — 30p. 10 off £2.50  
I.C. SOCKETS 10 pin-10p; 22pin-15p; 14pin-8p 100 off £5  
36pin-15p; 40pin-25p; 16pin-8p 100 off £5  
RIBBON CABLE 10 way — 50p per metre. 10 metres £4  
14 way — 75p per metre 10 metres £5  
PCB KEYBOARD PAD 19 Push Contacts. 0-9: A-F plus 3 optional — £1.50 ea. 10 off £12  
KEYBOARD PAD 12 Alma Reed Switches Push to make 0-9: & Blank — £4 ea. 5 off £15 P&P £3  
TOKIN NOISE FILTER VG215FU. 250VAC 15A 50/60 HZ With fixing bracket. £2 ea  
BLACK RIBBONS for Teletypes/Teleprinters 75p ea 6 off £4  
I.T.T. LOUDSPEAKER 2 1/4". 50ohm 0.2W-75pa 10 off £6.50  
FERRANTI PHOTOCELL type MS15-50p ea 10 off £4

VU METER Scaled 0-5. Size 1 1/2 x 7/8 — 50p ea. 10 off £4  
I.E.C. MAINS LEAD 2 metre Heavy duty-60p ea 10 off £5  
MICROPHONE/EARPIECE INSERTS — 75p ea. 10 off £5  
CINCH CONNECTOR STRIP 12 way. Screw connections 35p ea. 10 off £3  
CABLE TIES White 9cm; Black 12cm. 50 for 50p

**EXECUTIVE TELEPHONES — PUSH BUTTON**  
Many functions including 10 number memory, repeat dialing etc. Will connect to GPO system. Brand New. £25 ea P&P £4

**SAMPLE OF STOCK — SAE or TELEPHONE for LISTS** Please check availability before ordering. Min order of Goods £4. Min P&P £1.50 VAT at 15% MUST be added to TOTAL of Goods & Packaging.

**STEWART of READING**  
110 WYKEHAM ROAD, READING, BERKS RG5 1PL Tel: 0734 68041  
Callers welcome 9am-5.30pm Monday to Saturday inclusive



# HATELY ANTENNA TECHNOLOGY

GM3HAT



GM3HAT/A

## DIPOLE OF DELIGHT

The DIPOLE of DELIGHT is the familiar name for the new type of antenna with a really effective balance to unbalance (BALUN) feed system recently invented by GM3HAT and now being patented in the major industrial countries.

This antenna has created a lot of interest in amateur and professional circles because practical trials of early production models verify the expected advantages this outstanding antenna possesses attributable to its:-

1. built-in lightweight capacitive BALUN card.
2. ability to achieve multi-resonant behaviour when constructed with multiple wires.
3. rugged behaviour and 800W transmit capability due to there being NO TRAPS.
4. wide bandwidth so that NO ANTENNA TUNER is required.
5. exceptional rejection of local interference such as machine hash, TV timebase noise, and computer pulses.

### VERSIONS AVAILABLE

There are presently available seven versions made for the international amateur HF bands, and more will follow. The models are designated by a code which indicates the frequency band (or bands) of operation, defined as being the band across which the antenna has less than SWR of 1.5 to 1. The length of the DD is a full space half-wave at the lowest frequency of operation, and the antenna is fully protected against the weather including a drip-protected SO239 socket (UHF) for connection of the 50 ohm coax required. Due to variability of site length etc, coax is not supplied, but the 5mm types such as URM 76 or 43 are recommended. Larger 10mm cables (such as URM67 and RG8U) can be supported if the antenna is used as an inverted V, or if held by reduced tension. Each antenna is supplied with a helpful USER'S INSTRUCTION SHEET describing the best way to support a DD in any open or cluttered situation, as well as giving hints on how to make a low cost and inconspicuous fixed YAGI with gain at high angles for one hop paths, and how to use an ATU to make the DD work on lower amateur frequencies as a 'T' against Earth.

### ECONOMIC AND OPERATIONAL ADVANTAGE

As there is no ATU needed, a DD is an ideal first antenna. The DD is superb for amateurs who have, or intend getting, a modern semi-conductor 'NO-TUNE' PA or Linear. To change bands, flick the switch, listen on frequency and speak. Great in a contest. The wide bandwidths allow the user to make contacts away from the over-crowded central frequencies to which trap and coil-resonated antennas are tuned.

In regard to TVI the particular circumstances determine the outcome. The DD is so efficient that it will produce amateur field strengths greater than a traditional dipole. But by virtue of its excellent balance, a horizontally slung DD will produce considerable less vertical induction field (which links to TV downleads) than would an old style coax fed dipole with its unbalance current flowing down the outside of the screen. A DD has a genuine RF Earth point at its centre. Further details on SWR values and specimen input impedance plots on SMITH CHARTS may be obtained for the asking (send SAE or IRC please).

### AVAILABLE VERSIONS AND PRICES

The UK Price includes Packing Post and VAT (on 15% at time of drafting).

The DX Price includes Packing Air Mail Post, and currency exchange. Cheque may be written in ANY CURRENCY, equivalent on the day of signature to the amount in £ Sterling at published middle rate.

### SPECIFY CAREFULLY VERSION REQUIRED

	UK	DX
DD 7/14/21 length 21m (69ft)	£56.46	£56.00
DD 10/18/24 length 15m (50ft)	£56.46	£56.00
DD 14/21/28L length 10.7m (36ft)	£46.75	£46.00
DD 7/14/21/28L length 21m (69ft)	£58.50	£58.00
DDM 14 length 10.7m (36ft)	£15.98	£15.28
DDM 21 length 7m (24ft)	£11.64	£11.50
DDM 28 length 5.8m (19ft)	£11.64	£11.50

(28L antennas operate in the lower half of the band only, unless an ATU is used) Money back GUARANTEE if purchaser not satisfied if antenna returned undamaged within one month.

# HATELY ANTENNA TECHNOLOGY

1 Kenfield Place, ABERDEEN AB1 7UW  
SCOTLAND, UK

Proprietor:- Maurice C Hateley, B Sc (Eng), M Sc, MIEE, Chartered Electrical Engineer, (GM3HAT)

(NB We will be Exhibiting at the Anglo-Scottish Rally at Tait Hall, Kelso 6th May)

# HEMMINGS ELECTRONICS AND MICROCOMPUTERS

DEPT RE  
16 BRAND ST.  
HITCHIN  
HERTS SG5 1JE

Tel: (0462) 33031

Shop open Mon. - Sat. 9.30 - 5.30  
Closed Tuesday afternoon

Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft by order, payable to Hemmings Electronics Ltd. Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome. P & P. add 45p to all orders under £10. Telephone your Access orders, using our 24-hr. Ansaphone service. Please send SAE for full price list.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P & P. No VAT on export orders or books.

<b>COMPUTER ICs</b> 6502 380p 6522A 380p 6800 290p 6800B 450p 6801 345p 6809 750p 68809 1150p 6809E 995p 6810 120p 6821 160p 68821 215p 6840 390p 68840 580p 6844 1295p 6845 795p 6850 140p 6852 250p 6854 680p 6875 990p 8126A 120p 8128 120p 8195 90p 8196 90p 8197 90p 8198 90p 8025L 340p 8039L 320p 8080A 360p 8085A 450p 8155 450p 8212 155p 8213 100p 8224 160p 8226 195p 8228 250p 8251 300p 8253 450p 8255 280p 8257 450p 8259 450p 8259 450p 9017 12p 9018 12p 9019 12p 9721 12p 9722
---



# One Night's Work

Here is another useful little project from Stephen Ibbs, IF oscillators which will greatly assist alignment.

When aligning/tuning up receivers, it will be found that a crystal IF oscillator is a very useful piece of test gear. All it does is to oscillate at the IF frequency, but when placed close to the IF stages, the two frequencies beat together, producing an audible note. The receiver IF can then be tuned for zero beat, with the knowledge that it is now on frequency. The rest of the receiver can then be aligned using this as the reference point.

## Two circuits

The two most common IFs are 10.7MHz and 455kHz, and so two circuits are given here, both using a 74LS00 TTL IC as the

oscillator. Very little need be said about the circuits, which are slightly different because the frequencies are so separated that a common oscillator circuit wouldn't really have been feasible. Both circuits have a 5.1V zener diode incorporated so that they can be powered from any voltage from approx 7-15V, the most convenient being a PP3 9V battery.

Though not tried in the prototype, it should be possible to use a ceramic resonator (cheaper than a 455kHz crystal) with minor modifications to the one circuit.

A DC blocking capacitor can be placed in the output if desired, eg. 33pF.

Veroboard or PCBs can be used, designs for which are given in the *Figures*. Mount all the components, taking care with the crystal leads. After checking carefully, switch on and adjust the trimmer to give 10.7MHz output. The boards were designed to mount on one side of the smallest standard diecast box, with a battery on the other side. The output, (pin 8) is connected to a short length of wire which projects through the one end of the case, otherwise the metal would effectively screen the oscillator and prevent any RF getting out. SW1 is a miniature push button mounted on the top of the case.

The 455KHz oscillator


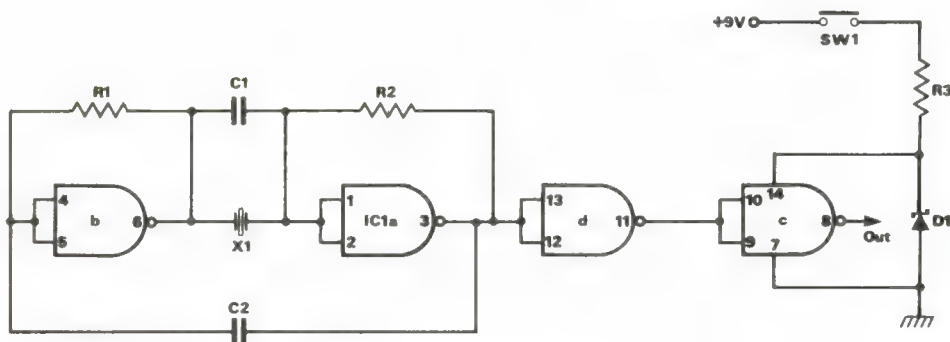


Fig 1a Crystal oscillator circuit

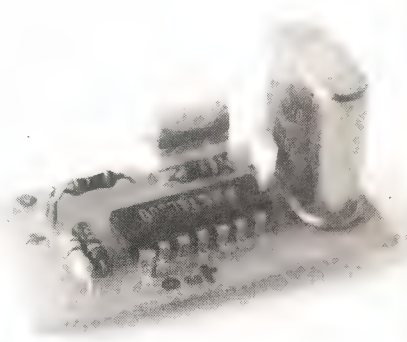

Assembly

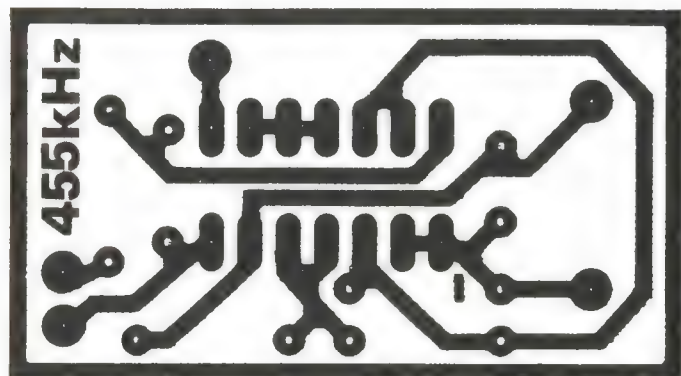


Fig 1b Foil pattern


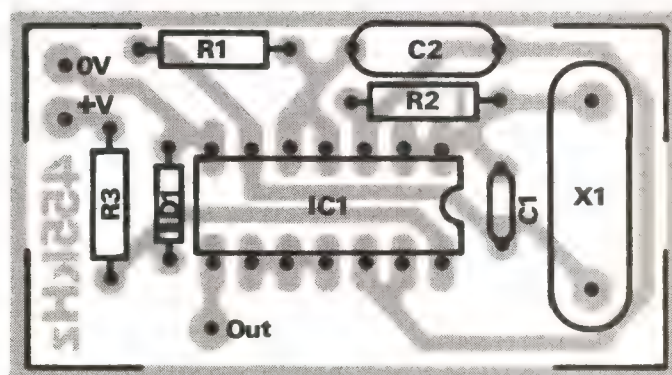


Fig 1c Component overlay

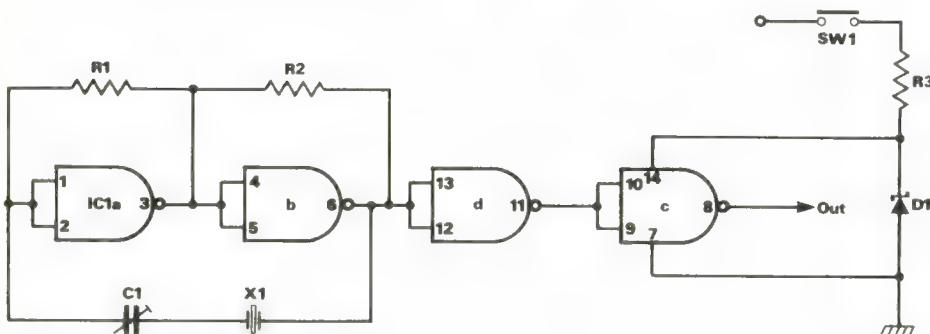


# ONE NIGHT'S WORK


Fig 2 the 10.7 MHz oscillator




(a) The circuit

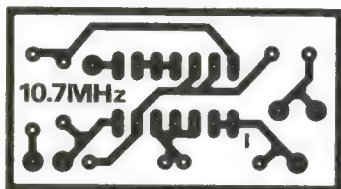

(c) Foil pattern

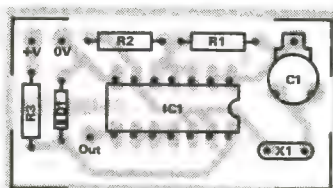

(d) Component overlay

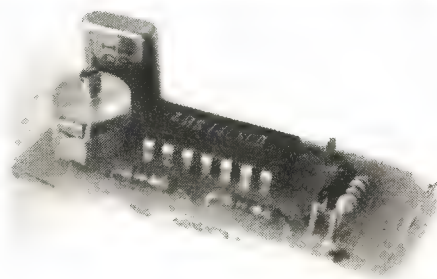

(b) Assembly

## PARTS LIST

455kHz crystal oscillator	
R1, R2	1kΩ
R3	100Ω
C1	220pF ceramic
C2	47nF polyester
D1	5.1V zener diode
IC1	74L 500
X1	455kHz crystal

## PARTS LIST

10.7MHz crystal oscillator	
R1, R2	560Ω
R3	100Ω
C1	5-60pF trimmer
D1	5.1V zener diode
IC	74L 500
X1	10.7MHz crystal

## C M HOWES Communications


139 HIGHVIEW, VIGO, MEOPHAM  
KENT DA13 0UT  
Fairseat (0732) 823129

### Home construction made easy

Enjoy the satisfaction of building your own equipment with one of our kits. We make construction a pleasure, the right parts, the right performance, and very good instructions. Our kits are designed to be easy to build, even for those with no previous experience of this absorbing side of the hobby.

All kits come complete with all board mounted components, a drilled, tinned, PCB that has the component locations screen printed on it for straightforward assembly (see example below), and full instructions that include a parts list and circuit diagram. The parts list in a HOWES kit details the colour code/markings information for each individual component.

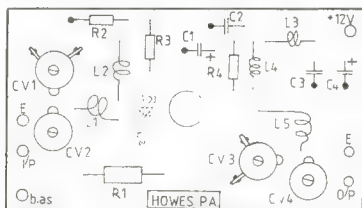Choose a worthwhile project from our expanding range:-



#### PA Series Linear Amplifiers

These linear amplifiers have been designed for use with the popular portable and hand-held 2 meter rigs. There are two versions available at the moment, one or other will probably suit your radio.

**PA2/15** Up to 15W output with a gain of approx 10dB, for hand-helds with up to 1½W output and 1W SSB portables. **Kit £18.90, assembled PCB £22.80.**

**PA2/30** Up to 30W output, gain approx 8dB. This unit has been designed to put out a 'clean', narrow signal on SSB with rigs such as the FT290 and IC202. We have not gone all-out for maximum gain, this unit will have plenty of power in hand with these popular rigs, there are too many small 'linears' on the market that try to get too much gain and power out of a 25W transistor with the resultant nasty effects for other band users. Build a linear that will put out a signal you will be proud of. **Kit £22.90, assembled PCB £26.90.** Both the above come complete with preformed inductors, so there is no problem in trying to decypher coil winding instructions! An RF or PTT operated switching unit for the above is available, type **CO1** this uses low-cost relays to give reasonable performance at a sensible price. **Kit £8.90, assembled PCB £11.90.** Yes, there is provision for connecting a pre-amp if you wish.

**AP3 Automatic Speech Processor.** Kit £14.80, assembled PCB £19.80 This is the excellent processor described by Dave, G4KQH in the September 83 edition of 'Ham Radio Today'. We have sold hundreds and hundreds of these and many customers have come back to buy a second, third or even fourth unit for use with their other rigs. The AP3 uses a combination of compression, clipping, and response tailoring to give you a really 'punchy' signal that enables you to make contacts that may not be possible without it. The unit will run from not in use, so saving batteries. Clipping level is selectable in 6dB steps, no other operational controls to fiddle with, operation is fully automatic, speak as loudly or quietly as you like, the AP3 will adjust itself. Suitable for high and low impedance mics.

**DcRx DIRECT CONVERSION COMMUNICATIONS RECEIVER,** Kit £13.95, built £18.90 DcRx is a low cost, easy to build amateur band receiver, designed so that a newcomer to the hobby can build a shortwave receiver with the minimum of trouble. The DcRx is also proving to be very popular with experienced QRP operators.

Two versions of the DcRx are available at the moment, one covering 10 or 14 MHz, and one covering 3.5MHz (80M). The kit comes complete with ready-wound coils and requires very little alignment. You will be amazed how well a simple receiver can work, don't be put off by the low price, this set performs well and is capable of world-wide reception. The DcRx runs from a nominal 12V supply and will drive a loudspeaker or headphones.

Modes: SSB and CW. PCB size 77 by 77 by 25mm approx.

**XM1 CRYSTAL CONTROLLED FREQUENCY MARKER** Kit £15.60, assembled £19.60. A really useful piece of test equipment, besides helping you meet amateur licence frequency measurement requirements. Our kit has a built in voltage stabiliser to maintain accuracy over a wide voltage range (8 to 24V DC). The XM1 provides marker outputs at 1MHz, 100kHz, 25kHz and 10kHz, these are usable up to 70cm, unlike some CMOS designs. The XM1 has a pulsed ident facility for distinguishing markers from off-air signals on crowded bands. This facility is very useful, and much preferable to tone modulated markers, whose bandwidth becomes larger as frequency increases. If you are going to invest in a piece of test equipment, it pays to go for a good quality design, the XM1 provides this.

**ST2 CW SIDE-TONE UNIT or PRACTICE OSCILLATOR** Kit £6.20, built £8.90. The ST2 provides a nice sounding sinewave note, either from your key or from the output of your TX by RF sensing. This design should not be confused with cheap and nasty squarewave circuits so common in horrible sounding practice units. We think side-tone, or a practice oscillator should sound like a good off-air signal received on a quality set. Output is up to approx. 1W at 800Hz, a volume control is included.

An SAE will bring you further information on any item.

**P&P charge is 60p**, please add this to your total order value.

We attempt to keep everything in stock and delivery to within 7 days, but we do sometimes get caught out, no matter how hard we try!



# R WITHERS COMMUNICATIONS

584 HAGLEY ROAD WEST, OLDBURY, WARLEY

B68 OBS

Tel: 021-421 8201/2



Our workshops are equipped up to 3GHz and have the advantage of G4KZH's expert crew of engineers under his supervision, and Ray also has the help of our new Spectrum Analyser.

Some of the lines presently in stock.

Kenwood/Trio DFC230 **£59.95** — look at the saving!

Kenwood/Trio TR7950 45 watt FM Mobile..... **£329.00**

Kenwood/Trio TR7800 45 watt FM Mobile..... **£249.00**

The scanner you can buy!! AM/FM Revco/Gemscan 60 MHz to 515 with airband ..... **£249.00**

Diawa auto ATU CNA1001 Special Price..... **£139.00**

Diawa 1.2 k/watt CNW 518 Special Price..... **£189.00**

Yaesu World Clock QTR 24D only ..... **£29.95**

Diawa CN 510 Cross Needle..... **£39.95**

Diawa CN 560 Cross Needle..... **£49.95**

Diawa 2030 30 watt FM Booster..... **£55.00**

Spring Silly Price Rotator Offer — Kopek Straight Through Rotator only ..... **£38.95**

New Kenpro handheld 140-150 MHz 3 watts H/Power out **£159.95** includes Nicad pack & charger.

PLUS HUNDREDS OF MAIN LINE ITEMS FROM ICOM, YAESU, FDK, KENWOOD, TRIO, WELZ, TONNA.

'10 METRE' FM MOBILE RIGS '2740' from the company who have converted over '600' units.

**We** have obtained the last 200 units we believe available in the UK. Take this opportunity to obtain any of the following options:-

2740 modified to 6 watt output 29.310 to 29.700..... **£47.50 inc**

2740 as above but inc repeater shift ..... **£10.50 extra inc**

2740 unmodified less crystals ..... **£33.00 inc**

Crystals for above **£4.75** each plus 50p p&p = 2 req'd plus one for repeater shift.

Suitable 25 watt linear 'Relay Switched' only ..... **£16.50 inc**  
plus £1.50 p&p

IF Crystal filter **£2.00** inc + 50p p&p

MOD Sheet for above including improved audio also applies to DNT rigs ..... **£1.00** plus SAE

Delux mic ready wired 5 pin din **£3.50** inc plus 50p p&p.(Also suitable for all VHF rigs).

Delux 10 metre dipole inc wall/loft bracket..... **£8.50**  
& £2.50 p&p.

Ten metre HB9CV including p&p ..... **£33.00**

Oskerblock SWR 200 maximum power 2kw. Normal price £59.95 100 to clear at only..... **£39.95**

Ray Withers G4KZH says now is the opportunity for all progressive radio amateurs to work real DX for less than £50.00.

Please note all orders will be dealt with strictly on a first come first served basis. This offer is available only while stocks last. All lines we will be pleased to send mail order.

'73's, GUD, DX's, FBOM. See you on ten'

Ray Withers. G4KZH

Some of these lines are also available at CQ Centre, 10 Merton Park Parade, Kingston Road, London SW19.  
Tel: 01-543 5150



# HF Linear Amplifier

*This article describes the construction of a 200 watt amplifier, designed by the M-O Valve Company.*

*It will provide excellent linearity and is suitable for professional or amateur use*

## Why use tubes?

An amplifying device may be either a tube or a transistor (bipolar or fet). When the smallness of the transistor, its low voltage operation and absence of heater are regarded as deciding factors, there is no point in advocating the use of a tube. However, tubes do have distinct advantages of their own.

An important one is their better high frequency capability, particularly at output power levels of 50W and over. Examples are the VHF/UHF tubes such as the forced air cooled 4CX250B and its conduction cooled variants the CCS1 and CCS2. There is also the conduction cooled YL1550, which is used in the Clansman military communications system, to give a VHF output of 50W with a low power semiconductor drive circuit.

Glass envelope tubes have a particular advantage concerned with cooling. Transistors

need to be conduction cooled and, if the heat has to be carried away by the chassis, semiconductors elsewhere in the circuit may suffer. A separate system of metalwork, thermally isolated from the chassis, can be used for cooling, but this may be bulkier than the tube which could be used instead. With adequate ventilation it is usually fairly easy to get the heat away from a glass envelope tube and a fan is sometimes used, especially when a large power handling capability is packed into a small space.


Although the linear amplifier is commonly used in conjunction with a pi-coupler output circuit, which is capable of good harmonic rejection, and further filtering is often added, it is worth noting

that a tube, because of its smoother characteristic, usually generates a rather lower proportion of harmonic output than a transistor. The tube's intermodulation products are also likely to be less, especially at moderate signal levels.

In the absence of faults, one may expect a transistor to have a longer life than a tube, but a tube will usually survive such contingencies as aerial short or open circuits, provided they do not last too long, whereas a transistor may well be burnt out by them. Also, in the event of a failure, a tube is often easier to replace.

## Operating bands


The amplifier is suitable for single sideband transmitters giving a peak envelope power output of 220W at 3.5MHz and 130W at 30MHz from an ht supply of 1200V. Band switching is provided to cover the 3, 5, 7, 14, 21 and 28

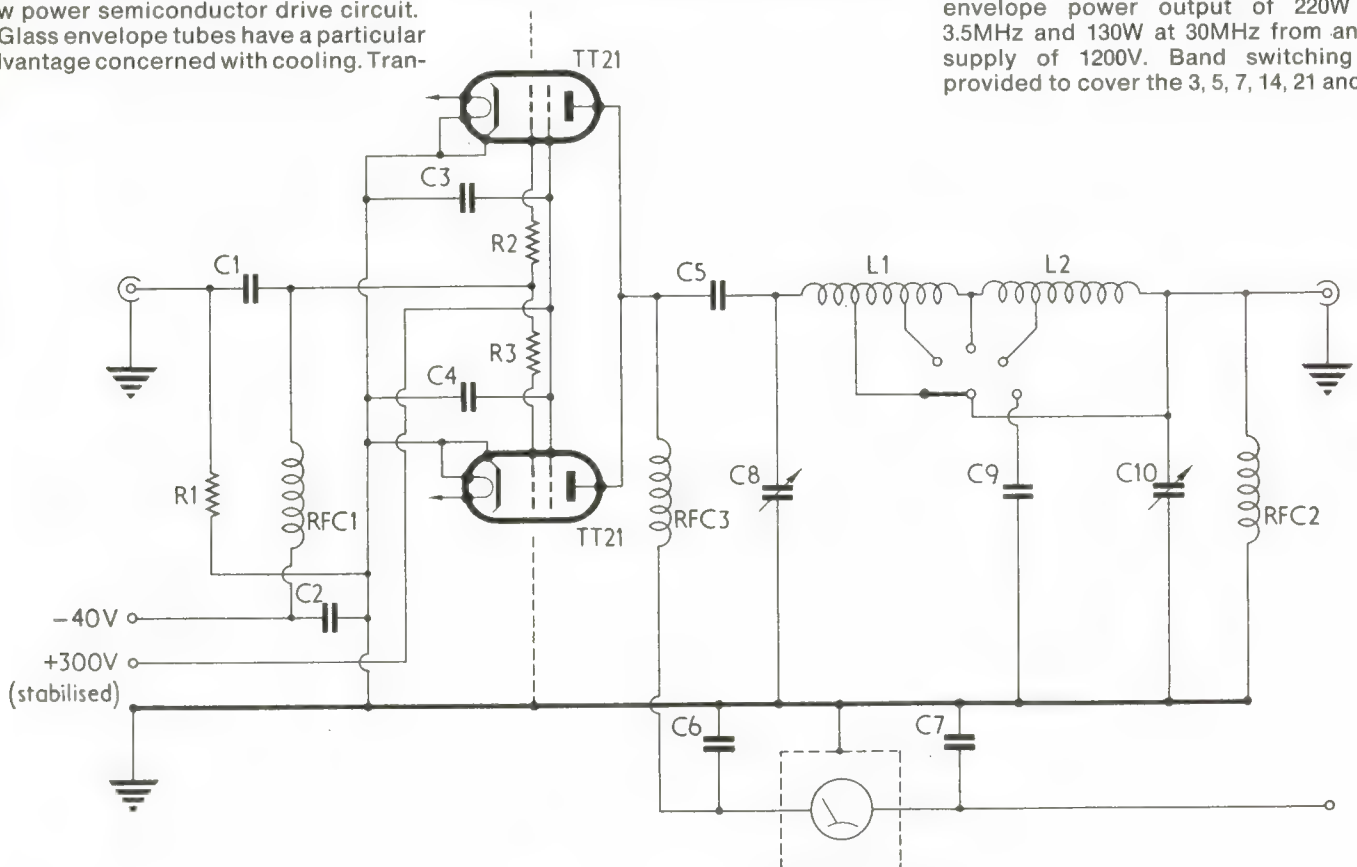

**Fig 1** Circuit diagram 200W amplifier



# HF LINEAR AMPLIFIER

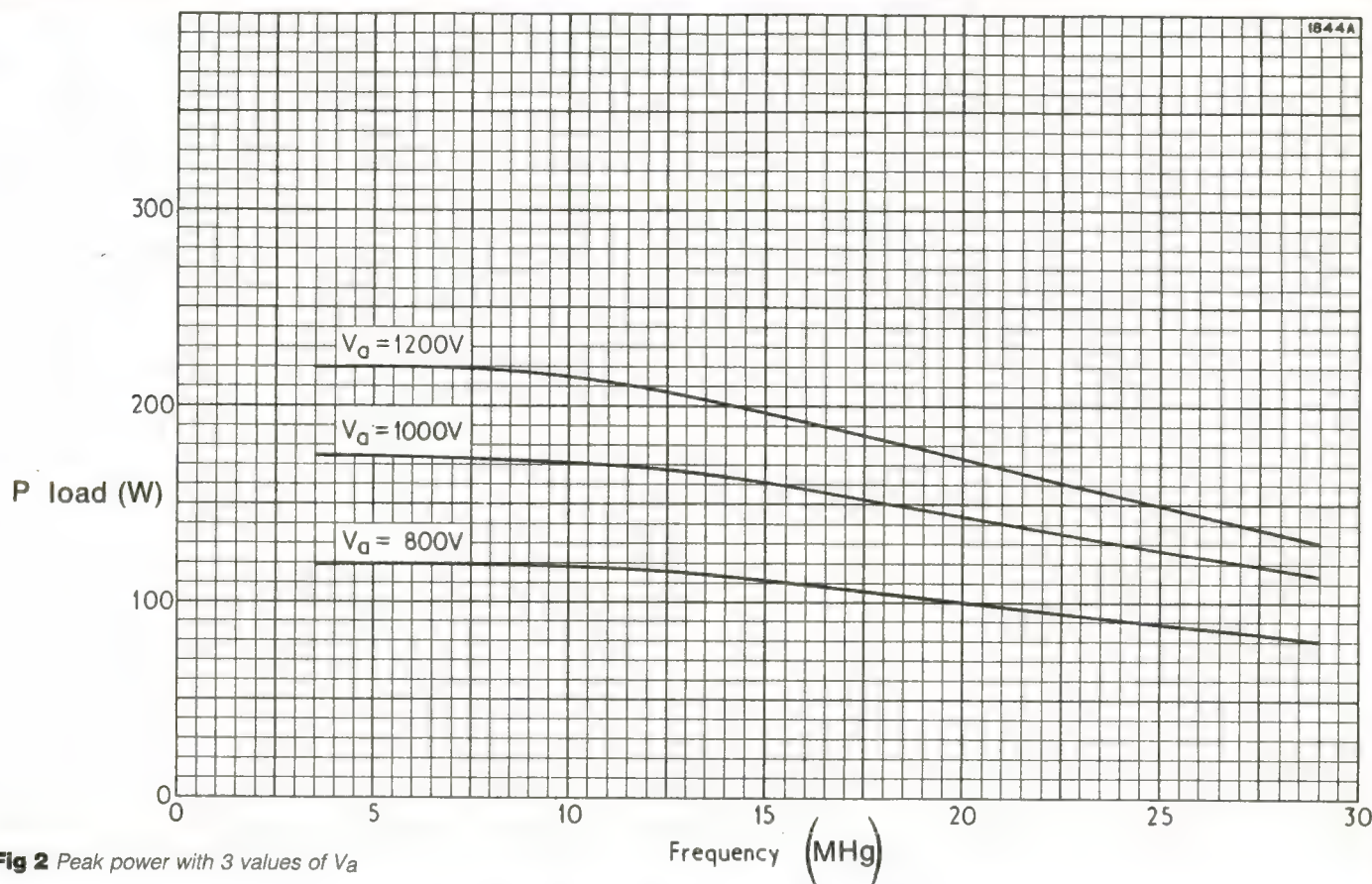

**Fig 2** Peak power with 3 values of  $V_a$

MHz amateur bands and could be readily adapted for other frequencies.

## Circuit description

Two TT21 tetrode valves are connected in parallel to a conventional 'pi' output coupling system which provides adjustment for load matching. In order to ensure complete stability without the inconvenience of neutralising, the so called 'passive grid' input circuit is used, in which the input tuned circuit is replaced by a resistor, in this case of 1000Ω. This results in some increase of drive power requirements but the amplifier can be driven to full output with a drive of 5W at 30MHz. The TT21 valves are not driven into grid current and the drive power is dissipated in the grid input resistor and in circuit losses.

## Operating conditions and performance

The peak envelope output power (PEP) obtainable at frequencies up to 30MHz is shown in *Figure 2* for anode voltages of 800, 1000 and 1200V; the corresponding operating conditions are shown in Table 1.

It should be noted that continuous operation at full peak envelope conditions with an anode supply of 1200V is not permissible since the ICAS anode dissipation rating of 45W is exceeded. However, for modulation waveforms having a peak-to-mean ratio greater than 3:1, these conditions are permissible and apply to most practical systems of speech transmission.

The inter-modulation performance is shown on Table 2 under two tone test

conditions; third order inter-modulation of -45dB and fifth order of -46dB relative to either tone is obtainable without the use of feedback.

**Table 2 Inter-modulation Performance**

$V_a$	800	1000	1200	V
$V_{g2}$	300	300	300	V
$-V_{g1}$	34	37	39	V
$V_{g1}$ (pk)	34	37	39	V
$I_a$ (o)	94	75	65	mA
$I_a$ (2 tone)	160	165	180	mA
$I_{g2}$	12	10	8	mA
$I_{g1}$	0	0	0	mA
$P_{load}$ (2 tone)	60	87.5	110	W
D3	45	33	29	dB
D5	46	46	43	dB

**Table 1 Performance of Amplifier**


Frequency	≤7	≤7	≤7	14	14	14	21	21	21	29	29	29	MHz
$V_a$	800	1000	1200	800	1000	1200	800	1000	1200	800	1000	1200	V
$V_{g2}$	300	300	300	300	300	300	300	300	300	300	300	300	V
$*V_{g1}$	34	37	39	34	37	39	34	37	39	34	37	39	V
$I_a$ (o) (2 valves)	94	75	62.5	94	75	62.5	94	75	62.5	94	75	62.5	mA
$I_a$ (max sig) (2 valves)	210	260	270	190	230	250	210	240	250	210	215	235	mA
$I_{g2}$ (max sig) (2 valves)	19	18	18	16	16	14	16	16	17	16	16	14	mA
$I_{g1}$ (max sig)	0	0	0	0	0	0	0	0	0	0	0	0	mA
$P_{in}$	168	260	320	152	230	300	168	240	300	168	215	282	W
$P_{load}$	120	175	220	114	167	204	98	140	170	80	115	130	W
$P_{in} P_{load}$ (per valve)	24	43	50	19	32	48	39	50	65	44	50	76	W

\*Adjusted to obtain the stated value of  $I_a$  (o)



# HF LINEAR AMPLIFIER

Top view of amplifier (cover removed)

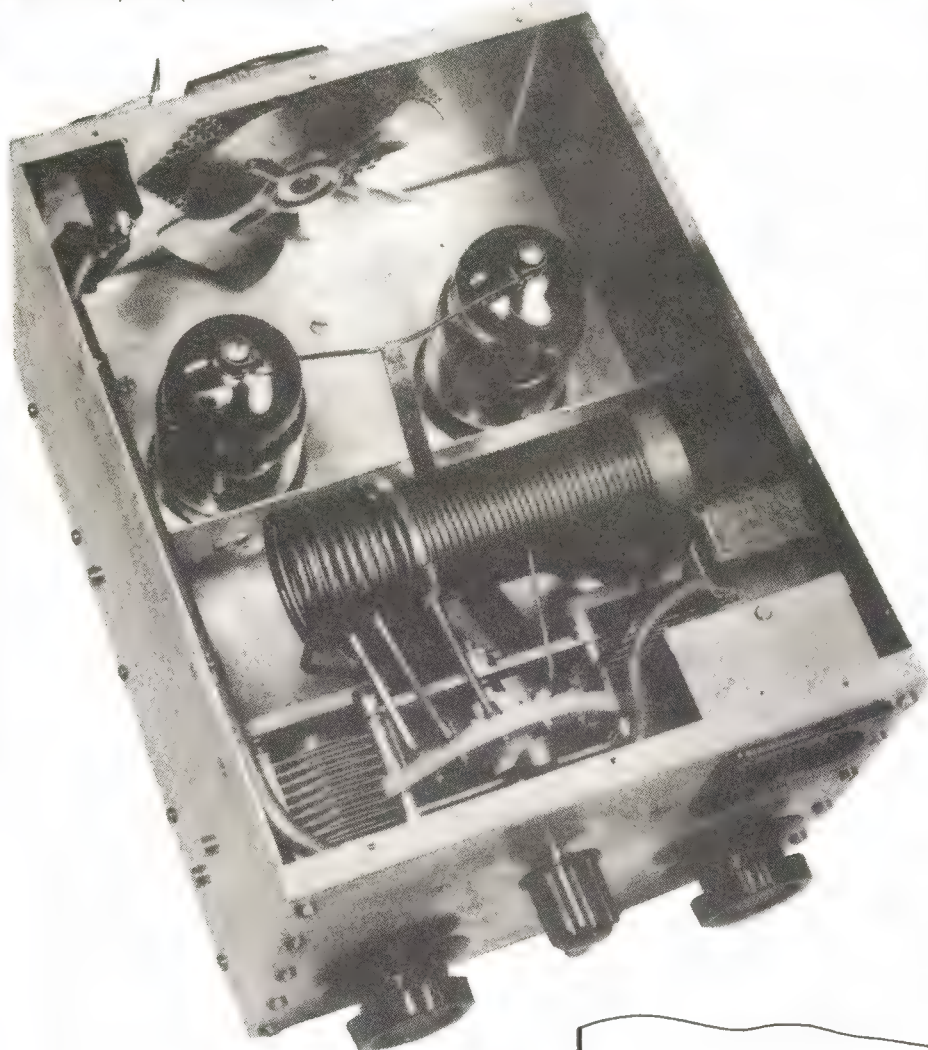

## Component Values

R1	1000 $\Omega$	2W
R2	100 $\Omega$	1/2W
R3	100 $\Omega$	1/2W

RFC1	2.5mH
RFC2	2.5mH

Meter 0 - 300mA

C1, C2	0.01 $\mu$ F	500V	(0.01 $\mu$ F disc ceramic)
--------	--------------	------	-----------------------------

C3, C4	0.03 $\mu$ F	500V	(3 x 0.01 $\mu$ F disc ceramic)
--------	--------------	------	---------------------------------

C5	2500pF	2.5kV
----	--------	-------

C6, C7	2500pF
--------	--------

C8	17 - 200pF
----	------------

C9	500pF
----	-------

C10	40 - 500pF
-----	------------

## Construction

The amplifier is constructed in an aluminium box 10½in x 8in x 6½in. Because of this small size, positive steps have to be taken to prevent over-heating. The inside faces of the box nearest the valves should be painted matt black in order to reduce reflected heat. The base and top plates and the intermediate shield should have a number of holes around the valves in order to assist natural convection. Some additional air movement is necessary and is provided by a small fan mounted through the rear wall of the box. Checks should be made on prototype equipment that the maximum bulb temperature of the valves does not exceed 250°C under the most onerous conditions of service. Temperature-sensitive paints are convenient for this purpose.

To prevent feed-back in common return circuits, a single earthing point should be established on the chassis midway between the valves (Figure 3). In particular, the two variable capacitors which make up the output tuning system should have their rotors connected to this earth point by a copper strap about 3/16in wide and should not be earthed at

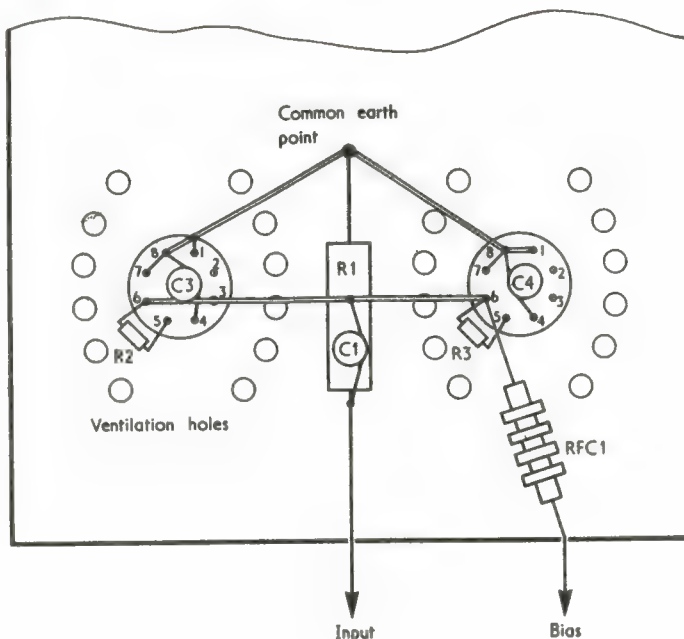



Fig 3 RF connections to valve sockets

any other point. The earthed side of the type N output socket should be similarly returned to the earth point even though it is earthed to the chassis by its mounting.



## HF LINEAR AMPLIFIER

Output tuning assembly

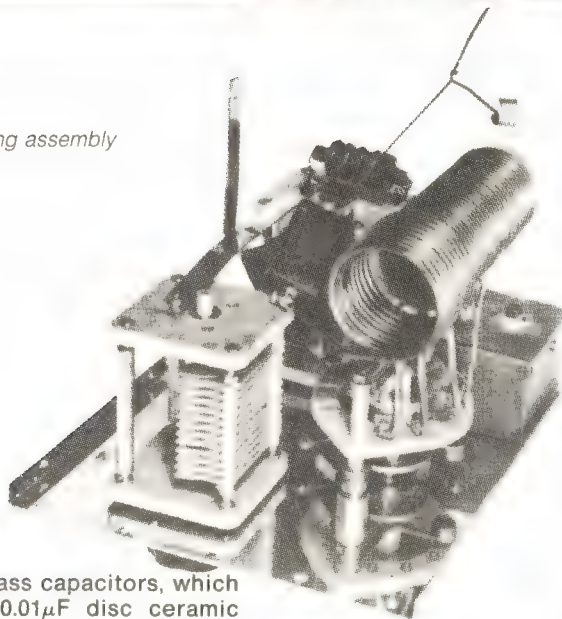

The screen by-pass capacitors, which consist of three 0.01 $\mu$ F disc ceramic types in parallel should be connected directly across the valve holder between pins 4 and 8, since they are concerned only with the rf circulatory currents associated with each separate valve. On the underside of the chassis, the cathode pins of the two valve holders should be separately connected to the earth point by a heavy gauge conductor.

Grid stoppers of 100 $\Omega$  are needed to ensure freedom from parasitic oscillation.

These are connected between pins 5 and 6 of the valve holder, the latter pin having no connection within the valve. A heavy gauge conductor joins pins 6 of the two valve holders and the drive is introduced at the centre of this through a 0.01 $\mu$ F capacitor. With particular circuit layouts, further suppression of parasitic oscillation may be necessary; a 100 $\Omega$  1/4W resistor overwound with 2 1/2 turns of

18SWG copper wire connected close to each anode cap will normally be effective.

### Components

#### Anode Coil

This coil consists of two windings in series; L1 in the circuit diagram consists of 9 turns of 1/8in diameter copper wire with the turns spaced 1/8in and with an internal diameter of 1 1/2in. The entire coil is used at 14MHz/s and taps at 3 and 5 turns from the anode end are used for the 28 and 21 bands respectively. L2 consists of 31 turns of 16SWG wire wound on an epoxy resin former 1 1/2in diameter. The turns are spaced so as to occupy a winding length of 3 1/2in. For use at 7MHz a tap at 12 turns from the anode end is used.


#### Anode Choke (RFC3)

This choke has to have high impedance over the entire frequency range, since it is effectively in parallel with the anode-tuned circuit. A single layer solenoid 1/2in diameter close wound with 24SWG enamelled copper wire to a winding length of 2 1/2in is satisfactory. The connections should be designed to minimise shunt capacitance across the choke.

*This Article is reproduced by kind permission of the M-O Valve Company.*

## COMMUNICATION RECEIVER

NEW

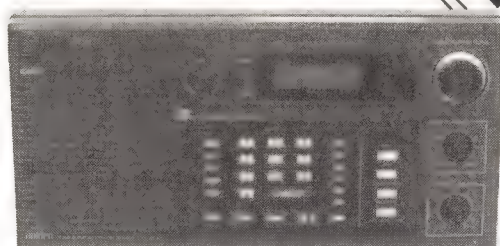

### uniden MODEL CR-2021

A compact communications receiver with full professional specifications and facilities.

- ☐ Full frequency coverage of 150KHz to 29.999MHz and 78 to 108MHz.
- ☐ Maximum sensitivity on AM/SSB/CW, also FM, with narrow/wide filter.
- ☐ Memory for any 6 AM/SSB and 6FM frequencies, plus automatic scanning between any two frequencies.
- ☐ Keyboard entry of frequency shown on LCD display.
- ☐ External sockets for aerial, earth, headphones, and loudspeaker.
- ☐ Operation from internal batteries, 12VDC, or 240VAC.
- ☐ Only £189.75 inc VAT and P&P.

### LECMAR ELECTRONICS

Vectis Yard, Cowes, Isle of Wight  
Tel: (0983) 293996

DEALER ENQUIRIES INVITED

BARCLAYCARD/ACCESS

## S.E.M.

UNION MILL, ISLE OF MAN  
Tel: MAROWN (0624) 851277



### S.E.M. TRANZMATCH. Now has wider range on 160M

THE BEST aerial matching system. Matches 15-5000 ohms BALANCED or UNBALANCED

Up to 1KW. Air coupled BALUN means no connection to equipment which can cure TVI both ways.

NO TOROIDS -SO239 & 4mm sockets for CO-AX, END FED or TWIN FEED 3.5-30MHz £74. 1.8-30MHz £83. EZITUNE built in £29.50 extra. (See below for our much acclaimed EZITUNE)

ALL EX-STOCK. Please note that 90% we sell have the EZITUNE option

**S.E.M. IMAGIC KEYS.** We have replaced its plastic box, with an attractive plated steel case. No better fully auto keyer anywhere. Uses Curtis chip. R.F. proof £38. A first class twin paddle 4 key £15. **Ex-stock**

**BRAID BREAKER/HI PASS FILTER.** Put in TV ant lead to cure TVI £6.50. **Ex-stock.**

**RF NOISE BRIDGE.** Adjustable 0-1,000ohms 3" x 1 1/2" x 2" only. SO239s, 1-170 MHz. Neat accurate & economical £29.50 **Ex-stock.**

**3-WAY ANTENNA SWITCH** 1Kw SO239s. Good 2metres. £15.00 **Ex-stock.** Or 4th position to earth output £17.50 **Ex-stock.**

**S.E.M. 2 METRE TRANZMATCH** 5 1/2" x 2" deep. SO239s. £24.90 **Ex-stock**

### S.E.M. EZITUNE NEW CIRCUIT

Gives MORE noise a bomb proof operation. Because no similar unit is made, its usefulness is not appreciated until you have used one. Eliminates need for S.W.R. bridge.

Clean up the bands by tuning up without transmitting. Connects in aerial lead, produces S9 + (1-170MHz) noise in receiver. Adjust A.T.U. or aerial for minimum noise. You have now put an exact 50 Ohms into your transceiver. Fully protected, you can transmit through, save your P.A. and stop QRM SO239s. 3" x 1 1/2" x 2" £34.50 **Ex-stock.** P.c.b. to fit any A.T.U. £29.50 **Ex-stock.**

### 12 MONTHS COMPLETE GUARANTEE INCLUDING ALL TRANSISTORS

Prices include VAT and delivery. C.W.O. or phone your credit card number for same day service.

\* Means Belling Lee Sockets add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders on request information on our Ansaphone at cheap-rate times.



## REGULATORS

LM317T Plastic TO220 variable.....	£1.00
LM317T Metal .....	£2.00
7812 Metal .....	£1.00
L036 TO3 Metal 12v L037 15v .....	ea 50p
7805/12/15/24 plastic .....	40p
7905/12/15/24 plastic .....	50p
CA3085 TO99 .....	50p
LM723 14 dil or TO99 .....	50p

## EPROMS

2732A 450nS .....	£2.50
2716 Ex eqpt. ....	£2.00

## POWER TRANSISTORS

2N3055 Motorola .....	50p 5/£2.00
2N3055 Ex eqpt tested .....	5/£1.00
MJE3055 .....	50p
MJE2955 equiv .....	50p

## DISPLAYS

Futaba 4 digit clock fluorescent display	
FLT-02-8 .....	£1.50
Futaba 8 digit calculator fluorescent display 9CT-01-3L .....	£1.50
LCD Clock display 0.7" digits .....	£3.00
Large Clock display 1" digits .....	£3.00
7 seg 0.3" display comm cathode .....	50p

## MISCELLANEOUS

### QUARTZ HALOGEN LAMPS

A1/216 24v 150w .....	£2.25
H1 12v 55w (car spot) .....	£1.25

### WOUND POT CORES

with adjusted unused	
RM7 LA4245 .....	3/£1.00
RM8 LA4344 .....	2/£1.00

### TOK KEY SWITCH 2 POLE 3 KEYS

ideal for car/home alarms £3...	100+ £2.00
fit AUDI/VW TR7 VOLVO .....	10/£1.00
14v 0.75w MES lamps .....	8/£1.00
Heat shrink sleeving pack .....	£1.00
PTFE sleeving pack asstd colours ..	£1.00
250 mixed res diodes, zeners .....	£1.00
Convergence pots asstd .....	10/£1.00
Mixed electrolytic caps .....	100/£2.00
ITT CASS RECORD/PLAY AMP+cct ..	£2.00

Stereo cassette deck .....	£5.00
Stereo cass R/P head .....	£2.50
Mono head £1 Erase head .....	50p
Thermal cut-out 50°C, 77°C or 85°C .....	50p
Thermal fuse 121°C 240v 15A .....	5/£1.00
sim RS 413-563 .....	

Vero pins fit 0.1" Vero .....	100/50p
Double sided PCB pins .....	100/50p
TO220 Micas + bushes 10/50p ..	100/£2.00
TO3 Micas + bushes .....	10/50p

Mains coins relays PCB mounting	
2 pole changeover .....	£1.00
3 pole changeover .....	£1.00
Varley 24v dc 2p c/o relay .....	75p
Varley 24v dc 4p c/o relay .....	80p
Fig 8 mains cassette leads .....	3/£1.00

KYNAR wire wrapping wire 2oz reel	£1.00
PTFE min screened cable .....	10m/£1.00
TOKIN MAINS RFI FILTER 250v 15A ..	£3.00
TDK MAINS RFI FILTER 115v 15A ..	£1.00

Epoxy potting compound 500g .....	£2.00
Mercury tilt switch small .....	50p
Min rotary sw 4p c/o 1/8" shaft .....	2/£1.00
Thorn 9000 TV audio o/p stage .....	2/£1.00
10m7 CERAMIC FILTER 50p .....	100/£20.00
6m CERAMIC FILTER .....	50p

240v AC FAN 4.6" SQUARE NEW .....	£5.50
-----------------------------------	-------

12v DC Brushless fan reversible 2.5" sq 2"	
deep QUIET .....	£9.00

KLIPPON terminal block EKS 12/4 12 way	
20A term block .....	3/£1.00

BELLING-LEE 12 way block L1469. 4/	£1.00
------------------------------------	-------

POTENTIOMETERS short spindle 2k5 10k	
2m5 Lin .....	5/£1.00

500k lin 500k log long spindle .....	4/£1.00
--------------------------------------	---------

555 Timers .....	5/£1.00
------------------	---------

40KHZ ULTRASONIC TRANSDUCERS	
EX-EQPT.NO DATA .....	PAIR/£1.00

## RECTIFIERS

120v 35A stud .....	40p
12FR400 12A 400v small stud .....	4/£1.50
BY127 1200V 1.2A .....	10/£1.00
1N5401 100v 3A .....	10/£1.00
BY254 800v 3A .....	8/£1.00
BY255 1300v 3A .....	6/£1.00
1A 800v bridge rectifier .....	4/£1.00
6A 100v bridge .....	50p
10A 100v bridge .....	£1.25
15A 100v bridge .....	£1.25
25A 200V bridge .....	£2.00
25A 400v bridge .....	£2.50

## SCRs

2N6399A 10A 600v .....	£1.00
BTX95 800v 15A .....	£1.20
35A 800v stud .....	£2.00
70A 500v large stud .....	£3.00
MCR106 equiv 4A 400v 40p ea ..	100/£20.00
2N5061 8A 60V TO92 4/£1.00 ..	100/£10.00
TICV10D 8A 400v TO92 3/£1.00 ..	100/£15.00

100/£15.00	
------------	--

TXAL 228 8A 400 visoltab 2/£11.00/£30.00	
--	--

25A 800v ex eqpt tested .....	£1.50
-------------------------------	-------

20A 500v isolated ex eqpt. tested ..	£1.50
--------------------------------------	-------

## CONNECTORS

'D' 9 way £1.00 15 way £1.25 25 way £2.00	
---	--

37 way £2.00 50 way £2.50	
---------------------------	--

(EX EQPT price perpair) covers 50p ea	
---------------------------------------	--

AMPHENOL (Centronics) 36 way plug +	
skt ex eqpt .....	£2.50

0.1" double sided edge connector 32 way	
ideal ZX81/SPECTRUM .....	£1.50

0.1" d/sided PCB Plug 24 + 25 way ..	£1.50
--------------------------------------	-------

2 pole sub min connectors ideal radio	
control RS 466/472/488/343 5 pairs/£2.00	

## IDC CONNECTORS

25 WAY 'D' SOCKET .....	£2.00
-------------------------	-------

20 WAY SOCKET (ORIC PRINTER) ..	£1.00
---------------------------------	-------

26 WAY SOCKET (BBC PRINTER) ..	£1.50
--------------------------------	-------

34 WAY SOCKET (BBC DISC DRIVE)	
.....	£2.00

40 WAY SOCKET .....	£2.00
---------------------	-------

50 WAY SOCKET .....	£2.50
---------------------	-------

IDC EDGE CONNECTORS D/S EX-EQPT	
34 WAY (FITS DISC DRIVE PCB) .....	£3.00
40 WAY (FITS CENTRONICS 739 PCB)	
.....	£3.00

50 WAY .....	£3.50
--------------	-------

WIRE WOUND RESISTORS 2.5W (W21 or	
sim) .....	£3.50

R10, 1R0, 2R0, 2R7, 3R9, 5R0, 4R7, 10R,	
12R, 15R, 18R, 20R, 27R, 33R, 36R 47R 100R	
120R 180R 270R 330R 390R 470R 560R 680R	
820R 1K 1K2 1K3 1K8 2K7 3K3 10K	
.....	10 FOR £1.00

W22 or sim 6 watt .....	7 for £1.00
-------------------------	-------------

R22 1R5 9R1 10R 12R 20R 33R 51R 56R 62R	
120R 180R 270R 390R 560R 620R 1K2 2K2	
3K3 3K9 10K	
W23 or sim 9 watt .....	6 for £1.00

R22 1R0 3R0 6R8 56R 62R 100R 270R 1KB	
10K	

W24 or sim 12 watt .....	4 for £1.00
--------------------------	-------------

10R 68R 75R 200R 270R 400R 620R 1K	
------------------------------------	--

## PHOTO DEVICES

Slotted opto-switch OPCOA OPB815	
.....	£1.30

2N5777 (Photo darlington) 50p 100/£26.00	
--	--

TIL81 T018 Photo transistor .....	£1.00
-----------------------------------	-------

TIL38 Infra red LED .....	2/50p
---------------------------	-------

OPI2252 Opto isolator .....	50p
-----------------------------	-----

Photo diode 50p .....	6/£2.00
-----------------------	---------

MEL12 (Photo darlington base o/c) ..	50p
--------------------------------------	-----

RPY58 LDR .....	50p
-----------------	-----

T018 LDR .....	50p
----------------	-----

LEDs RED 3mm or 5mm 12/£1.00 ..	£5/100
---------------------------------	--------

GREEN + YELLOW 3/5mm 10/£1.00	£6/100
-------------------------------	--------

FLASHING RED 5mm .....	50p
------------------------	-----

BICOLOUR RED/GREEN 5MM OR RECT	
50p .....	5/£2.00

## DIODES

1N4151 sim 1N4148 .....	100/£1.25
-------------------------	-----------

1N4148 .....	100/£1.50
--------------	-----------

1S3740 Germanium .....	100/£2.00
------------------------	-----------

1N4004 or SD4 1A 300v .....	100/£3.00
-----------------------------	-----------

1N5401 3A 100V .....	10/£1.00
----------------------	----------

BA157 1A 400V Fast Recovery ..	100/£2.50
--------------------------------	-----------

BA159 1A 1000V Fast Recovery ..	100/£3.50
---------------------------------	-----------

## MULTI TURN PRESETS

10R 20R 100R 200R 500R ..	40p
---------------------------	-----

2K 5K 22K 50K 100K 200K	
-------------------------	--

## IC SOCKETS

8 pin 12/£1.00 14 pin 10/£1.00	
--------------------------------	--

18/20 pin 7/£1.00 22/24/28 pin .....	25p
--------------------------------------	-----

## TRIMMER CAPACITORS small

Grey 1.5-6.4pF GREEN 2-22pF .....	6 for 50p
-----------------------------------	-----------

YELLOW 2-16pF	
---------------	--

SOLID STATE SWITCHES NEW 10A 250v	
AC zero voltage switching	
control voltage 8-28v DC .....	£2.00

VARIAC 0 to 270v 12A new uncased	
.....	£20.00

VARIAC 0 to 130v 6A new uncased ..	£6.00
------------------------------------	-------

## POLYESTER/POLYCARB CAPS

10n/15n ax 100/£2.00 22n radial 100/£2.50	
---	--

47n rad 100/£2.50	
-------------------	--

1u 250v Polyester C280	
5/£1.00 100/£10.00	

1u2 P/carb 15mm rad .....	100/£5.00
---------------------------	-----------

2u2 160v red 28mm .....	100/£10.00
-------------------------	------------

470n 250v AC X rated rad .....	4/£1.00
--------------------------------	---------

100N 250V AC X rated rad 20mm ..	4/£1.00
----------------------------------	---------

33n 250v AC X rated rad 15mm ..	10/£1.00
---------------------------------	----------

## BEAD THERMISTORS

GLASS BEAD NTC Res @ 20°C .....	80p
---------------------------------	-----

250R 1K2 50K 220K 1M4	
-----------------------	--

R53 THERMISTOR .....	£1.50
----------------------	-------

GLASS BEAD PTC Res @ 20°C .....	£1.00
---------------------------------	-------

## BEAD TANTALUM CAPS

47u 3V 10u 6V3 68u 6V 12/£1.00 ..	100/£6.00
-----------------------------------	-----------

## SMALL AXIAL CERAMIC CAPS 50V

15p 18p 22p 27p 33p 47p 68p 82p 470p in 10n	
(25v) .....	100/£3.00

STEPPER MOTOR 4 PHASE 2 9v	
----------------------------	--

WINDINGS .....	£4.50
----------------	-------

# KEYTRONICS

332 LEY STREET, ILFORD, ESSEX

Shop open Mon-Sat 10am-2pm

TELEPHONE: 01-553 1863

MIN ORDER £2.50 OFFICIAL ORDERS WELCOME  
UNIVERSITIES · COLLEGES · SCHOOLS · GOVT DEPARTMENTS  
P&P AS SHOWN IN BRACKETS (HEAVY ITEMS)  
50p OTHERWISE (LIGHT ITEMS)

**ADD 15% VAT TO TOTAL**

**ELECTRONIC COMPONENTS BOUGHT FOR CASH**







# South Midlands

★FREE FINANCE ● 2 YEAR GUARANTEE

Branches at SOUTHAMPTON, LEEDS, CHESTER

## TIRED OF THE QRM AND LACK OPERATING SPACE ON 2M?

Then QSY to 70cm and begin to enjoy your hobby again after all 70cm is 10MHz wide in most of the UK, that's plenty of room for all to enjoy their favourite mode.

In order to help promote further activity on 70cm we have been able to reduce prices of many of Yaesu's UHF transceivers. This has been possible due to SMC's bulk purchasing from Yaesu together with reduced production costs at the factory due to increasing demand on the Japanese home market since the introduction of UHF repeaters in Japan.


Check out the prices of Yaesu's UHF Transceivers against other manufacturers models and you will probably agree Yaesu leads the way to 70cm.

Just consider with lower equipment costs than equivalent 2M transceivers, a larger number of UHF repeaters in the UK per amateur population than anywhere else worldwide and remember 70cm antennas because of their smaller size and similarity to TV antennas make them far more environmentally acceptable than 2M long Yagis.

\*Need we say more except see you on 70cms!!!



**FT708R**  
Now only  
£179 inc

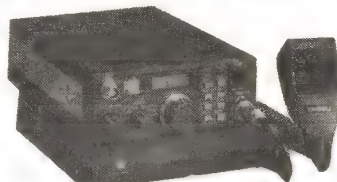

shown with FL7010  
optional amplifier

**FT790R**  
Now only  
£249 inc



**FT730R**  
Now only  
£229 inc

### COAXIAL FEEDERS

Don't throw away those valuable watts by using a poor quality feeder. Remember approximately 20M of UR67 will have an approximate attenuator of 3dB at 432MHz. This means if you invest around £250 for a 100W PA you will only end up with about 50W at the antenna.

UR67	att 3.9dB per 25M approx.....	£0.69 p/m	
Pope H100	att 2.25dB per 25M approx.....	£0.79 p/m	
*Eupen 5121	att 1.4dB per 25M approx.....	£2.93 p/m	NEW
*Andrews LDF2.50	att 1.9dB per 25M approx.....	£3.00 p/m	
*Andrews LDF4.50	att 1.3dB per 25M approx.....	£3.58 p/m	

\*Helical Foam-Dielectric cables

Carriage on cables £2.40 up to 20M over 20M ..... £3.20


70cm ANTENNAS	
D8/70	8 over 8 Yagi ..... £25.87
PBM18/70	18 ele Parabeam ..... £32.20
PBM24/70	24 ele Parabeam ..... £44.55
LW24/70	24 ele Yagi..... £27.02
MBM28/70	28 ele Multibeam..... £21.27
MDB48/70	48 ele Multibeam..... £35.65
MBM88/70	88 ele Multibeam..... £48.87
8XY/70	8 ele crossed Yagi..... £42.55
12XY/70	12 ele crossed Yagi..... £52.90
SMCGP432X	3x3/4 wave colinear..... £32.20
SMCGP714	14 step coaxial colinear 10DBI..... £78.60
SMC70N2V	2/70cm Colinear..... £32.20

NEW

Carriage on antennas..... £2.65
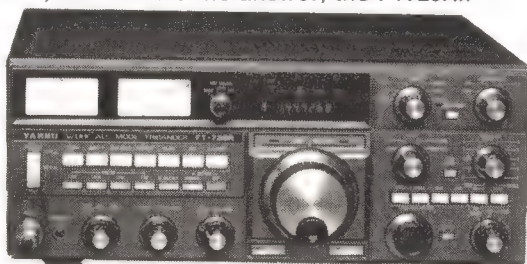
## Looking for a Satellite Transceiver System?

Those clever men at Yaesu have put together your total satellite transceiver requirements in one package. If you are interested in the RS satellite with 2M to 10M transponders, the answer is FT726R + HF module and satellite unit, or if you want to use Oscar 10 with 70cms to 2M transponder, the answer is FT726R + 70cms module and satellite unit. You can even use the FT726R with the mode L transponder on Oscar 10. However in this case the FT726R does require a little help from Microwave Modules and their MMX1268/144. For mode L the answer is FT726R + 70cms module, satellite unit and MMX1268/144 on all the above combinations, full duplex is possible when the satellite unit is fitted to the FT726R. So look no further, Yaesu have the answer, the FT726R!!



FT726R (2)	Transceiver c/w 2M .....	£739.00 inc
FT726R	Transceiver Main frame .....	£589.00 inc
21/24/28	HF Module.....	£200.00 inc
50/726	6M Module .....	£185.00 inc
144/726	2M Module .....	£155.00 inc
430/726	70cms module.....	£250.00 inc
SAT726	Full duplex module.....	£95.00 inc
XF455MC	600 Hz CW filter .....	£39.85 inc

MMX1268/144 Satellite transmit transverter..... £135.00 inc

### SMC SERVICE

Free Securicor delivery on major equipment.  
Access or Barclaycard over the phone.  
Biggest branch agent and dealer network.  
Securicor 'B' Service contract at  
Biggest stockists of amateur equipment.  
Same day despatch whenever possible.

### FREE FINANCE

\*On many regular priced items SMC offers.  
Free Finance (on invoice balance over £120).  
20% down and the balance over 6 months or 50%  
down and the balance over a year.  
You pay no more than the cash price!!  
Further details and eligible items available on request

### GUARANTEE

Importer warranty on Yaesu Musen products.  
Able staffed and equipped Service Department.  
Daily contact with the Yaesu Musen factory.  
Tens of thousands of spares and test equipment.  
Twenty-five years of professional experience.  
2 year warranty on regular priced Yaesu products.

### SMC STOCK CARRYING AGENTS WITH DEMONSTRATION FACILITIES

Neath John GW4FO1 (0639) 52374 Day  
(0639) 2942 Eve

Bangor John  
Tandrages Mervyn

G13 KDR (0247) 55162  
G13 WWY (0762) 840656

Stourbridge Andrew G4BJY (03843) 72632



# ommunications Ltd.

— MAIN DISTRIBUTOR FACTORY BACKED

LD, BUCKLEY, STOKE, GRIMSBY, JERSEY, EDINBURGH



## FACILITIES + UNEQUALLED PERFORMANCE BY YAESU


### FT203R YAESU'S NEW COMPACT 2M HANDIE



The ultra compactness of the FT203R is due mainly to Yaesu's chip component circuit board assembly, the chip components being installed automatically by robots. The 203's features include thumbwheel frequency selection, built in S/PO meter, 2.5W RF O/P at 10.8V, (3.5W O/P with FNB4). Vox activated switching is possible when used in conjunction with YH-2. Accessories supplied include FNB3, FTE-2 tone unit, CSC6 case and YHA-14A antenna.

FT203R	2.5W transceiver.....	<b>£169.00 inc</b>
FBA5	Case for 6AA cells .....	<b>£6.50 inc</b>
FNB4	12V Nicad pack .....	<b>£36.40 inc</b>
CSC7	Soft case (when FNB4 is used).....	<b>£6.50 inc</b>
YH-2	Headset/Mic.....	<b>£13.80 inc</b>
MH-12A2b	Speaker Mic.....	<b>£16.85 inc</b>
SMC8.9AA	Charger (13A style).....	<b>£8.05 inc</b>
MMB21	Mobile Mounting bracket .....	<b>£7.65 inc</b>

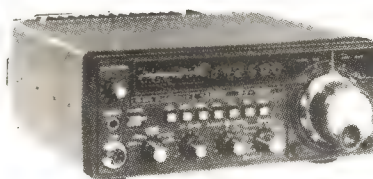
### THE BUY OF THE YEAR FT707 8 BAND HF TRANSCEIVER



~~£499.00~~  
now only  
**£425 inc**

FP707	Matching AC PSU.....	<b>£125.00 inc</b>
FV707DM	Digital VFO .....	<b>£149.00 inc</b>

### FT980

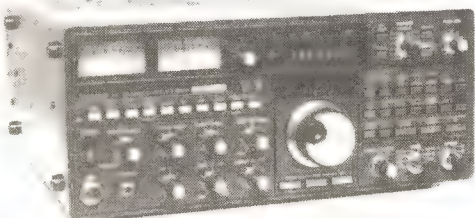


FT980	Transceiver with general coverage RX .....	<b>£1265.00 inc</b>
SP980	External L/S with audio filter .....	<b>£58.65 inc</b>
SP980P	External L/S with phone patch .....	<b>£74.85 inc</b>
FIF80	Computer interface for NEC PC8001 .....	<b>£99.65 inc</b>
FIF65	Computer interface for Apple II .....	<b>£51.35 inc</b>
FIF232c	Computer interface RS232 .....	<b>£54.80 inc</b>

### FT77



FT77	8 Band RX/TX 100w output .....	<b>£459.00 inc</b>
FT77S	8 Band RX/TX 10w output .....	<b>£425.00 inc</b>
FP700	Matching AC PSU.....	<b>£135.00 inc</b>
FC700	Matching Antenna Tuner.....	<b>£98.90 inc</b>
FV700DM	Digital VFD Unit.....	<b>£200.00 inc</b>
MKT77	Marker Unit .....	<b>£10.35 inc</b>
FMUT77	FM Unit.....	<b>£27.20 inc</b>
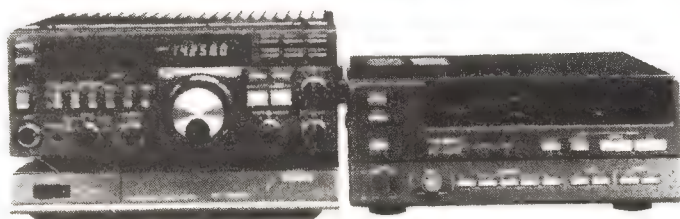
## YAESU'S LINE UP FOR '84 THE FT757 SYSTEM



FT757GX	All Modes and Filters Fitted.....	<b>£685.00 inc</b>
FP757GX	Switched Mode PSU 50% Duty .....	<b>£149.00 inc</b>
FP757HD	Heavy Duty PSU 100% Duty .....	<b>£162.50 inc</b>
FC757AT	Automatic Antenna Tuner .....	<b>£231.50 inc</b>

Frequency range 160-10m Tx general coverage Rx. 10Hz VFO steps and 500kHz band steps.  
Modes, USB, LSB, CW, AM, FM all as standard  
Power output 100W SSB, CW, AM, FM 25W carrier AM, 3rd order products - 40dB at 100W on 14MHz.  
Dynamic range better than 100dB CW(N) at 14MHz.  
Frequency stability better than  $\pm 10$ ppm after warm up.  
Dual VFO's and 8 memories with VFO/memory transfer feature allowing more flexible split frequency operation.  
Programmable memory scanning with scanstop threshold adjustable with the RF Gain control.  
All accessories installed including AM, FM, Marker, Speech processor, shift filters, 600Hz CW filter and keyer.  
New heatsink design and ducted cooling system allow 100W o/p at 100% transmitter duty cycle \*.  
Selectable semi break-in or full break-in and built in inambic keyer with dot-dash memory.  
Three microprocessors control most of the switching and adjusting functions normally done by hand and optional CAT interface unit allow further operating flexibility with an external computer.  
\* 100% duty cycle only with the FP757HD.


SOUTHAMPTON	GRIMSBY	STOKE	LEEDS	CHESTERFIELD	BUCKLEY	JERSEY	EDINBURGH
SMC Ltd 36/38 Rumbidge St Totton, Southampton Southampton (0703) 867333 9-5.30 Mon-Sat	SMC (Humbidge) 247A Freeman St Grimsby, Lincolnshire Grimsby (0742) 59388 9.30-5.30 Mon-Sat	SMC (Stoke) 76 High Street Tolke Pits, Stoke Kidsgrove (07816) 72644 9-5.30 Tue-Sat	SMC (Leeds) 257 Otley Road Leeds 16, Yorkshire Leeds (0532) 782326 9-5.30 Mon-Sat	SMC (Jack Tweedy) Ltd 102 High Street New Whittington, Chesterfield Chesterfield (0246) 453340 9-5.30 Tue-Sat	SMC (T.M.P) Unit 27 Pinfold Workshops Pinfold Lane, Buckley Buckley (0244) 549563 9.30-5.00 (Lunch 11.45) Tue-Sat	SMC (Jersey) 1 Belmont Gardens St Helier, Jersey Jersey (0534) 77067 9-5pm Mon-Sat	SMC (Scottcomm) 23 Morton Street EH15 2HN 031-457 2430 10-5.00 Tue-Fri (9-4 Sat)

Head office  
Mail orders  
Service & Spares

**S.M. HOUSE, RUMBRIDGE STREET, TOTTON, SOUTHAMPTON SO4 4DP, ENGLAND**  
Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegrams: "Aerial" Southampton  
See preceding pages for telephone numbers of Agents and above for Branches.



# GAREX (G3ZVI) SX200-N

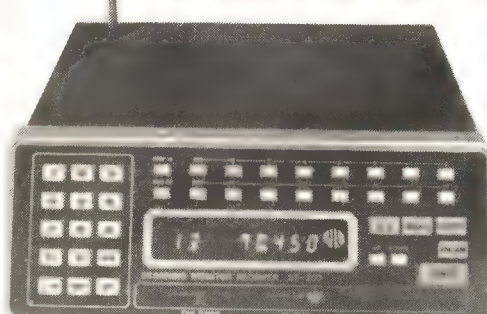

THE  
SUPERIOR  
SCANNER

## COMPARE THESE FEATURES

### THE CHOICE OF THE PROFESSIONALS

- ★ SPECIALLY DESIGNED FOR EUROPEAN MARKET
- ★ MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- ★ AM & FM ALL BANDS
- ★ WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 6m, 4m, 2m & 70cm Amateur bands
- ★ 5kHz & 12½kHz FREQUENCY INCREMENTS
- ★ 16 MEMORY CHANNELS WITH DIRECT ACCESS
- ★ 2 SPEED SCAN/SCAN DELAY CONTROL
- ★ 2 SPEED SEARCH UP AND DOWN
- ★ SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- ★ 3 SQUELCH MODES inc CARRIER & AUDIO
- ★ RELAY OUTPUT FOR Aux CONTROL
- ★ INTERNAL SPEAKER
- ★ EXTERNAL SPEAKER & TAPE OUTPUTS
- ★ LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- ★ AM-PM CLOCK DISPLAY
- ★ 12V DC, 230V AC OPERATION
- ★ 12 MONTH WARRANTY FACTORY-BACKED SPARES & 'KNOW-HOW' AND THE ALL-IMPORTANT PREDELIVERY CHECK by GAREX THE MAIN SERVICE & SALES AGENTS £299.00 inc VAT DELIVERED
- ★ EXCITING NEW RANGE OF SCANNERS AVAILABLE SOON, INCLUDING THE SX-400. SAE FOR DETAILS

### ★ REVCON ★

A superb quality 16 element, all British made, VHF/UHF broadband fixed aerial from Revco. Ideally suited to SX200 and other VHF/UHF Receivers.  
**Covers 50-500MHz PRICE £24.95 inc**

**SR-9** monitor: 2m FM with 144-146 MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed, M/P use, 12V DC operation £47.50.  
**CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B** All 2m channels from 0 (145.00) to 33 (145.825). Also 144.80, 144.825, 144.85 Raynet at £2.60 (+ 20p post per order). Over 40 popular marine channels at £3.00 (+ 20p P&P)  
**RESISTOR KITS** a top selling line for many years. E12 series, 5% carbon film, 10Ω to 1m, 61 values, general purpose rating ¼W or ½W (state which) Starter pack 5 each value (305 pieces) £3.10  
Standard pack 10 each value (610 pieces) £5.55  
Mixed pack, 5 each ¼W + ½W (610 pieces) £5.55  
Giant pack, 25 each value (1525 pieces) £13.60

SCOOP PURCHASE OF BRAND NEW PYE WESTMINSTER  
& PF-70 SERIES SPARES SAE LIST.

**PYE RADIOTELEPHONE SPARES** (SAE full list) Ex equip, fully guaranteed, Cambridge AM10 10.7MHz I.F. £3.65 2nd mixer £3.45 455KHz block filter 12½kHz £9.40 ditto 25kHz £3. 455KHz AMIF £4.95 Audio bd. £1.95

**WESTMINSTER W15/W30AM** Rx/Rf 68.88MHz or 148.174MHz £6.95 10.7MHz IF (inc. 12½kHz xtal filter) £8.25 2nd Osc £2.10 455KHz IF £5.65 455KHz block filter (12½kHz) £7.35 Squelch £1.45 Aerial relays £1.50 **PYE SPARES ARE OUR SPECIALITY COMPLETE UNITS ALSO AVAILABLE**

**GAREX FM DETECTOR** and squelch conversion for Pye R/T equipment Ready Assembled, full instructions. Tailor-made, easy-fit design, replaces existing squelch board, with minimum of modifications. For AM Cambridge £6.30; for Vanguard AM25B (Valve RX) £6.10; for Transistor Vanguard AM25T £6.95

MAIN DISTRIBUTOR OF REVCO PRODUCTS

PRICES INCLUDE UK P&P and 15% VAT



VISA

**GAREX ELECTRONICS**

7 NORVIC ROAD, MARSWORTH, TRING,  
HERTS HP23 4LS

Phone 0296 668684. Callers by appointment only

## ELECTRO — TECH CO

72 PRIMROSE HILL, HAVERHILL, SUFFOLK CB9 9LS, UK  
Tel: (0440) 61113

**TERMS:** Cash, Postal Order, Cheque. Postage — 50 pence. Goods over £15 post free — (60p extra for every heavy item). All items brand new and guaranteed. Goods normally sent within 24hrs, unless out of stock. Orders welcomed from clubs, schools, colleges etc. **PRICES ARE INCLUSIVE OF A 5% DISCOUNT FOR A LIMITED PERIOD ONLY, so order soon.** No VAT on Export, Catalogue 20p, SAE for free lists. Phone for appointments.

<b>Transistors</b> AC127 22p AC128 31p AC141 37p AC142 33p AC176 27p AD149 88p AD161 44p AF127 80p BC107 12p BC108 12p BC109 12p BC142 28p BC143 28p BC149 10p BC159 9p BC182L 8p BC184L 8p BC212L 11p BC213L 11p BC214L 9p BC307 10p BC327 15p BC337 15p BC441 37p BC478 33p BC183L 11p BD115 61p BD131 39p BD135 44p ED136 33p BD244B 30p BF259 39p BU205 176p BU208 187p	<b>BCY70 20p</b> <b>BCY71 20p</b> <b>BFY50 25p</b> <b>BFY51 22p</b> <b>BFY52 25p</b> <b>BFY53 25p</b> <b>BRY39 47p</b> <b>MJE340 55p</b> <b>TIP31A 38p</b> <b>TIP32A 38p</b> <b>TIP41A 49p</b> <b>TIP42A 49p</b> <b>TIP2955 66p</b> <b>TIP3055 59p</b> <b>ZTX300 15p</b> <b>ZTX500 15p</b> <b>MPF102 44p</b> <b>SK88 90p</b> <b>2N697 23p</b> <b>2N222A22p</b> <b>2N2646 49p</b> <b>2N2905 23p</b> <b>2N2905A 23p</b> <b>2N3053 25p</b> <b>2N3054 60p</b> <b>2N3055 45p</b> <b>2N6027 32p</b> <b>2N3703 10p</b> <b>2N3705 10p</b> <b>2N3773 214p</b> <b>2N3819 25p</b> <b>2N3920 44p</b> <b>2N3904 11p</b> <b>2N3906 11p</b> <b>2N5457 39p</b>	<b>Main Transistors</b> 9-0-9 1 Amp 297p 12- 0-12 1 Amp 352p —AnMax Soldering CS 17 Watt 544p XS 25 Watt 575p C 15 Watt 535p Spare tips 85p IC Desolder bit XS 270p ST4 Iron stand with sponge 190p Hook and finger protector CS, XS 15p Sponge for ST4 30p Solder 5 core size 12 18SWG 400p. Desold- ering Pump 625p Spare nozzle 77p	<b>0.2 LED's</b> Led Red 8p Led green 11p Led yellow 11p Clips 4p each ORP 12 90p MEL 111 NPN photo darlington cost 35p each	<b>Bridge Rectifiers</b> 1 Amp 50v 20p 1 Amp 100v 20p 1 Amp 200v 25p 2 Amp 50v 33p 2 Amp 100v 35p 2 Amp 200v 44p 5 Amp 220v 90p 6 Amp 440v 109p	<b>Chokes</b> High Q Ferrite Cored 2.5 mh 58p 5 mh 64p 7.5mh 64p 10 mh 65p 1.5 mh 58p 5 mh 65p Trimmer Capacitor compres- sion. Type 3-40pf 33p Type 50-450pf 34p RG 58 50ohms 25p/yd DRR2 High gain dual range coil 1, 2, IC receivers, build your own. Cost 190p	<b>SCR</b> C1060 33p 10 Amp 400v 90p 16 Amp 100v 110p 1 Amp 50v 65p 1 Amp 200v 75p	<b>Triacs</b> 2 Amp 400v 80p 4 Amp 400v 82p 8 Amp 600v 110p 10 Amp 400v 140p	<b>Capacitors</b> Electrolytic, suitable PCB 16v Radial 10, 22mf 7p 47, 100mf 9p 470mf 13p 1000mf 31p 2200mf 41p 35v Radial 4.7mf 10p 100mf 18p 22mf 23p 470mf 33p 1000mf 50p 2200mf 82p 63v Range 22mf 9p 4.7mf 9p 10mf 9p 22mf 10p 33mf 11p 47mf 12p 100mf 20p 220mf 23p 470mf 35p 63v Range Axial 0.47mf, 1, 2.2, 4.7mf 9p, 10mf 10p 22mf 17p 1000mf 85p 2200 mf 169p 470mf 50v axial 37p 1000mf 25v axial 30p 4700mf 63v tag can 263p Clip for above 10p
---	--	--	--	---	--	---	--	--

**INS 8080A 8 bit microprocessor 244p.** TDA 1022 550p, ZN 414 90p, LM 3909 83p, CA 3140 40p.  
Heat sinks, Aluminium boxes, knobs, insulators, tools, plugs, computer sockets and plugs,  
ribbon cable, capacitors etc, listed in our catalogue and price lists.

## RADIO AND ELECTRONICS WORLD

Printed Circuit Boards from Edwardschild Ltd

<b>Dec 83</b>	<b>Jan 84 cont</b>
SL6440 mixer.....£2.25	Zener diode checker.....£0.99
Continuity tester.....£0.99	REW Bichron IIB.....£4.55
4001/4011 tester.....£0.99	<b>Feb 84</b>
SL6270 Data Brief.....£0.99	Real time clock.....£2.45
<b>Jan 84</b>	NiCad charger.....£1.65
FAX receiver.....£4.65	Step attenuator.....£1.30
FAX processor.....£4.35	Crowbar protection.....£0.99
8211.....£0.99	<b>March 84</b>
7665.....£10.99	LM380 Audio amplifier.....£0.99
Capacitance meter ctrl.....£3.85	<b>April 84</b>
Capacitance meter disp.....£1.40	10.7MHz oscillator.....£0.99
Cymar Q meter.....£2.65	455KHz oscillator.....£0.99

All prices are inclusive of postage, packing etc

**EDWARDSCHILD LTD,**

453a Becontree Ave, Dagenham, Essex RM8 3UL

# ALARMS

FREE CATALOGUE!  
Our Great New Illustrated Catalogue is packed with  
information on superb quality, professional burglar  
alarm equipment.

IT TELLS YOU ALL YOU NEED TO KNOW!  
TRADE ENQUIRIES WELCOME

NO CHARGE FOR POST & PACKING. SEND SAE OR TELEPHONE  
NOW FOR YOUR FREE COPY!

**A. D. ELECTRONICS**  
SECURITY MANUFACTURERS

217 Warbreck Moor, Aintree, Liverpool L9 0HU  
Tel: 051-523 8440




Dept  
REW





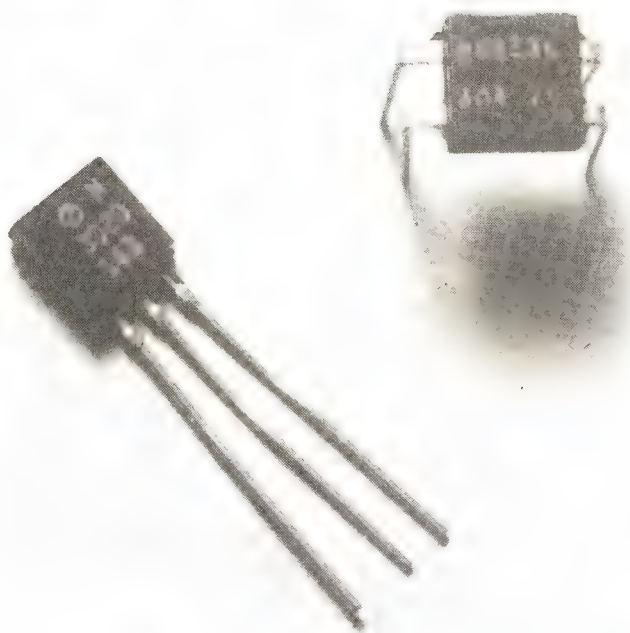
# HALL EFFECT DEVICES


**James Dick  
takes a look  
at two  
devices  
which exploit  
magnetism's  
effect on  
conductors.**



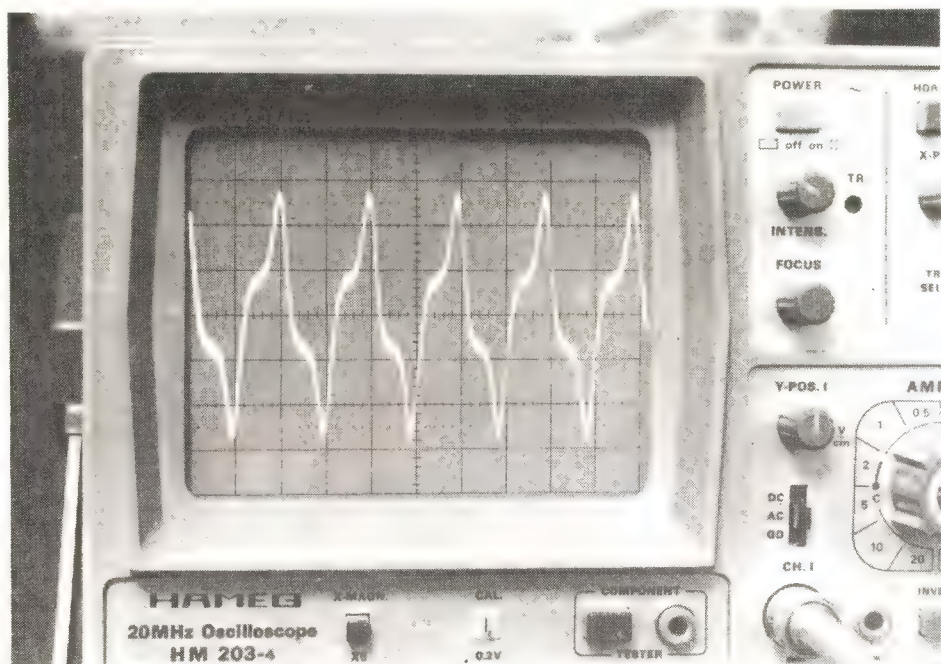*The Sprague 3020 and 634552 Hall effect devices*



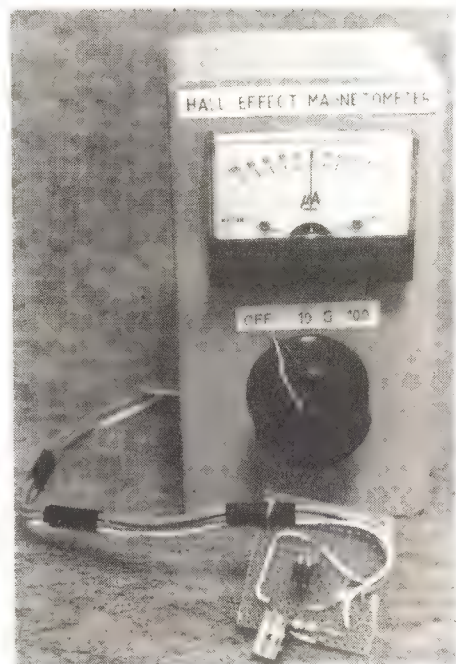*Oscilloscope trace of signal obtained from placing sensor in magnetic field of small transformer*



*Hall effect Magnetometer with sensor mounted on bare board in front of main unit*

The early 19th century saw the discovery of the magnetic effects of electric current by Oersted in Copenhagen; the Professor had noticed how a nearby electric current affected a magnetic compass.

Faraday, some ten years later, discovered that not only did an electric current produce a magnetic field but that a changing magnetic field would induce a current in a conductor – this interaction between magnetism and electricity is

now known as electro-magnetic induction.

Perhaps its most important use today is in the generation of electricity; power stations have developed almost unbelievably since Edison's first station (circa 1880) which supplied a handful of consumers in New York.

## **The Hall effect**

One of the consequences of the interplay between magnetism and


electricity is that placing a current-carrying conductor in a magnetic field causes it to experience a force; the electric motor relies on this phenomenon to turn its rotor. Because the current is the net effect of a large number of moving electrons, it is reasonable to assume that force experienced by the conductor is the result of the sum of the forces undergone by the electrons – and so each electron is subjected to an individual force. The



# NEW IDEA

**PERSONAL COMMUNICATIONS**

**OPEN MON-SAT 10am-7pm  
SUN 11am-2pm**

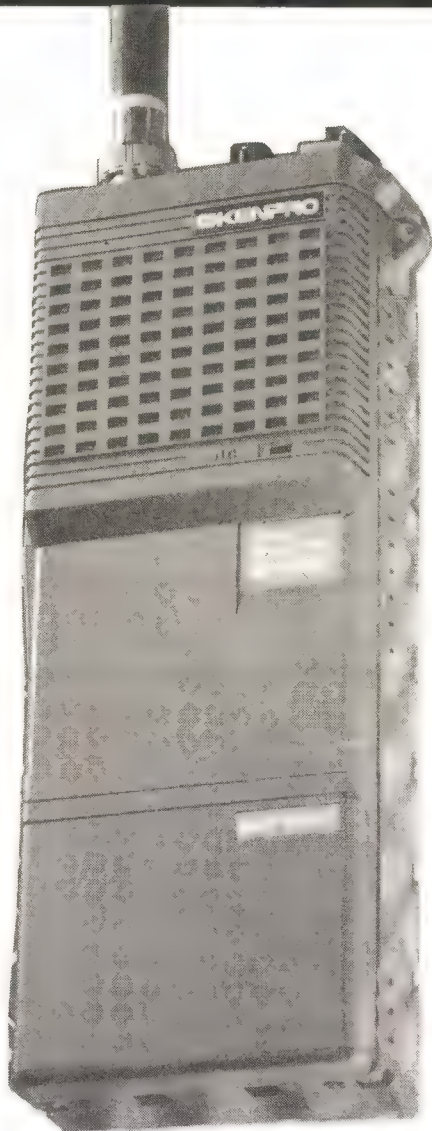

## KENDY

### NEW APPEARANCE 2M FM HANDHELD ITS CALLED KENDY KT200E

- ★ Small size and light weight synthesised 800 channel.
- ★ Desired frequency can be selected by thumb wheel switch.
- ★ Transmitting output power can be changed in two steps of High (1.5W) or Low (150mW)
- ★ Good for fluctuation of power voltage, and can operate within 5.5V (min) 12v (max)

**PRICE £159.00**

ACCESS. VISA. INSTANT FINANCE. WITH CALL SIGN FOR CALLERS AT THE SHOP.

### NEW RANGE OF SUN ANTENNA

Mobile 2m KG-5 3db $\frac{1}{2}\lambda$ .....	<b>£12.90</b>
Mobile 2m KG.209 SE2 $\frac{7}{8}\lambda$ 4.6db .....	<b>£19.90</b>
Base 2m KG.144-GP3 $\frac{5}{8} + \frac{5}{8} + \frac{5}{8}$ 7.8db .....	<b>£29.00</b>

### FULL AUTOMATIC ANTENNA ROTATOR

- ★ Vertical load 50Kg
- ★ Mast size 22-40mm diameter
- ★ Stationary Braking Torque: 1000 Kg-cur Min.
- ★ Rotation 360° — with mechanical stop.
- ★ Drive motor voltage AC 24V.
- ★ Wind Load Area 0.25m<sup>2</sup>.
- ★ Rotation torque: 200 Kg cm min.
- ★ Rotation Time 50Hz — 70° seconds.

**PRICE £39.90**

### SPECIAL OFFERS

HAM-MASTER 2025 2m FM mobile .....	<b>£179</b>
TOTSUKO 2m SSB 1w and 10w PEP .....	<b>£115</b>
RADIO PRODUCTS RTTY INTERFACE FOR 80V mechanical printers or 5v TTL computers .....	<b>£79</b>

PLUGS, CONNECTORS, CABLE, POLES, ROTORS, FERRITE RING. ALWAYS IN STOCK. H100 CO-AX.

REPAIRS & SERVICE CARRIED OUT ON ANY RADIO EQUIPMENT. 10m conversions carried out.

SURPLUS AMATEUR RADIO EQUIPMENT BOUGHT FOR CASH ANYTHING CONSIDERED WORKING OR FAULTY. BEST PRICES PAID.

Full range of  
OSKERBLOCK  
SWR  
BRIDGES.  
PRO-TEL  
ALINCO  
B.N.O.S.  
TONNA.

**NEW IDEA LIMITED**  
**PERSONAL RADIO COMMUNICATIONS**  
**133 FLAXLEY ROAD, STECHFORD**  
**BIRMINGHAM B33 9HQ**  
**021-784 3129**

Full range of Hi-  
Mould Keys.  
Lots of cheap  
2m Antennas.  
Slim Jim folded  
Di Pole HB9CY  
3 element  
70cms 2m Co-  
linear Lasling  
Kits Wall  
Brackets.



# HALL EFFECT DEVICES

result of the force on each electron manifests itself as a migration of the electrons to one side of the conductor. The surplus density of electrons on one side creates a potential difference across the sides of the current-carrying conductor when it is in a magnetic field. The phenomenon was discovered in 1879 by E H Hall, after whom it is named.

Figure 1 shows what happens. The force on the electrons acts orthogonally to the direction of the current and the magnetic field – so it pushes them to one of the side walls of the conductor. The charge builds up until the electrostatic force acting on like-sign carriers balances the magnetic force.

The magnitude of the Hall voltage is given by the expression:

$$V_{\text{Hall}} = \frac{BI}{nQW}$$

where B is the magnetic field, I the current, Q the electron's charge, n the density of charge carriers, and W, the width of the conductor.

## Unit of flux density

For a given size of conductor, the Hall voltage can be optimised by increasing the current carried and minimising the density of charge carriers. Semiconductors are preferred because the carrier density is low – although high enough to allow suitable currents to be passed. While the Hall voltage is created by electrons in conductors, the dominant charge carrier may be positive or negative in semiconductors (depending on the semiconductor type) and hence the potential is signed accordingly. Typically, a small volume of semiconductor will generate a millivolt or so with a few milliamps of current per Gauss; conductors carrying a few amps only produce a few microvolts.

The Gauss is a convenient unit of magnetic flux density – the Earth's magnetic field is approximately 0.5 Gauss. Magnets around the home may have field strengths of several hundred Gauss. Perhaps the strongest fields are those around pulsars where incredibly high densities of matter support fields of one million million Gauss which are believed to cause electron-positron annihilation – one hypothesised source for the pulsar's electromagnetic emissions.

## Devices

The Hall voltage may be measured by connecting wires onto the sides of the (semi-)conductor. Once brought outside the source, it may be processed as required. There are two common device types which use the Hall effect. The first is the magnetic switch, typified by the Sprague 3020 – a low-cost digital switch whose interior is shown schematically in Figure 2.

The sensor, amplifier, and Schmitt

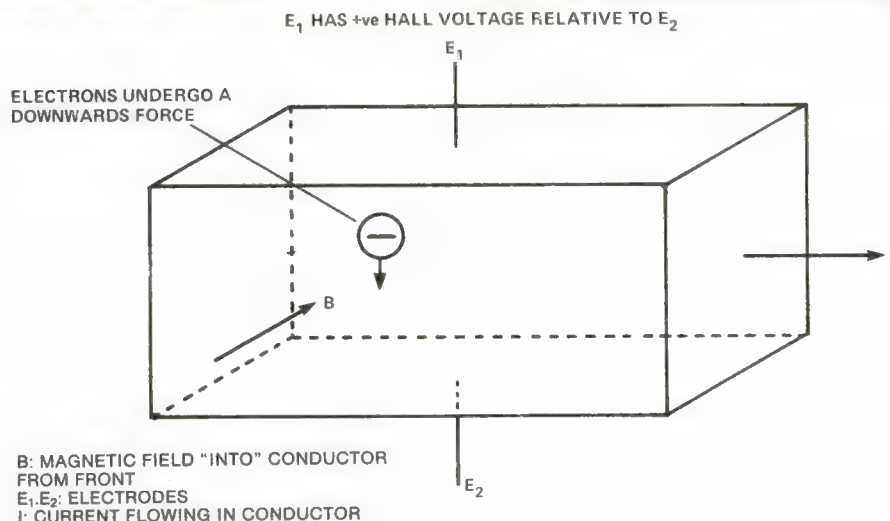


Fig 1 Schematic of Hall effect on current-carrying conductor

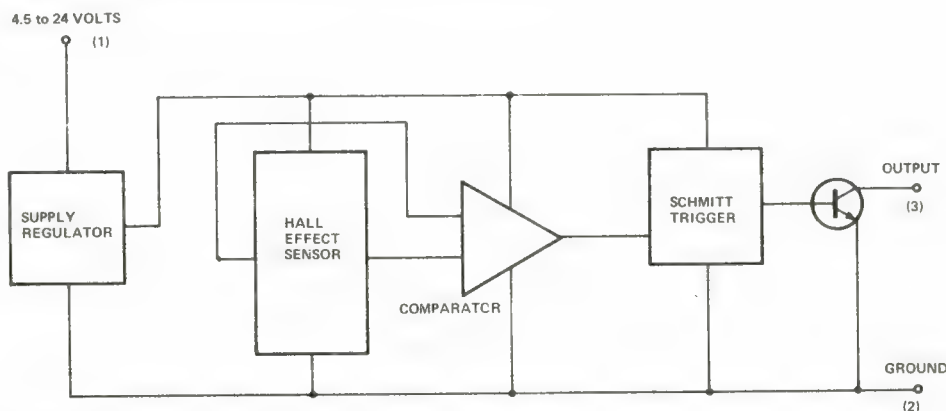


Fig 2 Schematic of Sprague 3020-type Hall effect switch


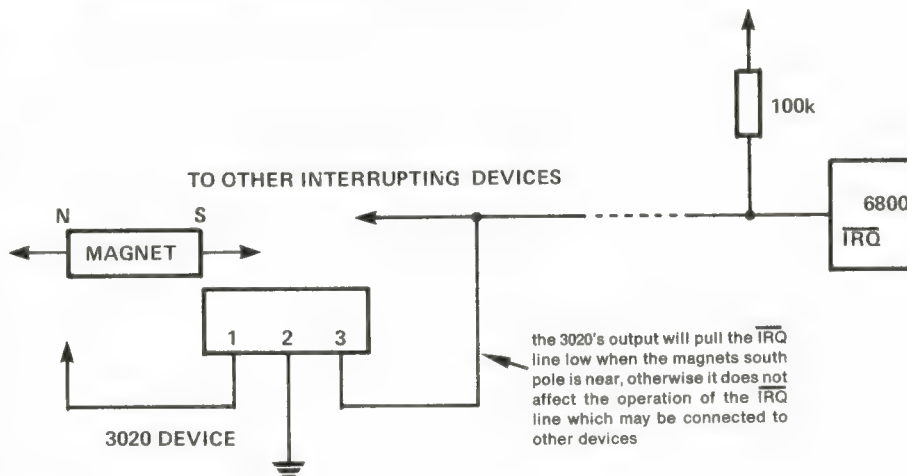


Fig 3 Using the 3020's open-collector output to drive a 6800 microprocessor's  $\overline{\text{IRQ}}$  line

trigger are supplied via a voltage regulator to stabilise the switch against changes in supply potential. The amplifier magnifies the potential difference across the sensor and passes the amplified voltage to the trigger circuit to clean-up the level to digital '1' or '0' standards. The output is an open-collector transistor which is used as a current sink – simplifying connection to a bus, for instance. Figure 3 shows a typical application.

By fabricating the various sections on a monolithic structure the good matching of components obtained allows operation over a wide range of temperatures. The magnetic field required to operate the switch is (approx) 200 Gauss, with a hysteresis of a few tens of Gauss to prevent erroneous switching when the field strength is near the critical value. The Hall effect is sensitive to the polarity of the field, so it is important to use the correct 'end' of the magnet – with this

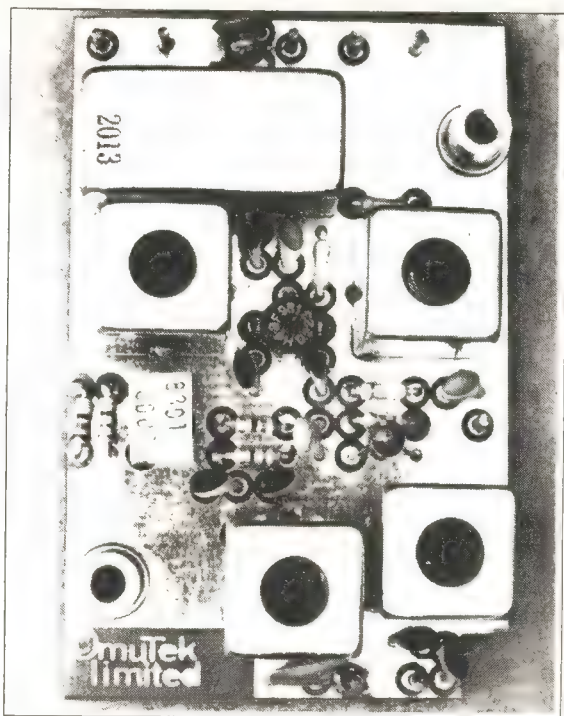



## **SLNA 145sb preamplifier for Yaesu's FT290 transceiver.**

**£27.40 + £1.20  
p&p inc VAT**

Why is it that in a little over a year muTek's SLNA 145sb preamplifier for the FT290 has been a hit on such a big scale?

The answer isn't really obvious. Good engineering often isn't. But that IS the answer: good engineering. But why is it that muTek products work so well? You see there's an awful lot more to good engineering than merely finding the 'right' transistor for example. There's a lot more to it even than the extensive use of computer-aided systems analysis and design techniques, or the use of quality components and printed circuit boards. There's experience, and that's one item that's always in stock at muTek. Experience in the design of everything from synthesised uhf signal generators, to downconverters for microwave pay-tv systems, to antenna test equipment. Lessons learnt in such projects benefit our amateur radio customers today. There's another thing too — backup. How many people do you know who've paid for factory service or repair of their muTek products, in or out of guarantee? We care! What about reliability? That's simple — we couldn't afford to offer such deep support if we had reliability problems!! Delivery? We've had problems in the past, and we've admitted it! However, these problems are now receding into history, and we are now usually able to supply most of our range if not from stock, then within a few days.

We enjoy making amateur radio equipment: it's an extraordinary challenge to do it well. We may make equipment for radio amateurs, but we're anything but amateur in our attitudes to our work!


**muTek limited — the rf technology company**

Dept RW, Bradworthy, Holsworthy, Devon EX22 7TU (040924) 543





# HALL EFFECT DEVICES

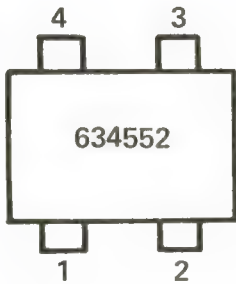

PIN	FUNCTION
1	GROUND
2	} HALL VOLTAGE OUTPUTS
3	
4	POSITIVE SUPPLY

Fig 4 634552 pin-out

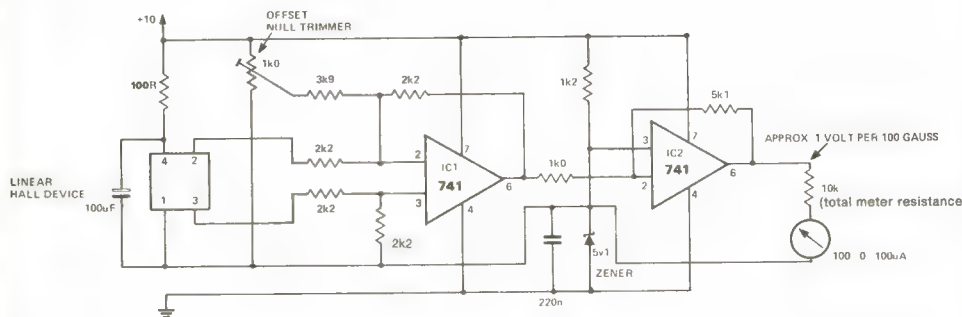


Fig 5 Simple DC amplifier for use with the 634552 device

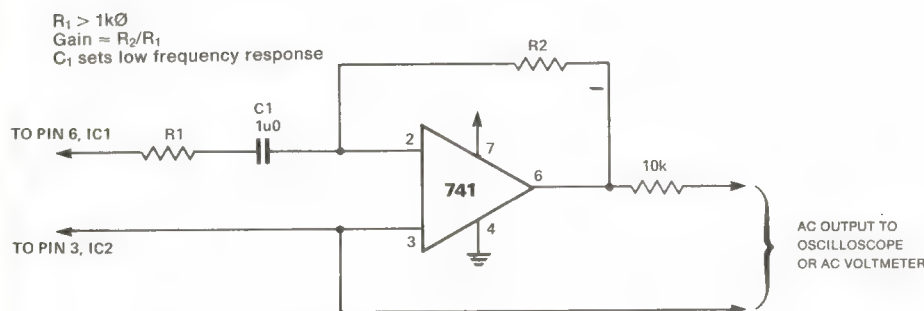


Fig 6 AC amplifier for oscillating fields

device, as the South pole of the magnet approaches the sensor, the output transistor is switched on.

The other type of sensor allows the user to have access to the Hall voltage. The 634SS2, available from Maplin, RS Components, and other suppliers, has the pin-out shown in Figure 4. Two supply connections are used to provide the basic current from which the Hall effect is derived, and two signal connections allow extraction of the Hall voltage – one

output increases by approximately one millivolt per Gauss while the other decreases. The exact potential developed is dependent on the supply voltage and load on the outputs. The device is reasonably linear over a range of -400 to +400 Gauss. Note that the potential between the outputs is not zero for a zero magnetic field; offsets in Hall devices can easily be caused by the non-alignment of the Hall voltage taps on the sensing semiconductor.

## Measurements

A simple circuit to measure the output is shown in Figure 5. The sensor is placed on a remote board to allow movement of the sensor – a calibration coil may also be attached to this board, and its construction is described later. Audio coaxial cable carries the transducer's output to the straightforward DC amplifier circuit. IC1 is a DC-coupled differential amplifier which nulls most of the bias voltage on the outputs; a potentiometer, VR1, is used to remove the remaining bias between the inputs which is present even when there is no external magnetic field. IC2 acts as a simple DC amplifier to multiply the residual signal from IC1. If only alternating magnetic fields were of interest, IC2 and its associated components could be replaced by the AC equivalent shown in Figure 6 with output to an oscilloscope.

The range of magnetic fields that can be measured (as calculated from the manufacturer's data) is 1 to 500 Gauss (approx). Because it is difficult to calibrate the instrument, the readings are best interpreted as a guide to the field strength – use of the probe shows how rapidly the magnetic flux from a simple bar magnet decreases with distance from the magnet; comparing the flux density at the transducer caused by a magnet physically touching the plastic package and that of a magnet with a package-magnet distance of 1mm, shows a 25% drop.

The Hall effect sensor and its circuit shown in Figure 5 may be roughly calibrated by passing a known current through a coil as shown in Figure 7. The magnetic field at the centre of a scramble-wound coil of minimal length may be shown to be

$$B = \frac{CNI}{R} \text{ Gauss}$$

where N is the number of turns in the coil, i is the current, R is the radius of the coil, and C is a constant of value  $6.282 \times 10^{-7}$ . (MKS system of units)


A current of 25mA in a coil of 1cm radius should produce a field of 5 Gauss; as shown by the equation, the field scales directly with the current. Note that in order to achieve the correct coil geometry, fine wire (42 swg) should be used for the 250 turns used as the N in the above equation.

## Applications


The Hall effect has found its uses in diverse situations. Perhaps the most common use is in keyboard switches. Normal conductive switches use the downward motion of the key to rub two contacts together, or flex a metallic dome onto another connector. With a magnetic switch, the key motion moves a small permanent magnet towards a Hall effect switch, like the 3020 described earlier. When the flux reaches a critical value, the electrical output is activated –



# HALL EFFECT DEVICES

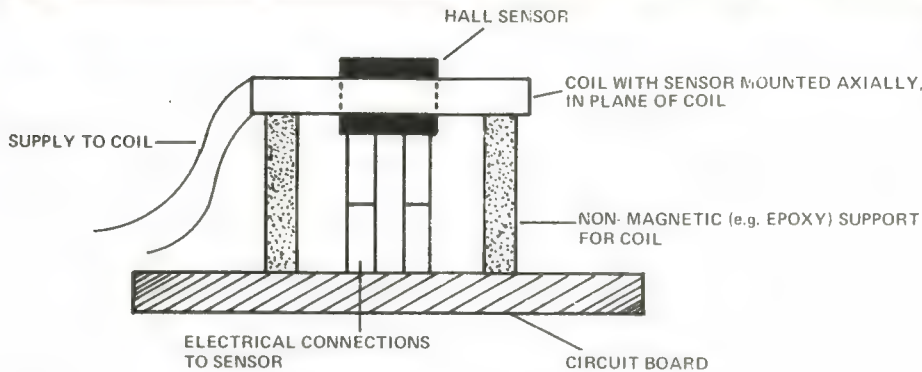

**Fig 7** Location of coil and sensor

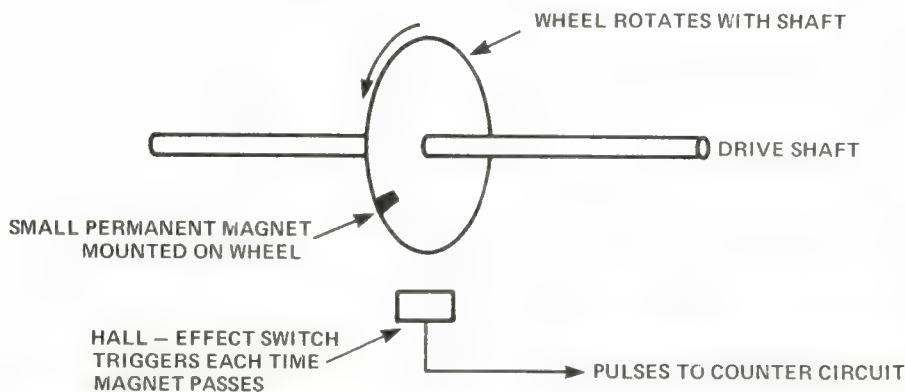

**Fig 8** Simple revolution counter

owing to the sensor's hysteresis, there is seldom any problem with bounce.

Because there is no physical switching, there is no danger of a spark (however small) being generated. Hence, Hall effect devices may be used in hazardous environments where a spark could cause an explosion or where the environment may severely corrode any metallic switch contacts.

Linear and rotational motion can be sensed by placing a small permanent magnet on the moving object and siting the Hall effect switch in the object's path as required. *Figure 8* shows how a revolution recorder may be made. There are many situations (in photographic equipment and astronomical instruments, for instance) where light in the visible or infrared parts of the spectrum cannot be tolerated – again the Hall effect switch makes a suitable alternative to the optical encoder or opto-interrupter whose light might stray.

Commercial magnetometers based on Hall devices typically cover field strengths from a few Gauss to a few tens of kilogauss with accuracies round the few per cent level. The Hall effect may seem an ideal method to use – but the flip-coil is still important. This has the advantage of being based on fundamental physical principles – a moving coil in a magnetic field can have its roots traced back to Faraday.



## Northern Amateur Radio Societies Association

The Association is holding its 22nd Annual Radio/Electronics Exhibition at Pontins Holiday Village, Ainsdale, Southport, on Saturday 7th April and Sunday 8th April 1984, opening at 11.00am each day.

It will include inter-club quiz, construction contest, grand raffle, RSGB book stall, amateur computers, NARSA stands and trophy, a demonstration station, and Trade Stands featuring all types of radio/electronic equipment. Bring-Buy Stand.

Admission will be £1 per day, but lots of 20 or more tickets may be booked in advance from Mike Bainbridge G4G5Y, 7 Rothbury Close, Bury BL8 2TT at a 20% discount by sending the appropriate cash and SAE.

Chalets may be booked direct from Pontins 0704 77165 and range from £11 + VAT (2 persons) to £31 + VAT (6 persons).

Bar and Restaurant facilities will be available during the day while the Restaurant will be open for breakfasts and from 1700 to 1900 on the Saturday evening. There will be evening entertainment limited by the capacity of the entertainment hall. Children's play areas will be available during the days.

Car parking will be available at a small charge but please follow all instructions of attendants to avoid congestion.

Talk in will be available on S22 or other available simplex channels.

Come along and enjoy yourself at this family weekend exhibition and make it a great success.

# ALYNTRONICS

(0632)  
761002

APPROVED  
DEALER

(0632)  
761002




YAESU




FT-980



FT-726R

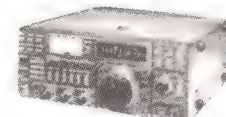

IC-271

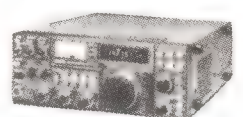

IC-751

AUTHORISED DEALERS FOR ALL ITEMS STOCKED  
ICOM, YAESU, KDK, TONNA, DATONG, MICROWAVE  
MODULES, WELTZ SHURE  
HANSEN, KENPRO, C.D.E., DAIWA, TONO HY-GAIN,  
A.E.A., T.A.L., G-WHIP  
A.K.D., HI-MOUND, SMC ANTENNAS, WESTERN  
ANTENNAS

**Comprehensive stock of plugs — sockets — antenna  
mounting Hardware R-F. Cables Rotator control  
cables,**

**Mail Orders Welcome  
129 Chillingham Road  
Newcastle-upon-Tyne**



**Open Tues-Sat 10am to 6pm**



# COMPUTER WAREHOUSE

1000's OF  
BARGAINS  
FOR CALLERS

## THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

### HARD DISK DRIVES

Fully refurbished DIABLO/DRE series 30 2.5 Mb disk drives.  
DEC RK05, NOVA, TEXAS compatible.  
Front load. Free stand or rack mount **£350.00**  
Exchangeable type (via lid removal) **£295.00**  
me3029 PSU unit for 2 drives **£125.00**  
DIABLO/DRE 44-4000A/B 5+5 ex stock from **£995.00**  
1000's of spares for S30, 4000, 3200, HAWK ex stock.  
Plus in house repair, refurbishing service.  
Call for details or quotation.

### HOT LINE DATA BASE

## DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base.  
1000's of stock items and one off bargains.  
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit  
word, no parity.

01-679 1888

### MAINS FILTERS

Cure those unnerving hang ups and data glitches caused  
by mains interference.  
SD5A as recommended by ZX81 news letter, matchbox  
size up to 1000 watt load **£5.95**  
L2127 compact completely cased unit with 3 pin fitted  
socket. Up to 750 watts **£9.99**

### COMPUTER 'CAB'

All in one quality computer  
cabinet with integral switched  
mode PSU, Mains filtering, and twin fan cooling.  
Originally made for the famous DEC PDP8 computer  
system costing thousands of pounds. Made to run 24  
hours per day the PSU is fully screened and will deliver a  
massive +5v DC at 17 amps, +15v DC at 1 amp and -15v  
DC at 5 amps. The complete unit is fully enclosed with  
removable top lid, filtering, trip switch, 'Power' and 'Run'  
LEDs mounted on All front panel, rear cable entries, etc.  
etc. Units are in good but used condition - supplied for  
240v operation complete with full circuit and tech. man.  
Give your system that professional finish for only  
£49.95 + Carr. Dim. 19" wide 16" deep 10.5" high.  
Useable area 16" w 10.5" h 11.5" d.  
Also available LESS PSU, with FANS etc. Internal dim.  
19" w 16" d. 10.5" h. **£19.95**. Carriage & Insurance £9.50.

### SOLID STATE SWITCHES

Matchbox size solid state switch type IR D2402  
enables on off control of 240 V AC loads up to  
600 watts, direct from your micro etc. Fully isolated  
3-32 V DC input with zero voltage switching.  
Complete with data **£6.99** + pp  
250,000 other relays EX STOCK call for details.

### COOLING FANS

Keep your hot parts COOL and RELIABLE  
with our range of BRAND NEW professional  
cooling fans.  
ETRI 99XU01 Dim. 92 x 92 x 25 mm.  
Miniature 240 v equipment fan complete with  
finger guard. **£9.95**.  
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact  
very quiet running 240 v operation. NEW **£6.95**  
BUHLER 66.11.22. 8-16 v DC micro  
miniature reversible fan. Uses a brushless  
servo motor for extremely high air flow,  
almost silent running and guaranteed 10,000  
hr life. Measures only 62 x 62 x 22 mm.  
Current cost **£32.00**. OUR PRICE ONLY  
**£12.95** complete with data.  
MUFFIN-CENTAU standard 4" x 4" x 1.25"  
fan supplied tested EX EQUIPMENT 240 v at  
£6.25 or 110 v at £4.95 or BRAND NEW 240 v  
at £10.50. 1000's of other fans EX Stock.  
Call for Details. Post & Packing on all fans **£1.60**

### 8" WINCHESTERS

BASF 6172 23 mb 8" winchester disk  
drive. Complete unit consists of sealed  
cavity with 3 x 8" platters and CPU based  
control logic on 3 pcbs. Multiplexed i/o  
with the BASF "DISK BUS" interface is via  
a single 40 way cable. Units have been  
carefully removed from believed working  
equipment - but at the staggering price of  
ONLY **£125.00** are sold without guarantee.  
Supplied complete with 200 + page tech  
manual. Additional +5V DC, -12VDC,  
+24VDC **£65.00**  
Carriage & Ins £10.00

### SOFTY 2

The amazing SOFTY 2. The complete "toolkit"  
for the open heart software surgeon. Copies,  
Displays, Emulates ROM, RAM and EPROMS  
of the 2516, 2532 variety. Many other features  
include keyboard, UHF modulator. Cassette  
interface etc. Functions exceed capabilities of  
units costing 7 times the price! Only  
**£169.00** pp £1.95 Data sheet on request

### DATA MODEMS

Join the communications revolution with our  
range of EX TELECOM data modems. Made to  
meet most stringent spec and designed to operate  
for 24 hrs per day. Units are made to the  
CCITT tone spec. With RS232 i/o levels via  
a 25 way 'D' skt. Units are sold in a tested  
and working condition with data. Permission  
may be required for connection to PO lines.

MODEM 2B "Hackers Special" fully fledged  
up to 300 baud full duplex. ANSWER or CALL  
modes. AUTO ANSWER. Data i/o via  
standard RS232 25 way 'D' socket. Just 2 wire  
connection to comms line. Ideal networks etc.  
Complete with data, tested, ready to run at a  
NEW SUPER LOW PRICE of **ONLY £65.00** +  
VAT + Carr.

MODEM 20-1 Compact unit for use with  
MICRONET, PRESTEL or TELECOM GOLD  
etc. 2 wire direct connect. 75 baud transmit  
1200 baud receive. Data i/o via RS232 'D'  
socket. Guaranteed working with data **£49.95**  
MODEM 20-2 same as 20-1 but 75 baud  
receive 1200 baud transmit. **£130.00**

DATL 4800 sync service. RACAL type  
MPS4800 ex TELECOM good condition.  
**£295.00** + VAT.


NEW DSL2123 Multi Standard modem  
selectable V21 300-300 bps, V23 75-1200,  
V23 1200-75 full duplex. Or 1200-1200 half  
duplex modes. Full auto answer via modem or  
CPU. LED status indicators. CALL or ANS  
modes Switchable CCITT or BELL 103 &  
202. Housed in ABS case size only 2.5" x 8.5"  
x 9". **£286.00** + VAT.

For further data or details on other EX STOCK  
modems contact sales office.

Carriage on all modems £10.00 + VAT.

### SAVE £250 SUPER PRINTER SCOOP

## BRAND NEW CENTRONICS 739-2

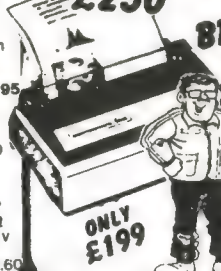

ONLY  
£199

The "Do Everything Printer" at a price that will  
NEVER be repeated. Standard CENTRONICS  
parallel interface for direct connection to BBC,  
ORIC, DRAGON etc. Superb print quality with full  
pin addressable graphics and 4 type fonts plus  
HIGH DEFINITION internal PROPORTIONAL SPACED  
MODE for WORD PROCESSOR applications. 80-132  
columns, single sheet, sprocket or roll paper handling plus  
much more. Available ONLY from DISPLAY ELECTRONICS  
at the ridiculous price of **ONLY £199.00** + VAT Complete with  
full manual etc. Limited quantity - Hurry while stocks last.  
Options. Interface cable (specify) for BBC, ORIC,  
DRAGON or CENTRONICS 36 way plg **£12.50**. Spare ribbon  
**£3.00** each. BBC graphics screen dump utility program **£8.50**.  
Carriage and Insurance **£10.00**

### GE TERMPRINTER

A massive purchase of these desk top  
printer - terminals enables us to offer you  
these quality 30 cps printers at a SUPER  
LOW PRICE against their original cost of  
over £1000. Unit comprises of full QWERTY,  
electronic keyboard and printer mech with  
print face similar to correspondence quality  
typewriter. Variable forms tractor unit  
enables full width - up to 13.5" 120 column  
paper, upper - lower case, standard RS232  
serial interface, internal vertical and  
horizontal tab settings, standard ribbon  
adjustable baud rates, quiet operation plus  
many other features. Supplied complete  
with manual. Guaranteed working **£130.00** or  
untested **£85.00**, optional floor stand **£12.50**  
Carr & Ins £10.00.

### TELETYPE ASR33

I/O TERMINALS  
FROM **£195** + CAR. + VAT  
Fully fledged industry standard ASR33 data  
terminal. Many features including ASCII  
keyboard and printer for data i/o auto data  
detect circuitry. RS232 serial interface. 110  
baud, 8 bit paper tape punch and reader for  
off line data preparation and ridiculously  
cheap and reliable data storage. Supplied in  
good condition and in working order  
Options: Floor stand **£12.50** + VAT  
KSR33 with 20ma loop interface **£125.00** +  
Sound proof enclosure **£25.00** + VAT

### PROFESSIONAL KEYBOARD OFFER


An advantageous purchase of brand new surplus allows a great QWERTY, full travel,  
chassis keyboard offer at fractions of their original costs.  
ALPHAMERIC 7204/60 full ASCII 60 key, upper, lower + control key, parallel TTL  
output plus strobe. Dim 12" x 6" x 5" + 12 DC. **£39.50**  
DEC LA36 Uncoiled keyboard with 67 quality, GOLD, normally open switches on  
standard X, Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro  
conversions etc. pcb DIM 15" x 4.5" **£34.95**  
Carriage on keyboards **£3.00**.

### SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter

BRAND NEW AT ONLY **£499** + VAT

Made to the very highest  
spec the TEC Starwriter.  
FP1500-25 features a  
heavy duty die cast  
chassis and DIABLO type  
print mechanism giving  
superb registration and  
print quality. Micro-  
processor electronics  
offer full DIABLO/QUME  
command compatibility  
and full control via CPM Wordstar etc.  
Many other features include bi directional  
printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto  
163 characters per line, friction feed rollers for single sheet or continuous paper,  
internal buffer, standard RS232 serial interface with handshake.  
Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel  
and dust cover. Order NOW or contact sales office for more information.  
Optional extras: RS232 data cable **£10.00**. Tech manual **£7.50**. Tractor feed  
**£140.00**. Spare daisy wheel **£3.00**. Carriage & Ins. (UK Mainland) **£10.00**.

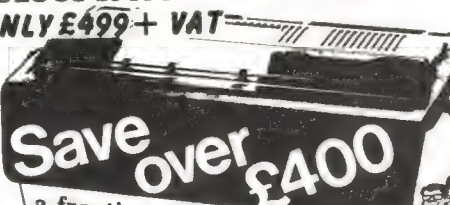

### 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible  
bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies,  
Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any  
one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A  
LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth  
at least 3 times what you pay. Unbeatable value!! Sold by weight.

2.5kls **£4.25** + pp **£1.25**  
10kls **£10.25** + pp **£2.25**

5kls **£5.90** + **£1.80**  
20 kls **£17.50** + **£4.75**

ELECTRONIC  
COMPONENTS  
EQUIPMENT

### ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit  
Card order **£10.00**. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies  
**£20.00** Where post and packing not indicated please ADD **£1.00**. + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat 10.15 - 5.30  
We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF

Telephone 01-679 4414 Telex 27924

### SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents  
include transistors, digital, linear, I.C.'s triacs,  
diodes, bridge recs, etc. etc. All devices  
guaranteed brand new full spec. with manu-  
facturer's markings, fully guaranteed,  
50+ **£2.95** 100+ **£5.15**.  
TTL 74 Series A gigantic purchase of an  
"across the board" range of 74 TTL series  
I.C.'s enables us to offer 100+ mixed  
"mostly TTL" grab bags at a price which two  
or three chips in the bag would normally  
cost to buy. Fully guaranteed all I.C.'s full  
spec. 100+ **£6.90** 200+ **£12.30** 300+ **£19.50**

### DEC CORNER

MOSTEK CRT 80E Brand new dual  
eurocard, Z80 based VT100 PLUS  
emulator with graphics etc **£999.00**  
BA11-MB 3.5" Box, PSU, LTC **£385.00**  
DLV11-J 4 x EIA interface **£310.00**  
RK05-J 2.5 Mb disk drives **£650.00**  
PDP1105 Cpu, Ram, i/o, etc. **£450.00**  
RT11 ver. 3B doc kit **£70.00**  
LA36 Decoder EIA or 20 ma **£270.00**  
KLBJA PDP 8 async i/o **£175.00**  
M8E PDP 8 Bootstrap option **£75.00**  
DILOG DQ100 RK05 LSI 4 x RK05 disk  
controller **£450.00**  
LAXX-NW LA180 RS232 serial interface  
and buffer option **£230.00**  
LAX34-AL LA34 tractor feed **£85.00**  
1000's of EX STOCK spares for DEC  
PDP8 PDP11 PDP15 & peripherals.  
Call for details. All types of Computer  
equipment and spares wanted for prompt  
CASH PAYMENT



# DISPLAY ELECTRONICS



# AMATEUR RADIO WORLD

Compiled by Arthur C Gee, G2UK

## A variety of interesting topics are presented by Dr Gee in this month's article

The British Amateur Radio Teleprinter Group (BARTG) celebrates its Silver Jubilee this year. Your scribe was a founder member of this Group and it seems incredible that twenty five years has passed since he made the first RTTY QSO's in this country with Bill Brennan, G3CQE.

Compared with the Microwave Modules Microprocessor Controlled RTTY-TV Converter – a small black box only 7 x 4½ x 2 inches in size – and its TV VDU

monitor, used by the writer now, the equipment used in those early experiments, which practically filled the shack, is nothing short of a miracle of miniaturisation.

One of the chief complaints about RTTY equipment in those early days was the noise the printer made! Nowadays, with a modern transceiver, an up to date RTTY computerised terminal unit, a VDU, a computer keyboard and a computer type printer, you can get the whole lot on

the smallest of shack benches. And if you already have a home computer, the set-up can be even smaller. And as the whole lot makes no noise whatsoever, even the xyl cannot complain on this score!

### The shuttle

Postmortems on the Shuttle amateur radio experiment continue, with the amateur radio journalists vying with one another in their attempts to describe the exercise! We will say no more than we did before – it was Bedlam! However, five British radio amateurs are officially credited with contacts. They are – G4UYL, G6DEF, G6EGY, GM8NXC and GW60JK. Our congratulations to them.

### The satellites

A new term has appeared in the satellite field, viz., the 'eclipse season'. As its name suggests, this is the period when the satellite is in the Earth's shadow for a sufficient period of time to affect its operation. The Earth's shadow is a variable feature because of its change in relationship between the earth and the sun, which of course is also responsible for our winter and summer seasons. It is even apparent on OSCAR-10, which was in an eclipse state for some weeks, but came out of it towards the beginning of January. Since then, the available solar energy has increased, so the battery state has improved. At the time of writing, OSCAR 10 has been 'turned off' from its position around its elliptical orbit (designated by the term 'Mean Anomaly' from MA 40 to MA 220, which is about one third of its orbit.

The Russian satellites too have been affected by their passage into an eclipse, as we reported previously. They should



Part of the author's amateur radio station, G2UK, showing equipment used in the first RTTY QSO's to take place in this country 25 years ago



be out of eclipse shortly, but will enter it again soon, so it will be sometime yet, before we can enjoy the good service they provided earlier.

There is a rumour that the Russians are building two more satellites of the 'RS' type, ie., they will be in a low, circular orbit, with 29 MHz to 145 MHz transponders, similar to the present ones. The expected date of launch is for 1985.

The date for the launch of the University of Surrey's second satellite is around now, and much interest is being generated by this event. We wish them a successful launch.

### Home computers

These really come into their own in the satellite field.

The 'bright boys' are coming up with all sorts of programs relating to satellites. Everything from orbital calculations to earth shadow patterns. A great variety of programs and tapes are now appearing which makes the application of this type of computer a most interesting field of activity. A recent survey of the makes of home computers used by satellite enthusiasts produced some interesting facts. ZX81's were used by 25%, 24% used the BBC Home computer, 8% used Spectrums, 2% used TRS80's and the rest 'others'.

### Top band

DX on Top Band has been good throughout the winter months, which has resulted in a considerable increase in

activity. This band is a shared band and since the increase in activity some QRM has been caused to its other users. One of these is a French coastal services station on 1820 KHz, which has complained officially about this interference. Amateur operators are asked to be particularly careful to avoid this frequency.

### Ten metres

The 10 metre band has been pretty well closed for long distance use throughout the winter but should open again soon. Before it closed some really good conditions were experienced. On one occasion, fourteen 10 metre beacons could be heard from all around the world.

### 50MHz experimental permits

The number of 50 MHz experimental transmitting licences granted by the Post Office is to be increased from the present forty to one hundred. New aspirants, and those who previously applied and were disappointed, should apply again by 31st March.

The experimental results being obtained by those using this frequency are justifying the extension of this facility. There seems to be a lot of scope still for the amateur radio enthusiast to take part in useful work in the sphere of radio wave propagation.

A good example of this is in relation to Sporadic-E propagation. Long distance communication by means of radio waves takes place because a layer of charged

particles called ions is around the earth. The layer is known as the ionosphere. It occurs in our atmosphere about 25 to 250 miles above the earth and is caused by radiation from the sun.

It can be divided into layers concentric with the earth's surface. Each layer has a maximum density in its middle, thinning out towards its edges. The thickness of the layers and their actual position above the earth are constantly changing depending on solar activity, time of the day and night, and so on. The lowest layer is called the 'D' layer. Above this is the 'E' layer and above that the 'F' layer. Each has its own characteristics. The 'E' layer has the property of being able to refract VHF radio waves, but in a somewhat unusual manner. It seems that it has clouds of ionised particles within it, which are more heavily ionised than the rest of the layer. These may last from a few minutes to hours, and when present, refract any VHF radio waves which may happen to pass through them, over very long distances. These distances are not consistent, neither are the times when the Sporadic-E clouds occur.

Many explanations have been put forward for their occurrence, but no really acceptable theory has yet been put forward. A major investigation is to be undertaken by the Radio Society of Gt Britain to try and throw more light on this phenomenon in which both amateur radio signals and BBC and other short-wave broadcasting station signals will play an important role.

## MOBILE ANTENNAE AND ACCESSORIES




Boot lip Mount £3.95 inc.



Gutter Mount £4.50 inc.



Standard Mount (SO239/PL259) £1.70 inc.

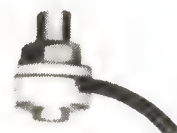

Centre roof Mount £1.70 inc.



UHF 5/8th Wave over 5/8th Wave mobile collinear frequency 420+480 Mhz 6db gain. £13.50 inc.

VHF 5/8th Wave antenna. 140+180 Mhz 3db gain £12.50 inc.



At your emporium or:-

*Les Waller*  
Manufacturing

**PEMBROKE WORKS, RAMSGATE ROAD,  
SANDWICH, KENT CT13 9NW  
Telephone: 0304 614598**



**OPENING IN BIRMINGHAM  
ON 10th MARCH 1984**



**Autronics Amateur Radio (G8RWM)  
& Electronics Shop**

Special opening offers, everyone welcome.  
Easy parking + 38 bus stop outside the door!

**Opening Hours:** Tues-Fri: 10.30-6.30pm  
Sat: 10am-5pm (Lunch 2pm-3pm)

**AUTRONICS LTD,**

142 PRIORY ROAD, HALL GREEN, BIRMINGHAM B28 0TB  
TEL: 021-474 4638

**G8KBQ**

**AVCOMM LIMITED**

**G6HKT**

25 Northload Street, Glastonbury, Somerset BA6 9HB  
TEL: 0458 33145

Electret mic inserts, 600 ohm imp 1½V 35p. 3B30L20 200V 5A Bridge rectifiers 40p. 25 AMP 200V Bridge rectifiers £1.50. LITTON model 3100 MICRODIAL, for ¼" dia spindle, turns counter dial 0-100, panel mntg, with internal light £2.50. 240V red mains neons, 30p. 12 way tag strips, with ceramic insulation, 35p. Black collet knobs, for use with ¼" spindles, 40p. Assorted resistor bags, many values, 75p. Assorted capacitor bags, many types, 75p. 250V AC @ 4Amp rotary mains switches, 35p. 500pf leadless chip capacitors, 5p. 1000pf 500V Bolt — in feedthrough capacitors, 35p. 1000pf 350V Solder — in feedthroughs, 10/45p, 20/85p. BNC 50 ohm single hole fixing sockets, 50p. PANEL METERS: Single nut fixing type, £2.80, 50uA, 1mA, 50mA, 500mA, 2A, 5A, 25V DC. PANEL METERS: Type MU38, price £5.50. 50uA, 100uA, 500uA, 1mA, 5mA, 10mA, 50mA, 500mA, 1A, 2A, 10A, 30V DC. Toggle switches, DPCO with centre off, 12V 15A rated, 45p. Panel mntg fuse holders, 1" type 25p, 1¼" type 30p. ALL prices exclusive 15% VAT. Carriage 50p. Large catalogue + bargain lists 80p. Goods normally by return




## PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape punch and reader	£22.50
Bench isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£1.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Battery condition tester, less box	£1.75
Nicad chargers, mains	£0.75
Flourescent inventor 13 watt from 12v	£3.50
Ten digit stitch pad-pb phone etc.	£1.95
Unselector 2 pole 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23 1/2" wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Solenoid with slug 8-12v battery op.	£1.82
ditto 230v mains	£2.30
Timer Omron STP NH 110v AC Coil	£6.90
Key switch with 2 keys dp mains	£1.75
Air valve mains operated	£3.75
Latching relay mains operated	£3.50
Dry film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60


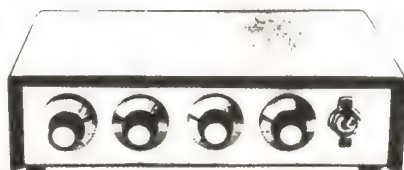
### 8 POWERFUL MODEL MOTORS (all different)

for robots, meccanos, drills, remote control planes, boats, etc. £2.95.



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

### 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3 1/2" dia. They have a good length of 1/4" spindle - Price £3.45.

ditto, but double ended £4.25.

ditto, but permanent magnet £3.75.



### EXTRA POWERFUL 12v MOTOR


Probably develops up to 1/2 h.p. so it could be used to power a go-kart or to drive a compressor, etc. £7.95 + £1.50 post

### THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses, appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pad which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 however, you can have the parcel for £2.50.
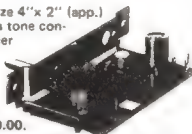
### MINI MONO AMP

on p.c.b., size 4"x2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



### — BARGAIN OF THE YEAR — The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio - easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 - 270 KHz, medium wave band 525 - 1650KHz, FM band 87 - 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or head-phones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00**  
+ £1.50 post + insurance.

## THIS MONTH'S SNIP

If you order 4 Amstrad Stereo Tuners, as described in bottom left-hand column, you can have the lot for **£20.00** including post. Offer closes April 30th.

**REVERSIBLE MOTOR with control gear** Made by the famous Framco Company this robust motor is approx 7 1/2" long, 3 1/2" dia. 3/8" shaft. Very powerful, almost impossible to stop. Ideal for operating stage curtains, doors, ventilators, etc. Even garage doors if properly balanced. Offered complete with control gear as follows:  
1 Framco motor with gear box 1 push to start switch  
1 manual reversing & on/off switch 2 limit stop switches  
1 circuit diag. of connections **ONLY £19.50 + postage £2.50.**

### FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play 'Happy Birthday', 'Merry Christmas', 'Wedding March', etc., or 'Home Sweet Home', etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work £12.5.

### JOYSTICK

**WHY PAY £10 OR MORE** — Make yourself a Joystick full details were given in Dec/Jan 'Sinclair Projects'. We will supply complete kit for £2.30. Although designed for the Spectrum or ZX81 it is equally suitable for any home computer

### TELEPHONE ITEMS

Plug and Wall socket - 4 pin or 5 pin	£3.45
Plugs only 4 pin or 5 pin	£1.15
Modern desk telephone	£7.50
Heavy black old type	£5.50
External bell unit	£6.50
Bell ringing power unit	£4.50
Pick up coil	£1.15

### STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation, 1% with input variations up to 20% - load regulation 1% from no load to full load - or full load to no load. Complete in heavy duty case. Models available 5v - 9A £23. 12v - 1.5A £13.25 15v - 1.2A £13.25. 24v - 2A £23.

### PRESTEL UNIT

brand new and complete except for 7 plug in IC's — Price: £19.75

+ £2.00 p&p

Note: British Telecom may not connect this equipment as there is no manufacturer to guarantee it, however it is well worth buying for its immense breakdown value sold originally at over £150



### 25A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm towel to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch Independent 60 minute memory jogger. A beautiful unit at £2.50.



**FROZEN PIPES.** Can be avoided by winding our heating cable around them - 15 mtrs connected to mains costs only about 10p per week to run. Hundreds of other uses as it is waterproof and very flexible. Resistance 60 ohms/metre. Price 28p/metre or 15m for £3.95

**24 HOUR TIME SWITCH** — Made for control of Randall Central Heating Boilers these give 2 on/off's per 24 hrs. Equal to suitable for control of immersion heaters of heating systems. £4.60.

## 50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

### MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures:  
DC volts 10, 50, 250, 1000.  
AC volts 10, 50, 250, 1000.  
DC amps 0 - 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

**J. BULL (Electrical) Ltd.**  
(Dept RE), 34 - 36 AMERICA LANE,  
HAYWARDS HEATH, SUSSEX RH16 3QU. **Established 50 YEARS**

**MAIL ORDER TERMS:** Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 - 5.30, mon to Fri, not Saturday.

### STORE CLOSING SALE

All stocks must go from one of our big warehouses. 10,000,000 items, everything from AERIALS to ZENER will be cleared at fantastically low prices - if you are a manufacturer you can save yourself a fortune - send for our Sale List, not for small buyers as minimum order £100.

## EXTRACTOR FANS — MAINS OPERATED


Woods extractor.  
5" — £5.75, Post £1.25.  
6" — £6.95, Post £1.25.  
5" Planair extractor  
£6.50. Post £1.25.  
4"x4" Muffin 115v  
£4.50. Post 75p.  
4"x4" Muffin 230v  
£5.75. Post 75p

All the above ex-computer, those below are unused  
4"x4" £8.50 Post 75p  
9" American made  
£11.50. post £2.00.  
Tangential Blower 10x3  
air outlet, dual speed  
£4.60. Post £1.50.


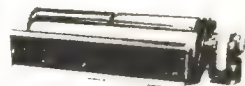
## TANGENTIAL BLOW HEATER

By British Solartron, as used in best blow heaters. 2Kw approx 9" wide £5.95, 3Kw either 9" or 12" wide (your choice) £6.95 complete with 'cold' 'half' and 'full' heat switch, safety cut out and connection dig. Please add post £1.50 for 1 or £2.30 for two.



**2.5 Kw KIT** Still available. £4.95 + £1.50 post.



## MINIATURE WAFER SWITCHES

2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 6 way - 1 pole, 12 way. All at 25p each or 10 for £2.00

**BLEEP TONE** These work off 12v and have an unusual and pleasant bleep 69p each.

**CONNECTING WIRE PACK** 48 lengths of connecting wire, each 1 metre long and differently colour coded, a must for those difficult interconnecting jobs. 85p the lot.

**RED LEDS** 10 for 69p, 100 for £5.75, 1000 for £52.

**IN LINE SIMMERSTAT** Ideal heat controller for soldering iron and many other hand-held appliances £2.30. 10 for £17.25.



## VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case - £1.75 or metal case - £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

## IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included.

£11.95 plus £2.00 post.

## OTHER POPULAR PROJECTS

Short Wave Set - covers all the short wave bands using plug-in coils. Kit complete	£14.50
R C Bridge Kit	£9.95
3 Channel Sound to Light - with fully prepared metal case.	£14.95
ditto - made up	£25.00
Big Ear, listen through walls	£9.50
Robot controller - receiver/transmitter	£9.50
Ignition kit - helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Mr Light 'left on' alarm	£3.50
Secret switch - fools friends and enemies alike	£1.95
3 - 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser - three modes	£17.50
Mullard Unilex HiFi stereo amplifier with speakers	£16.75
Radio stethoscope - fault finding aid	£4.80
Mug stop - emits piercing squawk	£2.50
Morse Trainer - complete with key	£2.99
Drill control kit	£3.95
Drill control kit - made up	£6.95
Interrupted beam. Kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£6.90
FM receiver kit - for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£15.50
Soil heater for plants and seeds	£16.50
Insulation Tester - electronic megger	£7.95
Battery shaver or fluorescent from 12v	£6.90
Matchbox Radio - receives Medium Wave	£2.95
Mixer Pre-amp - disco special with case	£16.00
Aerial Rotator - mains operated	£29.50
Aerial direction indicator	£5.50
40 watt amp - hifi 20Hz - 20KHz	£9.50
Microvolt multiplier - measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Linear Power output meter	£11.50
115 Watt Amplifier 5Hz 25KHz	£13.50
Power supply for 115 watt amps	£8.50
Stereo Bass Booster, most items	£9.95



# DATA FILE

## Ray Marston takes an in-depth look at CMOS bilateral switches and multiplexer/demultiplexer ICs in this latest edition of 'The File'

A CMOS bilateral switch or 'transmission gate' can be regarded as a near-perfect single-pole single-throw (SPST) electronic switch that can pass analogue or digital signals in either direction and can be turned on (closed) or off (opened) by applying a logic 1 or logic 0 signal to a single high-impedance 'control' terminal. Practical versions of such switches have a near-infinite OFF impedance, and a typical ON impedance in the range 90R to 300R.

Standard CMOS bilateral switches can be switched at frequencies ranging from zero to several MHz, and have a multitude of practical uses. They can, for example, be used to replace conventional mechanical switches in signal-carrying applications, the bilateral switch being dc-controlled and placed directly on the PCB where it is needed, thus eliminating the problems of signal radiation and interaction that normally occur when such signals are mechanically switched via lengthy cables.

At higher frequencies, CMOS bilateral switches can be used in such diverse applications as signal gating, multiplexing, A-to-D and D-to-A conversion, digital control of frequency, impedance and signal gain, the synthesising of multi-gang pots and capacitors, and the implementation of sample-and-hold circuits. Examples of most of these applications are shown later in this edition of 'Data File'.

Several types of CMOS 'multiple bilateral switch' ICs are available. These range from the simple 4016B and 4066B types, which each house four independently-accessible SPST bilateral switches, to the 4097B, which houses an array of bilateral switches and logic networks arranged in the form of two independently-accessible single-pole 8-way bilateral switches or multiplexers/demultiplexers. Before we take a detailed look at the range of such ICs, however, let's look at the basic operating principles and terminology, etc, of the bilateral switch.

### Basic operating principles

Figure 1 shows (a) the basic circuit and (b) the equivalent circuit of a simple CMOS bilateral switch. Here, an n-type and a p-type MOSFET are effectively wired in inverse parallel (drain-to-source and source-to-drain), but have their gates biased in anti-phase from the control terminal via a pair of inverters. When the control signal is at logic level '0', the gate of Q2 is driven to VDD and the gate of Q1 is driven to VSS; under this condition both MOSFETs are cut off, and

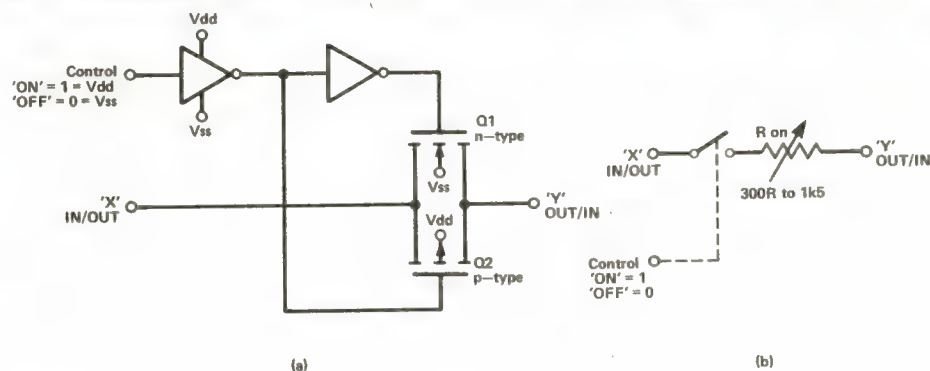


Fig 1 Basic circuit (a) and equivalent circuit (b) of the simple CMOS bilateral switch.

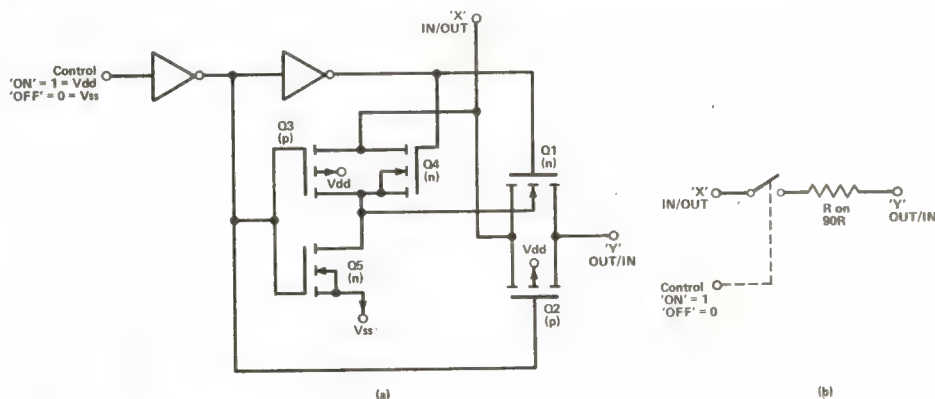


Fig 2 Basic circuit (a) and equivalent circuit (b) of the improved CMOS bilateral switch

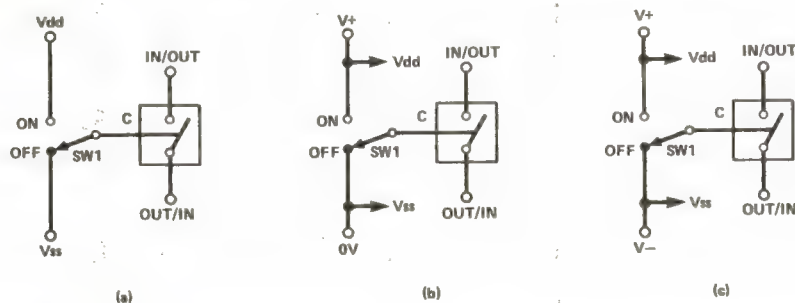


Fig 3 Basic method of turning the bilateral switch on and off (a), and power supply connections for use with (b) digital and (c) analogue IN/OUT signals

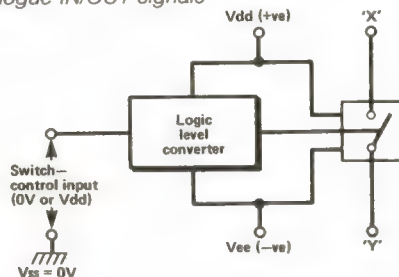
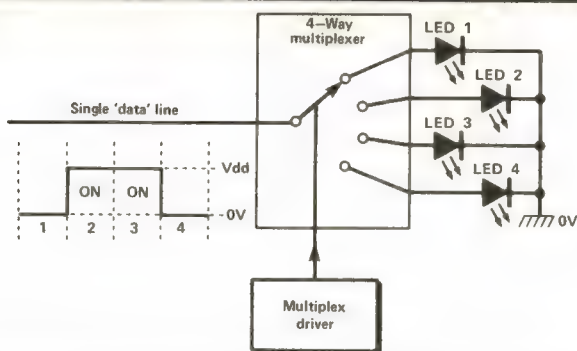
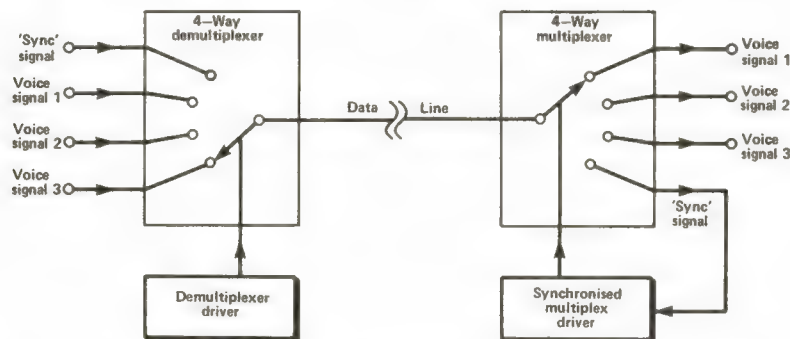


Fig 4 Some ICs feature internal 'logic level conversion', enabling an analogue switch to be controlled via a single-ended input

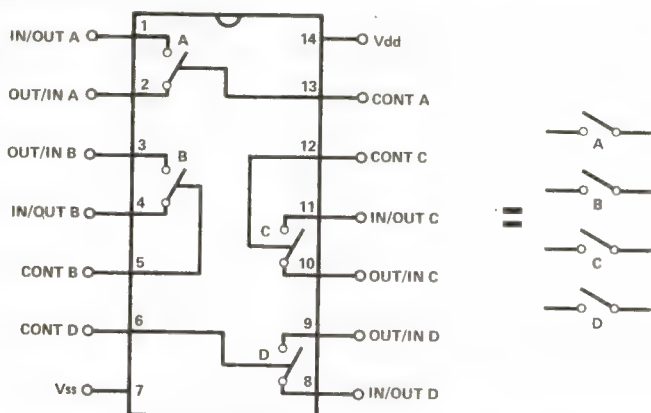





**Fig 5** A 4-way multiplexer used to control four LEDs via a single DATA line



**Fig 6** A 4-way multiplexer/demultiplexer combination used to feed three independent voice signals through a single DATA line



**Fig 7** The 4016B and 4066B quad bilateral switches each act as 4 independent SPST switches

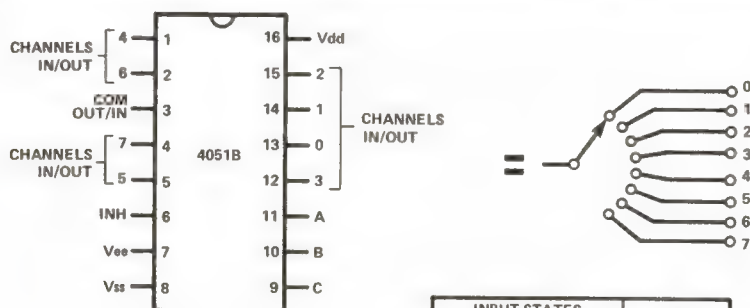

INPUT STATES				'ON' CHANNEL
INH	C	B	A	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	X	X	X	NONE

X = DON'T CARE

**Fig 8** The 4051B 8-channel multiplexer/demultiplexer acts as single-pole 8-way switch

an effective open circuit exists between the 'X' and 'Y' points of the circuit. When, on the other hand, the control signal is at logic level '1', the gate of Q2 is driven to VSS and the gate of Q1 is driven to VDD, and under this condition both MOSFETs are driven to saturation, and a 'near short circuit' exists between the 'X' and 'Y' points of the circuit.

Note that, when Q1 and Q2 are saturated, signal currents can flow in either direction between the 'X' and 'Y' terminals, provided that the signal voltages on these terminals are within the VSS-to-VDD limits. Each of the 'X' and 'Y' terminals can thus be used as either an IN or OUT terminal.

In practice, Q1 and Q2 exhibit a finite resistance ( $R_{on}$ ) when they are saturated, and in this simple circuit the actual value of ( $R_{on}$ ) may vary from 300R to 1k5, depending on the magnitude of the VSS-to-VDD supply voltage and on the magnitude and polarity of the actual input signal. The simple bilateral switch can thus be represented by the equivalent circuit of Figure 1b.

Figure 2 shows an improved version of the CMOS bilateral switch, together with its equivalent circuit. This circuit is similar to the above, except for the addition of a second bilateral switch (Q3-Q4) that is wired in series with Q5, with the 'well' of Q1 tied to Q5 drain. These modifications cause the well of Q1 to switch to VSS when the Q1-Q2 bilateral switch is off, but to be tied to the 'X' input terminal when the switch is on. This modification reduces the ON resistance of the Q1-Q2 bilateral switch to about 90R and virtually eliminates variations in its value with varying signal voltages, etc, as indicated by the equivalent circuit of Figure 2b. The only disadvantage of the Figure 2 circuit is that it has a slightly lower leakage resistance than Figure 1.

## Switch biasing

A CMOS bilateral switch can be used to switch or gate either digital or analogue signals, but must be correctly biased to suit the type of signal being controlled. Figure 3 shows the basic ways of activating and biasing the bilateral switch. Figure 3a shows that the switch can be turned ON (closed) by taking the control terminal to VDD, or turned OFF (open) by taking the control terminal to VSS.

In digital-signal switching applications (Figure 3b) the bilateral switch can be used with a single ended supply, with VSS at zero volts and VDD at a positive value equal to (or greater than) that of the digital signal (up to a maximum of +18 volts). In analogue switching applications (Figure 3c) a split power supply (either true or effective) must be used, so that the signal is held at a mean value of half-supply volts: the positive supply rail goes to VDD, which must have a value greater than the peak positive voltage value of the input signal, and the negative rail goes to VSS and must be greater than the peak negative value of the input signal: the supply values are



limited to  $\pm 9$  volts maximum. Typically, the bilateral switch introduces less than 0.5% of signal distortion when used in the analogue mode.

## Logic level conversion

Note from the above description of the analogue switching system that, if a split power supply is used, the switch control signals must switch to the positive rail to turn the bilateral switch on, and to the negative rail to turn the switch off. This arrangement is inconvenient in many practical applications; consequently, some 'multiple bilateral switch' ICs (notably the 4051B to 4053B family) have built-in 'logic level conversion' circuitry which enables the bilateral switches to be controlled by a digital signal that switches between zero (VSS) volts and positive (VDD), while still using split supplies to give correct biasing for analogue operation, as shown in Figure 4.

## Multiplexing/demultiplexing

A multiplexer can be regarded as any system that enables information from a single 'Data' line to be distributed (on a sequential time/share basis) to a number 'n' of independent data lines. Figure 5, for example shows how a 4-way multiplexer (represented by a 4-way switch) can be used to control (turn on or off) four LEDs down a single data line.


In Figure 5, assume that the multiplex driver continuously sequences the multiplexer through the 1-2-3-4 cycle at a fairly rapid rate, and is synchronised to the 1-2-3-4 segments on the DATA line. Thus, in each cycle, in the '1' period LED 1 is off; in the '2' period LED 2 is on; in the '3' period LED 3 is on, and in the '4' period LED 4 is off. The state of each of the four LEDs is thus controlled via the logic 'bit' of the single (sequentially time/shared) DATA line.

A demultiplexer is the opposite of a multiplexer. It enables information from a number 'n' of independent data lines to be sequentially applied to a single DATA line. Figure 6 shows how a 4-way demultiplexer can be used to feed three independent 'voice' signals down a single cable, and how a multiplexer can be used to convert these signals back into three independent voice signals at the other end. In practice, each 'sample' period of the DATA line must be short relative to the period of the highest voice frequency: Period 1 is used to synchronise the signals at the two ends of the DATA line.


From the above description it can be seen that a CMOS 'n'-channel multiplexer can be regarded as a single-pole 'n'-way bilateral switch, and that a CMOS multiplexer can be converted into a demultiplexer by simply transposing the notations of the input and output terminals. An 'n'-way single-pole bilateral switch can thus be described as an 'n'-channel multiplexer/demultiplexer.

## Practical ICs


There are three major 'families' of CMOS bilateral-switch ICs. The best

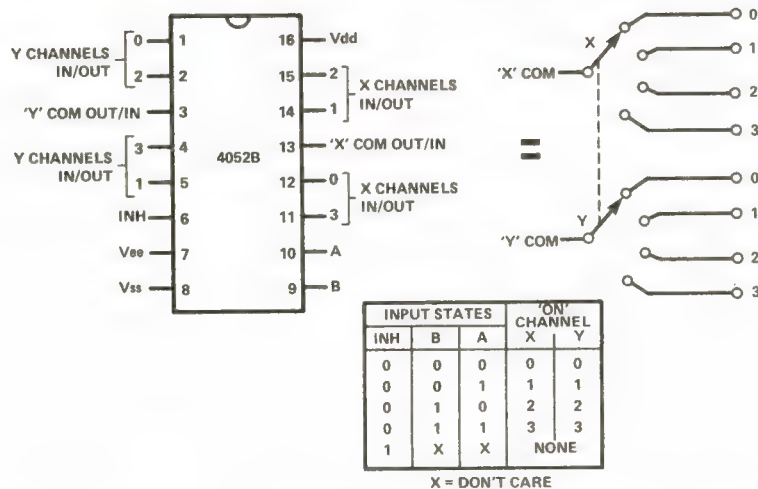

**Fig 9** The 4052B differential 4-channel multiplexer/demultiplexer acts as a ganged 2-pole 4-way switch

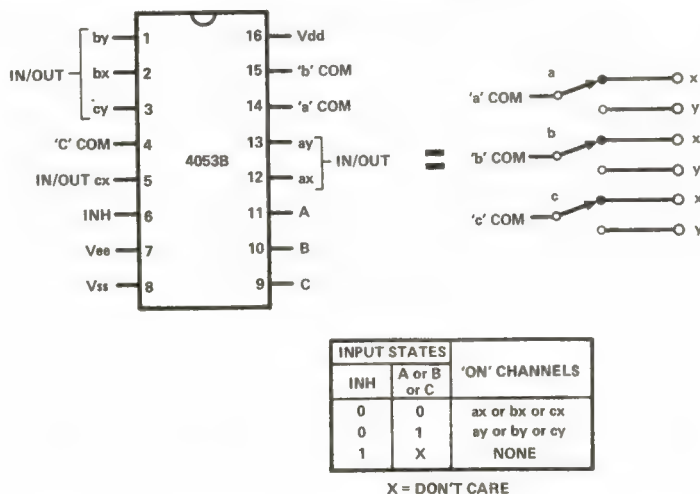

**Fig 10** The 4053B triple 2-channel multiplexer/demultiplexer acts as three independent single-pole 2-way switches

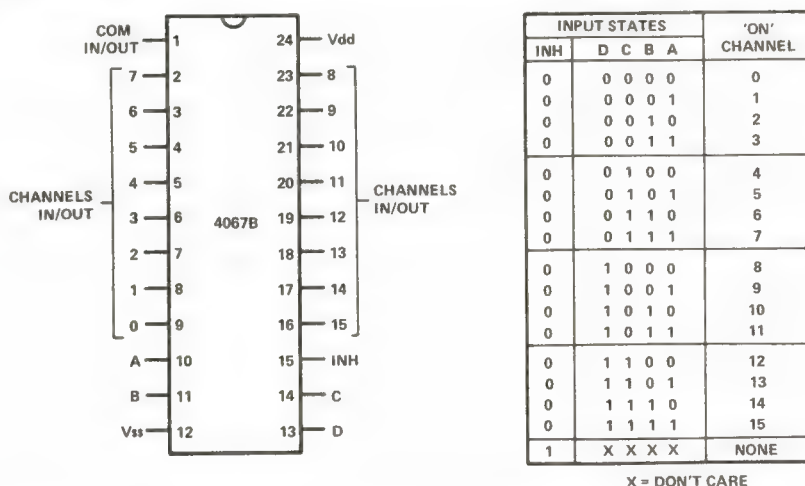

**Fig 11** The 4067B 16-channel multiplexer/demultiplexer acts as a single-pole 16-way switch

known of these are the 4016B/4066B types. These are quad bilateral switches, each housing four independently-accessible SPST bilateral switches, as shown in Figure 7. The 4016B uses the simple form of construction shown in Figure 1, and is recommended for use in sample-

and-hold applications where low leakage impedance is of prime importance. The 4066B uses the improved type of construction of Figure 2, and is recommended for use in all applications where a low ON resistance is of prime importance.



# ATTENTION 10 METRE OPERATORS!

**NEW** — especially for the 10 Metre users who have converted CB rigs

## The AKD 10 Metre Linear Amplifier


- ★ 25 Watts FM out for 4 Watts in
- ★ 50 Watts PEP on SSB
- ★ About 10 Watts out for ½ Watt in (13.8V)
- ★ Automatic RF sensing
- ★ Fully protected output
- ★ Relay switching employed
- ★ Requires nominal 12 volts @ 5 amps (15 volts maximum)
- ★ In-line fused
- ★ 2 year guarantee (including output device)
- ★ British made



**£25.50**  
Incl VAT, p&p
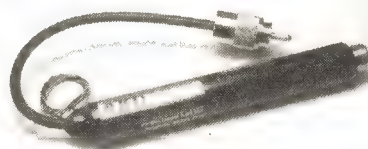
## 10 Metre RF Switched, In-Line Pre-Amp.

- ★ 3SK45 Dual Gate Fet, 15 dB gain
- ★ Fail safe, will handle 10 watts through power
- ★ 2 year guarantee




**£14.50**  
Incl VAT, p&p

★★★★★

Also available, the AKD range of RF INTERFERENCE FILTERS — high performance, sleek appearance.

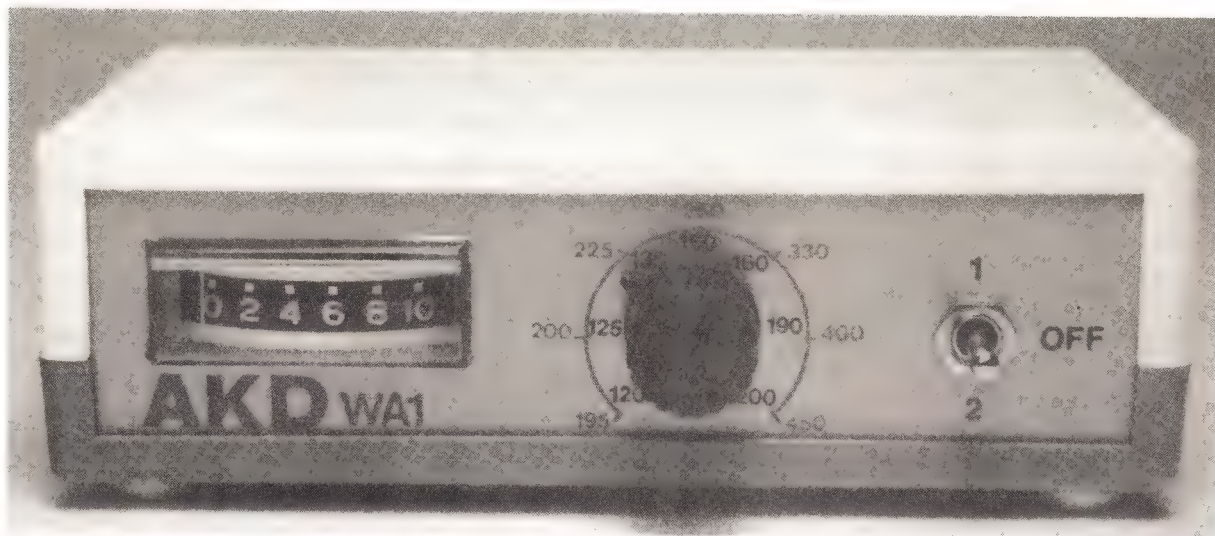Used by British Telecom, Granada, ITT, Thorn-EMI and other prominent companies.




### STOP PRESS!

JUST OUT — The WA1 VHF/UHF absorption wave meter, covering 140 MHz — 450 MHz. **£24.95** inclusive of postage & packing.

Direct from the Manufacture — or from your local Amateur Radio dealer.  
Trade enquiries welcome

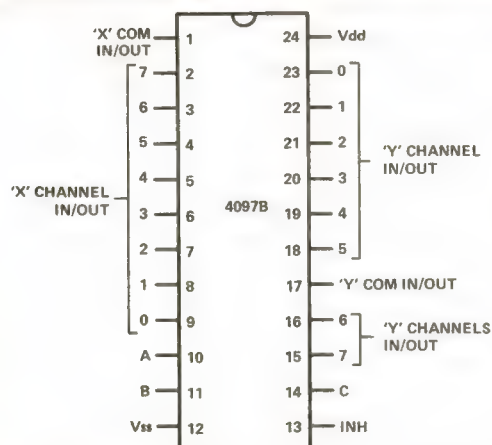**\* AKD \* ARMSTRONG KIRKWOOD DEVELOPMENTS**  
62 Marcourt Road, Stokenchurch, High Wycombe, Bucks, HP14 3QU  
Tel. 024-026-2360





INPUT STATES				SELECTED CHANNELS	
INH	C	B	A	X	Y
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	2	2
0	0	1	1	3	3
0	1	0	0	4	4
0	1	0	1	5	5
0	1	1	0	6	6
0	1	1	1	7	7
1	X	X	X	NONE	

X = DON'T CARE

The second family of ICs are the 4051B to 4053B types (Figures 8 to 10). These are multi-channel multiplexer/demultiplexer ICs featuring built-in logic-level conversion. These ICs have three 'power supply' terminals (VDD, VSS, and VEE). In all applications, VDD is taken to the positive supply rail, VSS is grounded, and all digital control signals (for channel-select, inhibit, etc) use these two terminals as their logic-reference values, i.e., logic-1 = VDD and logic-0 = VSS. In digital-signal processing applications, terminal VEE is grounded (tied to VSS). In analogue-signal processing applications, VEE must be taken to a negative supply rail; ideally,  $VEE = - (VDD)$ . In all cases, the VEE-to-VDD voltage must be limited to 18 volts maximum.

The 4051B (Figure 8) is an 8-channel multiplexer/demultiplexer, and can be regarded as a single-pole, 8-way bilateral switch. The IC has three binary control inputs (A, B, & C) and an INHIBIT input. The three binary signals select the one of the 8 channels to be turned on, as shown in the table.

The 4052 (Figure 9) is a differential 4-channel multiplexer/demultiplexer, and can be regarded as a ganged 2-pole, 4-way bilateral switch. It has two binary control inputs, which select the one of the 4 pairs of channels to be turned on, as shown.

The 4053B (Figure 10) is a triple 2-channel multiplexer/demultiplexer, and can be regarded as a set of three independently-accessible single-pole 3-way bilateral switches, each controlled via a single terminal (A, B, or C).

The final family of devices is the 4067B and 4097B multiplexer/demultiplexer types (Figures 11 and 12). These devices can be used in both analogue and digital applications, but do not feature built-in logic-level conversion. The 4067B is a 16-channel device, and can be regarded as a single-pole, 16-way bilateral switch. The 4097B is a differential 8-channel device, and can be regarded as a ganged 2-pole, 8-way bilateral switch. Each IC is housed in a 24-pin d.i.l package.

## USING 4016B/4066B ICs


The 4016B and 4066B are very versatile ICs, but a few simple precautions must be taken when using them, as follows:-

(1). Input and switching signals must never be allowed to rise above VDD or below VSS.


(2). Each unused section of the IC must be disabled (see Figure 13) either by taking its control terminal to VDD and wiring one of its switch terminals to VDD or VSS, or by taking all three terminals to VSS.

Figures 14 to 19 show some simple applications of the 4066B (or 4016B). Figure 14 shows the device used to implement the four basic switching functions of SPST, SPDT, DPST and DPDT. Figure 14a shows the SPST

**Fig 12** The 4097B differential 8-channel multiplexer/demultiplexer acts as a 2-pole ganged 8-way switch

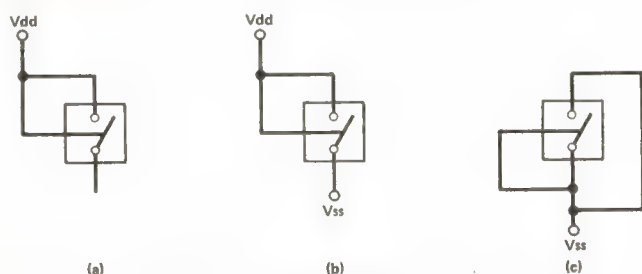


**Fig 13** Unused sections of the 4066B must be disabled, using any one of the connections shown here

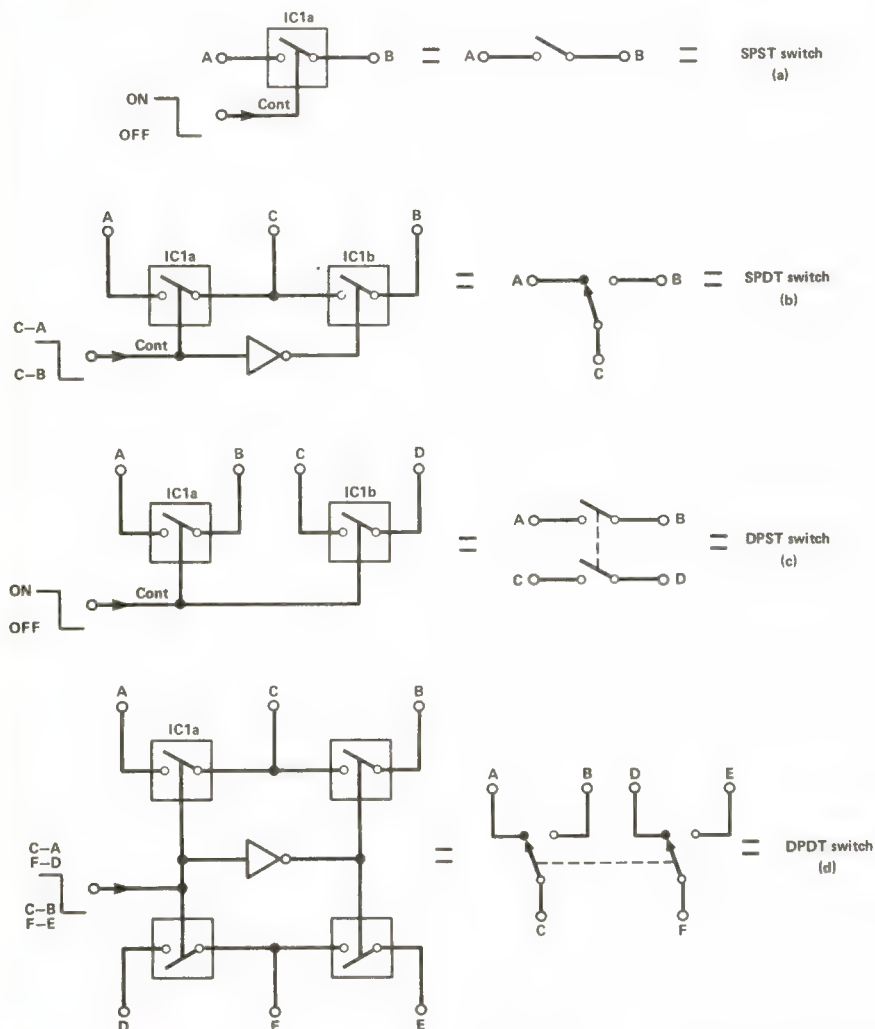


**Fig 14** Implementation of the four basic switching functions via the 4066B (IC1)



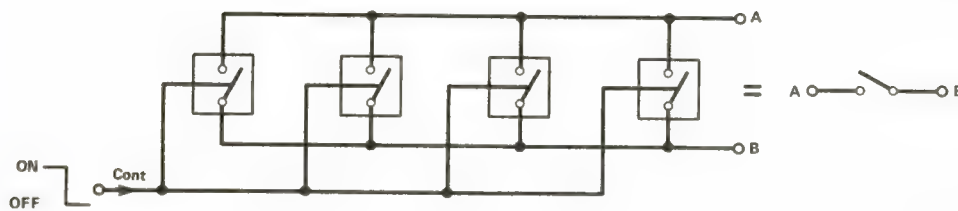

**Fig 15** This SPST switch has a typical ON resistance of only 22.5 ohms

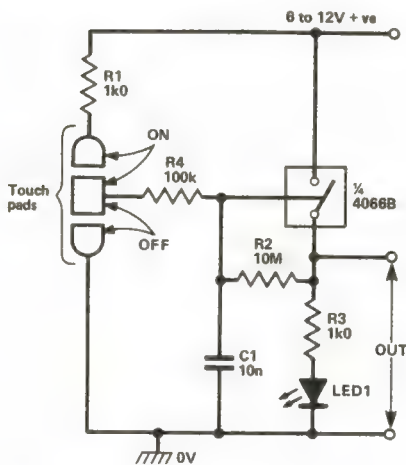


**Fig 17** Latching touch switch

connections, which we have already discussed. The SPDT function (Figure 14b) is implemented by wiring an inverter stage (a 4001B or 4011B, etc) between the IC1a and IC1b control terminals. The DPST switch (Figure 14c) is simply two SPST switches sharing a common control terminal, and the DPDT switch (Figure 14d) is two SPDT switches sharing an inverter stage in the control line.


Note that the switching functions of Figure 14 can be expanded or combined in any desired way by using more IC stages. Thus, a 10-pole 2-way switch can be made by using five of the Figure 14d circuits with their control lines tied together.

Each 4066B bilateral switch has a typical ON resistance of about 90Ω. Figure 15 shows how four standard switch elements can be wired in parallel to make a single switch with a typical ON resistance of only 22.5 ohms.


Figures 16 to 19 show ways of using a bilateral switch as a self-latching device. In these circuits, the switch current flows to ground via R3, and the control terminal is tied to the top of R3 via R2. Thus, in Figure 16, when PB1 is briefly closed the control terminal is pulled to the positive rail and the bilateral switch closes: with the bilateral switch closed, the top of R3 is at supply-line potential and, since the

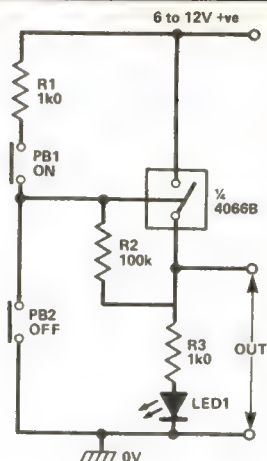


**Fig 16** Latching push-button switch

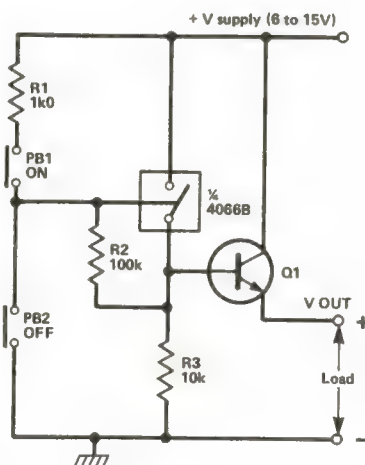

**Fig 18** Latching push-button power switch

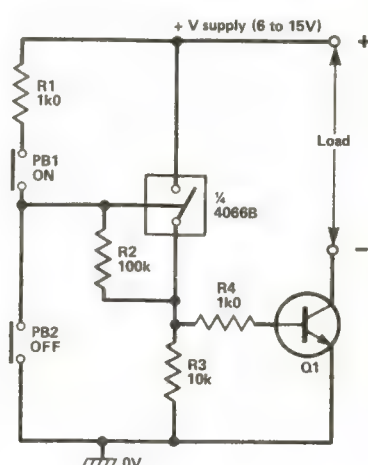

**Fig 19** Alternative version of the latching power switch

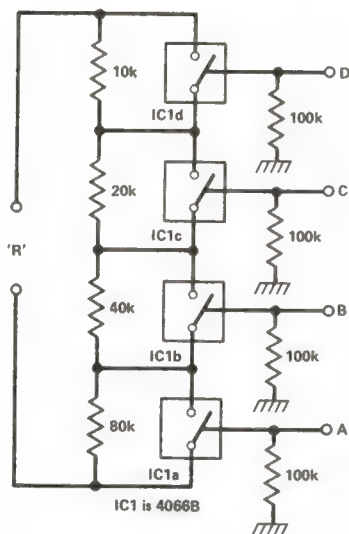

**Fig 20** 16-step digital control of resistance. 'R' can be varied from zero to 150k in 10k steps

A	B	C	D	'R'
0	0	0	0	150k
0	0	0	1	140k
0	0	1	0	130k
0	0	1	1	120k
0	1	0	0	110k
0	1	0	1	100k
0	1	1	0	90k
0	1	1	1	80k
1	0	0	0	70k
1	0	0	1	60k
1	0	1	0	50k
1	0	1	1	40k
1	1	0	0	30k
1	1	0	1	20k
1	1	1	0	10k
1	1	1	1	0k


control terminal is tied to R3 via R2, the bilateral switch is consequently latched on. Once latched, the switch can only be turned off again by briefly closing PB2, at which point the bilateral switch opens and the R3 voltage falls to zero. Note in this circuit that LED1 merely indicates the state of the bilateral switch, and R1 prevents supply line shorts if PB1 and PB2 are both closed at the same time.

Figure 17 shows how the above circuit

can be made to operate as a latching touch-operated switch by increasing the value of R2 to 10M and using R4-C1 as a 'hum' filter.

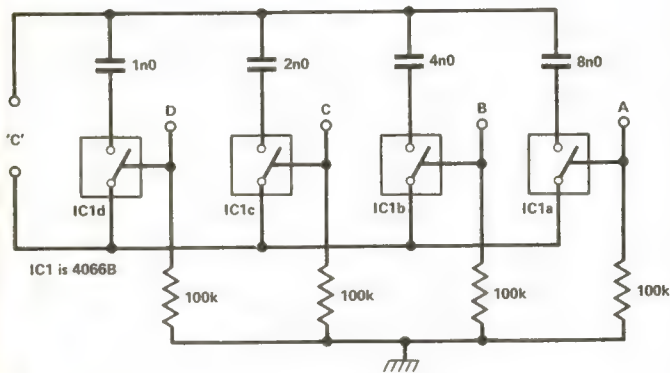
Figures 18 and 19 show alternative ways of using the Figure 16 circuit to connect power to external circuitry. The Figure 18 circuit connects the power via a voltage follower stage, and the Figure 19 design connects the power via a common-emitter amplifier.






A	B	C	D	'C'
0	0	0	0	0
0	0	0	1	1n0
0	0	1	0	2n0
0	0	1	1	3n0
0	1	0	0	4n0
0	1	0	1	5n0
0	1	1	0	6n0
0	1	1	1	7n0
1	0	0	0	8n0
1	0	0	1	9n0
1	0	1	0	10n
1	0	1	1	11n
1	1	0	0	12n
1	1	0	1	13n
1	1	1	0	14n
1	1	1	1	15n


**Fig 21** 16-step digital control of capacitance. 'C' can be varied from zero to 15n in 1n0 steps

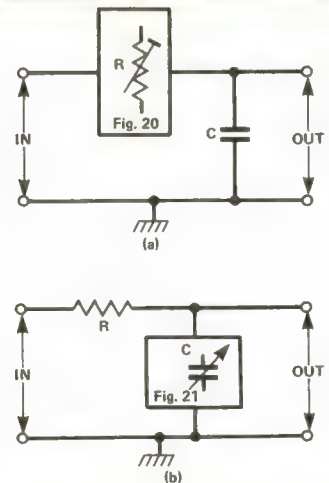


**Fig 22** Alternative ways of using Fig 20 or 21 to make a digitally-controlled 1st-order low-pass filter

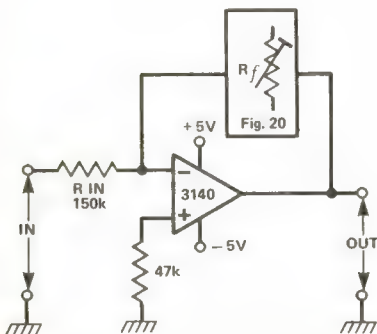


**Fig 23** Digital control of gain, using the Fig 20 circuit. Gain is variable from zero to unity in 16 steps

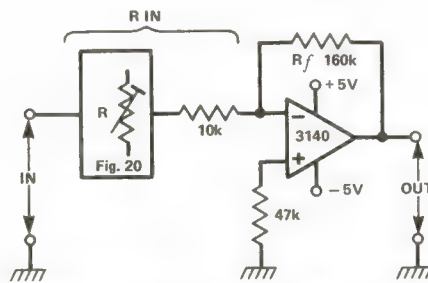

**Fig 24** Digital control of gain, using the Fig 20 circuit. Gain can be varied from unity to x16, in sixteen steps

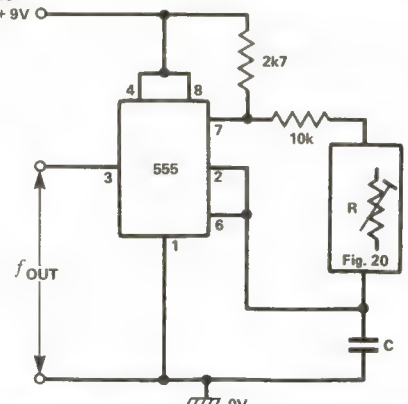

**Fig 25** Digital control of 555 astable frequency, in sixteen steps

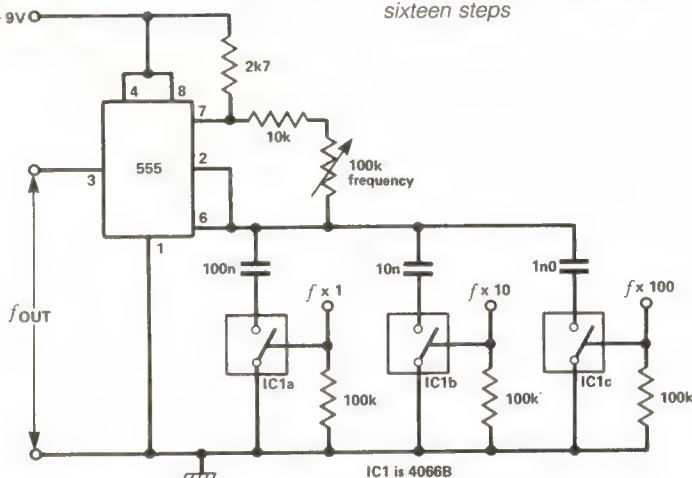

**Fig 26** Digital control of decade range selection of a 555 astable

## Digital control circuits

Bilateral switches can easily be used to digitally control or vary the effective values of resistance, capacitance, impedance, amplifier gain, oscillator frequency, etc, in any desired number of discrete steps. Figure 20 shows how the four switches of a single 4066B can be used to vary the effective value of a resistance in sixteen digitally-controlled steps of 10k each. In practice, the step magnitudes can be given any desired value (determined by the value of the smallest resistor) so long as the four resistors are kept in the ratio 1-2-4-8.

The number of 'steps' can be increased by adding more resistor/switch stages; thus, a six-stage circuit (with resistors in the ratio 1-2-4-8-16-32) will give resistance variation in 64 steps.

Figure 21 shows how four switches can be used to make a digitally-controlled capacitor that can be varied in sixteen steps of 1n0 each. Again, the circuit can be expanded to give more 'steps' by simply adding more stages.

Note in the Figures 20 and 21 circuits that the resistor/capacitor values can be controlled by operating the 4066B switches manually, or automatically via

simple logic networks, or by up/down counters, or via microprocessor control, etc.

The circuits of Figures 20 and 21 can be combined in a variety of ways to make digitally-controlled impedance and filter networks, etc. Figure 22, for example, shows two alternative ways of using them to make a digitally-controlled 1st-order low-pass filter.

Digital control of amplifier gain can be obtained by hooking the Figure 20 circuit into the feedback or input path of a standard op-amp inverting circuit, as shown in Figures 23 and 24. The gain of such a circuit equals  $R_f/R_{in}$ , where  $R_f$  is the feedback resistance and  $R_{in}$  is the input resistance. Thus, in Figure 23 the gain can be varied from zero to unity in sixteen steps of  $1/16$ th each, giving a sequence of 0,  $1/16$ ,  $2/16$ , etc, up to  $15/16$  and (finally)  $16/16$ .

In the Figure 24 circuit the gain can be varied from unity to x16 in sixteen steps, giving a gain sequence of 1, 2, 3, 4, 5, etc. Note in both of these circuits that the op-amp uses a split power supply, so the 4066B control voltage must switch between the negative and positive supply rails.

Figure 25 shows how the Figure 20 circuit can be used to vary the frequency of a 555 astable oscillator in sixteen discrete steps. Finally, Figure 26 shows how three bistable switches can be used



# THE GAMMA TWIN 2 METRE FOLDED 1/2 WAVE ANTENNA

Copyright Gamma Aerial Products 1982

This antenna is based on the very popular and successful "SLIM JIM" design.

The GAMMA TWIN has the following unique features:

★ VERY LOW ANGLE OF RADIATION.

★ ADJUSTABLE RADIATOR.  
(140—150 MHZ)

★ COMPLETELY WEATHERPROOF CONNECTING BOX

★ VERTICAL FIX DIRECTLY TO MAST

**£7.95**  
incl. VAT  
+ £1.15 p&p

Available from your usual stockist or direct from the manufacturers

Please quote Dept RE

## Gamma Aerial Products

MANUFACTURERS OF AMATEUR RADIO & CB ANTENNA

BALDS LANE, LYE, STOURBRIDGE

WEST MIDLANDS LYE (0384) 891132/891474

TRADE ENQUIRIES WELCOME

# HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

## STEREO TUNER/AMPLIFIER

4 wave-band stereo tuner amplifier by GEC MW/LW/SW/stereo FM radio. 10 + 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units. **£21.95** - easy to connect. (UK C/P £1.50)

## THERMAL MATRIX & LINE PRINTER

**NEW LOW PRICE**

COMPLETE WITH FULL HANDBOOK 3 ROLLS PAPER (UK post etc £1.05) (List approx £187) **£69.95** inc. VAT  
SUITABLE FOR: TANDY • BBC • ORIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc etc (Interface unit with leads £15 - state model) (Your enquiries invited)

## PRESTEL ADAPTOR

3 card set with data etc (P/S +/- 12V and -5V) **£29.95** inc. VAT

## MODEM CARD

BT approved ready assembled unit with data and accessories **£39.95** inc. VAT

## CHERRY ADD-ON KEYPAD

16 button pad non-encoded **£5.95**

## SANYO DM2112 HIGH RESOLUTION MONITOR

12" green display. Composite video. 1280 characters. Over 15 MHz B/W. 240V AC 34 W. 16 x 11 1/4" x 12 1/4". Alphanumeric and Graphic display. Usually **£89.95 - £99.95** incl. VAT **£69.95** (UK C/P & ins £2.05)

## I.T.T. 2020 CABINET

Professional Computer Case. 18" x 15 1/2" x 4 1/2" (front slopes). As previously advertised. **£27.50** inc. VAT (UK C/P £2.50)

## LOGIC PROBES

LP10 10 MHz **£22.95**  
DLP50 50 MHz with carry case and accessories **£49.95**

## HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. **£23.00** (UK C/P 65p)

## DIGITAL CAPACITANCE METER

(UK C/P 65p)  
0.1 pF to 2000 mF LCD 8 ranges **DM6013** **£52.75**

## VARIABLE POWER SUPPLIES

(UK C/P £1.00)  
PP241 0/12/24V 0/1A **£35.00**  
PP243 3 amp version **£59.95**  
230W 0/30V 1A twin meter **£59.50**

## FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED **£77.60**  
MET100B digit LED bench 2 ranges 100 MHz **£102.35**  
MET600B digit LED bench 3 ranges 600 MHz **£132.25**  
MET1000 8 digit LED 3 ranges 1 GHz **£182.85**  
TF400 8 digit LCD 40 MHz. Thandar **£126.50**  
TF200 3 digit LCD 200 MHz. Thandar **£166.75**

## DIGITAL MULTIMETERS

■ with case (rotary switches)  
+ Side button - case **£2.95**  
KD25C ■ 13 range 0.2A DC 2 meg ohm **£23.50**  
KD30S ■ 16 range 10A DC 2 meg ohm **£26.95**  
KD30C ■ 26 range 1A AC/DC 20 meg ohm **£29.50**  
KD55C ■ 28 range 10A AC/DC 20 meg ohm **£33.50**  
Metex 3000 ■ 30 range 10A AC/DC 20 meg ohm **£33.24**  
G010 ■ 28 range 10A AC/DC 20 meg ohm **£34.40**  
7030 4- AS6010 high acc. 0.1% basic **£41.30**  
KD615 ■ 16 range 10A DC 2 meg plus Hfe tester **£39.95**  
SIFAM 2200B 21 range 2A AC/DC 20 meg Bench Models **£29.95**  
TM355 29 range LED 10A AC/DC 20 meg Thandar **£86.25**  
TM356 26 range LCD 10A AC/DC 20 meg Thandar (Replaces TM353) **£97.75**  
TM351 29 range LCD 10A AC/DC 20 meg Thandar **£120.75**

ALSO IN STOCK Thurlby, Metrix and Beckman. Professional series incl. True Rms. etc.

## MULTIMETERS (UK C/P 65p)

M200 20K/volt. 30 ranges. AC/DC. 20 KHZ. List **£1.85** **£12.95**  
HM102B 20K/V 10A DC 22 range & cont. buzzer **£13.50**  
TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer **£23.95**  
NM56R 20K/V. 22 range pocket **£10.95**  
B30A 26 range 30K/V. 10A AC/DC overload protection, etc. **£23.95**  
360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe **£39.95**  
AT1200 31 range 100K/V deluxe 12A AC/DC **£33.50**  
AT1020 18 range 20K/V. Deluxe plus Hfe tester **£18.95**  
YM360TR 19 range 20K/V plus Hfe tester **£15.95**

## SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL etc  
TG101 0.02HZ-200KHZ **£113.85**  
TG102 0.2HZ-2 MHz **£166.75**  
PULSE  
TG105 Various facilities 5 Hz-5 MHz **£97.75**  
AU010: Multiband Sine/Square  
LAG27 10 Hz to 1 MHz **£90.85**  
AG20A 20 Hz to 200 KHZ (list £94.50) **£83.50**  
LAG 120A 10 Hz-1MHz Low Distortion **£159.85**  
RF  
SG402 100 KHZ to 30 MHz (list £79.50) **£69.50**  
LS617 100 KHZ to 150 MHz **£79.35**

## OSCILLOSCOPES

Full specification any model on request. SAE by post  
HM Series NAMEG: SC THANDAR: CS TRIO: '3' CROTECH 'Y' HITACHI  
SINGLE TRACE UK C/P £3.00  
3030 15 MHz 5mV 95mm tube plus component tester **£177.10**  
SC110A ■ Miniature 10 MHz battery portable Post free **£171.00**  
■ Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50  
HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00 **£181.70**  
DUAL TRACE (UK C/P £4.00):  
HM203/4 Dual 20 MHz plus component tester **£303.60**  
CS1562A Dual 10 MHz (List £321.00) **£269.50**  
3132 Dual 20 MHz + component tester **£325.45**  
CS1566A Dual 20 MHz All facilities (List £401.35) **£349.50**  
HM204 Dual 20 MHz plus component tester sweep delay **£419.75**  
HM705 Dual 70 MHz sweep delay **£676.00**  
V212 Dual 20 MHz **£399.25**  
V222 Dual 20 MHz plus extra facilities **£391.00**  
V422 Dual 40 MHz portable **£586.50**  
V230F Dual Trace 20MHz sweep delay **£408.25**  
V134 Dual Trace 10 MHz storage **£1092.50**  
All HITACHI, CROTECH TRIO & NAMEG MODELS AVAILABLE • With probes

## SCOPE PROBE KITS

X1 £7.95 X10 £9.45 X1 - X10 £10.50

## ORDER BY POST OR PHONE

Order by Post with CHEQUES: ACCESS: VISA or you can telephone your orders. All orders despatched within 5 days unless advised

## HENRY'S

404-406 Edgware Road, London, W2 1ED  
Computer: 01-402 6822 Components: 01-723 1008  
Test Equipment & Communications: 01-724 0323

## AUDIO ELECTRONICS

301 Edgware Road, London, W2 1BN 01-724 3564


CALL IN AND SEE FOR YOURSELF

## CATALOGUE


Send large S.A.E. (20p UK)

All mail to Cubegate Ltd 1st floor, 406 Edgware Road, London, W2 1ED



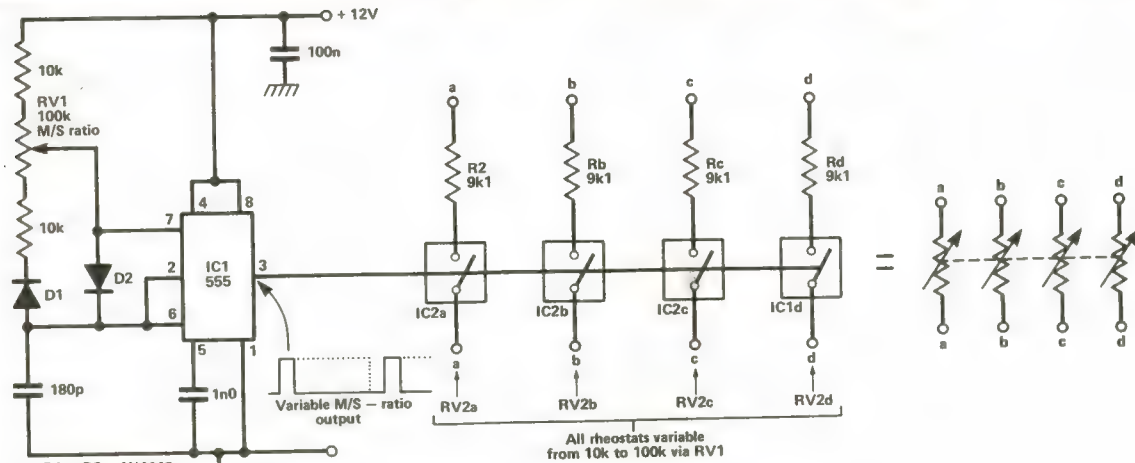

**Fig 27** Synthesised precision 4-gang 'rheostat'

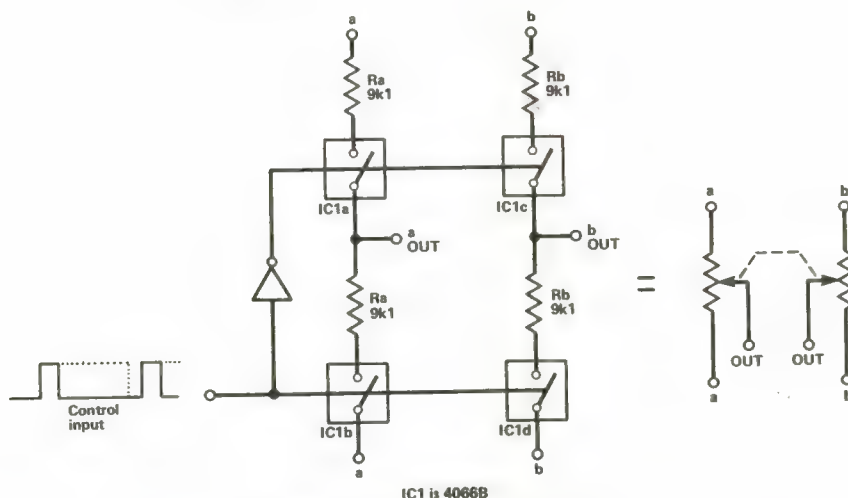

**Fig 28** Synthesised precision 2-gang 'pot'

to implement digital control of decade range selection of a 555 astable. Here, only one of the switches must be turned on at any time. Naturally, the circuits of *Figures 25 and 26* can easily be combined, to form a wide-range oscillator that can be digitally controlled by a micro, etc.

## Synthesised multi-gang pots, etc

One of the most useful applications of the bilateral switch is in synthesising multi-gang rheostats, pots, and variable capacitors in ac signal-processing applications. The synthesising principle is quite simple and is illustrated in *Figure 27*, which shows the circuit of a 4-gang 10k-to-100k rheostat for use at signal frequencies up to about 15 kHz.

Here, the 555 is used to generate a 50kHz rectangular waveform that has its mark/space ratio variable from 11:1 to 1:11 via RV1, and this wave-form is used to control the switching of the 4066B stages. All of the 4066B switches are fed with the same control waveform, and each switch is wired in series with a range resistor (Ra, Rb, etc), to form one gang of the 'rheostat' between the 'a' - 'a', 'b' - 'b', etc, terminals.

Remembering that the switching rate

of this circuit is very fast (50 kHz) relative to the intended maximum signal frequency (15 kHz), it can be seen that the MEAN or effective value of each 'rheostat' resistance can be varied via M/S-ratio control RV1. Thus, if IC2a is closed for 90% and open for 10% of each duty cycle (M/S-ratio = 9:1), the apparent (mean) value of the 'a' - 'a' resistance will be 10% greater than Ra, i.e., 10k. If the duty cycle is reduced to 50%, the apparent Ra value will double, to 18.2k. If the duty cycle is further decreased, so that IC2a is closed for only 10% of each duty cycle (M/S-ratio = 1:9), the apparent value of Ra will increase by a decade, to 91k. Thus, the apparent value of each gang of the 'rheostat' can be varied via RV1.

There are some important points to note about the above circuit. First, it can be given any desired number of 'gangs' by simply adding an appropriate number of switch stages and range resistors. Since all switches are controlled by the same M/S-ratio waveform, perfect tracking is automatically assured. Individual gangs can be given different ranges, without effecting the tracking, by giving them different range resistor values. The 'sweep' range and the 'law' of the

rheostat can be changed by altering the characteristics of the M/S-ratio generator. Finally, it must be noted that the control frequency of the M/S-ratio signal MUST be far higher than the maximum signal frequency that is to be handled, or the circuit will not perform correctly.

The 'rheostat' circuit of *Figure 27* can be made to function as a multi-gang variable capacitor by using ranging capacitors in place of the ranging resistors. In this case, however, the apparent capacitance value decreases as the duty cycle is decreased.

The *Figure 27* principle can be expanded, to make synthesised multi-gang pots, by using the basic technique shown in *Figure 28*.

Here in each gang, two 'rheostats' are wired in series but have their switch control signals fed in anti-phase, so that one rheostat value increases as the other decreases.


This basic circuit can be expanded, to incorporate any desired number of gangs, by simply adding more double-rheostat stages.

## Miscellaneous applications


To complete this look at the CMOS bilateral switch, *Figures 29 and 30* show



## DATA FILE

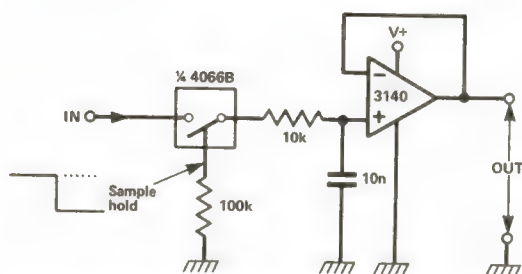

**Fig 29** Using a bilateral switch as a sample-and-hold element

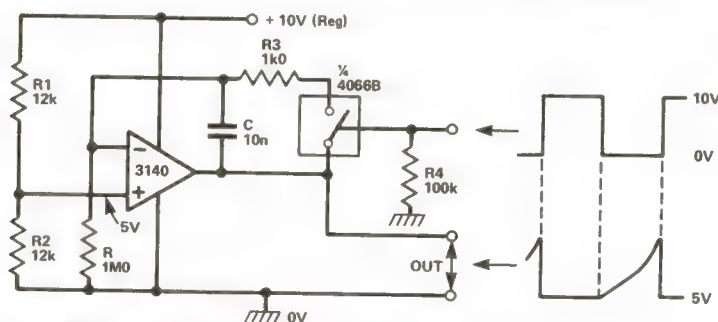

**Fig 30** Using the 4066B to implement a ramp generator circuit

a couple of 'miscellaneous' fast-switching applications of the device. Figure 29 shows how it can be used as a sample-and-hold element. The 3140 is used as a voltage follower and has a near-infinite

input impedance, just as the 4016B switch has a near-infinite impedance when open. Thus, when the 4016B switch is closed, the 10nF capacitor rapidly follows all variations in input voltage, but

when the switch opens the prevailing capacitance-charge is 'stored' and the resulting voltage remains available at the op-amp output.

Finally, Figure 30 shows a bilateral switch used in a linear ramp generator. Here, the op-amp is used as an integrator, with its non-inverting pin biased at 5 volts via R1-R2, so that a constant current of 5  $\mu$ A flows into the inverting pin via R. When the bilateral switch is open, this current linearly charges capacitor C, causing a rising ramp to appear at the op-amp output. When the bilateral switch closes, C is rapidly discharged via R3 and the output switches down to 5 volts.

The basic Figure 30 circuit is quite versatile. The switching can be activated automatically via a free-running oscillator or via a voltage-trigger circuit. Bias levels can be shifted by changing the R1-R2 values or can be switched automatically via another 4066B stage, enabling a variety of ramp waveform types to be generated.

**Next month's Data File takes an in-depth look at a particularly versatile CMOS chip, the 4046B phase-locked loop**

## Hitachi Oscilloscopes performance, reliability, value



## New Models! immediate delivery!

New from Hitachi are three low-cost bench 'scopes with bigger screens and extra features in a new slimline ultra-lightweight format. The range now extends to 13 models:—

- 4 dual trace single timebase models 20MHz to 40MHz
- 2 dual trace sweep delay models 20MHz and 35MHz
- 2 dual timebase multi-trace models 60MHz and 100MHz
- 2 miniature field portable models, 20MHz and 50MHz
- 3 storage models, one tube storage, two digital storage

Prices start at £295 plus vat (model illustrated) including 2 probes and a 2-year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving specifications and prices ring (0480) 63570.

Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

## FREQUENCY COUNTERS


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz 1.2GHz
- ★ Sensitivity <50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.07
METEOR 600	(600MHz)	£133.97
METEOR 1000	(1GHz)	£184.57

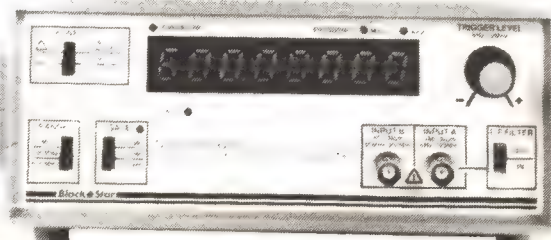Illustrated colour brochure with technical specification and prices available on request.



Designed and  
Manufactured  
in Britain.





**Black Star**

BLACK STAR LTD, 9A Crown Street, St Ives,  
Huntingdon, Cambs, PE17 4EB, England  
Tel: (0480) 62440 Telex: 32339



# BI-PAK BARGAINS

## MINIATURE TOOLS FOR HOBBYISTS

-  Miniature round nose side cutters - insulated handles 5 1/2 inch length. Order No: Y043.
-  Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No: Y044.
-  Miniature bend nose pliers - insulated handles 5 1/2 inch length. Order No: Y045.
-  Miniature end nippers - insulated handles 5 1/2 inch length. Order No: Y046.

**FLEXEY DRIVER**

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No: FS-1 Flat blade 4mm FS-2 Cross point no. 1 £1.75 each.

**GRIP-DRIVER**

Binch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No: SD-1 Flat blade 4mm SD-2 Cross point no. 0. £95p each.

**ALL AT 1.25 each**

Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 1/2 inch length. Order No: Y042

### VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2 Watt Pre-Formed	£1.00
VP3	200		
VP4	150	1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - .015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc. Ceramic 750v - 8kv Mixed	£1.00
VP16	50	Wirewound Res. 9W (avg) Ass 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1.00
VP26	20	Small 125° Red LED'S	£1.00
VP27	20	Large 2° Red LED'S	£1.00
VP28	10	Rectangular 2° Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vits. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vits. Coded	£1.00
VP31	10	5 Amp SCR'S TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR'S TO-66 Up To 400v Uncoded	£1.00
VP33	200	5A Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	5A Diodes Gen. Purpose Like OA200/BA131/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vits. Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1 1/2 Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00

### TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year! This collection of Components & Semiconductors for the

hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for just £6.50 ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3412 and order with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. V.P. 95.

### SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 amp rectifiers mounted on PCB.

VRM - 150 vits

IFM - 1.5 Amps

Size: 1 inch square

10 off £1.00

50 off £4.50

100 off £7.50

Order No. As:4R1

BRect.

### MULTITESTERS

1,000 opv Including test leads b Battery  
AC volts - 0-15-150-500-1,000  
DC volts - 0-15-150-500-1,000  
DC currents - 0-1ma 150ma  
Resistance - 0-25 K ohms 100 K ohms  
Dims - 90 x 61 x 30mm

O/No.1322.OUR PRICE £8.50 ONLY

### 5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm

£1.75

### 5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm.

£1.75

### 5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers - H0 and H1 Hex key wrenches - 1.5, 2 and 2.5mm

£1.75

### 5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm

£1.75

### ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia.) 60mm (depth). Power - 12v DC.

Our Price: £5.50

### BRAND NEW LCD DISPLAY MULTITESTER

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
\*3 1/2 digit \*16 ranges plus hFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single-handed, pushbutton operation \*Over range indication \*12.5mm (1/2 inch) large LCD readout \*Diode check \*Fast circuit protection \*Test leads, battery and instructions included.

Max indication 1999 or -1999  
Polarity indication Negative only  
Positive readings appear without + sign

Input Impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds

Temperature range -5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery

Consumption 20mW  
Size 155x88x31mm

RANGES £35.00 each

DC Voltage 0-200mV  
0-2-20-200-1000V Acc. 0.8%

AC Voltage 0-200-1000V  
Acc. 1.2% DC Current 0-200uA

0-2-20-200mA, 0-10A Acc. 1.2%  
Resistance 0-2-20-200K ohms

0-2 Megohms. Acc. 1%  
BI-PAK VERY LOWEST PRICE

### DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit 0-2V - instructions provided to extend voltage & current ranges  
Operating voltage 9/12v  
Typ Power Consumption 50mA  
O/N0 SX99 Once only price £9.95

### OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

### SIREN ALARM MODULE

American Police type screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. 5 watt, 12v max.

£3.85

Order No. BP124.

### The Third and Fourth Hand . . .

... you always need but have never got until now. This helpful unit with Rod mounted horizontally on Heavy Base Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2 diam magnifier giving 25x magnification. Helping hand unit available with or without magnifier. Our price with magnifier as illustrated ORDER NO. T402 £5.50. Without magnifier ORDER NO. T400 £4.75

### TRANSISTOR CLEARANCE

All Sorts Transistors: A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions For Making Simple Transistor Tester. Super Value. Order No. VP60 £1.00

### MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid Charge/Test switch. LED indicators at each of the five charging points.

Charges - Power -  
PP3 (9V) 220-240V AC  
U12 (1.5V penlite) Dims -  
U11 (1.5V "C") 210 x 100 x 50mm  
U2 (1.5V "D") £6.95

### POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug Input - 240V AC 50Hz, Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma MW88.

### TRIACS - PLASTIC

4 AMP - 400v - T0202 - TAG 136G.			
1 OFF	10 OFF	50 OFF	100 OFF
40p	£3.75	£17.50	£30.00
8 AMP 400v - T0202 - TAG 425			
60p	£5.75	£27.50	£50.00

### VOLTAGE REGULATORS T0220

Positive +	Negative +
7805 - 40p	7905 - 50p
7812 - 40p	7912 - 50p
7815 - 40p	7915 - 50p
7824 - 40p	7924 - 50p

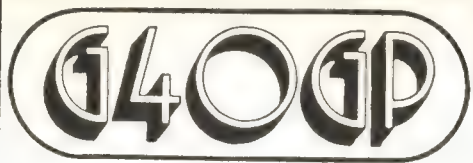
# BI-PAK

Send your orders to Dept RE3 BI-PAK PO BOX 6 WARE, HERTS  
SHOP AT 3 BALDOCK ST. WARE, HERTS  
TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS.  
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GYRO 388 7006  
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even later. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order.





# ELECTRONICS



For variable capacitors. Roller coasters, Thermo Couple Meters. VHF, HF Aerial matching units, low power and high power, in kit form or ready built. The G40GP multi-band aerial still only **£16.00** + p&p.

Our unique Aerial Feeder Spreader to make up feeders of 75,300,400 and 600 OHM open wire feeders, to withstand power rating of 3 kilowatts is not affected by rain, snow or sun and don't forget these clip on feeders made in seconds.

Baluns from **£5.95**, specials on request. Convert your antenna tuner to balanced input from twin feeder etc, by fitting our external box. **£15.95** & all information. Send large SAE for further details. 73 Tony


## G40GP ELECTRONICS

Works & Sales

**UNIT 4, GLADDEN PLACE, WEST GILLIBRANDS  
SKELMERSDALE, LANCs**

Phone: 0695-26345 or 27948

## BUILD A BETTER AMPLIFIER!

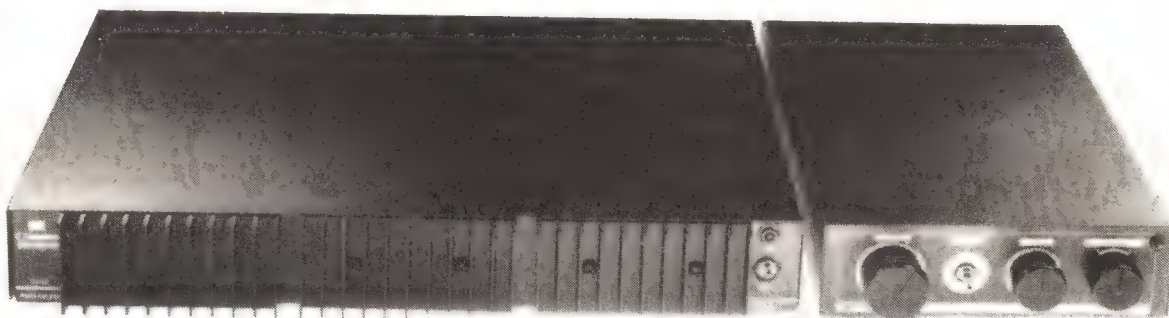

How can you own a top class HiFi amplifier, of comparable standard to Naims, Meridians, Quads etc., for an outlay of less than £250? — Simple! Build it yourself — with a Crimson kit.

It is not necessary to spend a small fortune to obtain true Hifi performance. Crimson Kits offer all the features and sound quality of the most esoteric amplifiers available and their ease of assembly ensures that they work first time and continue to do so. Not only do Crimson Kits offer outstanding value, but they also have the flexibility to adapt to any users needs. All the P.C.B.'s are ready assembled and tested (they are **not** "pot-ted" as we believe disposable modules are rather extravagant!) therefore constructing a kit is pleasurable in itself and, once built, will give years of untroubled service. So, whether you use a simple record player or a compact disc, you can be sure to get the most from your system. E.T.I. said, in their review of the CK1010/1100: "I can say no more than that for £250 it is a bargain and one that will become the reference point for kit amplifiers from now on." Need we say more?

### PRICES

CK1010 — STEREO PRE-AMPLIFIER (moving magnet, tape, tuner input) takes power from any CK power amp or separate p.s.u. type P.S.K.	£92.00
CK1040 — STEREO POWER-AMPLIFIER 40 watts R.M.S./Chanel	£121.00
CK1080 — STEREO POWER-AMPLIFIER 80 watts R.M.S./Chanel	£134.00
CK1100 — STEREO POWER-AMPLIFIER 100 watts R.M.S./Chanel	£151.00
MC2K — Moving coil add on kit for CK1010	£25.00
P.S.K. — power supply for CK1010 (if not used with a CK power amp)	£20.00

CRIMSON also supply power amp, pre amp and electronic crossover modules, power supplies and hardware — too much to list here — but on receipt of an S.A.E. we will be happy to supply full details.

**TO ORDER** Send C.W.O. or quote your access card no (phone orders accepted) Crimson Products are also available from Bradley Marshall Ltd, 325 Edgware Road, London, and Wilmslow Audio Ltd, 35-39 Church St, Wilmslow, Cheshire SK9 1A5.



# CRIMSON ELEKTRIK STOKE

MANUFACTURERS OF PROFESSIONAL, DOMESTIC & INDUSTRIAL AMPLIFICATION  
PHOENIX WORKS, 500 KING STREET, LONGTON, STOKE-ON-TRENT, STAFFORDSHIRE. ST2 1EZ ☎ 0782 330520



# LATEST LITERATURE

Clubs, manufacturers, publishers and agents are invited to send details of new books, catalogues, data sheets, etc for inclusion on this page

## NEW FROM GRANADA

Here are three new books from Granada.

**THE ORIC PROGRAMMER** (Price £6.95).

This teaches BASIC from first steps to a high level of competence, paying special attention to the Oric's graphics and sound capabilities.

Most chapters contain at least one complete program listing to enjoy as you learn, and many examples of shorter programs are provided to help you master the techniques.

Everything you need to know is set out clearly and logically so that you are soon in complete control of this powerful machine.

**DISK SYSTEM FOR THE BBC MICRO** (Price £6.95)

The costs of disks are now comparable to cassettes, and the prices of disk drives – once a luxury for the few – are falling fast.

Consider all the advantages of disk systems, including:

- High speed of operation.
- Random access to any point on the disk.
- One program can call another, enabling you to deal with much more complex operations.
- The ability to run long programs, up to many times the memory capacity of your micro.
- Parts of the disk itself can be edited or altered to retrieve damaged programs and read disks made on other machines.

This book sets out all the advantages of using disks, explains the jargon and covers the principles of disk operations, not only for the BBC disk system but also the AMCOM, the Watford and other systems suitable for use with the BBC Micro. Normal and advanced disk operations are described in detail and you are shown how to take full advantage of the various disk utilities. You will be amazed at how efficient and creative

your computing will become.

The author Ian Sinclair is a well-known contributor to journals such as *Personal Computing World*, *Computing Today*, *Electronics and Computing Monthly*, *Hobby Electronics*, and *Electronics Today International*. He has

written over forty books on electronics and computing aimed mainly at the beginner.

**SPECTRUM GRAPHICS & SOUND** (Price £6.95)

This book shows you how to make the most of the Spectrum's graphics and sound

capabilities, and you will be amazed by what you can achieve.

This book guides you through the basic principles of graphics on computers, and then covers the techniques of drawing, producing graphs and using colour. Later chapters deal with animation, including the techniques required for writing games programs and also three-dimensional displays. You are shown how to produce sound effects and music, and exploit the Spectrum's creative potential.

Many short, easily handled program listings are provided as well as several complete listings for you to try out and enjoy.

The author Steve Money is a well-known author of several books including *Microprocessor Data Book* published by Granada.

Granada Publishing Ltd, 8 Grafton Street, London. W1X 3LA. Tel: 01-493 7070.

## LISTENERS CHECK LIST

*Dial Search* (3rd edition) (Price £2.75) is designed as a guide for the home listener with a small portable radio, but it has proved popular with many expert hobbyists (DX-ers) and transmitting amateurs (hams).

The Dial-Search checklists serve as a chart. As well as your targets, they show the main landmarks and obstacles, and without these you cannot be sure precisely where you are on your small dial.

And like a landscape, it 'looks' different at different time of day or year, and as the weather changes. As evening sets in, we receive some stations much better for a few hours, others worse. Some reduce power. Some are closed down by 2200 hours. Some are only audible after midnight when stronger stations have gone off the air.

Thus Dial-Search saves you







## LATEST LITERATURE

hours of frustration and makes home listening really rewarding – as readers of previous editions have testified. This edition aims to save even more time, by indicating in its medium wave checklists the hours each station broadcasts and the period when (in SE England) it is worth searching for it.

Readers in the North, and on the continent of Europe, will also find a brief reference to the more powerful stations (on the fringes of our map) which they may expect to receive, though our portables here do not.

Whatever their location, all listeners can benefit from orienting their set (or aerial) towards the desired transmitter. Dial-Search has demonstrated how easy this can be, with the right map. This time our Europe map is larger and there is a map of Britain too.

Published by: George Wilcox,  
9 Thurrock Close, Eastbourne, Sussex BN20 9NF.

### MAIL ORDER CATALOGUE

A catalogue containing over 100 test and measuring instruments plus cables, connectors, kits and accessories is now available from Supercat Electronics.

This fully illustrated catalogue provides detailed electrical and mechanical specifications of all items mentioned and includes some handy reference tables.

Supercat Electronics Ltd, PO Box 201, St Albans, Herts. AL1 4EN.

### WIDE RANGE OF CIRCUIT BOARDS

BICC-Vero Electronics now has available its new circuit board catalogue which is claimed to contain the widest range offered by one manufacturer.

Of special note from the range of circuit boards offered are new eurocards, extender boards, the recently introduced Microbus euro-card backplane system, and the comprehensive range of microprocessor boards and backplanes. These include VME, S100, Motorola Exorsiser, Intel Multibus, STD bus and Apple.

The new catalogue, which has 40 full colour pages, details over 150 standard circuit boards plus a host of associated accessories such

as card handles, stand-offs, header and socket pins, pin insertion tools, spot face cutters and component carriers.

Hedge End Industrial Estate,  
Flanders Road, Hedge End,  
Southampton SO3 3LG  
Telephone: (04892) 81424/5.

### UPDATE ON STANDARD RANGE TRANSFORMERS

A leaflet available from Avel-Lindberg gives specification details including: primary voltages, nominal load, secondary volts and current, dimensions, weight, and mounting details for fifty 'Standard Range' power

transformers in a 15 to 130VA load rating.

Fifteen are provided with printed circuit style pins, ten with PCB pins and an extra wound screen, and twenty-five with flexible leads.

All the toroidal transformers are fully encapsulated in resin-filled thermoplastic cases which offer protection against mechanical damage and permit operation in hostile environmental conditions. They have the characteristics, inherent in toroidal construction, of an 8:1 lower radiated noise field, low volume, weight, and height profile, high efficiency and

low open circuit power. The leaflet also gives details of the various methods of connexion, performance details, and distributors.

Avel-Lindberg Limited, South Ockendon, Essex RM15 5TD.  
Tel: 070 885 3444.

### COMPATIBLE HIGHER-DEFINITION TELEVISION

A new volume – 'Compatible Higher-Definition Television' – has been published by the Independent Broadcasting Authority as the twenty-first in the series of occasional engineering texts that have been provided as a service to broadcast engineers and students since 1972.

This new 48-page book, with many two-colour illustrations, reflects recent interest in the development of television systems capable of providing significantly higher quality colour pictures than are possible on any of the present broadcast standards.

While a number of systems using more than 1000-lines per frame of picture definition and with an improved width-to-height ratio have been demonstrated, most of these would be incompatible with the hundreds of millions of existing 625-line or 525-line television receivers throughout the world.

In this book nine research engineers of the IBA and of Philips Research Laboratories discuss the requirements and technical problems still involved in enhancing television pictures seen in the home. They describe current work aimed at making this possible, including the use of low-cost digital processing in receivers in conjunction with an enhanced-MAC (multiplexed analogue component) satellite transmission system.

Contents: 'Introduction' by J B Sewter, IBA's Assistant Director of Engineering (Network and Development); 'Why non-compatible high-definition television?' by T J Long; 'Signal processing for higher-definition television' by G Tonge; 'Extended-definition MAC' by Dr M D Windram, R Morcom and T Hurley; 'Consumer displays for hi-fi television' by Dr C A A J Grebe, L J van de Polder and S L Tan.

Enquiries to IBA Engineering Information Service, Crawley Court, Winchester, SO21 2QA.  
Tel: Winchester (0962) 822444.







# AMATEUR RADIO

★ INSTANT HP FACILITIES ★ ACCESS ★ BARCLAYCARD ★ FREE FINANCE ★ MAIL ORDER

## YAESU

0010 FT1	Gen Cov HF 1'ceiver	PHONE
0020 Key T901	Curtis keyer for above	28.75
0030 DC11	DC power cable	10.35
0040 RAMT1	Non-volatile mem board	13.80
0050 FMU11	FM unit	42.85
0060 XF89KC	300Hz CW filter	18.40
0070 XF89KC	600Hz CW filter	18.40
0080 XF89KC	6kHz AM filter	18.40
0090 XF107KC	CW filter	16.65
0100 FT380	Gen cov HF 1'ceiver	PHONE
0110 SP980	Matching speaker	58.65
0120 FT102	9 band HF transceiver	PHONE
0130 FC102	9 band matching atu	179.00
0150 FV102DM	Remote vfo for above	230.00
0200 FM AM	External speaker	52.50
0240 MH1B8	Unit for above	46.75
0290 FT77	Scanning hand mic.	14.95
0450 Marker unit	8 band 100 watt 1'ceiver	PHONE
0460 FM unit		10.35
0410 FP100		27.20
0420 FC100	PSU for FT77	125.00
1449 FL100Z	ATU for FT77	98.30
0810 FT290R	160-10m linear amp	459.00
0840 FT390R	2m Multimode portable	269.00
0860 FC11C	70cm Multimode Portable	269.00
0880 C5C1A	FT290/790 AC charger	9.95
0870 MMB11	FT290/790 carrying case	4.20
0900 FL2010	FT290/790 Mob mount	26.85
0700 FT208R	290R Linear amplifier	63.25
0710 FT208R	2m FM handheld 21W	198.00
0750 NC9C	70cm FM handheld 1W	175.00
0720 FWB2	Slow charger	8.80
0740 FBA3	Spare Ni-cad battery pack	21.45
0760 NC7C	Charging sleeve	5.65
0770 NC8C	Base master charger	32.95
0780 PA3	Base master quick charger	54.05
0800 MMB10	Charger 12V DC	15.25
1000 FT238R	Mobile mounting bracket	8.05
1010 FT238R	2m 25W FM mob 1'ceiver	PHONE
1020 FT268R	70cms 10W FM mob 1'ceiver	229.00
1030 430T26	3 band all mode base station	PHONE
1050 40T26	70cms module	250.00
1051 41T26R	6 metre module	185.00
1060 41T26	HF module	200.00
1090 FRG7700	Full duplex x/band unit	55.00
1100 FRG7700M	0.2-30MHz gen cov rec	PHONE
1110 MEMGR7700	7700 with memory unit	69.00
1120 OCRG7700	Memory module	1.38
1130 FR17700	DC modification kit	46.00
1201 FRA7700	Antenna tuner unit	41.80
1140 F5	Active Antenna	10.75
1150 FRV7700A	Low pass filter	66.25
1160 FRV7700B	118-130, 130-140, 140-150MHz	90.85
1170 FRV7700C	118-130, 140-150, 50-59MHz	80.50
1180 FRV7700D	140-150, 150-160, 160-170MHz	87.40
1190 FRV7700E	118-130, 140-150, 70-80MHz	89.70
1200 FRV7700F	118-130, 140-150, 150-160MHz	89.70
0490 FT750GX	118-130, 150-160, 170-180MHz	PHONE
	Multi Mode Gen Cov	

## ICOM

IC751	* NEW * 100W H.F.	PHONE
IC745	* NEW * 100W H.F.	PHONE
RC10	Keyboard Freq. cont.	PHONE
PSU(int)	230v AC power supply	149.00
FMEX2421	FM module for above	32.50
KEYEREX2431	Keyer module for above	20.00
IC730	100W HF trans 12V DC	659.00
FL20	SSB pass band filter	29.00
IC720A	100W HF trans plus gen. cov.	989.00
PS15	230v p.s.u. for HF 1'ceivers	119.00
PS20	230v chopper type unit	195.00
FL45	500kHz filter for 740/730	38.00
FL44	2.4kHz SSB filter	79.00
FL32	CW narrow filter for 720	39.00
FL34	AM filter for 720	29.00
EX202	LDA unit for 730	13.50
EX203	CW audio filter for 730	14.50
EX205	TRV unit for 730	14.00
IL10	Memory back up for 720	5.95
IC2KL + PSU	500W solid state linear	1303.33
AT100	100 watt HF Auto ATU	269.00
AT500	500 watt HF Auto ATU	369.00
CF1	Cooling fan	24.00
SP3	Matching ext speaker	45.00
HP1	Communication phones	34.50
SMS	Base microphone	34.50
IC-R70	Comms rec 230v AC	549.00
FM unit	Plug in module	30.00
FL63	CW narrow filter	39.00
FL44	Xtal filter	79.00
IC250H	Multimode 2m 12v DC	469.00
BU1	Back up supply	24.50
IC471	Multimode 70cm	699.00

## ICOM CONT.

2450 IC490	Multimode 70cm 12v DC	495.00
2480 IC2E	2m synth h/held 1.5w Special	169.00
2490 IC4E	70cm synth h/held 1.5w	219.00
2475 IC2E	144MHz h/held with k/b + LCD	229.00
2476 IC4E	432MHz h/held with k/b + LCD	T.B.A.
2810 MMB10	Mobile mounting bracket	12.50
2840 MMB12	Mobile mounting bracket	12.50
2870 HM7	8 pin hand mic.	14.95
2880 HM9	L/S mic for IC2E/4E	16.50
2900 HM10	Up/down scan mic.	29.00
2950 SM2	4 pin desk mic.	34.50
2960 SM5	8 pin desk mic.	34.50
2962 SM6	Desk mic (745/751/271/471)	34.50
2970 SP3	External loudspeaker	45.00
2520 LC3	Cases for IC2E/4E	5.00
2570 BC25	Standard mains charger	6.69
2590 BC30	Base hnd type charger	56.35
2610 BP2	Low voltage pack	38.00
2620 BP3	Standard pack	25.00
2630 BP4	Empty battery box (AA cells)	7.95
2640 BPS	High power battery pack	48.00
2650 CP1	Charger lead for 12V supply	4.95
2660 DC1	12v Regulator pack	9.75

## TRIO/KENWOOD

1450 TS300S	160-10m 1'ceiver with gen cov	1095.00
1460 AT300	Automatic ATU 80-10m	141.75
1470 SP300	External speaker unit	98.00
1490 YK88A-1	6kHz AM filter	33.25
1500 YK88C-1	500Hz CW filter	33.25
1510 YG455C-1	500Hz CW filter	77.50
1520 YG455C-1	270Hz CW filter	91.75
1530 TS430S	160-10m with gen cov rec	736.00
1540 PS430	Mains PSU for TS430S	112.75
1550 SP430	Speaker for TS430S	28.50
1570 FM430	FM option unit TS430S	34.50
1580 YK88C	500Hz CW filter	31.75
1590 YK88CN	270Hz CW filter	37.25
1600 YK88SN	1.8kHz SSB filter	32.50
1850 TL32	160-10m 2kw linear	724.50
1870 MC60 N4	Desk microphone	51.50
1880 MC60 S6	Desk mic with up/down	53.50
1890 MC60A	Desk mic with pre-amp	55.25
1900 MC35S	Fist microphone 500ohm imp	14.75
1910 MC30S	Up/down mic for TR9000/7800	14.75
1920 MC40S	Up/down mic (TS930S)	15.25
1930 MC42S	LF low pass filter	21.25
1940 LF30A	2m/70cm all mode 1'ceiver	765.00
1950 TS780	2m multi mode mobile	433.50
1980 TR9130	FM transceiver 2m/70cm	425.00
1934 TW4000	2m FM synth handheld	219.00
1680 TR2500	Base stand and charger	51.75
1700 ST2	Soft case and belt hook	13.75
1710 SC4	Desk mic and power unit	31.75
1720 MS1	Speaker/microphone	18.80
1730 SMC25	Deluxe leather case	24.00
1750 LH2	Power supply from 12V	16.00
1770 DC25	70cm handheld trans.	225.00
1780 TR3500	70cm multimode mob.	395.00
1790 TR3500	Gen cov rec 150kHz-30MHz	239.00
1800 R600	Gen cov rec	389.00
1820 RC10	World time clock	62.00

## DATONG

3880 PC1	Gen cov converter	137.40
3870 VLF	Very low frequency converter	29.50
3670 ANF	Freq agile audio filter	67.85
3660 FL2	Multi-mode audio filter	89.70
3650 RL3	Auto filter for receivers	129.00
3700 ASP/B	r.f. speech clipper for Trio	82.80
3700 ASP/A	r.f. speech clipper for Yaesu	82.80
3710 DT5	Manual RF speech clipper	56.35
3740 OT0	Morse Tutor	56.35
3750 MK	Keyboard morse sender	137.40
3910 RFA	RF switched pre-amp	33.50
3800 AD270	Active dipole indoor	47.15
3820 AD370	Active dipole outdoor	64.40
3810 AD270-MPU	As above with mains p.s.u.	51.75
3830 AD370-MPU	As above with mains p.s.u.	69.00
3990 MPU	Mains power unit	6.90
3730 RFC/M	RF speech clipper module	29.90
3920 PTS1	Tone squelch unit	46.00
3640 SRB2	Auto Woodpecker blanker	86.25

## MICROWAVE MODULES RANGE

3130 MML28/100-S	10m 100W lin/preamp	129.95
3140 MML70/50	4m 50 watt lin/preamp	85.00
3150 MML70/100-S	4m 100W lin/preamp	139.95
3160 MML144/30S	2m 30W linear amp	69.95
3170 MML144/100-S	2m 50W lin/preamp	85.00
3180 MML144/100S	2m 100W (1 or 3W i/p)	139.95
3190 MML432/30L	70cm 30W lin/preamp	99.00
3200 MML432/50	70cm 50W lin/preamp	109.95
3210 MML432/100	70cm 100 watt linear	228.65
3220 MML432/50	70cm ATU con, VHF out	37.90
3250 MMC435/51	70cm ATU con, UHF out	27.90
3260 MMC435/600	70cm ATU 20W t'mitter	149.00
3270 MTV435	Converter with keyboard	99.95
3280 MM1000KB	RTTY to TV converter	189.00
3300 MM2001	RTTY term with keyboard	299.00
3320 MM4001KB	The MORSETALKER	115.00
3330 MM51	Advanced morse trainer	109.00
3340 MMS2	10m linear transverter	109.95
3350 MMT28/144	4m linear transverter	119.95
3360 MMT70/28	4m linear transverter	109.95
3370 MMT70/144	70cm linear transverter	159.95
3380 MMT144/28	70 cm linear transverter	184.00
3390 MMT432/28-S	23cm linear transverter	184.00
3400 MMT1236/14-R	27MHz to med wave conv	19.95
3410 MMT1236/14-R	10m to 2m up conv	29.90
3425 MMT27/MW	8m to 10m down conv	29.90
3430 MMT28/144	4m to 10m down conv	32.90
3440 MMT50/28	2m to 10m down conv	29.90
3450 MMT70/28	2m to 10m down conv	32.90
3460 MMT70/28L0	2m to 10m down conv	32.90
3470 MMT144/28L0	70cm to 2m down conv	37.90
3480 MMT432/28-S	70cm to 2m down conv	37.90
3500 MMT432/144-S	23cm to 2m down conv	34.90
3510 MMT1236/28	23cm to 2m down conv	69.95
3520 MMT1236/144	1691MHz Meteosat conv	129.95
3530 MMT1691/1375	10m low noise preamp	16.95
3540 MMTA28	2m RF switched preamp	34.90
3550 MMTA144V	23cm low noise preamp	75.00
3560 MMTA129	500MHz digital freq meter	29.90
3570 MMT6000/500	600MHz-10 precaler	14.90
3580 MMT6000P	Freq counter amp/probe	29.90
3590 MMTD1P	384MHz freq source	11.90
3600 MMT384	15dB, 10W attenuator	
3630 MMR15/10		

## AZDEN

4060 PCS4000	2mFM transceiver 25W	229.00
4130 MEX55	Mobile boom safety mic	28.50

## FDK

5779 M750XX	2m FM/SSB/CW 10W 1'ceiver	315.00
5782 EXP 430	M.750 70cm transverter	249.00
5772 KP100	AC/DC Electronic Keyer	69.00
5780 ATC720	Synth air monitor 110-138MHz	159.00
5781 RX40	Synth FM mon 140-180MHz	149.00

## MUTEK LTD

5850 SLNA 50s	50MHz low noise switched preamplifier using BF981	37.10
5860 SLNA 70s	70MHz low noise switched preamplifier using BF981	37.10
5870 SLNA 70u	70MHz low noise unswitched preamplifier using BF981	22.40
5880 SLNA 70ub	Unboxed version of SLNA 70u	13.70
5890 SLNA 144s	144MHz low noise switched preamplifier using BF981 (0.9dB noise figure)	37.10
5900 SLNA 144u	144MHz low noise unswitched preamplifier using BF981	27.40
5910 SLNA 144ub	Unboxed version of SLNA 144u	13.70
5920 SLNA 145ub	Transceiver optimised preamplifier with antenna c/o switching using BF981. Intended for the FT290R, but has many other applications! Ultra-high performance environmentally housed switched gasfet preamplifier using advanced negative feedback circuitry for superb dynamic performance. Supplied with ATCS 144c controller	129.95
5940 TLNA 432s	Very high performance bipolar transistor switched preamplifier for 430-440MHz using BF069 for 1.4dBnF and 0dBm input intercept performance	74.90
5950 TLNA 432u	Unswitched boxed variant of TLNA 432s	29.00
5960 TLNA 432ub	Unboxed TLNA 432u	28.40
5970 GLNA 432u	Series 432 MHz gasfet unswitched preamplifiers	PHONE
5980 BLNA 432ub	Sub-miniature 1.3dBnF BF069 preamplifier	13.70

## MUTEK LTD

5890 BLNA 129ub	Noise r	
6000 RPB 144ub	Comple	
6010 RPB 251ub	Comple	
6020 HDRA 95u-1	1.5dBn	
6030 HDRA 95u-2	11.5dB	
6040 BBBA 500u	20-500	
6050 BBBA 850u	250-850	
6060 XBP 700ub	Microst	
6070 PPSU 012	12V (inc	
6080 CISA 001	'UHF' (r	
6090 ATCS 144s	Transm	

## WRAASE ELECT

4720 SC140	SSV	
4730 SC160	SSV	
4740 SC42A	SSV	
4775 SC-1	SSV	
4750 FG422A	Light	
4760 KB422A	Keyba	
4780 Prince	12" gr	

## SCANNING REC

5573 Sony ICF7600D	Digital	
5574 Power supply mains, f		
5580 Bearcat BC100	synthe	
5510 Bearcat BC200FB	AM	
5650 JH SX200N AM/FM V		
5651 JH SX400 26-510MHz		
5659 Gemscan Synthesised		
5641 AOR2001 Synth. 26-52		
5770 Fairmate AS32320 AM	airband	
5780 Corona CD6000 AM ai		
5781 FDK RX40 pocket synt		
5780 FDK ATC720 pocket sy	receiver	

## VHF/UHF AMPL

TONO PRODUCTS		
5340	2M-50W	40W i/p
5350	2M-100W	90W i/p
5360	MR-150W	140W i/p
5370	MR-250W	210W i/p
5380	MR28	100W i/p
5390	4M60	50W i/p
TOKYO HY-POWER LABS		
5670	HC-150	3.5MHz
5680	HC2000	1.8MHz
5690	HL-82V	2M line includes I/P
5700	HL-160V	2M line includes I/P
5709	HL-45U	70cm i/p 50W Q
5711	HL90U	70cm i/p Q/P



# EXCHANGE



AVAILABLE ON ALL LISTED ITEMS ★ RAPID DESPATCH ★ PART EXCHANGE ★

## MORSE KEYS

### HI-MOUND KEYS

5430 HK702	Up/down on marble	26.94
5440 HK704	Up/down super deluxe	17.65
5450 HK705	Up/down deluxe	13.80
5460 HK706	Up/down economy	14.60
5461 HK707	Up/down popular	13.75
5470 HK708	Basic unit up/down	13.26
5480 MK704	Squeeze keyer manipulator	12.65
5490 MK705	As 0548 with metal base	21.28
5501	Ex-ministry No. 8 key, original packing	4.95

### Benchner Products

5220 BY1	Keyer paddle (black base)	37.95
5230 BY2	Keyer paddle (chrome base)	48.30
5240 BY3	Keyer paddle (gold plated)	92.00
5250 ZA1A	Balun 3.5-30MHz for dipoles	15.00
5260 ZA2A	Balun 14-30MHz for beam antennas	17.25

## RTTY/CW READERS

### Tasco Products

5400 CWR685E	Tele reader - RTTY/CW/ASCII	768.00
5410 CWR670	Tele reader - as above, RX only	349.00
5420 CWR610E	Tele reader - as above, basic unit	159.00

### Tono Products

5270 9000E	CW/RTTY/ASCII/Editor/lite pen, term L	669.00
5280 560E	CW/RTTY/ASCII/Terminal RX	299.00
5290 350	CW/RTTY/ASCII/Terminal RX only	259.00
5300 CRT120G	VDU 12 inch green screen - mains power	125.00
5310 CRT1200G	VDU 12 inch for 80 columns	136.00
5320 HC800	Line printer centronics	449.00
5330 SK7	Plug adaptors for printers	8.90

### ICS Electronics

4900 AMT-1	Amtror RX/TX	265.00
------------	--------------	--------

## BNOS ELECTRONICS

5800 12/6A	Power supply 13.8V 6 amp, fully protected	48.30
5810 12/12A	Power supply 13.8V 12 amp, fully protected	86.40
5820 12/24A	Power supply 13.8V 25 amp, fully protected	125.45
5830 12/40A	Power supply 13.8V 40 amp, fully protected	225.40
5831 L144/1/100	1 watt input linear	138.00
5832 L144/3/100	3 watt input linear	138.00
5833 L144/10/100	10 watt input linear	115.00
5834 LPM144/1/100	1 watt input linear/preamp	172.50
5835 LPM144/3/100	3 watt input linear/preamp	149.50
5836 LPM144/10/100	10 watt input linear/preamp	155.00
5837 L144/25/180	25 watt input linear	189.50
5838 LPM144/25/180	25 watt input linear/preamp	178.00
5839 L144/10/180	10 watt input linear	212.50
5840 LPM144/10/180	25 watt input linear/preamp	

## TONNA ANTENNAS F9FT

50MHz	L(M)	W(kg)	
6100 5 element	3.5	3.2	34.30
144MHz			
6103 4 element	0.87	0.5	14.95
6110 9 ele fixed	3.3	1.9	17.71
6120 9 ele portable	3.3	1.7	20.00
6130 9 ele crossed	3.5	2.0	32.43
6140 13 ele portable	4.5	2.5	31.05
6150 17 ele fixed	6.60	4.5	37.86
435MHz			
6190 19 element	3.2	1.1	20.70
6189 19 ele crossed	3.3	1.8	34.27
6200 21 element	4.6	2.6	29.62
6210 21 element ATV	4.6	2.6	29.67
144/435MHz			
Oscar Special			
6160 9 & 19 element	3.3	2.0	34.27
1.250MHz or 1.296MHz			
6213 23 element	1.8	0.9	25.90
6214 4 x 23 ele antennas - power splitter - stacking frame			148.00

Full range of J Beam, T.E.T. and Yaesu antennas available!

## WELZ

4980 SP200	1.8-160MHz PWR/SWR	88.95
4990 SP300	1.8-500MHz PWR/SWR	97.00
5000 SP400	130-500MHz PWR/SWR	88.95
5010 SP600	1.8-500MHz PWR/SWR	97.00
5040 SP10X	1.8-150MHz PWR/SWR	24.45
5020 SP15M	1.8-160MHz PWR/SWR	35.00
5030 SP45M	130-470MHz PWR/SWR	51.00
5050 SP250	1.8-600MHz PWR/SWR	49.50
5060 SP350	1.8-500MHz PWR/SWR	58.95
5080 AC38	3.5-30MHz ATU 400w PEP	65.00
5160 TP65X	50-500MHz 0-5W meter	13.95
5131 CA35A	Static protector	10.75
5132 CA23N	Static protector	12.80
5090 CT15A	15/50W dummy load PL259	7.95
5100 CT18N	15/20W dummy load N plug	13.95
5110 CT150	150/400W dummy load	35.50
5120 CT300	300/1kW dummy load	49.50
5130 CT03N	3W dummy load 1.3ghz	30.00
5140 CH20A	2 way coax switch SO239	17.95
5150 CH20N	2 way coax switch N socket	31.95
5133 DF72C	144/430MHz duplexer	19.95

## A.R.E. SPECIALS - OUR OWN IMPORTS

### ALINCO VHF/UHF AMPLIFIERS

5720	2m linear 30W O/P 1-3W I/P	49.00
5730	70cm linear 10W O/P 1-3W	59.00
5740	AS 5730 30W O/P	119.00
5741	AS 5720 but with switched pre-amp	69.95
5742	ELH260D 2m linear 50W O/P 1-3W I/P switched pre-amp	114.95

### VHF/UHF SCANNING RECEIVER

5770	Fairmate Airband VHF and UHF	149.00
------	------------------------------	--------

### ROTATORS

9121	EMR400 Alinco med. duty rotator	79.00
9271	EMRBB Lower mast clamp	10.00

### BOOKS

9680	Confidential Frequency List	10.95
------	-----------------------------	-------

### WRAASE SLOW SCAN

4730	SC160 TX/RX slow scan boards	299.00
4740	SC422A Complete TX/RX memories	645.00
	Display models of above	475.00
4775	SC1 Full s/scan + Fax TX/RX	795.00

### VHF/UHF TRANSVERTERS

FTV107 Yaesu Transverters modified for use with:

#### YAESU

FT102/FT980/FT ONE/FT757 = £125

#### TRIO

TS930/TS430 = £135

#### ICOM

IC740/IC745/IC751/IC720A = £125

All above complete with 2M module, cables.

Fitted with 2M/70cm card - £359

Free carriage on all A.R.E. Specials

Just write or pick up the phone, quote the Stock Number together with your Access or Barclaycard and the goods are despatched within 24 hours!

If the particular item you require is not listed, dial 01-992 5767 or 092 52 29881 - Brenda and Bernie pride themselves in supplying anything in Amateur Radio!

All items over £100 carriage free. For 24 hour Securicor add £6.00. Below £100 add £2, Books £1.

All Beam Antennas Securicor only.

Goods despatched within 24 hours if held in stock.

FULL DEMONSTRATION FACILITIES AVAILABLE AT LONDON AND MERSEYSIDE.

POP-IN, HAVE A CHAT ABOUT THAT NEW RIG AND A CUP OF BRENDA'S COFFEE!

24 HOUR ANSWERPHONE SERVICE AT BOTH PREMISES AVAILABLE


OPENING HOURS  
ACTON: 9.30 to 5.30. Closed  
Wednesday  
EARLESTOWN: 10.00 to 5.00.  
Closed Monday

BARCLAYCARD

VISA



# TRIMMING CAPACITORS

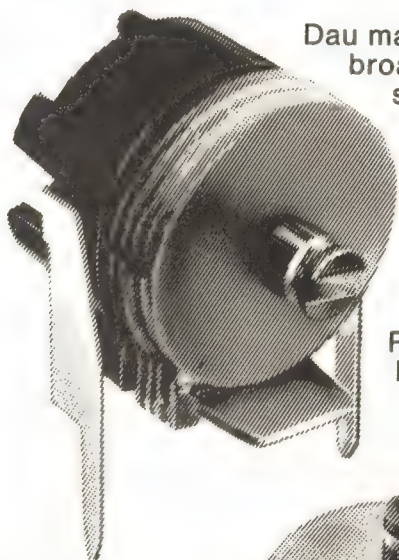

Dau manufacture the broadest range of single turn foil dielectric trimming capacitors in the world!

**Dielectrics Available:**  
Polyamid,  
Polycarbonate,  
Polypropylene  
and PTFE

## Capacitance Range:


Min C max from 3.5 pf up to 500 pf depending on series.

## Size:

5mm up to 16mm diameter.
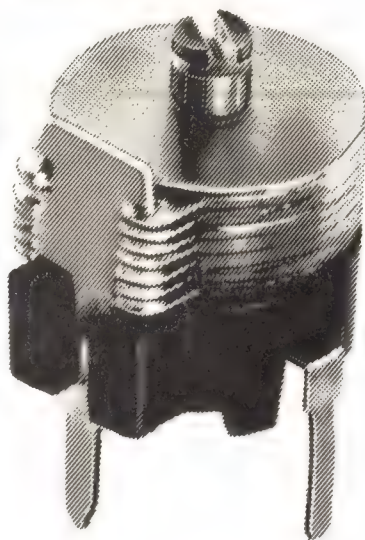
## Mounting Configurations:

Vertical and Horizontal with single or double adjustment.



## Distributor

Ambit International  
200 North Service Road, Brentwood, Essex CM14 4SG  
Tel: (0277) 230909 Telex: 995194 AMBIT G


# OEM Enquiries

TO

# DAU~UK LIMITED

Dau Components Ltd, 70-74 Barnham Rd, West Sussex  
Tel: (0243) 553031 Telex: 86843
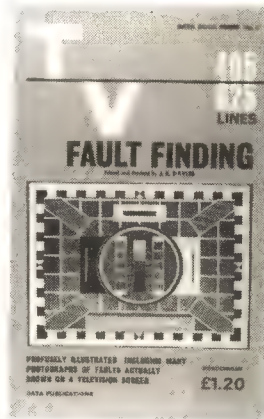
## REPAIR THAT OLD BLACK & WHITE TV with the aid of the best seller "TV FAULT FINDING"



Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

**5th Edition**  
**Edited by J R Davies**  
**132 pages**

(more than 200,000 copies sold)

Price **ONLY £1.50** (inc p&p)

Available only from:

## DATA PUBLICATIONS

45 Yeading Avenue, Rayners Lane, Harrow, Middx HA2 9RL

## Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

**My all-inclusive prices quoted in the catalogue are the lowest. All below Normal trade price — some at only one tenth of manufacturers quantity trade.**

Millions of components: thousands of different lines

Rechargeable Nickel cadmium batteries Ex-unused Equipment  
AA (HP7) 1.25V 500 MA ..... Set of 4 **£2.00** Container of 10 **£5.00**  
Clear LED illuminates red, green or yellow depending upon polarity/current,  
oblong 5 x 2 1/2mm face ..... **25p** or 100 for **£23** or 1000 for **£200.00**  
5mm Red Flashing LED ..... **25p** or 10 for **£2.25**  
Watch/Calculator/Lighter etc, Mercury batteries  
RW52 (PX 675) RW54 ..... made by Ray-O-Vac  
RW56 (DH 323, WH8) ..... **31p** Each or 10 for **2.60**, 100 for **£21.00**  
RW57, RW58 .....  
IN 4004 or IN 4006 Diodes ..... 300 for **£6.48**  
TO5 or TO18 Heatsinks ..... **7 1/2p** 100 for **£6.50**, 1000 for **£55.00**  
Clipover Heatsink for I/C or TO202 Device 21 x 18mm — **18p** or 100 for **£16.50**  
or 1000 for **£155**.  
Heatsink for TO3 or plastic power **19p** 100/**£17.50** 1000/**£165**  
Modern Telephone Handset and lead in white, red, blue, grey, yellow, green  
or black ..... **£2.00**  
Plessey SG403, 3wt amp. From bankrupt source hence sold as untested, at 4 for  
60p; 10 for ..... **£1.20**

**SEND PAYMENT PLUS 16p SAE OR LABEL ONLY**

Prices you would not believe before inflation!

## BRIAN J REED

TRADE COMPONENTS  
ESTABLISHED 27 YEARS

**161 St Johns Hill, Clapham Junction, London SW11 1TQ**

Open 11am till 6.30pm Tues. to Sat. Telephone: 01-223 5016




# THE PIANO KEYER

**For around a fiver you too can play perfect morse! G D Wilson, GM3NUF, describes how this can be done**



*The piano keyer in use*

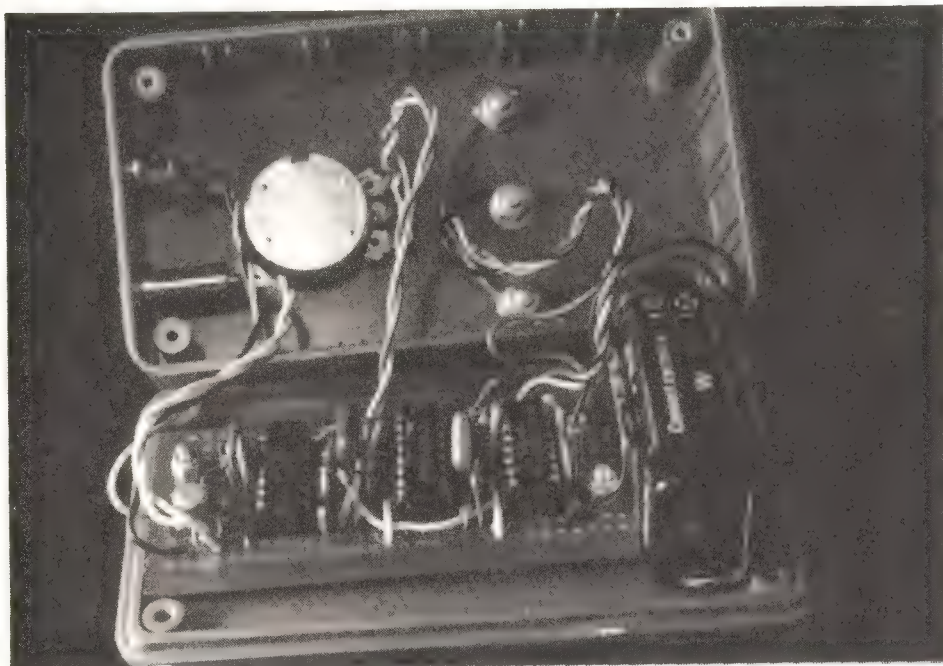

**General view:** in upper part of box, two output jacks, RV1, three key connections. Circuit board (left to right) TR1, IC3, IC2, IC1

The decision to develop and construct a fully automatic keyer was forced upon me after unsuccessfully trying to master a complicated semi-automatic bug key. This super-deluxe keyer cost nearly a week's pay (it was on loan, need I say!) It required several carefully set-up adjustments and it defeated my careful efforts to send correctly timed and spaced dots and dashes. One look at this chrome-plated 'mechanic's delight', (beautiful – but Heath Robinsonish), and it was immediately obvious that, with ICs at a few pence apiece, a cheaper and easier way to send perfect code would be possible.

## Requirements

The main criteria for the new electronic keyer were:-

1. Self-completing dots, dashes and spaces, thus allowing one to send perfect code with an effortless and sloppy action!
2. Speed to be continuously operator-adjustable from about 10 to 30 words per minute.
3. Mechanically simple, i.e. no awkward paddle to construct with its attendant pivot, adjustable stops and tension springs.
4. Compatibility with positive keying line transmitters, but with the possibility of easy modification to relay keying and interfacing with any transmitter.
- 5 Side-tone monitor. Although most modern transmitters have side-tone monitoring, this facility on the keyer allows it to be used for practice purposes.

Of the above points, the mechanical keying arrangements gave the most cause for head-scratching, though the final solution is delightfully simple. Several simplified forms of paddle were considered, some using lever operated microswitches. However, by chance I was led to try touch-sensitive switches with such promising results that further attempts to construct a suitable paddle were abandoned. The touch-sensitive keys are very positive and keying is effortless at high speeds. The downwards pressure keying operation elimin-



# PIANO KEYS

ates any tendency for the keyer to 'walk' across the table. Although the operation is very different from the old pump-handle brass-pounder, and the conventional bug key, only a few hours practice are necessary for keying to become almost instinctive.

## Additional features


As well as the initial criteria the following advantageous features were also achieved:-

1. Electronically simple, - only 3 ICs and one transistor are the active devices.
2. Low power consumption - about 0.5mA when keying. No standby drain, no ON/OFF switch required.
3. Mechanically simple - no moving parts.
4. Pocket size and light weight. Ideal portability.
5. Low cost - about a fiver should cover it, assuming that you have a few bits and pieces in your junk box.

## Morse code generation

The Morse Code timing is such that dot elements and element spaces are equal, and dash elements are equal to three dot elements, see Figure 1. A string of dots can be produced by a multivibrator (MVB) that has a 1:1 mark/space ratio. A string of dashes is more difficult as it must have a 3:1 mark/space ratio.

Some early electronic keyer circuits used two multivibrators with a ganged

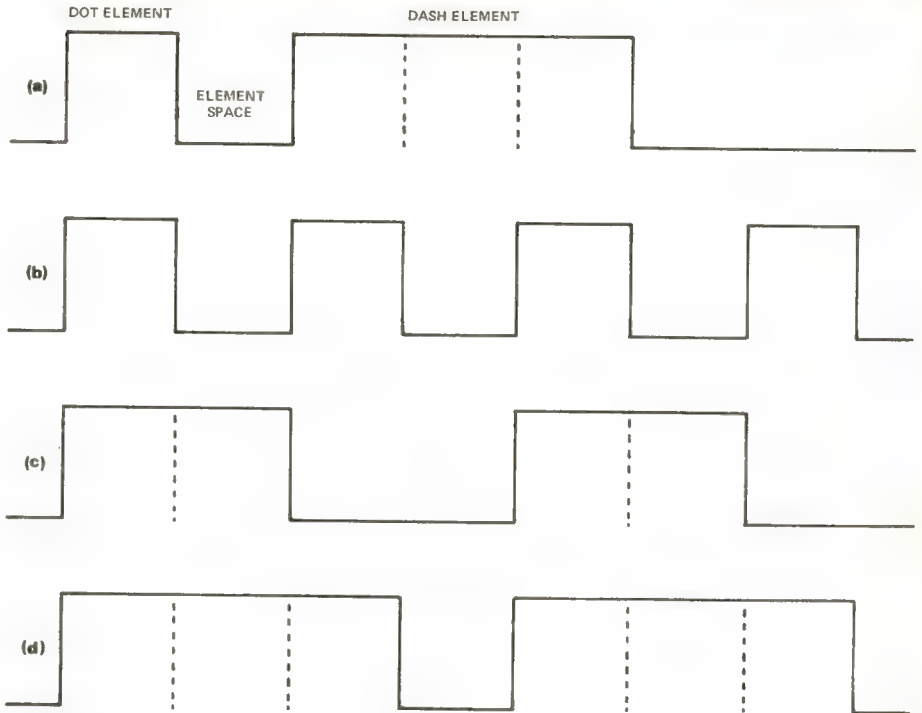


**Fig 1** Morse code generation **a)** Dot and dash timing **b)** Dot MVB output **c)** Divider output **d)** b+c = dashes

speed control, but apart from the problems of achieving accurate tracking of both speed and mark/space ratio over the speed range, the transitional ele-

ment space when going from dot to dash, or vice-versa, was entirely dependent on the speed of the operator.

One soon arrives at the conclusion that

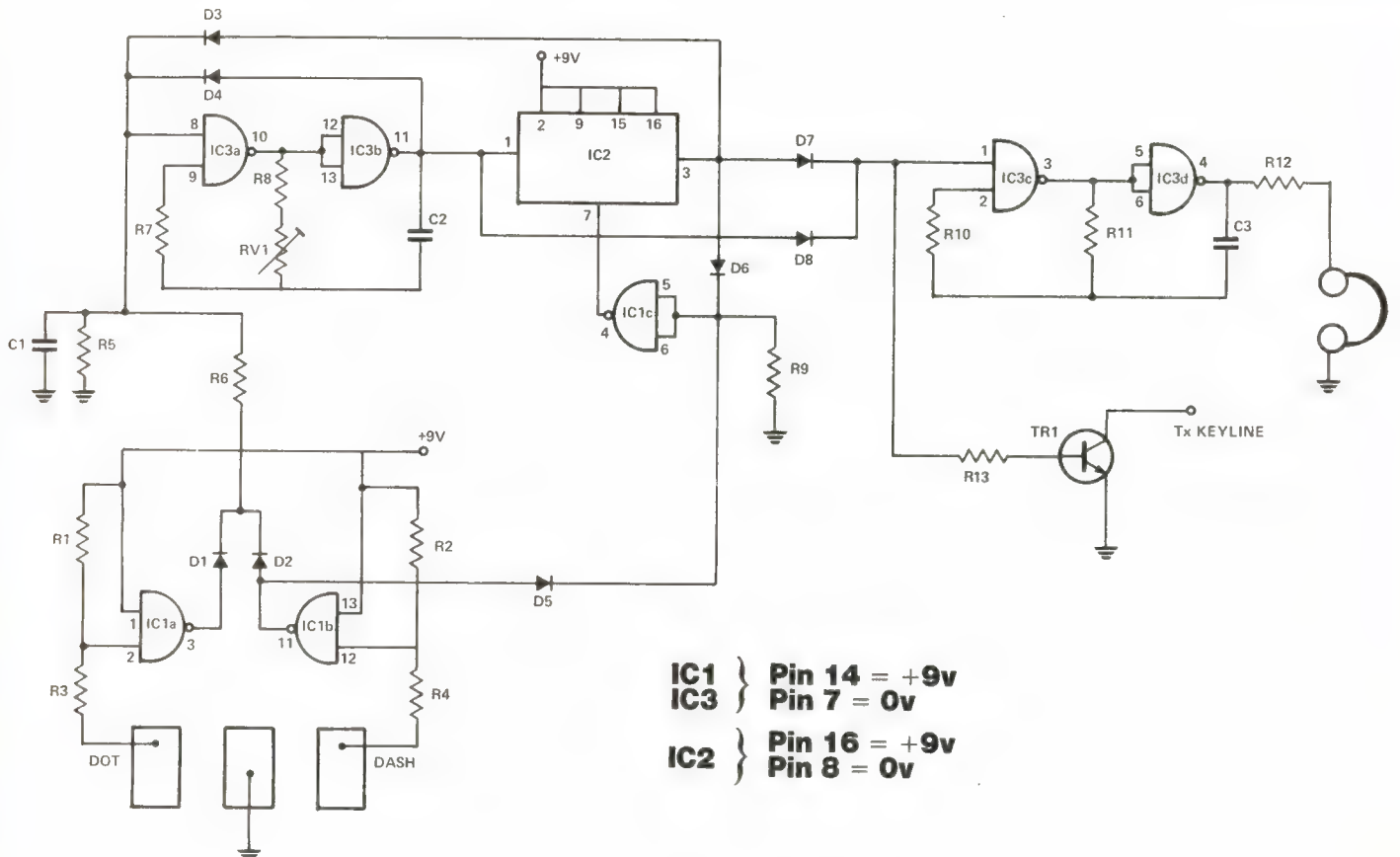

**Fig 2** The circuit diagram



# PIANO KEYER

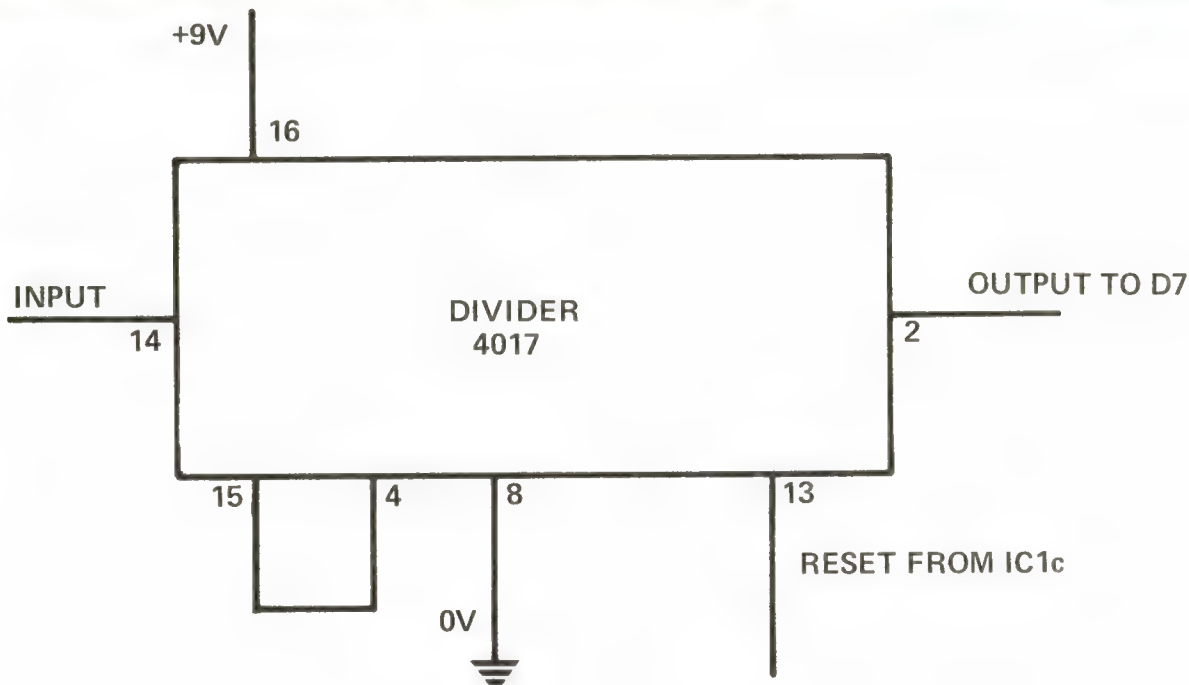


Fig 3 Alternative divide-by-two using 4017

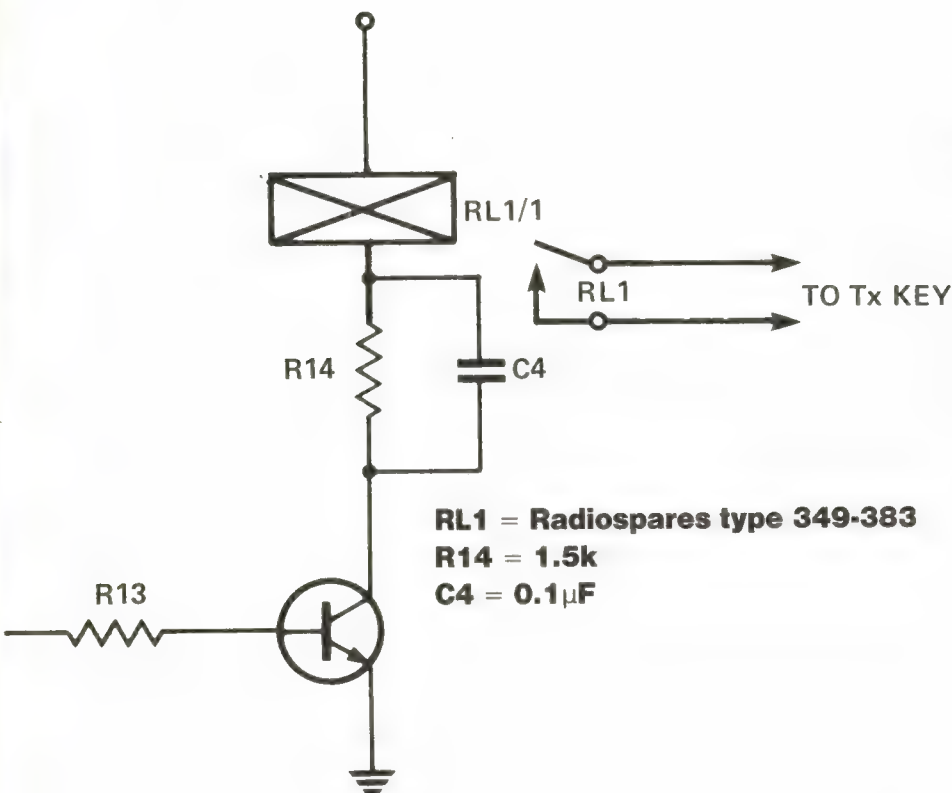


Fig 4 Alternative keying circuit using relay

with the third finger. The keyer is semi-iambic in that dashes can be produced without lifting the first finger off the dot contact.

## Circuit description (refer to Figure 2)

In the circuit to be described the divide-by-two is performed by a CMOS chip, the 4518, a package which contains two independent decade dividers one of which is not used. The 4518 just happened to be in the junk box at the time, but another popular divider, the 4017, was later tried and found to be satisfactory. However an advantage of the 4518 is that the redundant half could be used to divide the initial multivibrator by two to ensure an absolute 1:1 mark/space ratio. Scope observations indicate that this is not necessary and so it was not done in my case. In the following a '1' refers to a high positive voltage, and '0' is zero or low voltage.

## Dots

When the Dot and Earth keys are bridged by two fingers a '1' appears on IC1a pin 3, connected through D1 to IC3a, pin 8, the 'dot multivibrator/(MVB) enable'. IC3a & b form an astable multivibrator whose speed is controlled by RV1, and whose oscillation is dependent on a '1' on pin 8. The output mark/space ratio is as near as makes no matter 1:1, but this can be checked with a 'scope or a voltmeter. The dot stream passes through D8 and R13 to the base of TR1, the keying transistor. The dot element '1' drives TR1 ON and effectively grounds the TX keyline which is connected to the open collector of TR1. Within the keyer and up to the base of TR1 a '1' represents a key-down condi-

the easiest solution is to have one multivibrator for dots and to produce dashes by filling in the space between two adjacent dots.

This is done by dividing the dot speed by two (doubling its length), and combining the two waveforms (Figure 1). This method ensures correct spacing

between elements within any one letter.

## Keyer operation

To operate the keyer the middle finger is placed continuously on the Earth contact. Dots are produced by touching the dot contact with the index finger, and dashes by touching the Dash contact



# SCARAB SYSTEMS

39 Stafford St, Gillingham, Kent ME7 5EN  
(0634-570441)

## AMATEUR RADIO PROGRAMS

### RTTY

	ZX.81	SPECTRUM
Cassette & PCB	£13.45	£15.00
Complete package	£25.10	£29.55
Assembled & Tested	£30.00	£35.00
New for 48K Spectrum split screen version with type ahead buffer. Please add £2.50 to above Spectrum prices.		
BBC-B	£9.20	VIC-20
PET	£7.50	3K Version
MPTU-1 RTTY/AMTOR ASCII terminal unit for use with all computer based systems.		£9.00
		£69.70

Morse Tutor programs all at £5.00 each for:-  
BBC-B ★ DRAGON 32★ SPECTRUM ★

See us at NEC April 28/29th — Stand E19

### MORE BBC PROGRAMS

CW.QSO. Complete Rx/Tx program	£7.50
MULTIFILE. A versatile filing system	£10.25
TELLTEX. 21-page VIDEO MAGAZINE	£15.00

All prices include VAT & postage. Please allow 14 days delivery. Write for further details of these and other programs.

WANTED Amateur Radio, Technical & Business software for all popular home micro's.



### TRANSISTORS

BC107/8/9	- 12p	BC184L	- 8p	BFY50,51,52	- 20p
BC147/8/9	- 10p	BC212,212L	- 8p	BFX88	- 15p
BC157/8/9	- 10p	BC327,337,337L	- 10p	BSX19	- 14p
BC547/8/9	- 7p	BD135,136	- 25p	BSX20	- 15p
BC557/8/9	- 7p	BD137,138,139	- 25p	2N2926	- 7p
BC182L	- 8p	BF195,7	- 10p	2N3055	- 50p
BC183	- 8p	BCY70	- 15p	TIP31A,32A	- 25p

### ELECTROLYTIC CAPACITORS. (Mfds/Volts)

1/25, 1/50, 2.2/25, 2.2/50, 4.7/25, 4.7/50, 10/16, 10/25, 10/50	5p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50, 33/10 — 8p.	100/16, 100/25
100/50 — 12p. 100/100 — 14p. 220/16 — 8p. 220/25, 220/50	10p
470/16, 470/25 — 11p. 470/35 — 12p. 470/40 — 15p. 1000/16	15p
1000/35 — 22p. 1000/40 — 35p. 2200/10 — 8p. 2200/25	35p
Carbon Film resistors 1/4W 5% E24 series 0.51R to 10MO	1p

100 off per value — 75p, even hundreds per value totalling 1000 ..... £7.00

Metal Film resistors 1/4W 10R to 1MO 5% E12 series — 2p, 1% E24 series ..... 3p

Mixed metal/carbon film resistors 1/2W E12 series 1R to 10MO ..... 1 1/2p

Miniature polyester capacitors 250V working for vertical mounting

01, 015, 022, 033, 047, 068 4p. 01 5p. 015, 022 6p. 0.33 & 0.47 ..... 8p

Mylar (polyester) capacitors 100V working E12 series vertical mounting

1000p to 8200p — 3p. 01 to 068 mfd — 4p. 0.1 5p. 0.12 & 0.15 ..... 6p

Subminiature ceramic plate capacitors 100V wkg vertical mounting. E12 series

2% 1.8 pf to 47 pf — 3p. 2% 56 pf to 330 pf — 4p. 10% 390p — 4700p ..... 4p

Polystyrene capacitors 63V working E12 series long axial wires

10 pf to 820 pf — 3p. 1000 pf to 10,000 pf — 4p. 12,000 pf ..... 5p

### DIODES (p.i.v./amps)

75/25mA 1N4148 2p. 800/1A 1N4006 6p. 400/3A 1N5404 14p. 115/15mA OA91	6p
100/1A 1N4002 4p. 1000/1A 1N4007 7p. 60/1.5A 1S1M1 5p. 100/1A bridge	25p
400/1A 1N4004 5p. 1250/1A BY127 10p. 30/45mA OA90 6p. 30/15A OA47	8p
Zener diodes E24 series 3V3 to 33V 400 mW — 8p. 1 watt	12p
L.E.D's 3 & 5mm Red 10p. Green, Yellow 14p. Grommets 3mm — 1 1/2p, 5mm	2p
20mm fuses 100mA to 5A Q/blow 5p. A/surge 8p. Holders p.c. or chassis	5p
High speed p.c. drills 0.8, 1.0, 1.3, 1.5, 2.0m — 22p. Machines 12V d.c.	£6.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£4.50
AA/HP7 Nicad rechargeable cells £1.50 pair. Universal charger unit	£6.00
Glass reed switches with single pole make contacts — 8p. Magnets	12p
Ranges of tantalum electrolytic caps at competitive prices.	

All prices are inclusive of VAT. Postage 20p (free over £5). Lists Free.

## THE C. R. SUPPLY CO

127 Chesterfield Rd, Sheffield S8 0RN

Return posting

# WOOD & DOUGLAS

HAVE YOU an IC4E?

Would you like 10W output?

Then you need our NEW 70LIN10 UHF Linear

This module is based on our popular 70LIN3/10E pcb which incorporates not only a well designed linear amplifier stage but also a temperature compensated bias network and full r.f. changeover facility. The PIN diode circuitry allows a straight through path during receive periods or when the power supply is disconnected making the unit failsafe to accidental damage. If you wish to use it for SSB transmissions the internal 'hang-time' will be advantageous as will the hard switching capability. Just apply 1.5W of drive for 10W output or 1W for typically 7W output!

The board is available as a pcb kit or assembled tested module without external hardware although boxes and heatsinks are available if desired.

INTRODUCTORY PRICE Kit: £32.50 Assembled: £44.25

HAVE YOU SEEN OUR PACKAGE OFFERS?

1. 500mW TV Transmit	(70FM05T4+TVM1+BPF433)	30.00
2. 500mW TV Transceive	(As 1 above plus TVUP2+PSI 433)	50.00
3. 10W TV Transmit	(As 1 above plus 70FM10+BDX35)	50.00
4. 10W TV Transceive	(As 2 above plus 70FM10+BDX35)	70.00
5. 70cms 500mW FM Transceive	(70T4+70R5+SSR1)	70.00
6. 70cms 10W FM Transceive	(As 5 above plus 70FM10)	90.00
7. Linear/Pre-amp 10W	(144PA4/S+144LIN10B)	36.00
8. Linear/Pre-amp 25W	(144PA4/S+144LIN25B)	40.00
9. 70cms Synthesised 10W Transceive	(R5+SY+AX+MOD+SSR+70FM10)	120.00
10. 2M Synthesised 10W Transceive	(R5+SY+SY2T+SSR+144FM10)	100.00

Delivery of our products is usually from stock but due to the heavy demand we have experienced in past months please allow 28 days maximum. Please include 75p for postage and handling on your total order and an SAE with any written enquiries. Telephone orders are gladly accepted or try one of our many agents such as:-

ANNLEY TECHNICAL SERVICES

AIRCOM

DEWSBURY ELECTRONICS

J BIRKETT

Bristol 632622

Abergavenny 2566

Stourbridge 390063

Lincoln 20767



TRY A KIT WE KNOW YOU WILL ENJOY IT!



UNIT 13, YOUNGS INDUSTRIAL ESTATE

ALDERMASTON, READING RG7 4PQ

TEL: 07356 5324 TX: 848702

# VIDEO SPRAY 90 from Kontakt



A video recorder is an expensive and prized piece of equipment. It needs maintenance.

Over a period of time an often indiscernible phenomena occurs. Dust and other microscopic deposits cause contamination of the magnetic head and a vital reduction of recording and production quality occurs.

Keep your video in top condition with VIDEO 90. Spray the tape head and notice the difference.

Chemically pure (99.8%) it dries rapidly and leaves no trace except the improved quality of the sound.

If you value your equipment preserve its quality with VIDEO 90.

Distributed by:

**SPECIAL PRODUCTS DISTRIBUTORS LIMITED,**


**81, Piccadilly, London W1V 0HL**

**Tel: 01-629 9556**

Cables: Speciproduct, London W1Telex: 265200 A/B RACEN



## PIANO KEYS

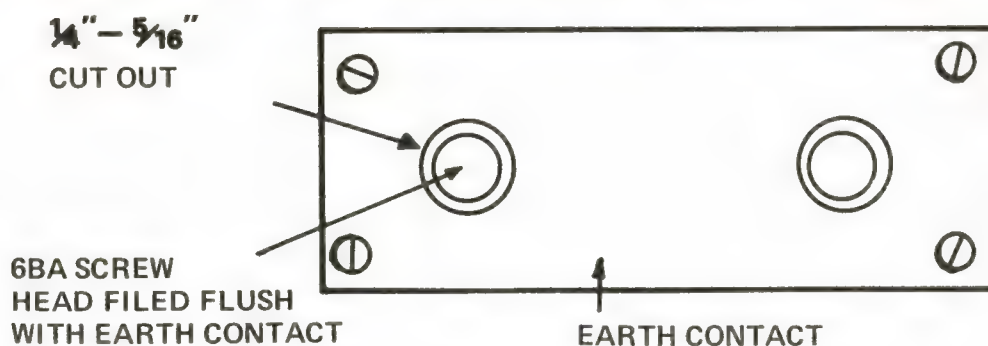

**Fig 5** Suggested alternative keying contact which may be easier to construct than three keys

tion. Note that when dots are being keyed, IC2 (the divider) is prevented from operating due to the reset pin (7) being held at '1' by the inverter IC1c.

### Dashes

When the Dash and Earth keys are bridged, a '1' appears on IC1b, pin 11, and the dot MVB is enabled as before. At the same time IC1c receives a '1' through D5 and puts a '0' on the reset pin of IC2, allowing it to operate. The output on pin 3 of IC2 is a half-speed version of the input on pin 1. This output is fed through D7 and R13 to the base of TR1. The second dot in the stream follows immediately afterwards thus completing a dash element equivalent to three dot elements. D7 and D8 form an OR gate to combine the dot stream with the output of IC2.

### Audio monitoring

IC3c & d form an astable multivibrator similar to IC3a & b except that the frequency of oscillation is of the order of 600-700 Hz. It is enabled by a '1' on pin 1 so that a key-down condition causes a tone to be heard in the headphones. The square-wave output is not unpleasant and the level is suitable for sensitive headphones of the 'Walkman' variety.

### Self-completing elements

Dots are self-completing due to the feedback action of D4 which holds the dot MVB enable at '1' regardless of whether there is a '1' coming from the key switch or not. Similarly, dashes are completed by D3 which keeps the dot MVB enabled and keeps C1 charged up, and also by D6 which, through IC3, keeps the reset pin at '0' until the output on pin 3 falls to '0'.

Capacitor C1 performs two functions in the production of dashes. Firstly, in conjunction with R6 it delays the start of the dot MVB until the capacitor has charged. This is only a question of 3 to 5mSecs and is not discernible to the operator. This delay allows the reset of IC2 to be at '0' (i.e. IC2 operative) before the '1' arrives from the dot MVB and ensures reliable switching of the divider. Secondly, C1 ensures self-completion of a dash when the key switch was only

momentarily operated. When the output of IC2 falls to '0' there is still one further dot element required to complete the dash. C1 holds the dot MVB enabled long enough to initiate this final dot, which is completed as before by the feedback of D4. If C1 were omitted, the dash would terminate after two elements only.

### Alternative circuits

A 4017 can be substituted for the 4518 and the alternative circuitry is shown in Figure 3. Almost certainly other divider circuits may be used using flip-flops etc., but I have only tried the 4017 and 4518.

### Transmitter keying

The circuit as described is suitable for my Icom IC701 and, I expect, for many of the current generation of Japanese transceivers with a positive keying line.

If the keyer is to be used with a variety of different transmitters, or to key currents in excess of, say, 20 milliamps, then it may be more practical to use a keying relay. The modified keying circuit is shown in Figure 4. TR1 now becomes the relay driver and R14 is a current-limiting resistor for battery economy. The Radio-Spares relay type 349-383 is a miniature type which mounts in a 14 pin DIL socket. Nominal operating current is of the order of 15 milliamps, so the battery consumption of the unit is drastically increased. However, reliable operation can be obtained at 4 to 5 milliamps if a speed-up capacitor is put across the current-limiting resistor. Assuming a 25-30% duty cycle during operating periods, the average battery current will be less than 2 milliamps, so several months reliable operation should be possible from one PP3.

### Construction

The keyer is built into a plastic project box which is approximately 4.5 x 2.5 x 1 inches, Radio Shack part number 270-221. The two output jacks, the speed control and the key switch contacts are mounted on the body of the box. The battery and circuit board are mounted on the inside of the lid (as shown in photos).

The circuit board is 0.1in pitch Vero-board. Layout is not critical and, no doubt, interested constructors have

their own ideas on how to get the maximum number of components into the minimum space. There is not a lot of space left over and if it is intended to include the keying relay it may be advisable to start out with the next larger size of project box.

In retrospect, a different form of key contact may be easier to construct and may give more reliability in the case of operators with exceptionally dry skin (see Figure 5). The Earth contact has two circular cut-outs (say 1/4in-5/16in) into which the dot and dash contacts are concentrically mounted (6 BA screws may be used). The decreased contact distance, and hence decreased skin resistance, may result in more reliable keying although there is no evidence of erratic behaviour by the original model.

### Conclusion

In digital logic terms there are several ways of achieving the same result, but this is the method I have used and because it worked, I have enquired no further.

Some basic corners have been cut in the interests of miniaturisation, e.g. the dot MVB is not buffered before going into the divider and the audio monitor is low level, LO-Fi. However the underlying principle adhered to throughout is that the quality of the transmitted signal is the criterion that counts the most.

### PARTS LIST

R1, R2	10M $\Omega$
R3, R4, R6, R9, R11	100K $\Omega$
R5	180K $\Omega$
R7, R10	1M $\Omega$
R8	330K $\Omega$
R12	15K $\Omega$
R13	27K $\Omega$
RV1	1M $\Omega$ Lin
C1	0.47 $\mu$ F
C2	0.1 $\mu$ F
C3	0.01 $\mu$ F
IC1, 3	4011
IC2	4518
TR1	Gen purpose NPN, BC107 etc
D1 D8	Gen purpose Si IN914 etc



**NEW 1983/84 CATALOGUE NOW AVAILABLE**—Many prices reduced—range increased—fully illustrated. Price 65p. per copy (free upon request with orders over £5)—includes 30p Credit Note, special offer sheets, order form and pre-paid envelope. **SEND NOW FOR YOUR COPY.**

TRANSISTORS			DIODES			TUBES			RESISTORS			CAPACITORS			POTENTIOMETERS			VALVES			
Type	Price (£)	Type	Type	Price (£)	Type	Type	Price (£)	Type	Type	Price (£)	Type	Type	Price (£)	Type	Type	Type	Price (£)	Type	Price (£)		
AC126	0.35	BC108	0.10	BC302	0.32	BD244A	0.55	BF258	0.30	BT101/300	1.15	BYX36/150	0.22	TIP32	0.40	VOLTAGE REGULATORS			Type	Price (£)	
AC127	0.30	ABoRc	0.12	BC303	0.32	BD375	0.32	BF259	0.32	BT101/500	1.25	BYX36/600	0.22	TIP32C	0.60	Type			Price (£)	Type	Price (£)
AC128	0.35	BC113	0.14	BC307	0.10	BD410	0.76	BF262	0.30	BT102/300	1.35	BYX48/300	0.72	TIP33A	0.63	78L05			0.30	DY802	0.88
AC128K	0.34	BC114	0.14	BC308A	0.10	BD434	0.76	BF263	0.30	BT102/500	1.40	BYX48/600	0.72	TIP33B	0.63	78L08			0.30	DY867	0.75
AC132	0.55	BC115	0.12	BC323	0.09	BD436	0.68	BF270	0.30	BT106	1.50	BYX55/350	0.29	TIP41C	0.30	78L12			0.30	ECC81	0.85
AC141	0.26	BC116	0.15	BC327	0.14	BD437	0.76	BF271	0.26	BT108	1.30	BYX55/600	0.33	TIP42A	0.52	78L15n			0.30	ECC82	0.85
AC141	0.26	BC117	0.12	BC328	0.14	BD438	0.76	BF273	0.18	BT109	1.18	BYX71/600	1.18	TIP47	0.60	78M05			0.30	ECC83	0.75
AC141K	0.40	BC118	0.17	BC337	0.12	BD439	0.68	BF274	0.32	BT116	1.25	BZ12	0.42	TIP110	0.88	78M12			0.50	ECC84	0.75
AC141K	0.40	BC119	0.12	BC338	0.12	BD440	0.68	BF275	0.42	BT119	1.62	CJ08D	0.60	P2955	0.60	78M15			0.50	ECC85	0.90
AC142K	0.48	BC125	0.12	BC350	0.14	BD450	0.59	BF336	0.26	BT120	1.80	E1222	0.30	TIP305S	0.32	78M24			0.50	ECCF9	0.95
AC151	0.45	BC140	0.28	BC440	0.30	BD509	0.54	BF337	0.26	BT121	3.02	E5024	0.30	TIS43	0.32	7805			0.30	ECH81	0.75
AC152	0.45	BC141	0.42	BC441	0.32	BD510	0.48	BF338	0.26	BT138/600	1.30	ET872	0.48	TIS88	0.40	7808			0.30	ECH85	0.75
AC176	0.28	BC142	0.30	BC461	0.32	BD517	0.55	BF355	0.42	BT151/560R	1.90	ITT44	0.04	TIS90	0.25	7812			0.55	ECL86	0.95
AC176K	0.28	BC143	0.45	BC457	0.12	BD518	0.66	BF363	0.82	BT151/300R	1.15	ITT2002	0.11	TIS91	0.11	7815			0.55	EF80	0.88
AC187	0.26	BC147	0.08	BC458	0.12	BD529	0.25	BF367	1.25	BT179/440/300R	2.30	MEO22	0.12	XI108	0.12	7818			0.55	EF86	1.75
AC187K	0.40	AoRc	0.08	BC549	0.12	BD707	0.88	BF371	0.27	BU100A	2.30	MEO40A/2	0.24	ZTX109	0.24	7824			0.55	EF86	1.75
AC188	0.28	BC148	0.08	BC550	0.18	BD718	2.35	BF422	0.38	BU104	2.00	MEU21	0.60	ZTX212	0.28	7905			0.75	F184	0.85
AC188K	0.40	AoRc	0.10	BC550C	0.18	BDX32	2.10	BF450	0.38	BU105	1.20	MJ400	1.25	IN4001	0.05	7912			0.55	EH90	0.54
AC1940	0.88	BC149	0.08	BC557	0.12	BF115	0.32	BF457	0.33	BU105/02	1.56	MJ2955	0.10	IN4003	0.03	7915			0.65	EL34	2.50
AD142	1.10	BC151	0.10	BC558	0.12	BF145	0.82	BF458	0.38	BU106	1.50	MJ3000	1.98	IN4004	0.06	7918			0.65	EL84	0.90
AD143	1.10	BC158	0.10	BC564	0.27	BF119	0.82	BF459	0.44	BU124	1.75	MJ240	0.40	IN4006	0.07	7924			0.65	EL509	5.50
AD149	0.96	BC159	0.10	BCV70	0.15	BF120	0.38	BF460	0.22	BU126	1.25	MJE340	0.54	IN4007	0.07	CA3085			0.30	EM87	2.55
AD161	0.42	BC160	0.30	BCV71	0.17	BF123	0.40	BF461	0.22	BU133	1.80	MJE370	0.88	IN4148	0.08	723C			0.30	EY86/87	0.87
AD162	0.42	BC161	0.30	BCV72	0.18	BF125	0.42	BF461A	0.22	BU204	1.35	MJE520	0.88	IN5400	0.12	LM317K			3.50	EY900A	1.65
AD162/AD162	0.96	BC168B	0.12	BC210	1.68	BF127	0.38	BF461S	0.30	BU205	1.30	MJE2955	0.10	IN5402	0.15	6035			0.15	PCB84	0.85
AF106	0.48	BC169C	0.14	BC211	1.68	BF132	0.16	BF461	0.30	BU206	1.70	MJE3000	1.98	IN5405	0.18	6035			0.15	PCB85	0.50
AF114	2.10	BC170	0.14	BD124P	0.60	BF154	0.23	BF462	0.28	BU208	1.20	MPSL01	0.29	IN5406	0.29	6035			0.15	PCB88	0.85
AF115	2.10	BC170B	0.12	BC130Y	0.68	BF157	0.40	BF468	0.34	BU208A	1.83	OA47	0.70	IN5408	0.20	6035			0.15	PCB89	0.74
AF116	2.10	BC171	0.10	BD131	0.34	BF158	0.22	BF490	1.72	BU208/02	2.05	OA90	0.08	IN5408	0.20	S, F, 10, 15, 10, 50, 100, 200, 500W			0.20	PCF80	0.75
AF117	2.10	BC171	0.10	BD132	0.34	BF159	0.22	BF491	0.38	BU326S	1.75	OA91	0.08	IN5408	0.20	20p each			0.20	PCF86	1.25
AF121	0.82	BC172	0.08	BD133/BD132	0.95	BF160	0.23	BF474	0.38	BU407	1.65	AB5	0.18	IN706A	0.55	20p each			0.20	PCF87	1.25
AF124	0.48	AoRc	0.12	BD136	0.36	BF173	0.32	BF470	0.38	BU407D	1.75	OA200	0.18	IN706A	0.55	20p each			0.20	PCF200	1.55
AF125	0.48	BC177	0.20	BD137	0.36	BF177	0.25	BF444	0.76	BUX80	3.70	OA202	0.15	IN706K	0.55	20p each			0.20	PCF801	1.45
AF127	0.48	BC178A	0.22	BD138	0.38	BF178	0.32	BF439	0.38	BUY20	1.75	OC25	2.10	IN2926G	0.15	30, 120, 270, 470, all at			0.20	PCF802	1.20
AF128	0.68	BC178B	0.22	BD139	0.38	BF179	0.32	BF430	3.58	BUY69B	1.98	OC28	1.70	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
AF178	0.68	ABoRc	0.08	BD140	0.38	BF180	0.32	BF438	0.38	BUY101	1.98	OC28	1.70	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
AF239	0.58	BC182L	0.09	BD144	1.60	BF181	0.35	BF255	0.28	BY118	0.68	OC35	1.70	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
BF279S	0.72	ABoRc	0.09	BD145	1.82	BF182	0.32	BF466	0.26	BY122	0.48	OC36	1.75	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
LI002	2.50	BC183	0.09	BD150A	0.51	BF183	0.32	BF487	0.26	BY126	0.12	OC42	1.72	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
LI020	1.88	ABoRc	0.10	BD159	0.85	BF184	0.32	BF489	0.65	BY127	0.10	OC42K	1.70	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
LI100	2.20	BC183L	0.06	BD160	1.65	BF185	0.32	BF490	0.21	BY133	0.16	OC44	1.72	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
SY890	1.75	ABoRc	0.12	BD165	0.45	BF184	0.32	BF490	0.21	BY135	0.16	OC44	1.72	IN3053	0.22	30, 120, 270, 470, all at			0.20	PCF802	1.20
UY110	1.40	BC184	0.10	BD175	0.60	BF185	0.32	BF490	0.21	BY152	0.44	OC71	1.50	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
UY102	4.32	ABoRc	0.10	BD182	1.00	BF196	0.10	BF490	0.40	BY179	0.65	OC72	1.50	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A102	0.34	BC207	0.15	BD183	1.10	BF197	0.10	BF490	0.90	BY182	0.87	OC81	0.68	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A110	0.67	BC208	0.16	BD184	1.10	BF198	0.14	BF490S	1.34	BY184	0.40	OC200	2.45	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A121	0.38	BC210	0.15	BD185	0.72	BF199	0.10	BF490	0.72	BY187	0.72	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A129	0.63	ABoRc	0.10	BD202	1.80	BF200	0.47	BF490	0.52	BY189	0.72	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A148	0.16	BC212L	0.08	BD204	0.80	BF222	0.48	BF490	0.58	BY198	0.44	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A154	0.08	ABoRc	0.10	BD222	0.80	BF224	0.20	BF490	1.78	BY199	0.44	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A155	0.10	BC213	0.09	BD225	0.88	BF224J	0.16	BF490	0.38	BY206	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A156	0.08	ABoRc	0.10	BD232	0.45	BF240	0.20	BF490	0.42	BY207	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A157	0.28	BC213L	0.10	BD233	0.10	BF241	0.20	BF490	0.42	BY210/400	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3A164	0.14	AoRc	0.10	BD234	0.82	BF244	0.26	BF490	0.56	BY210/600	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3B104B	0.52	BC237	0.11	BD235	0.63	BF244A	0.28	BF490	0.92	BY210/800	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3B105B	0.48	BC236	0.12	BD236	0.63	BF244C	0.24	BF490	0.34	BY210/800	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3B105G	0.40	BC239	0.14	BD237	0.66	BF245A	0.26	BF490	0.34	BY210/800	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
3B110B	0.38	BC251	0.12	BD238	0.66	BF254	0.15	BF490	0.62	BY210/800	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
BC107	0.10	ABoRc	0.14	BD241	0.80	BF256	0.60	BF490	0.60	BY210/800	0.24	OC202	2.20	IN3096	0.65	30, 120, 270, 470, all at			0.20	PCF802	1.20
AoRc	0.12	BC301	0.30	BD243A	0.80	BF257	0.30	BT109A/02	0.24	BYX10	0.24	TIP31C	0.54			30, 120, 270, 470, all at			0.20	PCF802	1.20

**ORDERING:** All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified) to all orders and then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome.

Send now for our latest catalogue, 65p per copy (includes 30p credit/pre paid envelopes, current special offers and lots lots more).



# R&EW Data Brief

TDA2002A

## TDA 2002A

### UNIVERSAL POWER OP-AMP AND AUDIO AMP

The TDA2002 and the slightly souped-up TDA2002A are one of the great standards in linear ICs. Most manufacturers of consumer linear ICs have a version in their range – and most enthusiasts will have seen at least a couple of circuits that feature these versatile devices.

The excessive current drain under no-signal conditions means that battery operation is out. Mains powered equipment would be better advised for using a lower current, higher voltage solution to 10W – but in a vehicular environment, the TDA2002 rules.


Apart from the obvious audio applications, the TDA2002A can drive vertical output circuits in TV sets and terminals, linear motors – and many applications where the versatility of the power op-amp configuration are applicable.

The difference between the TDA200 and the TDA2002A is that the maximum voltage rating of the latter has been enhanced to 26V DC, with a load current of 2.5A. The TDA2002A can handle up to 60 watts of power (with the right heatsink). The device is protected against thermal, transient and current overloads.

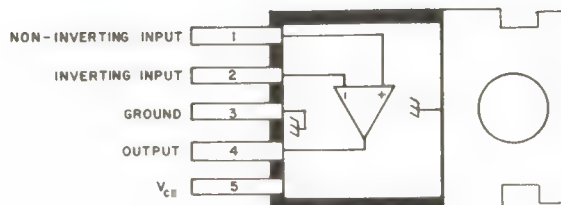
### Applications

When using the device, the usual precautions concerning high gain, high impedance, wide bandwidth devices apply: they 'take off' unless correctly earthed and decoupled. The high frequency oscillations can sometimes melt the loudspeaker voice coil before you realize what's happening, although the low frequency motorboating effects that arise from a combination of high impedance earth and supply leads will only serve to wake you up rather rudely.


The 2002A may substitute the 2002 in any application, although the cost penalty is such it is only worth the extra if you specifically require the additional voltage capabilities.


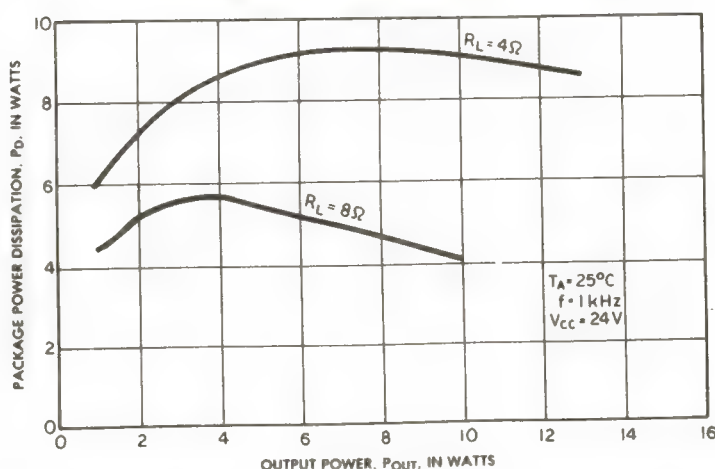
### POWER DISSIPATION AS A FUNCTION OF OUTPUT POWER



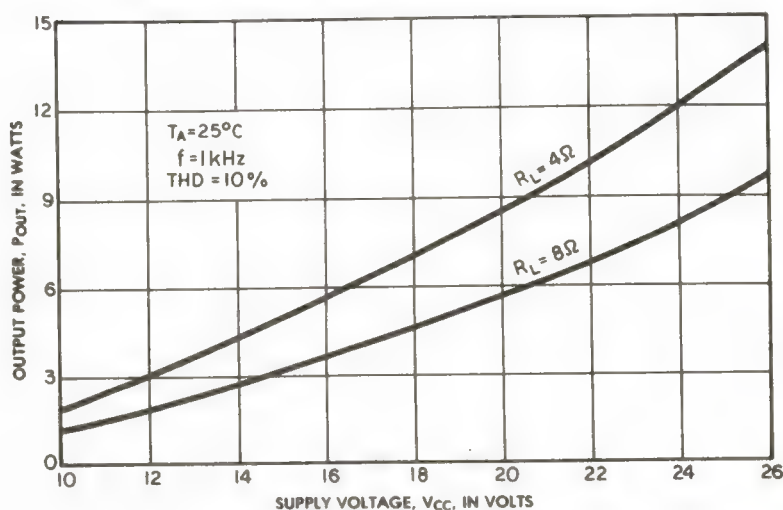
### OUTPUT POWER AS A FUNCTION OF SUPPLY VOLTAGE





# TYPICAL DC MOTOR DRIVE APPLICATIONS

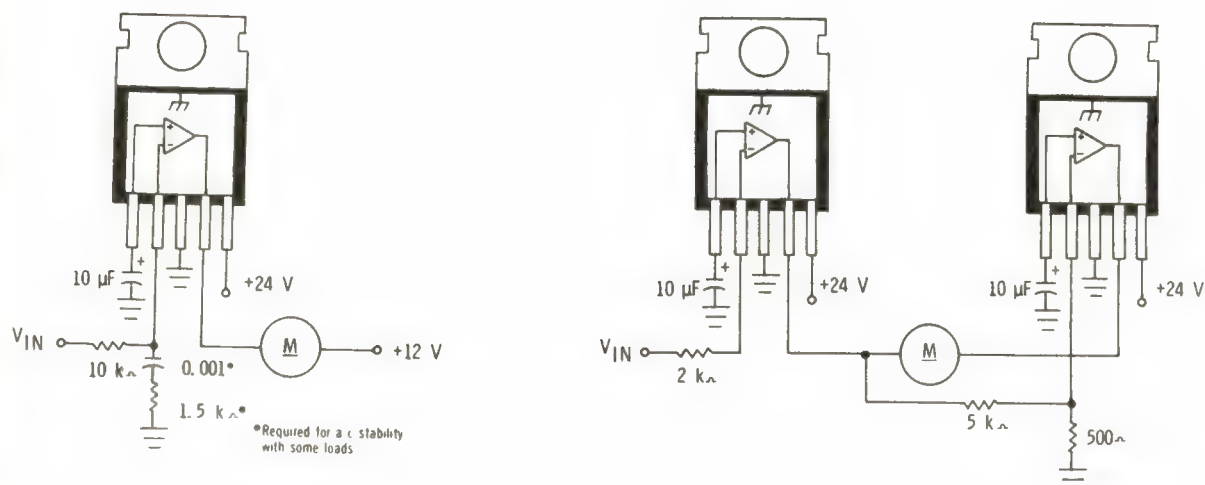

## ABSOLUTE MAXIMUM RATINGS

Supply Voltage, $V_{CC}$	28 V
Peak Supply Voltage (50 ms)	40 V
Peak Output Current, $I_{OUT}$	3.5 A
Non-Repetitive Peak Output Current	4.5 A
Package Power Dissipation, $P_D$	15 W*
Storage Temperature Range, $T_S$	-40°C to +150°C

\*Derate at the rate of 0.25 W/°C above  $T_{1AB}$  90°C

ELECTRICAL CHARACTERISTICS at  $T_A = +25^\circ\text{C}$ ,  
 $V_{CC} = +24\text{ V}$ ,  $R_L = 8\Omega$ ,  $f = 1\text{ kHz}$  (unless otherwise noted)

Characteristic	Symbol	Test Conditions	Limits			
			Min.	Typ.	Max.	Units
Supply Voltage Range	$V_{CC}$		8.0	24	26	V
Quiescent Supply Current	$I_{CC}$	No signal applied	—	80	120	mA
Quiescent Output Voltage	$V_L$	No signal applied	—	12	—	V
Open Loop Gain	$A_v$		—	80	—	dB
Closed Loop Gain	$A_v$		39.5	40	40.5	dB
Total Harmonic Distortion	THD	$P_{OUT} = 0.05$ to $3.5\text{ W}$ , $R_L = 8\Omega$	—	0.2	—	%
		$P_{OUT} = 0.05$ to $5.0\text{ W}$ , $R_L = 4\Omega$	—	0.2	—	%
Audio Power Output	$P_{OUT}$	THD = 10%, $R_L = 8\Omega$	—	8.0	—	W
		THD = 10%, $R_L = 4\Omega$	10	12	—	W
Input Impedance	$Z_i$		70	150	—	kΩ
Power Supply Rejection	PSRR	$f_{ripple} = 120\text{ Hz}$ , $V_{ripple} = 0.5\text{ V}$	30	35	—	dB
Equiv. Input Noise Voltage	$e_n$	$f = 40\text{ Hz}$ to $15\text{ kHz}$	—	4.0	—	μV
Equiv. Input Noise Current	$i_n$	$f = 40\text{ Hz}$ to $15\text{ kHz}$	—	60	—	pA
Input Sensitivity	$e_{in}$	$P_{OUT} = 0.5\text{ W}$ , $R_L = 4\Omega$	—	15	—	mV
		$P_{OUT} = 0.5\text{ W}$ , $R_L = 8\Omega$	—	21	—	mV
		$P_{OUT} = 8.0\text{ W}$ , $R_L = 4\Omega$	—	71	—	mV
Input Saturation Voltage	$e_{in}$		400	600	—	mV <sub>max</sub>
Frequency Response (-3 dB)		$C_{in} = 0.039\mu\text{F}$ , $R_{in} = 39\Omega$	40	—	15 k	Hz
Thermal Resistance	$R_{\theta JA}$		—	—	4.0	°C/W



# 'NOTES FROM THE PAST'

I have been greatly surprised at the very high proportion of hobbyists who, either by force of circumstances or choice, have a self-built workshop. They vary from lean-to's, erected against a blank wall and annexes tacked on behind the garage, to full-blown independent structures standing proudly in their own grounds.

A few years ago garden shedders were few and far between, although many handymen had some sort of outer-building used for storage, keeping the firewood dry, and rough or dirty work. Today's garden-shedders are in an altogether different category and sturdy modern buildings with space heating, strip lighting and curtained windows are apparently becoming commonplace.

With TV, FM etc., our hobby has become more and more complicated. The days have long since gone when one could get by with a soldering iron and a universal meter with the kitchen table as a workbench. Nowadays the keen types think nothing of carrying a comprehensive range of special tools and test equipment which would fill two sides of a medium-sized room.

Pre-war, too, one could practically build a set in a single evening, but a modern FM or TV receiver may well be several weeks in the making. Hence, it is nice to have a place where everything can be left undisturbed with tools and test gear right to hand.

Even those who in the past have been content with a spare corner in the house are beginning to turn to specially designed garden buildings. While a brick and concrete workshop is a mighty expensive proposition if a builder has to be called in, it is neither too costly nor beyond the capability of a versatile radio enthusiast (and most of us are that) especially if one can get the advice and assistance of someone in the building line. In fact, I have more than once been greatly surprised how economically it has been done.

## Money for old rope

Although no one has written specifically on the subject, most correspondents in recent weeks have mentioned their complete agreement with my comments on many of the ITV programmes which spell utter boredom to the intelligent viewer. Whenever I seem to have a little time to spare for casual viewing the screen is filled with interminably dreary Westerns, American quickies and stale films. It is amazing that we should spend dollars on such stuff, and to make it worse ITV are asking

the Government for another 21 hours a week – an example followed less eagerly by the BBC.

Both authorities, especially ITV would be better concerned with putting out improved programmes in their existing hours. It would be nice to have a few 'sensible' programmes. I shudder to think what is going to happen during those extra hours and can only imagine that it will be more programmes suitable for backward adolescents just merely to fill out time in order to justify even more advertising.

More readers feel it would be better, too, if ITV put the money spent on bubble cars, stole wraps, washing machines, bedroom suites, etc., into the programmes. It is to attract the lower types of mentality that such prizes are lavishly distributed for answering questions which should present no difficulty to school-children?

With the BBC sometimes even outdoing ITV in finding some of the worst of the American bookings, many people besides myself, are humbly grateful that 'steam' radio nowadays still carries a satisfying proportion of worthwhile programmes during peak listening hours. And the pleasure is doubled when one listens to them on FM.

Incidentally, three of the ITV programme contractors are increasing their advertising rates by 10% in the autumn, and a fourth on 1st January, but they will charge 20% more during peak hours (7.30 to 10.30 pm). The increases are made on the grounds that the audiences are now much larger. With this swelling of revenue no doubt we shall see really big quiz prizes (if you can only answer such questions as 'Where does Jamaican rum come from?') instead of such trifles as refrigerators and TV sets!

## Lucky for us

It is curious when you come to think of it that the additional TV hours now asked for exceed the total TV hours of a number of European countries. In Austria, for instance, they have three hours each evening except Tuesday, when there is no programme at all. A far higher proportion of their programmes are (if only for this reason) worth while sitting down to watch – instead of merely forming a background of time-filling trivialities which are allowed to drone on while various members of the family carry on doing something else and spare only an occasional glance at the screen.

It is nice, however, to think that we don't have to pay at the same rate for our TV. Their licences, which are renewable

every month cost fifty Austrian shillings (Exchange rate approx. 72 to the £1). Nor must it be overlooked that wages and salaries are considerably lower than they are here. Small wonder no one is expected to pay a year in advance at that rate, but even if one has got the cash a month is the longest period you can take.

Talking about money reminds me – suppose the BBC get the extra hours, where is the additional expenditure coming from? Surely the next move will be to put our licences up to a fiver!

I note also that the House of Commons Public Accounts Committee have turned their attention to ITA's huge profits and consider that future rentals should represent the contractor's full capacity to pay. At this, the Chairman of Associated-Rediffusion is reported as suggesting that if the commercial TV companies have to pay more rent, viewers will get inferior programmes. Which makes me wonder where they are going to find 'em.

## Magnetic attraction

Old timers will recall how we were apt to regard the early permanent magnet m.c. speakers with some suspicion, and wondered just how 'permanent' the magnets would prove to be. Well, just recently I gave the magnet of a very old one to a youngster as a plaything. Later, when he knocked over a boxful of his mother's dressmaking pins he, childlike, collected them up with his magnet. From then on, of course, every time she picked up her scissors she found scores of pins clinging and dangling all over them! Which only goes to prove we needn't have worried about the permanence of those magnets after all.

## Origin of Wharfedale speakers


Finally, more old-time memories, this time from W.G. (Bradford 3), were revived by my reference to early loudspeakers. His father-in-law, who was bedfast, was adept at making pleated paper cones which he scored lightly with a darning needle, gluing cork to the centre (instead of the sealing wax I mentioned). Also, instead of using stiff wire between the reed and cork, he used a matchstick. He considers (as did many others) that these were the best thing of their time. Later he bought one of the earliest moving coil speakers from Mr Briggs, whose newly-started business was then in a city centre Bradford basement. This enterprise has now grown into the world-famous Wharfedale business. Incidentally, that speaker gave sterling service right up to the end of the war and after.



# CONSTRUCT A PEAK-READING LED RF WATTMETER

*This practical piece of equipment will make a good addition to your test gear*

by R David Beard, WA4QGA

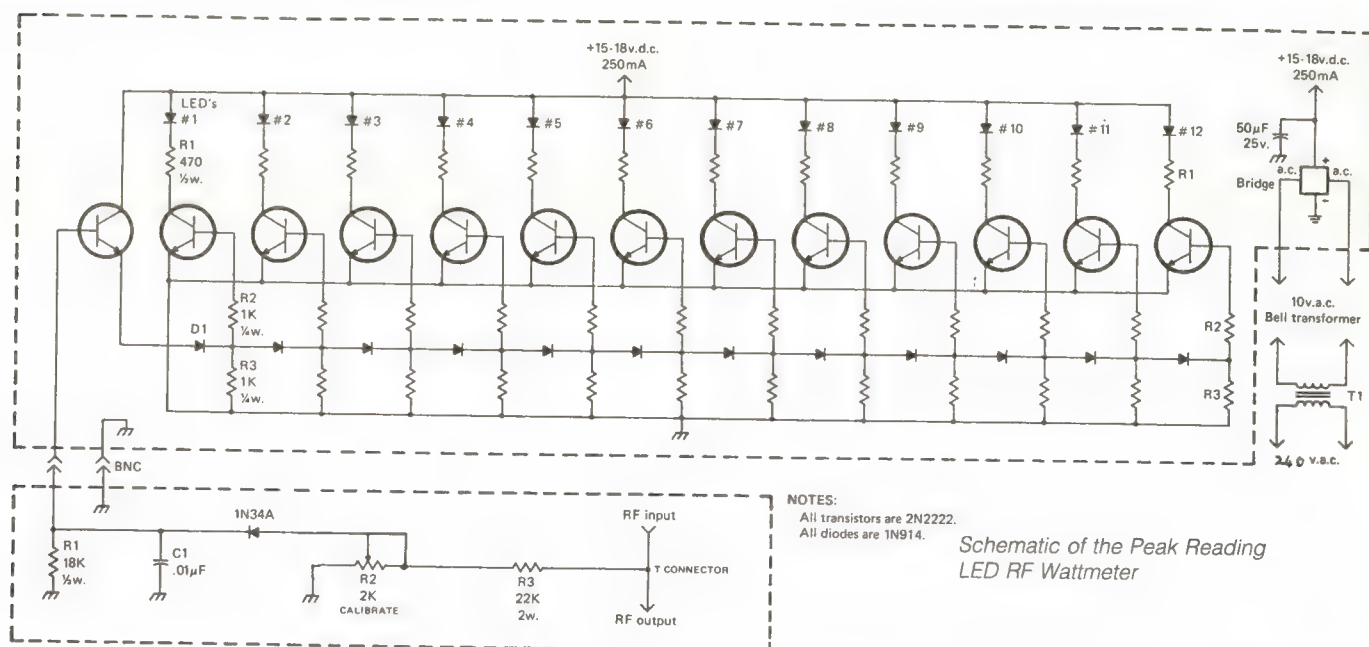


Have you ever wondered just how much power is actually travelling up the coax? The circuit diagram and following description will give you a device that is rugged, easy to build, simple to calibrate, and will tell you how much power you're running. The project is inexpensive to build and reliable in operation.

## Circuit description

The circuit, Figure 1, incorporates 12 LEDs. Each LED is driven by a 2N2222 transistor. Practically any small-signal NPN transistor will do. For turning on each LED at a discrete power levels 1N914 diodes (D1) are used. As the diodes are in series, the LEDs are turned on in sequence as each diode starts to conduct. Resistors R2 and R3 form a simple voltage divider, and resistor R1 limits collector current. Resistor values are not extremely critical as long as all


segments contain equal values. The values may be changed somewhat to accommodate on-hand junk-box values. Transistor types are also non-critical as long as all transistors are the same number.

The complete power meter is built on two separate chassis. One is the LED PCB and the other is the sampler unit. Transmission-line voltage is sampled via a 'T' connector connected to an SO-239 on a small chassis. The lower schematic enclosed in dotted lines is the sampler unit. The time constant of R1C1 is only critical in that if C1 is too large, the true peaks will not be indicated. If R1 is too large, the low-order LEDs will have a tendency to stay lit after the r.f. output has ceased, or the LEDs will have a tendency to glow upward as power increases instead of indicating discrete power levels.

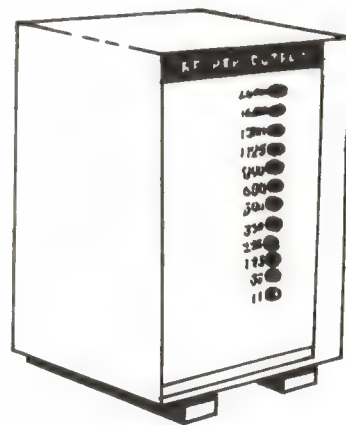

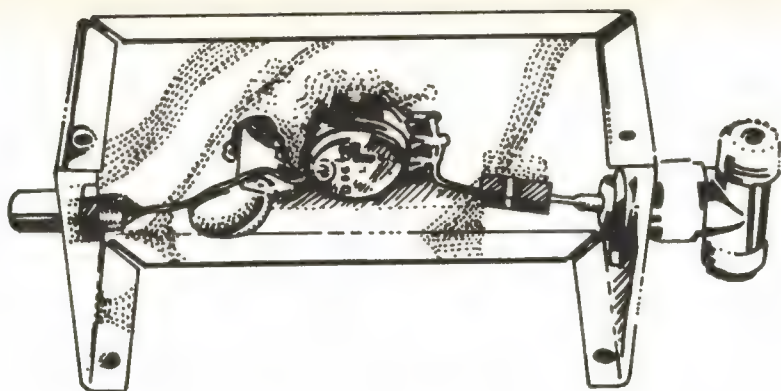Front view of the Wattmeter. You can dress up the completed project to suit your own taste





Interior view. Sampling is done via the T connector. Connection is straightforward and uses normally available components

As the unit is actually a voltmeter and we wish to read the output in watts, Table 1 is included to show the approximate power level each LED will indicate.

After the unit was built and calibrated, the LED display was compared to an oscilloscope (Tektronix 535) voice display on 20m, and true peak values of power were displayed by the meter. For ranges of 0-20 and 0-200 watts, the values of R2 and R3 in the sampler will have to be scaled to provide full-scale readings on the 20 and 200 watt levels.

### Testing and calibration

To calibrate the unit you will need an accurately calibrated r.f. voltmeter or an in-line wattmeter. The single-tone (or two-tone) output level will be the same value displayed by the LEDs as by the RMS value indicated by the two above methods. Calibrate at the highest power level available if a full-scale value cannot be reached.

With no speech 'processing' or 'compression', the highest order LED should flash only on occasions when the peaks of your voice reach the peak limits of

your transmitter. LED flash should *never* indicate higher power output than that reached during carrier condition tune-up.

To test the completed display unit to see that all LEDs light, temporarily connect the input lead, through a 1k $\Omega$  resistor, to the positive side of the power supply. All LEDs should light to their maximum brightness.

This article is from 'CQ' The Radio Amateur's Journal, August 1983, and is reproduced here by their kind permission.

**Table 1 - Relationship between LED numbers in the circuit diagram and the peak power output they reflect.**

LED No.*	Power Output
1 .....	14
2 .....	55
3 .....	125
4 .....	225
5 .....	350
6 .....	500
7 .....	680
8 .....	890
9 .....	1125
10 .....	1390
11 .....	1680
12 .....	2000

\*LED No. 1 is at the bottom of the display.

LED No. 12 is at the top of the display.

## B.N.O.S. ELECTRONICS

### The once and for all batteries!


How much do you spend each year on batteries for torches, cassette recorders, radios, shavers, children's toys, flash guns, and 101 other things?

#### HOW MUCH DO THEY COST YOU OVER FIVE YEARS?

The alternative - buy a complete NiCAD system from us and save £'s. We can supply, from stock, quality batteries from one or more of the following companies: Ever Ready, Saft and Hitachi, at unbelievable prices and a complete range of chargers.


ALL THESE PRODUCTS CARRY A FULL YEAR'S GUARANTEE

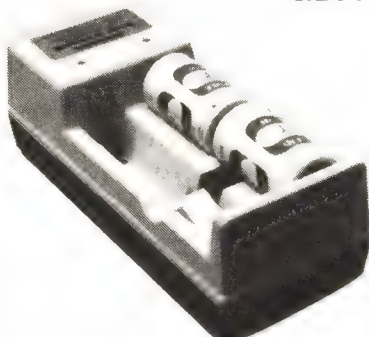RECOUP THE COST OF YOUR INVESTMENT IN JUST WEEKS



NiCAD Batteries						
Format	Capacity (AH)	Height (mm)	Diameter (mm)	Prices		
				1-9	10-24	25-99
AAA	0.18	45.0	10.5	1.34	1.27	1.22
1/2 AA*	0.10	18.0	14.3	1.58	1.50	1.44
1/2 AA*	0.24	28.1	14.3	1.45	1.37	1.32
AA	0.50	50.2	14.3	0.90	0.85	0.82
AA*	0.50	50.2	14.3	0.96	0.91	0.88
1.5A*	0.45	28.1	17.3	1.53	1.45	1.38
RR*	1.20	42.1	22.6	1.70	1.61	1.52
C	2.20	49.7	25.9	2.40	2.30	2.20
D (sub)	1.20	60.5	32.9	2.40	2.30	2.20
D	4.00	60.5	32.9	3.50	3.32	3.15
D*	4.00	60.5	32.9	3.59	3.41	3.24
F*	7.00	91.3	32.9	6.85	6.50	6.20
SF*	10.00	91.3	41.7	10.50	9.50	8.90
PP3	0.11	49 x 26.5 x 17.5		4.35	4.10	3.85

\* Denotes cell fitted with solder tags

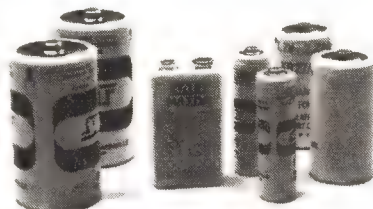

#### NiCAD Chargers


AC.1 SAFT MAZDA AA charger, charges 1 to 4 AA cells £5.90 MC.2 ALTAI MULTICHARGER, charges 1 to 4 AA, C & D cells plus 1 PP3 cell, also cell test facilities £8.50 PC.3 SAFT MAZDA PP3 charger, charges 1 of 2 PP3 cells £5.90 MC.4 JACKSON MULTICHARGER, charges 2 of 4 AA, C & D cells £7.00 MC.5 JACKSON MULTICHARGER, charges 2 of 4 AA, C & D cells, or 1 of 2 PP3 cells £8.50

**BNOS Electronics** (Dept RE) Greenarbour, Dutton Hill, Great Dunmow, Essex, CM6 3PT  
Telephone (0371 84) 767 SAE for further details

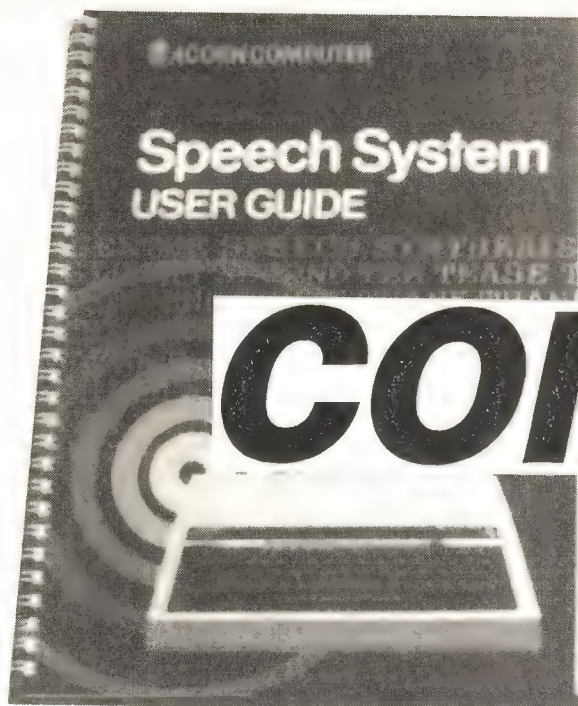All prices include VAT. Postage free on all Mainland UK orders, goods normally despatched by return.







# SPEECH

and the

# COMPUTER

In last month's issue, Terry Weatherley described the orbit of OSCAR -10 satellite. In this issue, the versatile Terry describes a method of making the Beeb computer articulate. What is the connection between these widely differing articles and why does he include the picture of his little daughter? For the answers to these two questions read on...



Exterminate! Exterminate! The harsh metallic voice of the Dalek is what most readily springs to mind when one hears the term 'computer - generated speech'. Until recently this was a fair reaction; beauty was to be found not in the eye but in the ear of the inventor - and inventors there have been.

In 1791 Baron Von Kempelen invented a speech machine in which bellows imitating the lungs forced air into a leather throat which was distorted by hand to make 'sounds'. It is even reported that Alexander Graham Bell was able to make his dog 'speak' by massaging the dog's throat while it growled. It was not until the 1950's that the first speech synthesizers were demonstrated.

Walter Lawrence in 1951 introduced PAT (Parametric Artificial Talker). Eight speech parameters were measured and their resulting waveforms were painted

onto a glass slide. This was scanned photo-electrically. Lawrence would control the pitch with a pot and was thus able to alter the emphasis.

There is a recording of a demonstration Lawrence gave of PAT in which PAT sang, Lawrence carefully twiddling the pitch control while PAT sang:-

(high) 'What did you say before'.  
(lower) 'What did you say before'.  
(bass) 'What did you say before that'.

It is easy to scoff at these early experiments but in their time they represented the state of the art. They also led directly to more academic research into the field of both human speech and speech synthesis. Interested readers are directed to two classic books 'Speech Analysis, Synthesis and Perception' by James Flanagan of Bell Labs in the USA and 'Speech Synthesis (1973)' by John Holmes of the Government Joint Speech Research Unit.

## Natural speech

People speak by passing air from their lungs into the larynx causing the vocal chords to vibrate. The vocal tract from larynx to lips acts as a resonant cavity amplifying certain frequencies while attenuating others. During speech the tongue and lips are in constant motion thus altering the shape of the vocal tract and hence the position of the resonances.

The sound produced by the vocal chords is rich in harmonics. The larynx cavity produces energy peaks which are called FORMANTS. Figure 1 shows the energy spectrum of speech with three such formants. Formant one is around 500Hz, formant two around 1500Hz and formant three around 2500Hz. This model holds good for a held vowel sound like *aaah*, but in real speech the resonances are constantly changing as the vocal cavity alters its shape. Young



# SPEECH AND THE COMPUTER

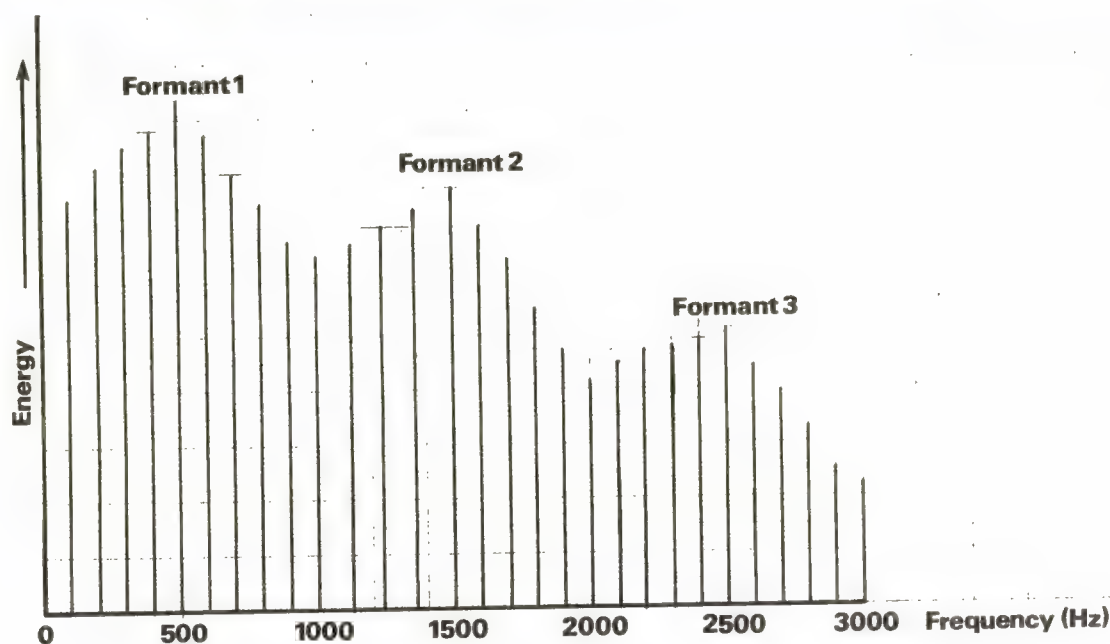


Fig 1 The energy spectrum of speech

children learn to speak by imitating the sounds they hear. (In *Photo 1* the young Miss Weatherley is imitating the sound of a train.)

## Computer speech

The complex waveforms of speech are examined using a sound spectrograph. Typical output is shown in **Figure 2**. It is from such analysis that computer speech is derived. Data from either whole words, allophones or phonemes, the latter two being variations of the basic sounds that make speech. The well known vowel sounds - aa, ee, ii, o, eau - are allophones, while the different 'a' sounds in the words ha, mat, taught, rage, army, about and hair, are all phonemes.

Current speech systems for popular micros using allophones are the Currah Microspeech unit for the Spectrum and the Adam Speech Synthesiser for the VIC 20. The Chatterbox which is available for most popular computers uses phonemes. Both systems have, in theory, an infinite vocabulary but it is up to the user to break the word up into its sounds and using the allophones or phonemes recreate it.

The Acorn Speech System for the BBC Computer uses another route. Speech data from individual words is held on one chip and passed through a 'vocal tract' held on another. The 'vocal tract' is a speech processor which contains a digital filter and requires a large number of parameters to produce the sounds necessary for making speech. Acorn provide a dictionary chip PHROM A (PHrase Read Only Memory) with the parameters of 160 words spoken by Kenneth Kendall the former BBC news-reader.

The speech data is obtained by dividing the speech into frames each

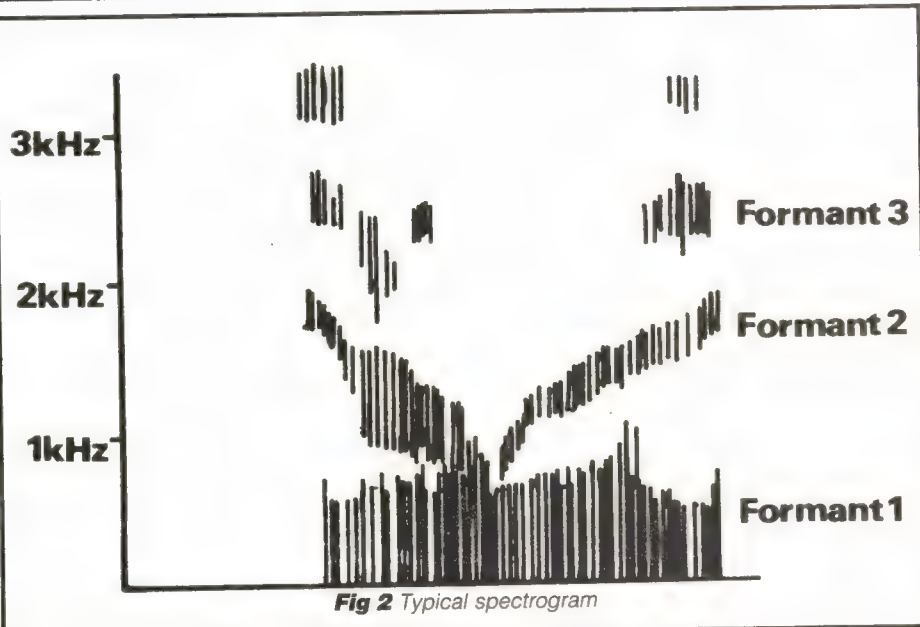


Fig 2 Typical spectrogram

$\frac{1}{40}$ th of a second long. Each frame consists of a number of parameters, the maximum being one energy parameter, one pitch parameter and ten reflection coefficients. The list of words and word parts available in the PHROM is given in *Table 1*. It will be seen that various compound words can be made from the words provided thus increasing the maximum vocabulary. Both chips are made by Texas Instruments. TMS 6100 is the memory PHROM and TMS 5220 the voice synthesis processor. Data Manuals for both these chips can be obtained from Texas Instruments Ltd.

## Beeb speech upgrade

The fitting of the speech upgrade to the Beeb is usually done by the dealer as it is fiddly and may require the cutting of

tracks on the main circuit board, this being dependent upon the issue number of the printed circuit board. If, however, like the writer you are some distance from a main dealer offering this service, then it is possible to fit your own.


It should be remembered that taking a track cutter and soldering it on to your computer is not to be undertaken lightly. Experience in soldering tiny electronic components, keen eyesight and a steady hand are essential. It must be remembered that fitting the upgrade yourself will almost certainly invalidate any warranty. Having said that, it is fair to say that the speech upgrade kit comes with an excellent step-by-step guide rather in the 'Heathkit' style and, if followed to the letter, no problems should be encountered.



# SPEECH AND THE COMPUTER

## TABLE 1

Word No	Word	Word No	Word	Word No	Word	Word No	Word	Word No	Word	Word No	Word
131	- D	158	NIN-	185	DOLLAR	211	K	238	P	265	THANK
132	- ED	159	A			212	KEY	239	PARAMETER		
133	- ING	160	ACORN	186	DON'T	213	L	240	PENCE	266	THAT
134	- S			187	DOWN	214	LARGE			267	THE
135	- TEE	161	AFTER	188	E	215	LAST	241	PLEASE	268	THEN
		162	AGAIN	189	EACH			242	PLUS	269	THIRD
136	- TH	163	AMOUNT	190	ELEVEN	216	LINE	243	POINT	270	THIS
137	- T	164	AN			217	M	244	POSITIVE		
138	-	165	AND	191	ENGAGED	218	MANY	245	POUN-	271	TIME
139	ZERO			192	ENTER	219	MINUS			272	TRY
140	HUNDRED	166	ANOTHER	193	ERROR	220	MORE	246	PRESS	273	TWELVE
		167	ANSWER	194	ESCAPE			247	PROGRAM	274	TYPE
141	THOUSAND	168	ANY	195	F	221	MUST	248	Q	275	U
142	ONE	169	AVAILABLE			222	N	249	R		
143	TWO	170	B	196	FEW	223	NAME	250	RED	276	UH
144	TWEN-			197	FILE	224	NEGATIVE			277	UP
145	THREE	171	BAD	198	FIRST	225	NEW	251	RESET	278	V
		172	BETWEEN	199	FOUND			252	RETURN	279	VERY
146	THIR-	173	BOTH	200	FROM	226	NO	253	RUN	280	W
147	FOUR	174	BUTTON			227	NOT	254	RUNNING		
148	FOR-	175	C	201	G	228	NOW	255	S	281	WANT
149	FIVE			202	GOOD	229	NUMBER			282	WAS
150	FIF-	176	CASSETTE	203	H	230	O	256	SAME	283	WERE
		177	CHARACTER	204	HAVE			257	SCORE	284	WHAT
151	SIX	178	COMPLETE	205	I	231	O'CLOCK	258	SECOND	285	WHICH
152	SIX-	179	COMPUTER			232	OF	259	SMALL		
153	SEVEN	180	CORRECT	206	ILLEGAL	233	OFF	260	START	286	X
154	SEVEN-			207	IN-	234	OLD			287	Y
155	EIGHT	181	D	208	INPUT	235	ON	261	STOP	288	YEAR
		182	DATA	209	IS			262	SWITCH	289	YES
156	EIGHT-	183	DATE	210	J	236	ONLY	263	T	290	YOUR
157	NINE	184	DO			237	OR	264	TEN	291	Z

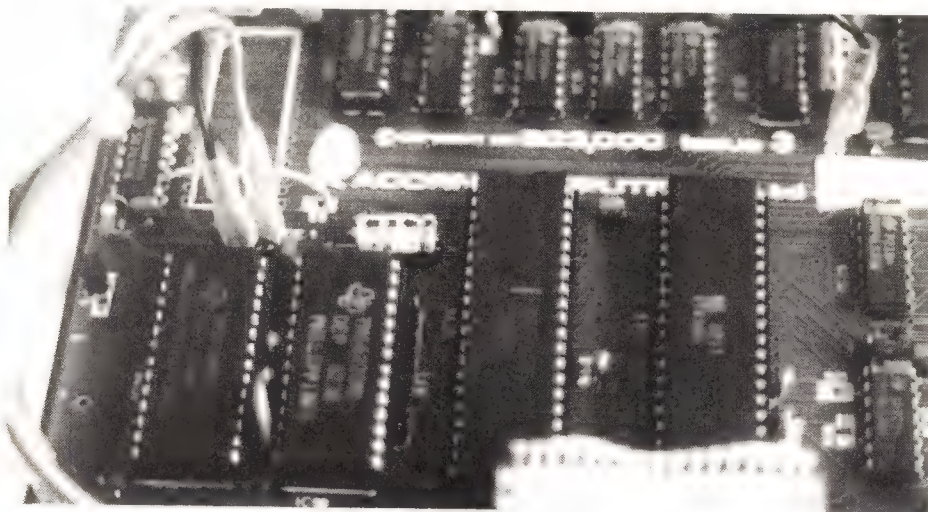

The two speech chips TMS6100 and TMS5220 in their sockets

Included in the kit are the edge connectors etc, enabling the famous 'hole in the keyboard' to be activated and a plastic cover fitted. The job is very fiddly and the cutting of the correct tracks which are very, very finely etched on the main board could be difficult. A lino knife might slip, but a 'veroboard' cutter is difficult to locate on the correct track.

### Checking the PHROM

Once fitted, the PHROM can be checked out. Each word in the PHROM

can be 'called' in various ways, by a word number, by its ASCII code number if it is a letter, or by its absolute address. To use the data for the letter 'A' there are three alternatives. The word number is 159, the ASCII value is 65 and the absolute address (in HEX) is B5D. In order to check out the upgrade, the following is typed in with the computer in command mode:- REPEAT:SOUND-1,GET,0,0:UNTIL FALSE. As each key is pressed the GET command returns its ASCII value and thus calls the sound from the PHROM. Lower case letters return

associated words, thus pressing 'p' and 'r' causes the computer to say 'Press Return'.

To add speech to a program, a PROCspeak might be:-

```
1000 DEF PROCspeak
1010 REPEAT
1020 READ A%
1030 SOUND-1,A%,0,0
1040 UNTIL A%=127
1050 ENDPROC
1060 DATA 284,209,267,271,127
```

This should result in the computer saying, 'What is the time'?

The speech is very clear and bears more than a passing resemblance to the data source. Apart from the novelty value it is a useful facility. The Writer's satellite programs need many numbers to be entered and it is very useful to have the computer repeat each digit as it is entered. The educational applications are many. In one program for young children it is essential that they 'press return'. The 'voice' can be made to prompt this after a suitable delay. In all, the Acorn Speech upgrade enhances what is already an excellent machine.

### References

*The Chatterbox*, Witten & Madams, Wireless World: December, 1978.

*Speech System User Guide* - Acorn Computers.

*Speech Upgrade Instructions* - Acorn Computers.



## POINT OF CONTACT

The general interests of some of our readers are shown below. If you have similar interests why not establish a point of contact at the time and on the band indicated

### BYOX:

Usually available early evenings on most days on 2m, 70cm and above. Uses phone, RTTY with computer, SSB, TV. Equipment includes, Icom TR1010 SSB TXCOR, H/brew linear, H/brew FM Synth Rig, 9ELE Tonna, 24 ELE Quad (23cms) and his special interests include VHF/UHF DX, meteor-scatter microwave propagation, homebrew equipment and computer-aided communication. Most interesting contact to date was made with Karl OK1KH/P. Czech 2m SSB.

### GAONF:

Available evenings after 19.30 on HF, 15, 20, 40 and 80 metres, CW only. Uses FT102 equipment and his special interests include DX (Award Hunter). Fifty-nine countries confirmed CW and 3 confirmed SSB. Most interesting contact to date was regular QSO with

VP8APQ during the Falklands War.

### G6LUI:

Usually available Wednesday and Thursday evenings between 19.00 and 20.00 and on Sunday mornings between 10.00 and 11.00 on 2m. Uses phone. Equipment includes TR7500, TR2200GX and TR2100M. His special interest is DXSSB.

### G2DHV:

Usually available most days during the afternoons on 160-80 (A3E/A1A), 20/15/10 (A1A), 10 (F3E) and 4/2 (A1A/T3E) and can be contacted mostly by CW and, occasionally, phone. Equipment is mostly home converted gear plus MX4-MX2-TR2100M, and his special interests include DX, AMSAT, VHF/UHF, Microwaves, ATV/SSTV propagation, aeriels, construction, mobile, satellites and contests (VHF). Most interesting

contact to date: QTH AL41F-JOO1F.

### G6YAK:

Usually available daily except Sundays between 09.00 and 18.00 on 70cm (RB2, GB3 05) using phone. Equipment includes Trio TR9500. His special interests include Amsat, Slow Scan and RTTY.

### G1CMZ:

Usually available most days on 2m FM. Equipment includes Yaesu FT-208R (2.5W/300mW). Indoor  $\lambda/4$  antenna. Special interests include Raynet.

### G2VF:

Usually available most afternoons and evenings on 40, 15, 20 and 10m (CW only). Equipment includes Heathkit HX1681 and DX100 transmitters, HF loop antenna. Special interests include loop antennae for HF bands. RSGB QSL awards. Bureau Sub Manager.

Had an interesting contact with OR4VN during the Antarctic expedition of 1964/65.

### G3AKG:

Usually available Monday to Friday: 08.00-09.00, 09.30-10.30, 15.00-17.00 on 10, 15 and 80 metres. Uses CW and SSB. Equipment includes FT101E (modified), Standard C8500 and Datong downconverter. Special interests are various nets, 80m, KSG, BTI, RNARS and RAOTA.

### G4ASR:

Usually available daily from 16.00 on 70, 144, 432, 1296 and 5760 MHz. Uses SSB, CW, FSTV, RTTY. Has various equipment and his special interests include EME on 144/432 MHz, MS on 144 (432), Auroral, Sporadic-E and DX Tropo. Most interesting contacts made to date: 5B4AZ on 70 MHz, LA6HL/TF Iceland, three QSO's on 144 MHz.

## POINT OF CONTACT

In order to facilitate ready contact between radio amateurs, **Radio & Electronics World** will publish a monthly updated list of licensed readers, including some of the bands they favour, approximate times and days of the week when they operate and a few other details.

**MOST IMPORTANT** – include a **telephone number** – if you have a particularly interesting contact so that we can contact you for details for publication.

If you wish to be included in this scheme, would you please complete and return the form below and send to: **Radio & Electronics World**, Sovereign House, Brentwood, Essex CM14 4SE.

We thank readers who have responded to this new scheme.  
Please keep them coming.

Name..... Address.....  
..... Postcode.....  
Telephone No..... Call Sign..... Date licensed.....  
Type of Licence A..... ☐ B..... ☐  
Bands usually preferred.....  
Operating days M T W T F S S Times.....  
Equipment.....  
Phone/CW.....  
Special interests eg DX, AMSAT etc.....  
Most interesting contact made to date.....

RE0484





# AMATEUR ELECTRONICS UK

**SERVING YOU SINCE 1962!**



THE SYMBOL OF TECHNICAL EXCELLENCE

**Your number one source for YAESU MUSEN**

**Mail Order - All stock items same day service**

When you buy from Amateur Electronics UK you are dealing with the **FACTORY APPOINTED IMPORTER** with the largest stocks of equipment and spares in the country. Our delivery and after-sales-service is second to none and for your convenience we offer the following facilities ● On-the-spot credit sales (against recognised bank or credit cards) ● Interest free finance (50% deposit - balance over 12 months) ● Free Securicor delivery on all major items ● **FACTORY BACKED EQUIPMENT** ● Extensive showroom demonstration facilities ● Private large car park ● Your choice just has to be **YAESU** - write or phone for all the details.


**Large stocks of: TET ANTENNAS • JAYBEAM • HI-MOUND • TOKYO • HY-POWER • DATONG • MICROWAVE MODULES • BNOS • DAVTREND • WELTZ • MUTEK • RSGB PUBLICATIONS**

**FT-757GX** The latest all-mode HF rig from YAESU

How do they do it? - To get so much in so small a package - Just look at the features.

- All-mode operation SSB, CW, AM and FM are included as standard features. ● Full CW break-in. ● Dual VFO plus eight memories. ● Programmable memory scanning.
- 600Hz CW filter fitted. ● Iambic keyer with dot-dash memory.
- IF shift and width filters. ● TX coverage 160 thru 10 metres.
- High performance general coverage RX 500 KHz - 29.999 MHz.

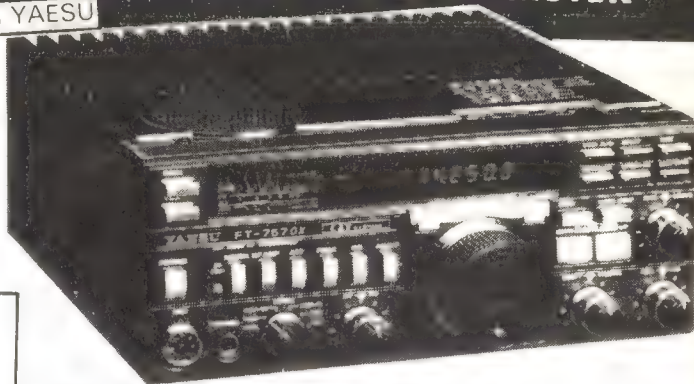Optional P.S.U.'s FP-757 (plinth type) FP-700.



**FT-77 HF transceiver**



Not just a mobile rig - with matching PSU and ATU this makes a first class budget station. FT-77s - (10W version)


**FRG-7700 General coverage receiver**



**Attention FRG-7700 owners!**

See us for your special requirements in converters and active antennas - complete range ex stock - Post free.

**FT-102 HF transceiver**

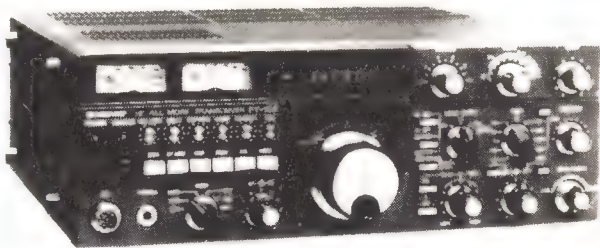

The superb 102 - Still the buy of a lifetime

**FT-980 All-mode HF transceiver**



The ultimate HF rig - Superb all-mode operation plus full general coverage receiver. Rolls Royce performance



# LATEST!

**COMING SOON - FT-203R  
NEW COMPACT 2m FM HAND-HELD**




## FT-726R VHF/UHF multi-mode

Fitted 2 metres with 70cm, 6 metres or HF options. Satellite unit available provides complete satellite operation with full Duplex.




## FT-480R 2 metre multi-mode

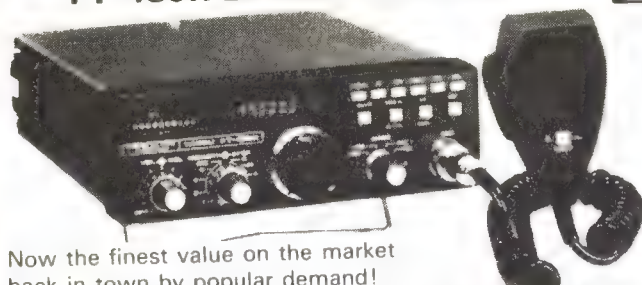

Now the finest value on the market back in town by popular demand!

## FT-290R 2 metre multi-mode portable

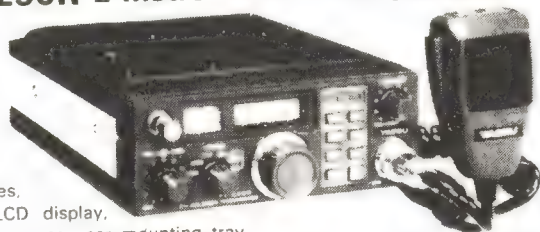

10 memories.  
2 VFO's, LCD display.  
C size battery, easy car mounting tray.  
FT-290R 0.5 low/2.5 high watts out

## FT-230R 2 metre 25 watt FM mobile



- Two independent VFO's ● 10 memories
- Priority function ● Memory and band scan
- 12.5/25KHz steps
- (25/100KHz FT-730R)
- Large LCD readout.

## FT-208R 2 metre FM hand-held

The finest hand-held bar none

- ACCESSORIES:**
- NC-7 - Standard charger
  - NC-8 - Standard/quick charger/DC Power supply
  - NC 9C - Compact charger (220-234V)
  - PA-3 - Car adapter
  - YM-24A - Speaker/microphone
  - FL-2010 - 10 watt power amplifier for FT-208R
  - FL-7010 - 10 watt power amplifier for FT-708R



XIV Olympic  
Winter Games  
Sarajevo 1984



## BRANCHES

For your convenience we now have fully stocked branches at the following locations where you will be assured of prompt and personal service.

### NORTHERN

Amateur Electronics UK/  
Holdings,  
45 Johnston St., Blackburn.  
Tel: 0254 59595  
Contact Harry G3LLL  
for all your requirements  
and specialised advice.

Open: 9.15 am - 5.15 pm  
closed Thurs.

### SOUTH-WEST

Amateur Electronics UK/  
Uppington,  
12-14 Pennywell Rd.,  
Bristol. Tel: 0272 557732  
Call Peter or Bert G2BAR  
for prompt and  
friendly service.

Open: 9 am - 6 pm.  
Sat: 9 am - 1 pm

### YORKSHIRE

Amateur Electronics UK/  
Hooker, 42 Nether Hall Rd.,  
Doncaster.  
Tel: 0302 25690  
Alan G4OEM has a large  
stock of our product range -  
why not give him a ring and  
save yourself some petrol?

Open: 9 am - 6 pm Mon. - Sat.

## AGENTS

Wales & West - Ross Clare, GW3NWS (0633) 880 146  
East Anglia - Amateur Electronics UK, East Anglia, Dr. T. Thirst (TIM) G4CTT Norwich (0603) 667 189  
North Staffs - Bob Ainge W5MJQ (0538) 754553  
Shropshire - Syd Poole G3IMP, Newport, SALOP (0952) 814275

For full details of these new and exciting models, send today for our latest SHORT FORM CATALOGUE. All you need do to obtain the latest information about these exciting developments from the World's No.1 manufacturer of amateur radio equipment is to send 36p in stamps and as an added bonus you will get our credit voucher value £3.60 - a 10 to 1 winner!

As factory appointed importers we offer you -  
widest choice, largest stocks, quickest deal and  
fast sure service right through

**504-516 Alum Rock Road - Birmingham 8 Telephone: 021-327 1497 or 021-327 6313**  
**Telex: 334312 PERLEC G Open: 9.30 to 5.30 Tues. to Sat. CLOSED all day Monday.**



The communications, electronics & computers magazine

All issues from October 1981 onwards are still available, with the exceptions of January 1982 and February 1982. All orders must be pre-paid, the cost of each issue being £1.00 inclusive of postage and packing. A contents index spanning the issues from October 1981 to September 1983 is available on receipt of a stamped addressed envelope. To ensure that you don't miss any future issues, we suggest that you place a regular order with your newsagent or complete the subscription order form found in this issue.



**PARADE & E**

**LOW-COST BROADBAND LINEAR APERTURE FORM**

**CENTRONICS INTERFACE FOR SUDS**

**High Performance SUDS**

**Power Medium**

**Electronics: New Wave**

**Power: Power**

**Control: Control**

SEPTEMBER 1983

Paul C. Thompson, Ph.D.  
Versatile Integrated Building Blocks

VERSILE INTEGRATED  
BUILDING  
BLOCKS

PAUL C. THOMPSON

OCTOBER 1983

**Radio &  
Electronic  
World**

NOVEMBER 1983

**Radio & Electronics**  
*The International Authority on Electronic Equipment* **World**

**FREE**

**QUARTZ CRYSTALS**

**TRANSISTORS**

**DIODES**

**IC'S**

**RESISTORS**

**CAPACITORS**

**COILS**

**RELAYS**

**TELEVISIONS**

**RADIO SETS**

**RECORDERS**

**AMPLIFIERS**

**POWER SUPPLIES**

**TEST EQUIPMENT**

**TOOLBOXES**

**BOOKS**

**AND MUCH MORE**

**CALL TODAY**

**1-800-451-7878**

DECEMBER 1983

[illegible]

JANUARY 1954

**Radio & Electronics**  
A complete, practical, & modern course

**FREE**

**AMATEURS HANDBOOK**  
A complete, practical & modern course

**FREE**

Images of electronic equipment: a vacuum tube radio, a portable radio, and a television set.

FEBRUARY 1984

MARCH 1984

APRIL 1984





# MICROWAVE MODULES LTD

## SIX OF THE BEST

### MM1001 KB MORSE KEYBOARD



This microprocessor Controlled Morse Keyboard is simply the ultimate in 'electronic keyers':-

#### FEATURES —

- ★ 12-30 wpm speed range.
- ★ 4 memories — each 256 characters.
- ★ 80 character buffer to ensure perfect morse.
- ★ Meteor scatter mode.
- ★ High quality full size Qwerty keyboard.
- ★ 12v DC operation

**£135 inc. VAT (p&p £3.50)**

### MM2001 RTTY TO TV CONVERTER




This converter contains a terminal unit and a microprocessor controlled TV interface and requires only an audio input from a receiver to enable a live display of 'off air' RTTY and ASCII on a domestic UHF TV set, or video monitor.

#### FEATURES —

- ★ RTTY — 45.5, 50, 75, 100 baud.
- ★ ASCII — 110, 300, 600, 1200 baud.
- ★ Switchable input filter.
- ★ Parallel printer output
- ★ UHF and Video outputs.
- ★ 16-line, 64 character display.
- ★ 12v DC operation.

**£189 inc. VAT (p&p £3)**

### MM4001 KB RTTY TRANSCEIVER

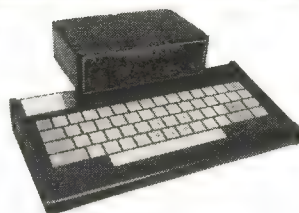


This package, when connected to a transceiver and a domestic UHF TV set provides a data communication capability at a cost of half of any similar system, for both RTTY and ASCII.

#### FEATURES —

- ★ RTTY — £45, 5, 50, 75, 100 baud.
- ★ ASCII — 110, 300, 600, 1200 baud.
- ★ Four message stores.
- ★ Stored test functions (RY, QBF, etc).
- ★ Auto CQ call.
- ★ Full size Qwerty keyboard.
- ★ Parallel printer output.
- ★ UHF and Video outputs.
- ★ 16 line, 64 character display.
- ★ 12v DC operation.

**£299 inc. VAT (p&p £4.50)**

### MTV435 435 MHz ATV TRANSMITTER

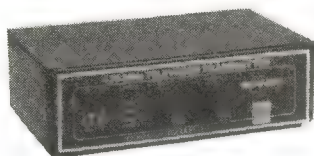

This high performance ATV transmitter consists of a dual channel exciter, video modulator and a two stage 20 watt linear amplifier. It is suitable for monochrome and colour transmissions, has two switch selectable video inputs, and includes a test wave form generator.

Full transmit/receive switching is incorporated and aerial changeover is achieved by a Pin diode switch, which allows connection of the 435 MHz aerial to a suitable receive converter, such as the MMC435/600 which is available at £29.90 inc VAT, p&p £1.25.

**£159.95 inc VAT (p&p £3)**

### MMS 1 THE MORSETALKER




This unique product is a self-contained speaking morse tutor and, as well as a random morse generator, the MMS1 incorporates a microprocessor speech synthesis system which provides talk back of the random morse. This product is a truly cost effectively means of obtaining a full class 'A' amateur licence, without having to rely on a third party for instruction.

- ★ Wide speed range: 2-20 wpm.
- ★ Segmented alphabet choice for novices.
- ★ Variable group length — 1, 5, 50 characters.
- ★ Truly random and accurate morse.
- ★ Internal loudspeaker.
- ★ 12v DC operation.

**£115 inc. VAT (p&p £3)**

### MMT 144/28 2m LINEAR TRANSVERTER

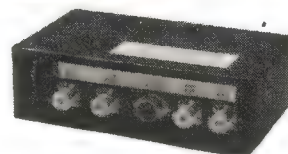

The MMT 144/28 2 metre linear transverter is intended for use with a 28 MHz transceiver to produce a high reliability transceive capability at a reasonable cost.

By using this transverter all the features of the prime mover are retained, resulting in a first-class system for the 144 MHz band. As the transverter is linear, it is suitable for SSB, FM, AM, CW and will work in conjunction with transceivers such as: FT101, FT102, FT902, FT-1, TS120/130, TS430, TS830, TS930 etc. (Please specify when ordering).

- ★ 10 Watts RF output power.
- ★ Low-noise receive converter — 2.5dB N.F.
- ★ Ultra-Linear transmit converter.
- ★ Highly stable regulator controlled oscillator
- ★ RV Vox provides automatic changeover.
- ★ 13.8v DC operation.

**£109.95 inc. VAT (p&p £3)**

**OUR ENTIRE RANGE OF PRODUCTS WILL BE EXHIBITED AND ON SALE AT MOST OF THE 1984 MOBILE RALLIES BY OUR OWN SALES TEAM, COME AND TAKE A CLOSER LOOK**

**ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS (INCLUDING PA TRANSISTORS)**



**WELCOME**

**MICROWAVE MODULES**  
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND  
Telephone: 051-523 4011 Telex 628608 MICRO G  
CALLERS ARE WELCOME PLEASE TELEPHONE FIRST

**HOURS:**  
**MONDAY TO FRIDAY**  
**9-12.30, 1-5.00**

**E.&O.E.**



# A 2 METRE TIGER ANTENNA

If you're looking for an inexpensive VHF high gain antenna this constructional project will interest you

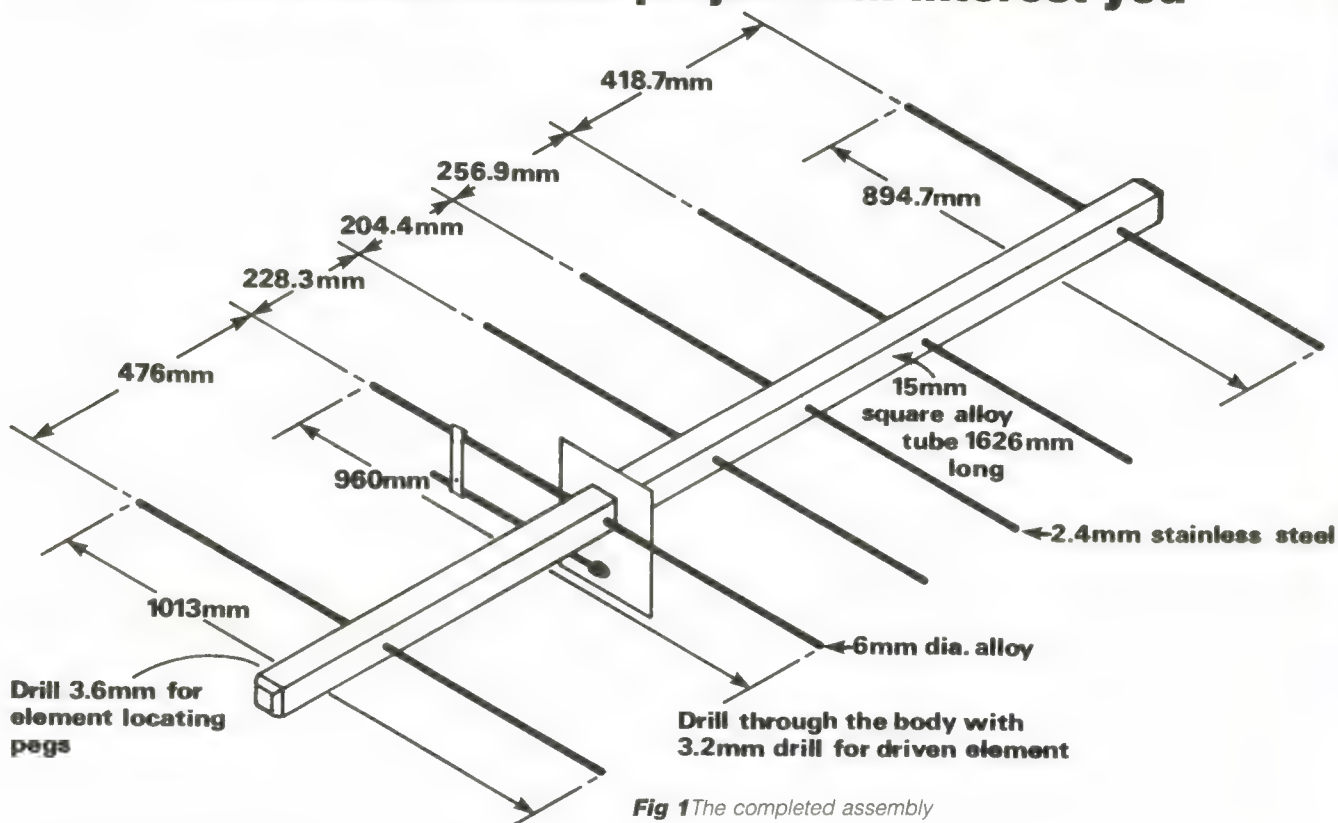


Fig 1 The completed assembly

A constructional project for many heralds the start of a new experience, a step taken very often into a facet of amateur radio previously unexplored, the beginning of new learning sometimes venturing into unrelated subjects in order to master a new interest. The end product provides satisfaction of the achievement and the knowledge of one's own ability to produce the finished work.

This high gain antenna will work extremely well, giving a very good performance in comparison with others in its class, providing the construction details are closely followed.

If you want a six element yagi with plus 9 dBd gain costing under ten pounds for use on the amateur two metre band, then read on.

## Construction

In order to construct the Tiger LY6 antenna, I purchased some components from Ant Products. This company make all the parts for their antenna range available as spares and taking advantage of this fact makes construction very simple, particularly for constructors with limited workshop facilities.

Figure 1 shows the antenna dimensions, boom length, element length and where to drill the holes, etc. The boom is cut from a length of high quality square

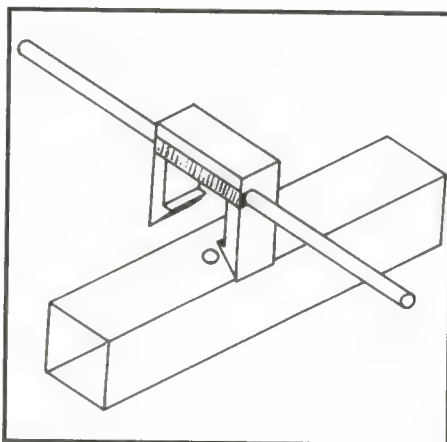


Fig 2 Fitting the element in plastic clip and mounting the clip on the boom

section aluminium tube. Taking care to avoid injury to oneself, deburr the sharp ends and then fit suitable plastic plugs. These will stop water ingress and wind from blowing into the boom. The author's antenna made quite a noise when the wind blew across the ends of the boom.

Care should be taken when marking out the hole positions on the boom and a little time spent in making sure that the holes are drilled in the centre of the boom will prevent difficulty in fitting the

plastic clips that hold the elements in place. Once the boom has been drilled it can then be placed to one side until the elements are cut and fastened into the plastic mounting clips.

As the four directors are all of the same length, a simple jig can be used to mark and cut the stainless steel rod, thus ensuring uniformity of length (see Appendix).

## Fitting the elements

Having cut all the stainless steel elements it is now necessary to fit them into the groove in the plastic clips (Figure 2). It is important that the element is centred accurately in the clip and again the jig can be used to mark the element centres. By utilising the cutting jig and using a felt tip marker pen, the element centres can be easily and quickly marked. Using the mark as a guide, the element is then pressed into the clip using a pair of bull-nosed pliers. A broad-bladed screwdriver can be carefully used to make sure that the element is firmly seated and, if desired, a spot of adhesive can be applied to ensure security, but in the author's case this was not required.

The driven element is the last element to be made and this is cut from a length of aluminium rod 6mm in diameter. First cut



# A 2 METRE TIGER ANTENNA

the element to length and deburr the ends, then find the centre of the rod and mark this position. It is necessary to drill through the rod at this point and to ream the hole to suit a 4BA bolt. Support the rod with a V-block, then using a 2.9mm drill, bore through the element. This drill is the correct tapping size for a 4BA thread.

## Method of tapping

When a pedestal drill is available for use, it is possible to ensure that the hole is squarely tapped by using a method employed by the author. Replace the drill in the chuck with a 4BA tap and with the power switched off, enter the tap into the hole in the rod. Rotating the chuck of the drill by hand will enable the tap to be started and run square. Leave the tap in the hole and release from the drill chuck so that the operation can now be finished by using a tap wrench in the normal way. Clean and remove any burrs from around the hole and check that the element fits into the boom, making a good fit, and will be secure when the fastening screw is tightened.

## Heat shrink tube

The 9.5mm diameter heat-shrink tube is cut to a length of 125mm and then placed over the driven element as shown in Figure 3. Ideally a hot air gun should be used to shrink the tube onto the element (the wife's hairdryer could be tried) but a butane gas blow lamp flame can otherwise be used if care is taken not to burn the heat-shrink tube.

## Support bracket

A bracket to support the SO239 single hole mounting socket is required. Mine was made from a piece of scrap alloy sheet, punched with a hole 16mm in diameter, then bent through 90° and fastened to the boom with two self-tapping screws or pop rivets. The bracket for the socket should be mounted to the boom before the SO239 socket is fitted, otherwise the socket obstructs the fastenings holding the bracket.

## Gamma rod and clips

The gamma rod is made from 8swg copper rod 225mm long, hammered flat at one end and drilled to suit the pin on the socket (Figure 4). Slip the end over the centre pin and solder so that the gamma rod lies parallel to the driven element and is on the same side of the boom as the heat-shrink tube. Make sure that the rod does not short to the body of the socket and when this is done, the assembly should look like the drawing in Figure 5.

It now only remains to make the gamma clip and then the assembly of the antenna can be completed by fitting the elements. The gamma clip is made from 13mm wide, 24 or 26swg brass or copper strip (Figure 6), wrapped around a piece of 6.3mm diameter rod to form the large end, and the small end formed around a piece of 3.2mm diameter rod. A hole is required in the flap part of the gamma

Fig 3 Heatshrink tube and method of fastening driven element

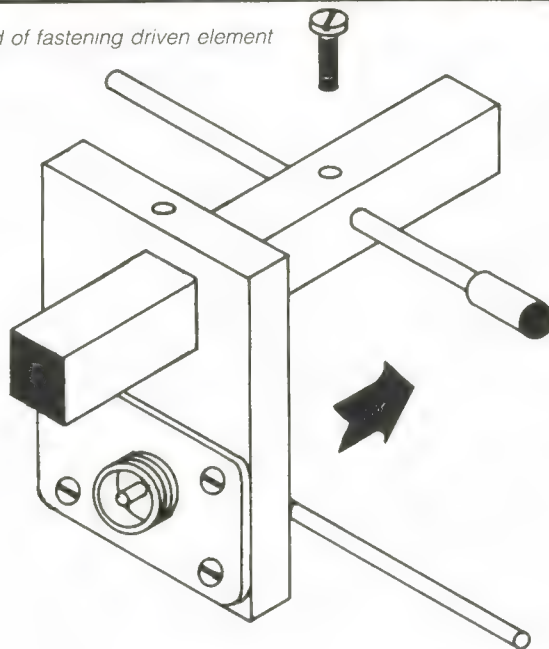


Fig 4 The gamma rod

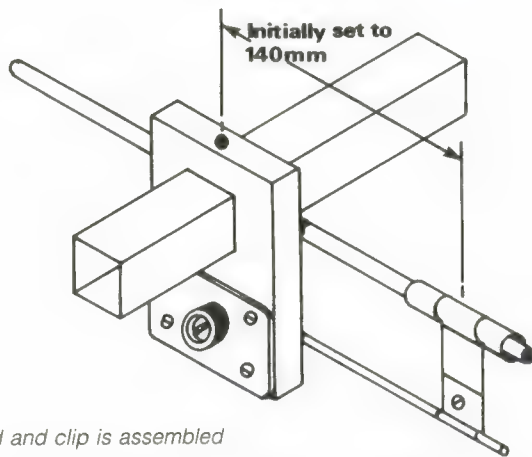
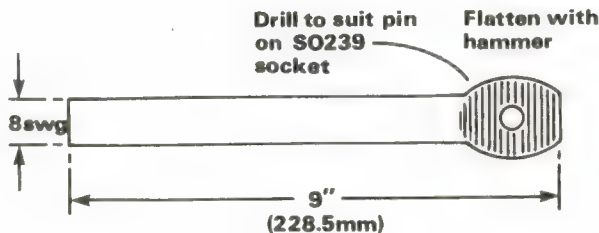


Fig 5 How the gamma rod and clip is assembled

clip so that a 4BA nut and bolt can be used to tighten the small end onto the gamma rod, or it may be better to make the small end of the clip over-tight and then later, after adjustment has been made and the antenna is on tune, solder the clip to the gamma rod. If securing with nut and bolt take care when drilling the thin metal because when the drill breaks through it tends to snatch and result in damaged fingers. Once the correct tuning point has been found, it should not need to be adjusted again, unless major changes are made to the design of the antenna system.

## Assembly and tuning

Fit the driven element and SO239 socket bracket first, then put the SO239 socket into the hole in the bracket and

secure with the nut provided. Discard the solder tag connection ring as it is not required in this application. Fit the gamma rod and solder to the pin on the socket. Put the gamma clip onto the element and slide down towards the boom. The clip should be a snug fit over the heat-shrink tube, sliding smoothly without sticking. Push the smallest end over the gamma rod and adjust to a position about 140mm from the boom. This is the starting point for adjustment. Fit the other elements and then fasten the completed antenna to a support so that it can be held three or four feet from the ground and pointing at the sky. Wooden step ladders are a good support for this exercise.

Opinions on how to set up and tune the antenna differ. However, the following



# A 2 METRE TIGER ANTENNA

Fig 6 Gamma clip details


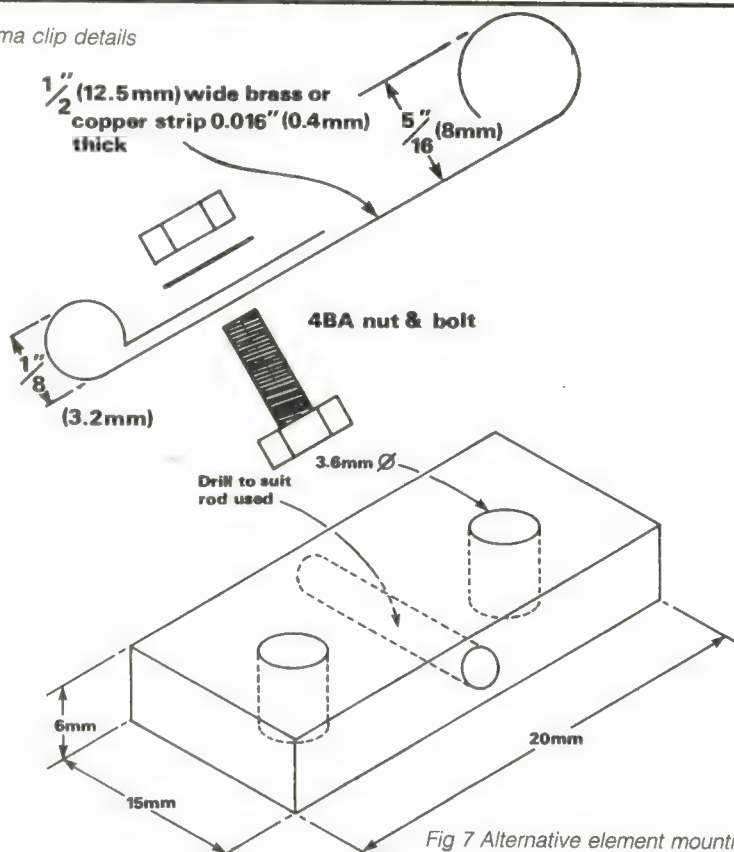


Fig 7 Alternative element mounting

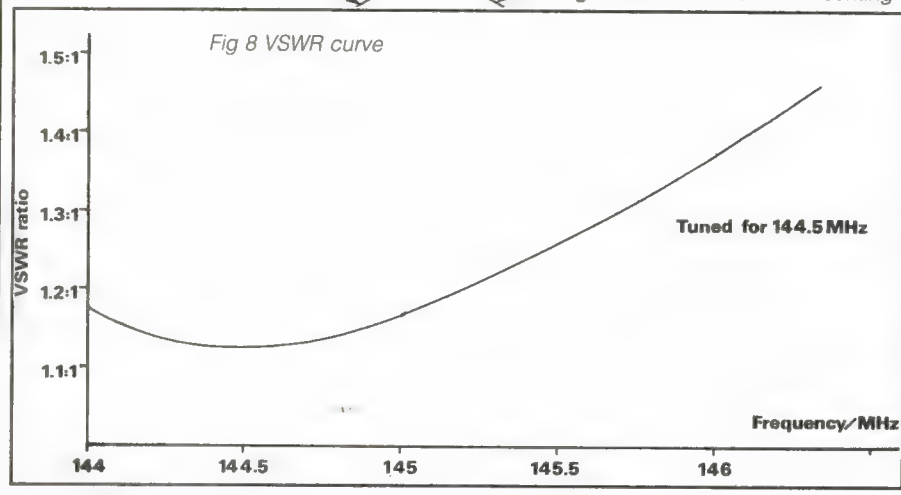

explanation and method is suggested by the author.

First a little transmission line theory. It is well known that a transmission line that is a half wavelength long will repeat any impedance that is placed at one end at the other end, regardless of its characteristic impedance. Therefore, if we take a length of co-axial cable that is a multiple of a half wavelength long and terminate one end with the antenna, we would expect to find the same value of impedance at the antenna repeated at the other end. Because a radio wave propagates more slowly in cables than in free space we must take this into account. The velocity factor, as it is known, affects the tuning frequency and in this case gives rise to the difference 145.5MHz to 144.5MHz, ie a difference of 1MHz.

However, the results will be similar whichever frequency is chosen, because the antenna tuning is very broad across the band. The main difference will be that the VSWR curve (Figure 8) will be lower at whichever frequency is used for setting up.

Back to our co-axial cable. All this means so far is that we can choose where we wish to make our VSWR measurement, either at the rig or at the antenna. My preference is to use a short length of cable three or four halfwave lengths long, not forgetting to include the length of the pin on the PL259 plug. This means that I can make adjustments at the antenna and see the VSWR bridge at the same time.

Because some constructors may have alloy or brass rod available that is not of the right diameter to fit into the clips

from Ant Products, I will describe an alternative method of mounting the elements.

A 20% diameter variation is permissible and because the antenna dimensions are calculated for elements that do not go through the boom but are insulated from it, insulating fastenings must be used (Figure 7). Small blocks made from perspex or polyvinylchloride (PVC) can be drilled to hold the elements and the blocks are secured to the boom with self tapping screws. As long as the diameter of the elements does not vary too greatly from the design value, then no corrections for length/diameter ratio will be necessary.

When the antenna and cable is set up the clip should be moved towards the boom in small amounts until the point of minimum VSWR is found. This should be better than 1.2:1 but may be higher. This is due to the difference in dielectric constant of the heat-shrink tube causing the capacitance value to be wrong. It may be necessary to increase or decrease the amount of capacitance needed by altering the width of the strap used for the clip. The size shown was correct for all of the antenna that I have built, using the specified heatshrink tube. Using the full length of the cable has the advantage that after adjustments are completed the VSWR bridge can be removed and the cable plugged into the rig with the knowledge that the whole system VSWR is satisfactory.

## Weatherproofing


Because the parasitic elements are made from stainless steel no special precautions need to be taken to weatherproof them. However, the alloy and copper parts will deteriorate in time, making the antenna visually unattractive; corrosion may weaken the boom making the joint between the driven element and the boom unsound, and chemical action caused by adverse climatic conditions acting on the aluminium may affect the antenna performance. The SO239 socket is not waterproof and water may migrate into the plug and then penetrate the co-axial cable.

A lesser known fact is that an antenna detunes low in frequency as the driven element corrodes and this reduces the gain of the assembly. This may be as much as 3dB at 144MHz. Tests carried out on new antenna compared against an old antenna (more than six months in use outdoors) show that a popular 19 element antenna lost nearly 2dB of gain and the frequency of resonance dropped by nearly 100KHz. Fortunately, many of these problems can be avoided by taking the time and trouble to use a good quality varnish, painting the antenna carefully using two coats.

However, be warned that some types of varnish are actually quite lossy at two metres and even more so at the UHF frequencies. 'Evostick' is a very good product for insulating and waterproofing the back of the SO239. This product dries



# A 2 METRE TIGER ANTENNA

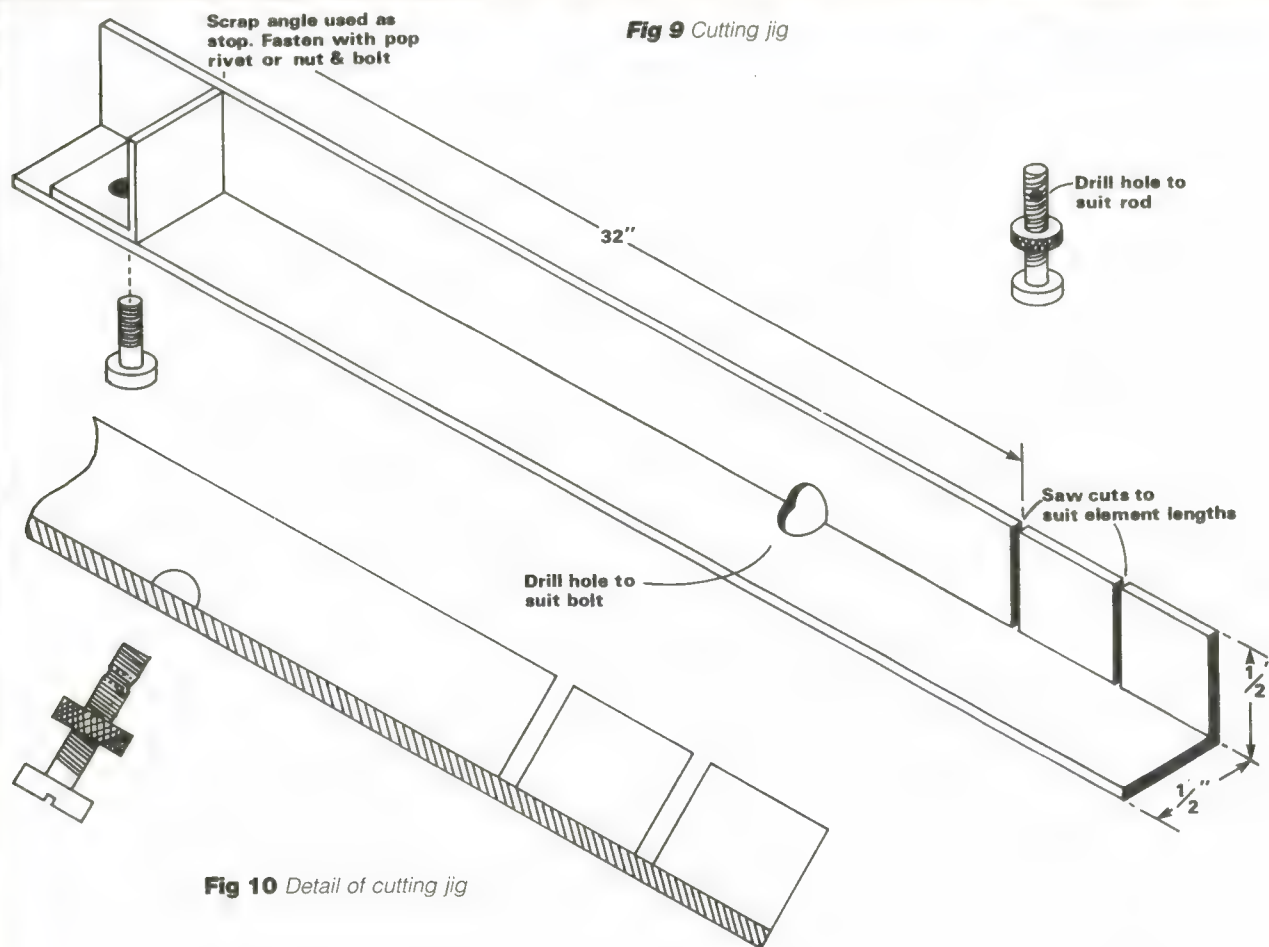

**Fig 10** Detail of cutting jig

quickly and leaves a tough rubbery coat, very effectively sealing the back of the connector.

Silicone grease inside the plug and shroud will also help to prevent water getting into the co-axial cable.

## Performance

When assembled, adjusted and used in operation, the performance of this aerial compared very favourably with those of a commercial 8-element unit and checks with the beacons showed a noteworthy increase in signal strength. The specification for the 2-metre Tiger is as follows:-

Boom length	1613mm
Weight	0.7Kg
Elements	6
Wind loading	0.5 sq ft
Gain	9dBd
Bandwidth at	2MHz
1 VSWR	
Beamwidth 1/2	50° 'E' Plane
Power points	
Front-to-back ratio	20dB
Parasitic elements	Stainless Steel
Driven element	Aluminium
Connector	SO239
Feed	Universal Gamma Match

## Appendix

Anybody who has tried cutting stainless steel will know how difficult it can be

and using the jig described simplifies the operation.

The jig, almost a constructional project in its own right, consists of a length of 13mm x 13mm x 1.6mm steel angle iron with a stop fitted at one end. This stop is made from an off-cut of angle iron and fastened with a pop rivet or nut and bolt (see Figure 9).

It is necessary to obtain a brass or steel OBA bolt and for a hole to be drilled through the bolt a short distance from the end. This hole should be slightly larger in diameter than the stainless steel rod used for the element. A nut should be screwed onto the bolt so that the bolt can be passed through a hole drilled in the bottom of the Vee of the angle iron, about 32 inches from the stop. This will enable the stainless steel rod to be held securely in the jig.

Carefully mark the angle iron the required distance from the stop to suit the director length and then carefully cut, using a fine bladed hacksaw, halfway through the angle as shown in Figure 10. Do the same for the reflector length.

If care is taken, the jig can be used again and again to produce enough elements for several antennae. To use the jig, pass the stainless steel rod through the bolt and butt up against the stop. Tighten the nut onto the angle iron and this will have the effect of clamping the rod in place, thus preventing it from turning or slipping whilst you are cutting.

## PARTS LIST

Boom 15 x 15mm square alloy tube 1626mm long.

End plugs to suit.

5 metres of stainless steel rod 2.4mm diameter type 308.

5 plastic clips or perspex sheet (see text).

1 metre of 6.3mm diameter alloy rod for driven element.

1 SO239 signal hole mounting socket.

1 length of copper rod or tube 8swg for gamma rod.

Short length of brass or copper strip 13mm wide, 0.4mm thick.

200mm length of 9.5mm diameter heat-shrink tube (Radio Spares).

Nuts, bolts and screws.

1040mm length of 13mm x 13mm angle iron for cutting jig.


1 mounting clamp.

1 plug shroud.



Every 90 seconds a home in Britain is burgled — Guarding your home is common sense — Act **NOW** — safeguard your home with "On Guard" — it could be your turn next!!

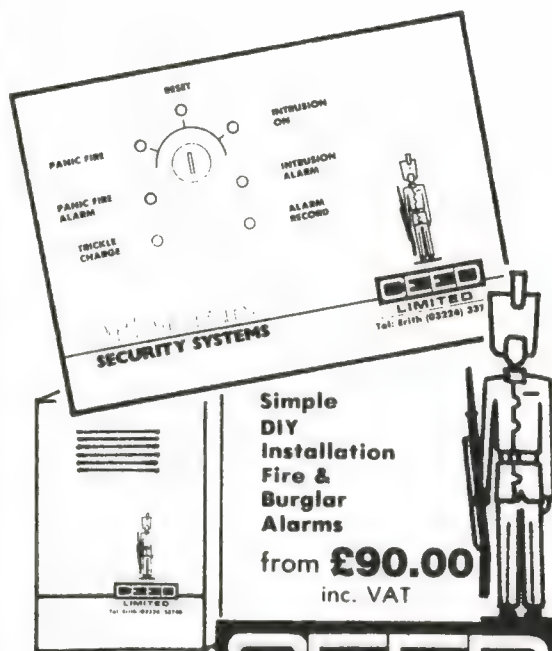- ☐ All doors and windows protected
- ☐ Simple two wire system
- ☐ Tamper proof
- ☐ 14 day protection against mains failure
- ☐ Entry and exit delay
- ☐ External siren or bell alarm (with timed cutout to avoid neighbour disturbance)
- ☐ Constant display of system status
- ☐ Available to suit any household
- ☐ DIY Economy kit available at £70.00 inc VAT



Simple  
DIY  
Installation  
Fire &  
Burglar  
Alarms  
from **£90.00**  
inc. VAT

**CEED  
LIMITED**

Tel: Erith (03224) 33740 24 hour service

**Charlton Electronic & Electrical Developments Ltd.**  
Unit S17 Europa House, Fraser Road, Erith, Kent DA8 1QL  
Telephone: Erith 33740  
Phone or write now for further details

## PM COMPONENTS LTD VALVE & COMPONENTS SPECIALIST

### INTEGRATED CIRCUITS

AN124 2.50	MC1351P 1.50	STK015 7.95	TBA540 1.25	TDA2523 1.95
AN214Q 2.50	MC1325P 1.25	STK433 7.95	TBA540Q 1.35	TDA2524 1.95
AN240P 2.80	MC1357 2.35	STK437 7.95	TBA560C 1.45	TDA2530 1.95
AN612 2.15	MC1358 1.95	STK439 7.95	TBA560Q 1.45	TDA2532 1.95
AN7140 3.80	MC1495 3.00	TA7081AP 3.95	TBA570 1.00	TDA2540 1.25
AN7145 3.90	MC1496 1.25	TA7108P 1.00	TBA841A12 2.50	TDA2541 2.15
AN7150 2.95	MC145106P 7.95	TA7120P 1.85	TBA851R 2.50	TDA2560 2.15
BA521 3.35		TA7130P 1.50	TBA720A 2.45	TDA2571 2.95
CA1352E 1.75	MC1723 0.50	TA7146 2.95	TBA750Q 2.65	TDA2581 2.95
CA3086 0.45	MC3357 2.75	TA7203 2.95	TBA750Q 2.65	TDA2593 2.95
ETT6016 2.95	ML231B 1.75	TA7204P 2.15	TBA810AS 1.85	TDA2600 5.50
HA1339A 2.80	ML232B 2.50	TA7205A 1.80	TBA810P 1.65	TDA2610 2.50
HA1377 3.90	MSM5607 6.75	TA7222AP 1.80	TBA820M 0.75	TDA2611A 1.95
HA1156W 1.50	PLL02A 5.75	TA7227P 4.35	TBA820Q 1.45	TDA2640 2.60
HA1551 2.95	SAA500A 3.90	TA7310P 1.80	TBA890 2.50	TDA2680A 2.75
LA1230 1.15	SAA1025 7.25	TA7313AP 2.95	TBA91 1.65	TDA2690 2.45
LA4102 2.95	SAA5010 6.35	TA7321P 2.25	TBA950/2X 2.35	TDA3560 3.95
LA4250 2.95	SAS5505 1.75	TA7699P 3.15	TBA970 2.95	UPC56H 5.50
LA4420 1.95	SAS5705 1.75	TA7611AP 2.95	TBA1441 2.15	UPC575C2 2.75
LA4430 2.80	SAS580 2.55	TAA550 0.25	TCA271 1.10	UPC1025H 2.90
LA4400 4.15	SL901B 4.65	TAA570 1.95	TCA270S0 1.10	UPC1028H 1.95
LA4422 2.50	SL917B 6.65	TAA621AXI 3.50	TCA650 2.50	UPC1032H 1.50
LC7120 3.25	SL1310 1.80	TAA661B 1.20	TCA800 2.15	UPC1156H 2.75
LC7130 3.50	SL1327 1.10	TAA700 1.70	TCA940 1.65	UPC1158H 0.75
LLC7131 3.50	SL1327Q 1.10	TBA120B 0.95	TCA440 2.20	UPC1167C2 1.15
LC7137 5.50	SN76003N 1.95	TBA120C 1.15	TDA1001 1.95	UPC1181H 1.25
LM324N 0.45	SN76013N 1.95	TBA120T 1.05	TDA1004A 3.25	UPC1182H 2.95
LM380N 0.95	SN76023N 1.95	TBA120U 1.00	TDA1006A 2.50	UPC1185H 3.95
LM383T 2.95	SN76033N 1.95	TBA231 1.25	TDA1010 2.15	UPC1191V 1.90
MS1513L 2.30	SN76110N 0.99	TBA396 0.75	TDA1035 2.50	UPC1350C 2.95
MS1551 2.95	SN76115N 1.55	TBA396 0.75	TDA1037 1.95	
MS1521L 1.50	SN76131N 1.30	TBA440N 2.55	TDA1170 1.95	
MB3712 2.00	SN76226DN 2.95	TBA480Q 1.25	TDA1180 2.15	
MC1307P 1.80	SN76227N 1.05	TBA510 2.50	TDA1270 3.95	
MC1310P 1.80	SN76533N 1.65	TBA510Q 2.50	TDA1327 1.70	
MC1327 0.95	SN76544N 1.95	TBA520 1.10	TDA1327 1.70	
MC1327Q 0.95	SN76570N 1.00	TBA520Q 1.10	TDA2002 1.95	
MC1330P 0.75	SN76570N 1.00	TBA530 1.10	TDA2020 2.45	
MC1349P 1.20	SN76600N 0.90	TBA530Q 1.10	TDA2030 2.80	
MC1350P 0.95				

### SEMICONDUCTORS

AA12 0.25	BC174 0.09	BD202 0.65	BF457 0.32	RCA1633A 0.90
AC127 0.20	BC174A 0.09	BD204 0.78	BF458 0.36	RCA1633S 0.90
AC128 0.28	BC177 0.15	BD222 0.48	BF467 0.68	SKE5F 1.45
AC128K 0.32	BC178 0.15	BD222 0.48	BF595 0.23	TP29C 0.42
AC141 0.28	BC182 0.10	BD223 0.48	BF597 0.25	TP29C 0.42
AC141K 0.34	BC182LB 0.10	BD225 0.48	BF597 0.25	TP29C 0.42
AC142K 0.30	BC183 0.10	BD232 0.35	BF597 0.25	TP29C 0.42
AC176 0.22	BC183L 0.09	BD233 0.35	BF597 0.25	TP29C 0.42
AC176K 0.31	BC184LB 0.09	BD234 0.35	BF597 0.25	TP29C 0.42
AC178 0.28	BC204 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
AC187 0.25	BC207B 0.13	BD236 0.35	BF597 0.25	TP29C 0.42
AC187K 0.28	BC208B 0.13	BD236 0.35	BF597 0.25	TP29C 0.42
AC188 0.25	BC212 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AC188K 0.37	BC212L 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD142 0.79	BC212LA 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD143 0.82	BC213 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD149 0.70	BC213L 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD161 0.38	BC214 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD162 0.39	BC214C 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AD161/2 0.30	BC214L 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AF114 1.80	BC237B 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AF124 0.85	BC238 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
AF125 0.35	BC239 0.12	BD236 0.35	BF597 0.25	TP29C 0.42
AF126 0.35	BC251A 0.15	BD236 0.35	BF597 0.25	TP29C 0.42
AF127 0.32	BC252A 0.15	BD236 0.35	BF597 0.25	TP29C 0.42
AF139 0.40	BC258 0.25	BD236 0.35	BF597 0.25	TP29C 0.42
AF178 1.95	BC258A 0.35	BD236 0.35	BF597 0.25	TP29C 0.42
AF229 0.42	BC284 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
AU108 3.25	BC300 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
AU110 2.00	BC301 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC107A 0.11	BC303 0.25	BD236 0.35	BF597 0.25	TP29C 0.42
BC107B 0.11	BC307B 0.09	BD236 0.35	BF597 0.25	TP29C 0.42
BC108 0.10	BC327 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC108A 0.11	BC328 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC108B 0.12	BC337 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC109 0.10	BC338 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC109B 0.12	BC347A 0.13	BD236 0.35	BF597 0.25	TP29C 0.42
BC109C 0.12	BC461 0.35	BD236 0.35	BF597 0.25	TP29C 0.42
BC114 0.11	BC478 0.20	BD236 0.35	BF597 0.25	TP29C 0.42
BC116A 0.15	BC527 0.20	BD236 0.35	BF597 0.25	TP29C 0.42
BC117 0.15	BC547 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC119 0.24	BC548 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC125 0.20	BC549A 0.08	BD236 0.35	BF597 0.25	TP29C 0.42
BC139 0.23	BC550 0.08	BD236 0.35	BF597 0.25	TP29C 0.42
BC140 0.31	BC557 0.08	BD236 0.35	BF597 0.25	TP29C 0.42
BC141 0.25	BC557B 0.08	BD236 0.35	BF597 0.25	TP29C 0.42
BC142 0.31	BC558 0.10	BD236 0.35	BF597 0.25	TP29C 0.42
BC143 0.24	BC573A 1.80	BD236 0.35	BF597 0.25	TP29C 0.42
BC147 0.09	BD115 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC147B 0.09	BD116 0.60	BD236 0.35	BF597 0.25	TP29C 0.42
BC148A 0.09	BD124P 0.59	BD236 0.35	BF597 0.25	TP29C 0.42
BC148B 0.09	BD131 0.32	BD236 0.35	BF597 0.25	TP29C 0.42
BC149 0.06	BD132 0.35	BD236 0.35	BF597 0.25	TP29C 0.42
BC157 0.12	BD133 0.40	BD236 0.35	BF597 0.25	TP29C 0.42
BC158 0.09	BD135 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC159 0.09	BD136 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC160 0.28	BD137 0.32	BD236 0.35	BF597 0.25	TP29C 0.42
BC161 0.28	BD138 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC170B 0.15	BD139 0.32	BD236 0.35	BF597 0.25	TP29C 0.42
BC171 0.09	BD140 0.30	BD236 0.35	BF597 0.25	TP29C 0.42
BC171A 0.10	BD144 0.11	BD236 0.35	BF597 0.25	TP29C 0.42
BC171B 0.10	BD159 0.65	BD236 0.35	BF597 0.25	TP29C 0.42
BC172 0.10	BD160 1.50	BD236 0.35	BF597 0.25	TP29C 0.42
BC172B 0.10	BD166 0.55	BD236 0.35	BF597 0.25	TP29C 0.42
BC172C 0.10	BD179 0.72	BD236 0.35	BF597 0.25	TP29C 0.42
BC173B 0.10	BD182 0.70	BD236 0.35	BF597 0.25	TP29C 0.42
	BD201 0.63	BD236 0.35	BF597 0.25	TP29C 0.42

### DIODES

AA119 0.05	BY199 0.40	IN4004 0.05	CRT TUBES
BA102 0.17	BY206 0.14	IN4005 0.05	A selection available. Prices on request.
BA115 0.13	BY208-800 0.33	IN4006 0.06	
BA145 0.16	BY210-800 0.33	IN4007 0.06	
BA148 0.17	BY223 0.90	IN4148 0.02	
BA154 0.06	BY228-400 0.22	IN4448 0.10	
BA155 0.13	BY296-800 0.22	IN5401 0.12	
BA156 0.13	BYX10 0.20	IN5402 0.14	
BA157 0.30	BYX36-150R 0.20	IN5403 0.12	
BA158 0.13		IN5404 0.12	
BA159 0.13		IN5405 0.13	
BA160 0.13		IN5406 0.13	
BA161 0.13		IN5407 0.16	
BA162 0.13		IN5408 0.16	
BA163 0.13		IN5409 0.16	
BA164 0.13		IN5410 0.16	
BA165 0.13		IN5411 0.16	
BA166 0.13		IN5412 0.16	
BA167 0.13		IN5413 0.16	
BA168 0.13		IN5414 0.16	
BA169 0.13		IN5415 0.16	
BA170 0.13		IN5416 0.16	
BA171 0.13		IN5417 0.16	
BA172 0.13		IN5418 0.16	
BA173 0.13		IN5419 0.16	
BA174 0.13		IN5420 0.16	
BA175 0.13		IN5421 0.16	
BA176 0.13		IN5422 0.16	
BA177 0.13		IN5423 0.16	
BA178 0.13		IN5424 0.16	
BA179 0.13		IN5425 0.16	
BA180 0.13		IN5426 0.16	
BA181 0.13		IN5427 0.16	
BA182 0.13		IN5428 0.16	
BA183 0.13		IN5429 0.16	
BA184 0.13		IN5430 0.16	

### CRT TUBES

36PI £13.50	D10-210GH £45
DG-732 £42	DH-71 £59
DP-7 £35	DP-71 £35
SE4DP7 £45	SE447 £135

### TV SPARES

We now have available from stock a range of popular TV Spares including: Line output transformers, Tuners - Triplers etc. Price List Available.



Has it with Access

[illegible]

★ ENTRANCE ON A22  
50 YDS SOUTH OF MEOPHAM GREEN  
**CAR PARKING AVAILABLE**  
Open Monday-Friday 9am-5.30pm  
★ 24 HOUR ANSWERPHONE SERVICE ★  
ACCESS AND BARCLAYCARD ORDERS WELCOME  
★ MANY OTHER ITEMS AVAILABLE ★

**UK ORDERS P&P 50p PLEASE ADD VAT AT 15%**  
EXPORT ORDERS WELCOME CARRIAGE/POST AT COS



# DX-TV RECEPTION REPORTS

Compiled by Keith Hamer and Garry Smith

With 1983 now firmly behind us perhaps a brief resume of DX conditions during the past year is in order. It was full of surprises with several tropospheric openings occurring during the early part but few enthusiasts thought the trend would continue. The more notable lifts appeared towards the end of August and during the final week of October when Spanish Band III and UHF signals arrived in the UK.

Sporadic-E (SpE) was unpredictable and produced a short but hectic summer season. However, from September onwards, Band I livened up and throughout October and November there were days when summer-like DX conditions returned. During the main SpE season conditions favoured countries in south-eastern Europe such as Italy, Yugoslavia and Rumania. The latter was a regular visitor during the year. For the lucky few, trans-Atlantic DX was a reality with 525-line signals from the West Indies on channels A2, A3 and even A4. Reception from the Middle East was noted on several occasions from Dubai by Hugh Cocks in East Sussex. Some enthusiasts noted mysterious unidentified signals emerging from darkest Africa but most of us were content with the sight of the Jordanian test card from JTV Amman as our 'exotic' of the season.

## Interference

Coping with interference problems caused by itinerants in Band I, such as illegal cordless telephone users, proved a headache especially for enthusiasts without any real knowledge of interference reduction techniques or those using receiver systems with insufficient selectivity. A few CB experts operating screwed-up rigs caused problems at times for some, but fortunately this form of CB activity seems to be on the decline.

Having reviewed the rest of 1983 let's now concentrate on December. There were two tropospheric openings during the month, one at the beginning and one at the end. Neither was spectacular since the number of transmitters logged was small, but the few that were noted provided excellent quality colour signals at consistently high levels. The 'usuals' logged here at Derby included Belgium and the Netherlands in Bands I, III and at UHF, North-East France (UHF) and West Germany in Band III and UHF from NDR and WDR.

Sporadic-E improved from the 20th producing a mid-winter peak which is often present around the festive season. One signal of note which appeared here for a few minutes on the 21st was a Finnish transmitter on channel E3 radiating the 'YLE TV 1' FuBK test card. The outlet is situated at Tervola which is almost within the Arctic Circle.

Meteor Shower (MS) activity caused a few 'pings' in Band III on channel E5/R6 on several days but nothing was positively identified. Perhaps the Quadrantids during early January will be better.

## Reception reports

Deryck Fentem (Mickleover, Derbyshire) noted several West German ZDF transmitters during the morning of December 4th with an orchestral concert.

BBC-1 North West and Granada TV could have fierce competition from TDF-France around the Wigan area. At least that is how it appears according to Andrew Webster's DX-TV report for the first few days of the month. His location is apparently good for reception of French TV stations and also British ones operating in the south of the UK.


A French ATV station was seen on the 1st, 2nd and 3rd using a pattern similar to

the Philips PM 5544 with the call-sign EDM (Le Havre). Andrew's reception was in PAL colour but the red was missing times. The TDF 'tf 1' (1st Network) PM5544 was noted on the 2nd during an experimental test transmission in Band III using line scrambling technique. Details about this new system were given in last month's column. Other test signals over the period came from West Germany at UHF and Band III and also Belgium, notably BRT on channels E3, E43 and E46. The latter was from the Egem transmitter which radiates the BF 2nd Network.

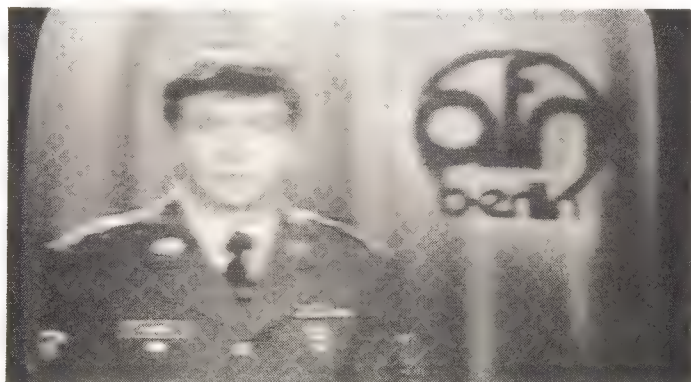
## Outstanding results

The Geminids meteor shower provided Clive Athowe (Blofield, Norfolk) with some outstanding reception in Band I. On the 12th he noted the TSS announcement with the familiar digital clock in the lower left-hand corner of the screen on channel R6 at 2105GMT. TSS were again seen on this channel with a globe caption on the 14th at 2000 and earlier in the day radiating the colour electronic test card. Other Band III MS successes included ORF on E5 (the signal also appeared on the more usual channel E2a) and Sweden on the same channel. Clive is delighted with the results obtained from his new aerial system. He now has a vertically polarised XG21K array which enables him to watch AFN-TV from the channel E34 outlet at Shape in Belgium. On the 29th the signal remained strong during the evening and he noted 'Dynasty' at 2010GMT. The programme was on the 525-line standard with 4.5MHz sound/video spacing (transmission system 'M'). During the early hours of the following morning (Clive had fallen asleep in his shack!) he awoke to note several British Forces Broadcasting Service transmitters on the air at around 0200. They were radiating the PM5544 test card with the identification 'BFBS COLOUR'. In fact Clive logged no fewer than 14 transmitters!

Simon Hamer has once again been very active with DX-TV at his farm near Presteigne in Powys. On the 23rd he noted the Norwegian PM5544 test card carrying the identification 'NORGE HEMNES' on channel E3. The following day reception was enhanced by a lift in trop which resulted in RTB:F on E3 and E8, BRT TV2 on E46 and E62 and NOS. The mischievous antics of Loeki the Lion were seen between Dutch commercials



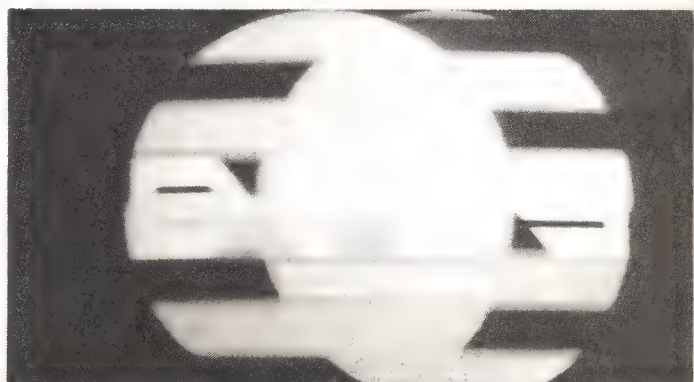One of the announcers at the American Forces Network in Berlin. AFN-TV uses the 525-line standard



Identification caption used by the British Forces Broadcasting Service in West Germany



E5 and E29. The West German TV services of ZDF, Westdeutscher Rundfunk and Hessischer Rundfunk were also all to the fore on UHF. Amongst some of the programmes logged were the ZDF news programme 'Heute' and ARD's news bulletin 'Tagesschau'. On the 29th I then received several ATV signals but they were too weak to positively identify. In the radio front, BFBS were romping in at 96.5MHz and managed to swamp the BBC Radio Derby programme which he was trying to listen to. 1984 Started well for Simon as he received a programme from Italy on the RAI channel 1A at 2200 on January 3rd. There were also several unidentified stations received in Band I during an SpE opening. Upon returning home at 1600 on the 10th Cyril Willis (Little Downham, Cambridgeshire) found the UHF band generally crammed with DX. He reports excellent ATV conditions with signals from 19 operators located throughout the UK, Belgium, France and the Netherlands. Two mystery broadcast TV services were also noted. The first consisted of colour bars with 5.5MHz sound from 2050 GMT until the early hours on channel E56. The second mystery was seen from 0030 onwards on channel E34 and was evidently a Dutch pirate station showing an English film with Dutch subtitles. The station closed at 0050 with the identification 'VCN'. It is thought that the initials stand for Video Centre Nederland.

#### Log for December

Meanwhile, here is our log for December:-

**2/12/83:** NOS-1 (Netherlands) Lopik channel E4, Roermond E5 and Smilde E6 on PM5544 test card; ZDF (West German 2nd Network) on E33 from Ostfriesland and E35 (Wesel) both on FuBK test card with 'ZDF' identification; WDR-3 (West Germany) E48 from Wesel on Schools-TV programme caption via early morning tropospheric reception. All these transmitters were also noted during the evening radiating programmes with the following additions: BRT (Belgium) channel E10 from Wavre, NOS-1 channel E39 (Wieringermeer), E47 (Smilde) and NOS-2 E45 (Wieringermeer), RTB:F 1 (Belgium) on E11 from Anlier.  
**3/12/83:** Early morning tropes (0730 until 0830 GMT) consisting of the following:- DDR:F 1 (East Germany) on E11 from Schwerin on test card; NOS 1 and 2 on E4

and E6 together with most UHF outlets using the EBU Bar pattern; NDR-1 (West Germany) from Lingen on E41 using the FuBK without a circle; ZDF E33, E35 and E37 on FuBK pattern with 'DBP ZDF' identification; WDR-1 Teutoburger Wald on E11 with programmes; programmes on channel R1 in Band 1 VHF via Sporadic-E. During the evening amateur TV activity was noted with PE1 DWA from the Netherlands showing a caption and a modified version of the BBC Test Card 'C'.

**4/12/83:** BRT E10, E43 (Egem) and E44 (Genk) on 'BRT TV 1' PM5544 test card; ZDF E34, E35 and E37 with a music programme; NDR-3 E40 (Hamburg) on progs; TDF (France) E42; Dutch ATV stations PE1 1XK and PA3 310.

**7/12/83:** Unidentified signals via MS on channels R1, R2 and E3 all with programme material.

**8/12/83:** CST (Czechoslovakia) R2 using the 'RS-KH' EZO test pattern; ORF (Austria) on E2a transmitting the PM5544; RTB: F 1 E11 showing pages from their teletext service called Percival, noted via weak trop.

**12/12/83:** Geminid MS activity noted in Band III with the PM5544 on E5 from an unidentified source.

**13/12/83:** Unidentified E5 signal via MS with the PM5544 at 0828 GMT, also programmes via MS on E5/R6 at 1755GMT.

**14/12/83/:** MS activity noted between 0730 and 0845 as follows: R2 and R6 programme for approx. 10 seconds; TSS (USSR) on R2 using the 0249 monoscopic test card at 0843 GMT.

**17/12/83:** Short SpE opening at 1322 consisting of ice skating on R1 and unidentified signals on R2.

**18/12/83:** NOS-1 E5 on PM5544 via weak tropospheric scatter; MS activity noted on R1, R2 and E5/R6 throughout the day; TSS R1 and R2 with the clock caption and progs via SpE in the late afternoon; DR (Denmark) E3 with clock caption and programmes via SpE at 1815.

**20/12/83:** CST R1 on 'RS-KH' test card; SR-1 (Sweden) E3 radiating the 'TV 1 SVERIGE' PM5544.

**21/12/83:** YLE (Finland) on E3 from Tervola on FuBK test card via SpE; DDR: F 1 test card on channel E4.

**22/12/83:** CST R1 and R2 with the EZO test card.

**23/12/83:** DR E3 with the 'DR DANMARK' PM5544; NRK (Norway) E3 on PM5544. A late afternoon SpE opening produced

CST on channel R2 with 'Bratislavsky Magazine'; TVP (Poland) R2 on 'TP 1' caption and programmes; MTV (Hungary) R1 with a quiz prog; unidentified programmes on E3 via SpE which are thought to be of Yugoslavian origin.

**24/12/83:** Unidentified MS activity on R2.  
**26/12/83:** TSS R2 using the electronic test card; unidentified colour bars on R1 at 0956.

**27/12/83:** TVP R1 on PM5544 which has a darker background than normal; enhanced tropes gave RTE (Eire) on channel 1H and TDF-2 on E39 from Dunkerque-Mont-des-Cats; BRT E10 on progs until closedown at 2205 GMT with very strong signals' RTB:F 1 E8 and E11 until closedown at 2230. The E11 outlet then radiated the PM5544 test card with 'LEGLISE CANAL 11' ident.

**28/12/83:** NRK E3 from Bagn using the PM5544; DR E3 on test card; early evening tropes consisting of BRT E10 and TDF on approximately channel E11 showing colour bars with text traversing the screen.

**29/12/83:** Excellent tropospheric lift during the evening producing BRT E10, NOS E4 and E5 (the latter was very strong from 2000GMT), RTB:F 1 E3 from Liege plus channels E8 and E11 until closedown at 2225. TDF were seen on E34, E39 and E42 and ZDF appeared on E35 and E37. First Network programmes from West Germany were received from 2200 on E5, E6, E9 and E11 plus a mystery channel located between E5 and E6.

**30/12/83:** SR-1 E2 on test card; unidentified programmes on R2 and R3 via meteor showers.

**31/12/83:** RTE from Gort on channel 1B via MS; TSS R1, R2 and R3 on progs. Weak tropes from Belgium were noted on E3, E8 and E11 from the 1st Network of RTB:F and on E10 from the BRT service.

#### Service information

**Denmark:** Danmarks Radio (DR) started an experimental regional TV service last October via the 60kW channel E7 transmitter at Sonderjylland. The service is known as 'TV-SYD'.

**Hungary:** There is a new 9kW outlet in service at Csavoly on channel R7. It is vertically polarised and radiates the 1st Network of Magyar Televizio (MTV-1).

**Netherlands:** The American Forces Radio & Television Service in Europe (AFN-tv) is expected to bring a 5kW



Transmitter identification caption shown in West Germany from Goettingen on Channel E59



FuBK test card radiated by Sender Freies Berlin. Photo courtesy of Juergen Klassen in West Berlin




transmitter into service at Soesterberg. It is anticipated that programmes will be received in colour (NTSC) at a distance of up to 15km from the base. It will broadcast on the American channel 82 which corresponds to an 'E' channel of 71/72 and therefore lies outside the standard UHF range.

**Czechoslovakia:** CST have a new method to indicate the TV network when radiating the EZO-type test card. CST-1 remains unaltered but CST-2 has a white square towards the top right-hand corner.

There is a new UHF transmitter on channel R22 located at Roznava. It has an ERP of 100kW.

**Luxembourg:** The channel E7 System B

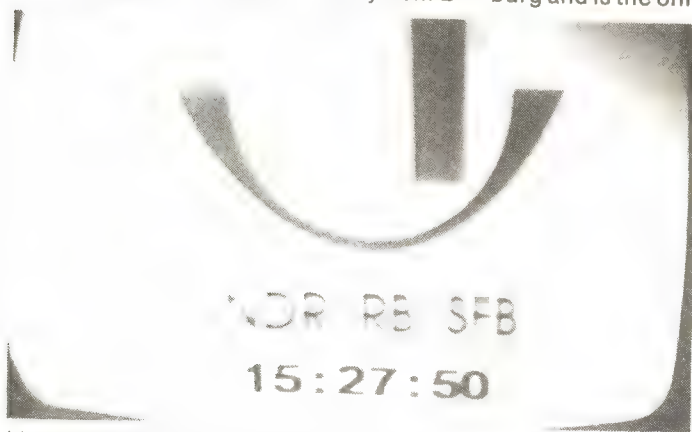

Identification caption used by three of West Germany's TV networks

outlet at Dudelange has been seen with new identification on their Philips PM5534 test card which is transmitted by the new German language service at certain times of the day. The inscription 'KANAL 7' appears at the top and 'RTL-PLUS' at the bottom.

**Turkey:** The FuBK test card minus the circle has now replaced the Telefunken TO5 test card following the introduction by TRT of colour programming using the PAL system.

**South Africa:** A new independent television service began on January 2nd of this year in one of South Africa's provinces. BOP-TV now beams programmes to black townships near Johannesburg and is the only rival in the country to

the main State-owned TV service operated by the South African Broadcasting Corporation.

BOP-TV radiates the PM5534 test card with identification and the opening caption is shown in Figure 1

**Rumania:** Yet another colour electronic test card is in use prior to the start of programmes. It is the FuBK with the identification 'TVR BUCURESTI' across the centre. The old monochrome EBU Bar is still radiated. Incidentally, the other new colour test card featured in the February issue of R&EW was inadvertently shown upside-down.

Our thanks go to Clive Athowe and Goesta van der Linden (Netherlands) for supplying most of this month's Service Information.




Opening caption of South Africa's first independent - BOP-TV. The first programme to be shown on January 2, 1984 was 'Woody Woodpecker'

**Radio & Electronics World —**  
The monthly communications,  
electronics &  
computers magazine

Don't take a chance on  
being able to get your copy

**AVOID DISAPPOINTMENT**  
Place a regular order  
with your newsagent

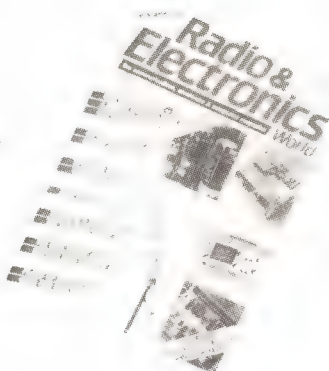Should you have any  
difficulties obtaining a  
copy, phone (0277) 219876  
or write to Circulation  
Department, **Radio &  
Electronics World**,  
Sovereign House,  
Brentwood, Essex CM14 4SE



## NEWSAGENT ORDER FORM

**Radio &  
Electronics**  
the communications, electronics & computers magazine **World**

To (name of newsagent)

Please order a copy of **Radio & Electronics World** for me every month

NAME.....

ADDRESS.....

Newstrade distributors: Seymour, 334 Brixton Road, London SW9  
7AG. Tel: 01-733 4444

## SECURITY Alarm Systems

**FREE COMPREHENSIVE CATALOGUE!**

- **LOWEST DISCOUNT PRICES**
- **HIGHEST QUALITY EQUIPMENT**
- **FREE DIY DESIGN GUIDE**
- **FULLY ILLUSTRATED**
- **MICROCHIP CIRCUITRY**
- **QUICK DESPATCH SERVICE**
- **FULL INSTRUCTIONS**

**SEND SAE OR PHONE**

**C-TEC SECURITY, Dept REW**  
60 Market St, Wigan WN1 1HX  
Telephone (0942) 42444

**Trade  
Enquiries  
Welcome**

### ANTENNES TONNA (F9FT)

<b>80MHz</b>		
5 element†	<b>£34.30(a)</b>	
<b>144MHz</b>		
4 element	<b>£14.95(a)</b>	
9 element fixed	<b>£17.71(a)</b>	
9 element portable	<b>£20.00(a)</b>	
9 element crossed†	<b>£32.43(a)</b>	
13 element portable†	<b>£31.05(a)</b>	
17 element fixed	<b>£37.66(a)</b>	
<b>435MHz</b>		
19 element	<b>£20.70(a)</b>	
19 element crossed†	<b>£34.27(a)</b>	
21 element 432MHz	<b>£29.67(a)</b>	
21 element ATV	<b>£29.67(a)</b>	
<b>144/435MHz</b>		
Oscar Special		
9 & 19 element†	<b>£34.27(a)</b>	
<b>1250MHz OR</b>		
<b>1296MHz</b>		
23 element†		<b>£25.90(b)</b>
4 x 23 ele antennas - power		
splitter - stacking frame		<b>£140.00(a)</b>
<b>Telescopic Portable Masts</b>		
4 x 1m	<b>£18.66(a)</b>	3 x 2m <b>£21.65(a)</b>
4 x 2m	<b>£33.20(a)</b>	
<b>ANDREW HELIJAX LDF4-50 COAXIAL CABLE</b>		
Attenuation per 100ft. 144MHz-0.8dB		
435MHz-1.6dB. 1296MHz-2.9dB		
<b>£3.40 per metre (a).</b> 'N' Type		
connectors for LDF4-50 male or female		
<b>£12.00</b>		
<b>MICROWAVE MODULES - ROTATORS -</b>		
<b>COAXIAL CABLES ETC.</b>		
<b>POWER SPLITTERS AVAILABLE FOR 2 OR 4</b>		
<b>ANTENNAS</b>		

†Denotes 50Ω ONLY - all others 50Ω or 75Ω impedance

**PLEASE ADD CARRIAGE AS SHOWN (a) £4.00, (b) £1.95. ALL PRICES INCLUDE VAT AT 15%**

Terms: Cash with order. ACCESS-VISA - telephone your card number.

**FOR FULL SPECIFICATION OF OUR RANGE SEND 30p FOR CATALOGUE.**  
Callers welcome, but by telephone appointment only please. Goods by return.

**RANDAM ELECTRONICS (Dept REW)**

12 Conduit Road, Abingdon, Oxon OX14 1DB. Tel: (0235) 23090 (24 hours)



# — DATES FOR — — YOUR DIARY —

Dates for your diary is updated every month.

club secretaries and organisers are requested to send information of forthcoming events as early as possible to *Radio & Electronics World*, Dates for your Diary, Sovereign House, Brentwood, Essex CM14 4SE


Date	Function	Location	Contact
March-16 April	Lectures on a variety of topics	IEEIE	Tel: 01-836 3357
March	Club project/construction night	S Bristol A.R. Club	L Baker G4RZY
March	Lecture - Amateur Radio on a Shoestring	Lincoln Short Wave Club	Pam Rose G4STO
March	BSC/Computing Award Winner	Lancaster Polytechnic	BSC, Coventry Branch
March	4th Annual Components Fair	Carleton Community Centre	A Mason G4TGU
		Pontefract	N Whittingham G4ISC
	SWL night	S Bristol A.R. Club	G8XIH/G4OPQ
March	Annual General Meeting	Lincoln Short Wave Club	Pam Rose G4STO
March	Computer Night	S Bristol A.R. Club	Terry G6SVR
April	White Rose ARS Rally	University of Leeds	A Bramley G4NDU
April	Microcomputers as applied to amateur	Chelmsford A.R. Society	J Martyr G3PMX
	Radio - talk by A Butcher G3KPJ	Marconi College	AC Mead G4KGB
April	Lecture - Data Comms RS232-X-25	S Bristol A.R. Club	Steve G4MCQ
April	Talk by visitor from Leighton Club	Dunstable Downs Radio Club	P Seaford G8XTW
3 April	Amateur Radio Exhib on computing and electronics	Northern A.R. Society Assocn	P Denton G6CGF
April	Lecture-UHF then and now with a look at	Lincoln Short Wave Club	Pam Rose G4STO
	RSGB Metre- Wave Awards System HF night		
	HF night	S Bristol A.R. Club	Alan G4TSS
	Bring & Buy Sale	Farnborough and District Radio Soc	P Taylor G4MBZ
5 April	Two-Metre FM contest	Stevenage & Dist A.R. Society	B Dean G6NZC
7 April	Display by D Howes G4KQH	Biggin Hill A.R. Club	I Mitchell G4NSD
	C M Howes Communications		
8 April	VHF NFD preparation night	S Bristol A.R. Club	Mark G4KUQ
5 April	Activity night/Night on the air	Lincoln Short Wave Club	Pam Rose G4STO
	'Brains Trust'	Farnborough and District Radio Soc	P Taylor G4MBZ
	10-metre FM night	S Bristol A.R. Club	Colin G4SQQ
7 April	DF Hunt 160 & 2 mt	Dunstable Downs Radio Club	P Seaford G8XTW
8-29 April	RSGB National AR Exhibition	NEC Birmingham	RSGB Potters Bar 59015
May	R F Power Transmitters talk by	Chelmsford A.R. Society	J Martyr G3PMX
	Dick Brocks G3WHR	Marconi College	AC Mead G4KGB
May	Lecture - 23 cms operation	S Bristol A.R. Club	Steve G4MCQ
-7 May	Midland Computer Fair	NEC Birmingham	Fiona Howell 01-643-8040
1 May	TV Show Repeat	Dunstable Downs Radio Club	P Seaford G8XTW
6 May	Fox hunt briefing	S Bristol A.R. Club	G8XIH/G4OPQ
23 May	2 Metre SSB Night	S Bristol A.R. Club	G6ZTX/G6ZTY
25 May	Oscar 10 by G3VZV	Dunstable Downs Radio Club	P Seaford G8XTW
30 May	ATV Night	S Bristol A.R. Club	Peter G8WAX
3 June	Lecture Radio Interference Service	S Bristol A.R. Club	Len G4RZY
3 June	Summer Barbecue at Old Warden	Dunstable Downs Radio Club	P Seaford G8XTV
13 June	Longleat Preparations	S Bristol A.R. Club	G4KUQ/G4RZY
17 June	Royal Navy ARS Mobile Rally	HMS Mercury nr Petersfield	A Walker G4DIU
20 June	Longleat Final Briefing	S Bristol A.R. Club	G4KUQ/G4RZY
22 June	VHF NFD Planning	Dunstable Downs Radio Club	P Seaford G8XTW
24 June	Car Boot Sale	Dunstable Downs Radio Club	P Seaford G8XTW
27 June	VHF NFD Final Preparations	S Bristol A.R. Club	G8XIH/G4OPQ


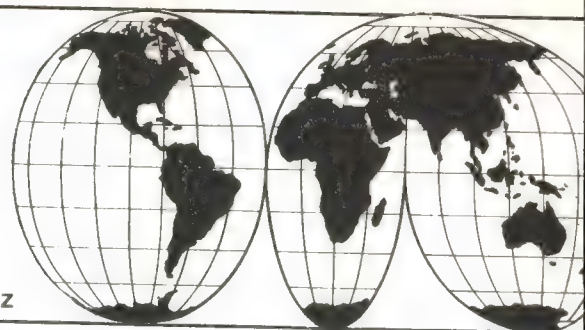
# SHORT WAVE NEWS FOR DX LISTENERS

by Frank A Baldwin

All times in GMT, **bold** figures indicate the frequency in kHz



It is during this month that the 'season' for the reception of comparatively low powered Far Eastern and South East Asian transmitters on the LF bands closes. But with luck you may hear some of the stations listed here in frequency order, all in the 60-metre band. (**4750** to **5050**).

At the extreme low end of the band may be found the Tibetan transmitter of Xizang PBS (Lhasa) with programmes in Chinese and Tibetan. Opening at 2300 and finally closing at 1545, it is just prior to these times that the DXer should tune to **4750** in order to log or tape the announcements and identification.

Yunnan PBS in Kunming operates on **4763** opening at 2150 and closing at 1600. This is Yunnan 1 which operates, of course, in Chinese.

On **4770** you may be fortunate enough to log Radio Pyongyang. When operating it is scheduled from 1200 to 1300 and from 1500 to 1555.

Radio Thailand, Bangkok, on **4830** is often reported in the SWL press, being on the air from 2245 to 0700 and from 1000 to 1600 with a power of 10kW. Best time to listen for this one is around the 1530 mark according to my experience.

On nearby **4835** you may be lucky enough to hear the signals from Radio Malaysia, Kuching in Sarawak. This one opens at 2200 and finally closes at 1600, the main language being Malayan. With its 10kW signal it is often heard here in the UK.

Tuning to **4840** around 2130 may result in entering into your log the details appertaining to Heilongjiang PBS, Haerbin (Harbin) with the Domestic Service 2 in Chinese and relays of Radio Beijing (Peking). It opens at 2055 (May to October from 2000) and finally closes at 1355. Final closing times are mentioned here for the reasons that (a) they are favourable for reception here in the UK, and (b) like many stations from this general

area of the world operating on the LF bands, they are on the air for two or more differing time-slots. Haerbin, for instance, is scheduled from 2055 (May to October from 2000) to 2300, from 0155 to 0500 and from 0850 to 1355.

Kuala Lumpur on **4845** provides programmes for the local Indian community but you are hardly likely to be confused as the nearest Indian transmitter is that of AIR Bombay on **4840**. Radio Malaysia has a power of 50kW and so is often heard here in the UK. It opens at 2130 Sunday to Friday and at 2200 on Saturday. It closes at 1530 except on Sunday when the sign-off is at 1500.

If you would like to have a go at Mongolia then you may care to tune to **4850** at which point on the dial is to be found Ulan Bator with the Home Service 1 programmes and including some Foreign Service transmissions in Russian and Chinese. For the Mongolian presentations listen at the opening and closing times of 2200 and 1600 respectively. The power is 100kW – and that helps!

Newcomers to the DXing game on the LF bands who have not, as yet, logged a Chinese station would be advised to set the dial pointer to **4865** where will be found the most often reported Gansu PBS in Lanzhou with the Domestic Service in Chinese and some relays of R. Beijing 1. It opens at 2115 and finally closes at 1600, featuring English language lessons weekdays from 0000 to 0030 and daily from 1330 to 1400.

The foreign Service in Mongolian and Russian of Radio Beijing operates on **4883** but is seasonal in that it is on the air from October to April inclusive, opening at 2200 and finally closing at 1600. For some reason I haven't managed to log this one so far this year, probably I have missed the favourable reception periods. Oh well, there is always the next season.

How about Papua New Guinea? Well, you could have a try – it has been reported from time to time by UK DXers. The channel is **4890** and it opens at 1930 and is scheduled through to 1400 continuous. The power is 10kW and probably the best time would be around 2030 and let's hope that the Senegal-based transmitter at Dakar on the same channel is not also making the trip.

Guangxi PBS at Nanning is fairly often heard on its **4915** channel where it opens at 2110 and finally closes at 1605. This is Guangxi 1 in Chinese and dialect, also relays of Radio Beijing 1.

Another Chinese transmitter is that of Qinghai PBS, Xining, on **4940** opening at 2220 and finally closing at 1520. This is the Domestic Service 1 but also has local programmes and some English language lessons, one of these being from 1400 to 1430.

On **4950** there is the often reported Radio Malaysia transmitter at Kuching in Sarawak from where it operates from 2200 to 0100 and from 0830 to 1600 in English and Chinese. The power is 10kW.

Not quite so often logged is Radio Malaysia, Kota Kinabalu, Sabah on **4970** which operates in English and Malayan from opening at 2130 and finally closing at 1600, also at 10kW.

The Chinese station sited at Hunan on **4990** (Hunan PBS, Changsha) can sometimes be heard when conditions are right. This one opens at 2120 and finally closes at 1600.

On **5005** the Malaysian station at Sibu, Sarawak radiates programmes in a local language, opening at 2200 and finally closing at 1500 with a power of 10kW. There is a snag, however, with this one in that it is mostly covered by signals emanating from Radio Nepal, Katmandu on the same channel, opening at 0020 and finally closing at 1720 but with a power of 100kW.

A good general 'marker'

enabling the judging reception conditions for nals from the Far East. South East Asia are th from Radio Singapore. language used is English being directed towards Malaysia – and the late afternoon programme is usually pop records with a announcer. If you can h this station at a fair sig strength then usually it is case that other transmitt in this part of the globe r also be logged – QRM perr ting. Radio Singapore op at 2230 through to 1610 c tinuous, the power be 50kW, the frequency **5052**.

At the high end of the ba is the Chinese transmitt Xinjiang PBS at Urumqi wh features both the R. Bei and local programmes Mongolian, opening at 23 and finally closing with t language transmission 1700. It also features the Beijing Foreign Servi transmission in Russian fr 1800 to 2055 but this, course, is jammed.

## AROUND THE DIAL

This month, a commencement is made by presenting some times and frequencies that may interest DXers who rove over the 90-metre band

## AFRICA

### Ghana

Ejura on **3350** at 0604, O with a talk in vernacular probably a newscast in th Home Service 1 which scheduled from 0530 to 0800 (Sunday until 0900) and from 1530 to 2305. The power is 20kW and this station is on th air irregularly.

Accra on a measured **3360** at 0608, OM with a newscast in English. On this frequency Accra is scheduled from 0530 to 0800 (Sunday until 0900) and from 1530 to 2305, the same as Ejura but with a power of 10kW.

### Liberia

ELWA ('Eternal Love Winning Africa') Monrovia on



0 at 2156, OM with a talk in vernaculars. This is the Home Service entirely in vernaculars and on the air from 0600 to 1800 and from 1805 to 2230 with a power of 10kW. Programmes are mainly religious.

**BS (Liberia Broadcasting System)** Monrovia on **3255** at 1803, OM with a newscast in English. This 25kW transmitter is on the air from 0458 (Sunday from 0558) to 0700 and from 1830 to 2400.

## Malagasey

**Tananarive** on **3287** at **1656**, OM with a song in vernacular complete with local orchestral backing. Earlier in the month however Tananarive is logged on a measured **35.8** at 1754. It is timed as operating from 0300 to 0500 and 1500 to 1900 in Malagasey and from 1900 to 2100 in French. The power is 100kW.

## Malawi

**Blantyre** on **3380** at 1750, OM and YL with announcements, OM's with songs, all in Chichewa. The schedule is 1555 to 0530 (until 1110 from April to September) and 1745 from 1300 April to September to 2215. The Foreign Service in English is from 1600 to 1700 and the power is 100kW.

## Namibia

**Windhoek** on **3270** at 1743, OM with announcements, OM with songs in vernacular. This is the SWABC local languages service which operates 0400 to 0515 and 1600 to 2200, at which latter time the SABC All Night Service commences and continues to 2400. The power is 100kW.

**SWABC Windhoek** on **3295** at 0140, YL with a pop song in English in a relay of the SABC. All Night Service timed from 2200 to 0400 which is in parallel with that mentioned above. The remainder of the schedule is from 0400 to 0615 and from 1600 to 2200 in English, Afrikaans and German. The power is 100kW.

## Nigeria

**Lagos** on **3326** at 0554, YL with songs in vernacular, OM with announcements. 'Radio Nigeria' is scheduled from 0430 to 1000 and 1700 to 2310 with a power of 50kW.

## South Africa

**SABC Johannesburg** on **3250** at 0156, pop records with announcements by OM in English during the All Night Service programme timed from 2200 to 0300. The 'Radio

5' schedule is from 0300 to 0545 and from 1530 to 2200. The power is 100kW.

## Togo

**Radio Difusion de Kara** on a measured **3222** at 0559, OM's with a song in vernacular backed by a rhythm section local-style. OM with station identification and announcements in French at 0600. This 10kW transmitter is scheduled from 0530 to 0830 and from 1630 to 2305.

## AMERICA-SOUTH

### Brazil

**Radio Riberao Preto** on **3205** at 0050, YL with a talk in Portuguese then OM with folk songs. On the air from 0800 to 0400 at 1kW. **Radio Cultura, Araraquara** on **3365** at 0242, OM with a talk about local events - mostly sports. In Portuguese from 0800 to 0300 at 1kW.

### Ecuador

**Radio Iris, Esmeraldas** on a measured **3381** at 0153, OM with a talk in Spanish this followed by some local-style music. The schedule is from 1000 (Sunday from 1100) to 0400 variable and the power is 10kW.

**Sistema de Emisora Atalaya, Guayaquil** on a measured **4792** at 0232, OM with a sports commentary in Spanish with much trilling of the R's - an accomplishment greatly admired in Latin America. The power is 5kW, the schedule 0100 to 0455.

### Peru

**Radio Inca, Lima** on a measured **4762** at 0225, YL with a talk in Spanish about the Peruvian President ('Presidente') followed at 0230 by OM with station identification and Andean pipe music. R Inca is on the air from 1000 to 0500 but has been reported varying the closing time up to 0600.

### Colombia

**La Voz de Yopal** on **5050** at 0200, OM with station identification in Spanish then a long talk about local politics with several mentions of Colombian place-names. The schedule is from 1030 to 0400 and the power is 1kW.

## EUROPE

### Denmark

**Copenhagen** on **15165** at 1058, interval signal then OM with station identification in English and target areas.

Chimes for 1100 then into the Danish transmission for Greenland and the Pacific, timed from 1100 to 1150.

## Greece

**Athens** on **11645** at 1140, YL with a newscast in Arabic to Egypt and Libya, scheduled from 1130 to 1150.

## Spain

**Madrid** on **9650** at 0832, OM with announcements in the Spanish-language 'Programa Mundial' (Worldwide Programme) scheduled on this channel from 0600 to 0930.

## Switzerland

**Berne** on **25780** at 1030, 'pips' time-check, YL with station identification in English followed by the Music Programme for Europe and Africa, timed from 1030 to 1100.

## Vatican

**Vatican City** on **11700** at 2055, OM with an English transmission to Africa. The daily schedule being from 2045 to 2100.

## FAR EAST

### China

**Jilin PBS (People's Broadcasting Station)** on **3310** at 2202, OM with a talk in Chinese. Jilin is on the air from 2050 to 0530 and from 0850 to 1500. From 2100 to 2130 there is an English language lesson and also from 1330 to 1400 but this one is unlikely to be heard here in the UK.

**Radio Beijing (Peking)** on **3220** at 2206, OM with a talk in Chinese in the Domestic Service 1 Programme from 2000 to 2330 (November to April until 2300) and 1400 to 1735.

## MIDDLE & NEAR EAST

### India

**AIR (All India Radio) Lucknow** on **3205** at 1520, OM with a talk in Hindi scheduled from 0025 to 0215 and 1215 to 1740 with a power of 10kW.

**AIR Gauhati** on **3235** at 1534, OM with a newscast in English. The schedule is from 1230 to 1700 (Saturday until 1740) and the power is 10kW.

**AIR Madras** on **4920** at 1527, YL with a song in Hindi, some local-style music. YL with announcements and station identification, 'pips' time-check at 1530 then OM with the local news in English.

**Madras** is scheduled from 0025 to 0215 and from 1200 to 1740. The power is 10kW.

## Israel

**Jerusalem** on **7410** at 2230, OM with station identification and the news at the start of the English transmission to Europe and the Americas, timed from 2230 to 2300.

## Pakistan

**Karachi** on **21800** at 1100, OM with station identification, time check as '1600 hours Pakistan time' then the news in English at dictation speed, scheduled from 1100 to 1115.

## SOUTH-EAST ASIA

### Australia

**ABC Brisbane** on **4920** at 1950, OM with announcements in English during a programme of local and UK pop records. Scheduled from 1900 (Sunday from 1930) to 1402, power is 10kW.

## INDONESIA

**RRI (Radio Republik Indonesia) Tanjung Pinang** on **3225** at 1528, OM with songs in Indonesian. This one closed at 1555.

**RRI Banjarmasin** on **3250** at 1526, YL with a song then some Gamelan music. This transmitter closes at 1520. Power is 10kW.

**RRI Bengkulu** on **3265** at 1533, OM with a talk in Indonesian. At 10kW, Bengkulu signs-off at 1600.

**RRI Padang** on **4002** at 1553, YL with songs in Indonesian. Padang is off at 1600 (Saturday at 1700) power is 10kW.

**RRI Medan** on **4764** at 1549, YL with a talk in Indonesian. Medan signs-off 1700 and has power 50kW.

## CLANDESTINE

Voice of the United Muslim Fighters of Afghanistan' on **15305** at 1552, OM with fiery sounding announcements in Pashto or Dari, I'm not sure which, OM with a quotation from the Holy Quran.

## NOW LOG THIS

**Radio Nepal, Kathmandu** on **3230** at 1524, YL with songs in Nepali, local-style music. Closing at 1720, it is in parallel on **5005** and the power is unknown but the latter frequency is listed as 100kW.

## NOW HEAR THESE

**Turkish State Meteorology Service, Ankara** on **6900** at 1530, YL with a local pop song then some Turkish-style music. This one is scheduled from 0358 to 0600, from 0700 to 0840 and from 1100 to 1550 with a power of 2.5kW. The address is Post Office Box 401, Ankara.




# T.V. SOUND TUNER

SERIES I

BUILT AND TESTED

£26.50 + £2.00 p&p.

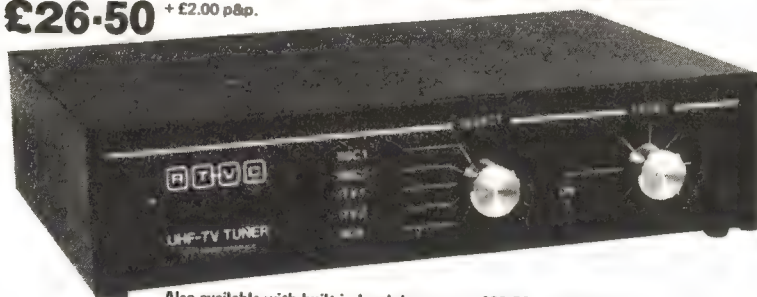

Also available with built-in headphone amp. £32.50 + £2.00 p&p.


In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound.

Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated.

This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10½" x 7½" x 2½"

E.T.I. kit version of above without chassis, case and hardware. £16.20 plus £1.50 p&p.
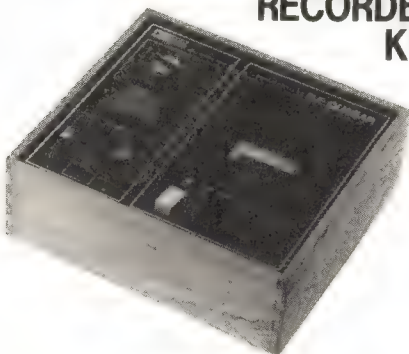
## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT



• NOISE REDUCTION SYSTEM • AUTO STOP • TAPE COUNTER • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS • TWIN V.U. METER • WOW & FLUTTER 0.1% • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES. — METAL, CHROME DIOXIDE, ETC.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire.

Featured in April issue P.E. Reprint 50p. Free with kit.

£34.50 + £2.75 p&p. Complete with case.

## SLEEP SAFELY AT NIGHT

### SMOKE DETECTOR ALARM!

Gamma ionization type smoke detector with built-in audible alarm. Model No. F227.

IDEAL FOR HOMES, HOTELS & GUEST HOUSES, CARAVANS, BOATS, ETC. • MICROCHIP technology, no mechanical parts. • Maintenance free. • No wiring needed. • Runs off transistor battery, lasts for a year. • Money back guarantee.



£4.95 plus 75p p&p. or 2 for £8.50 plus £1.50 p&p.

## QUALITY SPEAKER SYSTEMS

Made to sell for over £300! Must be heard to be believed. Made in England by World famous British manufacturer. SPECIFICATIONS: Bi-Directional 5 speaker system. Drive units: 2x25mm soft dome tweeters, 2x13cm polymer cone mid range speakers, one 24cm bass unit. Impedance: 8ohms. Rated power 200W peak max. Sensitivity: 87 dB @ 1W. Freq. range: 45 to 20,000 Hz. Finish: Satin walnut veneer, with brown trim. Size: 35½" x 8½" x 15½". Weight: 27kgs.

£99.95 a stereo pair. Buyer collect only!




## MONO MIXER AMP


Ideal for Church halls & Club houses.

£45.00 + £2.00 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape tuner, organs, etc. Eight slider controls six for level and two for master bass and treble, four extra treble controls for mic. and aux. inputs. Size: 13½" x 6½" x 3½" app. Power output 50 watts R.M.S. (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

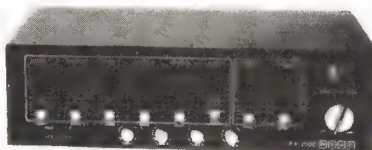

## VHF STEREO TUNER KIT

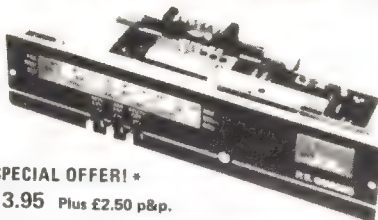

\* SPECIAL OFFER! \*

£13.95 Plus £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July '81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.


FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10½" x 2½" approx. Complete with diagram and instructions.

## HI-FI SPEAKER BARGAINS

### AUDAX 8" SPEAKER

High quality 40 watts RMS Bass/Mid. Ideal for either HiFi or Disco use this speaker features an aluminium voice coil and a heavy 70mm diameter magnet. Frequency res: 20Hz to 7KHz. Impedance: 8 ohms.

£5.95 + £2.20 p&p.

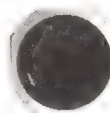

### AUDAX 40W FERRO-FLUID HI-FI TWEETER

Frequency response: 5kHz - 22kHz. Size: 60mm square. Impedance: 8 ohms.

£5.50 + 60p P&P.



### GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3½" sq.) for use in up to 40W systems;

£3.95 each plus £1.00 p&p, or £6.95 a pair plus £1.50 p&p.

## 125W HIGH POWER AMP MODULES

KIT BUILT

£10.50 £14.25

+ £1.15 p&p + £1.15 p&p

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use.

Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Stereo mains power supply w/transformer £10.50 + £2.00 p&p. Mono version, £7.50 + £2.00 p&p.





### SPECIFICATIONS:

Max. output power (RMS): 125W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohms. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100 watts: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205 x 90 and 190 x 36 mm.

## BSR RECORD DECKS

3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ceramic head. Ideally suited for home or disco use.

£17.50 plus £1.75 p&p.

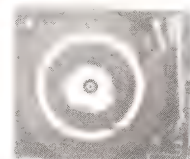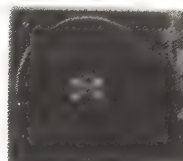

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge.

£12.95 plus £1.75 p&p.



Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx.

£14.95 + £1.75 p&p.

SPECIAL OFFER! Replacement stereo cassette tape heads £1.80 ea, add 50p p&p to order. Philips stereo magnetic cartridge. £3.95 + 60p p&p.

### PLINTH TO SUIT BSR RECORD PLAYER

DECK (with cover) Size: 16½" x 14½" x 2½". Cover size: 14½" x 13½" x 3½". Due to fragile nature of this item, buyer to collect only.

ONLY £8.95.

All mail to: 21C HIGH ST, ACTON W3 6NG. Callers Mon - Sat, 9.30 - 5.30. Half day Wednesday. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/11/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to up-

date their products without notice. All enquiries send S.A.E. All cheques & P.O.'s payable to RTVC Ltd.

CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.

Mail or 'phone orders by ACCESS. Tel: 01-992 8430.





# LETTERS to the EDITOR

Do you have an opinion to air? Do you know the answer to something which puzzles, or a tip that might help, fellow enthusiasts? Have you something to add to a feature or review?

Your letters are invaluable in helping us to develop the magazine for you

Write to Letters to the Editor, **Radio & Electronics World**, Sovereign House, Brentwood, Essex CM14 4SE.

## Class

ne magazine. Can we have some DIY  
als? HG V/UHF etc.

**Patchitt, Immingham**

tor's note: The February issue gave  
ails for extending the use of Bever-  
e aerials. We include a constructional  
ject for the 2 metre Tiger in this issue  
d a feature on a J-stick will appear in  
e near future. More later.

## was amazed'

Recently I saw *R & EW* magazine in WH  
miths. Quickly going through the  
ges, I found many items of interest and  
urchased it. At home and reading *Part*  
of the *Amateurs Handbook*, I was  
mazed at the information given.

For four years I have had an SRX 30  
ceiver (shortwave), but just trusted to  
ck what I might receive. Now, from *Part*  
of your *Handbook*, I know what to do  
d where to listen. I am an SWL and now  
el so much more interested.

Is it possible still, to purchase *Parts 1 &*  
of the *Amateurs Handbook*?

I will certainly buy *R & EW* magazine  
ach month in future.

**Plaice, Swansea**

Editor's note: The December 1983, and  
January and February 1984, issues of *R &*  
*W* which contain the *Amateurs Hand-*  
*book* supplements, are available from us  
at £1 each.

## Amplitude modulation transmissions

Arthur Gee, in his column in your  
February edition, says 'and why not AM,  
ou may ask?' in his attack on that  
mode's use on 80 metres. I most certainly  
o ask.

Dismissing the real issue in the single

Please note that we are no  
longer agents for VHF  
Magazine and enquiries  
relating to this publication  
should be directed to:-

VHF Magazine  
UKW — Berichte  
Jahnstrasse 14  
D-8523, Baiersdorf  
West Germany

throw-away word 'overmodulated', not  
referred to again, he criticises amplitude  
modulation for being old, associating  
QRM to the mode itself rather than the  
way it is applied.

As a modulation system AM is indeed  
old, highly successful and undoubtedly  
the most widely used form of modulation  
world-wide below about 50MHz. It is not  
precluded either by licence regulations  
or the UK HF band plans. A correctly set  
up AM transmission, whose spectrum  
(given a well designed modulator) can  
closely approach its theoretical mini-  
mum, is a much more comfortable  
neighbour to have in the next street than  
an SSB station (whose spreading is  
always well beyond the theoretical  
minimum).

Technical arguments aside, the most  
offensive aspect of the attack is the  
almost direct statement that amateurs  
have no right to use AM on 80 metres or  
any other crowded bands. This is a truly  
appalling thing for an amateur of G2UK's  
experience to say.

To refuse a legitimately licensed  
amateur this right, is virtually to forbid  
the newcomer to amateur radio to come

on the air using equipment he has built  
himself. The sophisticated equipment  
needed to compete in the rat-race, which  
this hobby has become, is well beyond  
the capability of most newcomers (and  
many old-timers) to construct and prob-  
ably also to afford.

Most of us started with AM equipment  
and I, for one, benefitted far more from  
that experience than from buying black  
boxes and learning jargon. This is what  
amateur radio is for (according to the  
licence, anyway,) and I welcome the  
news that someone has the originality to  
use it in this way. What on earth are  
things coming to?

If Arthur Gee dislikes things that are  
old, to such an extent, he should perhaps  
be aware that the term Kc/s became  
obsolete nearly 20 years ago.

**A J Henk, Epsom**

I am sorry Mr Henk found my comments  
on amplitude modulation 'offensive'.  
They were certainly not meant to be and  
if he found them so, my apologies to him.  
Apart from that, I agree with the sense of  
his letter, if not the detail. My point was  
that there is a 'time and place' for  
everything, and Sunday morning is not  
the time for amplitude modulation trans-  
missions on the 80 metre band. Any  
beginner trying out his home-built AM  
transmitter then and there, is likely to  
quickly give up amateur radio very  
disillusioned!

He is, of course, quite right about  
'Kc/s'. However, he cannot deny that the  
term has become part of amateur radio's  
jargon and is likely to remain so for a long  
time yet.

I love old things — in the right place. I  
even run a steam launch!

**Arthur C Gee G2UK**

**Do you make sure you get your copy of  
*Radio & Electronics World* each month by having a  
regular order at your newsagent?**

**Or are you a subscriber?**

**Help spread the word — make sure your fellow  
amateur radio enthusiasts have seen  
*Radio & Electronics World* — show them your copy.**



# ATV on the Air

**Presented by Andy Emmerson, G8PTH**

I heard a story recently which is possibly apocryphal, but it went along the lines that there was a guy at the Radio Regulatory Department whose job was to log and study anomalous propagation conditions ( 'lifts' to you and me). The bottom line was that in the last year there had been more openings than in all the previous years that they had been recording, which in fact was not very long. I have not bothered to check the accuracy of this little tale, but I can certainly say we have been well blessed in 1983. In fact, I knowingly *missed* more openings last year than I have ever worked in the past.

*Returning to the theme of putting slides on video here is a neat gadget from Canon. If you have a lens which will focus down to 1.7cm (0.7in) this DP-10 adaptor will enable you to film 35mm slides. This adaptor will work with the lenses of several cameras (I use one with a JVC G-71 camera) but the somewhat similar adaptor made by Olympus will not*

Why this should be I am not sure. It may be that we are keeping better watch for unusual conditions, or possibly we have more sensitive receivers these days and see more of what's going on. Anyway, I don't think anyone is complaining – not on the ATV front. There are usually a few muffled complaints from 70cm repeater users about strange buzzing on their audio, but fortunately these people tend to stay on their repeaters and dismiss it as atmospherics (sorry folks, only joking!).

What are the signs for a useful lift? Probably not found by monitoring the calling channel, 144.750MHz. This is said

for two reasons, firstly, because of always waiting for the other guy to CQ, and secondly, because the lift does not favour two metres.

An example in point occurred just before Christmas, on December 29th. A local amateur telephoned and asked me if I could identify the 'distorted' picture on 70cm.


Well, it was F3LP in Le Havre, sending positive modulation (the normal French broadcast standard). But there was French talkback audible on two metres.

## UHF openings

Even more frustrating was when Timms G8VBC later on saw F3LP on 2m with P5 – perfect quality – pictures, up near Derby. But there was no way he could raise F3LP on two metres, and for a number of reasons he was unable to contact F3LP. Rod is now threatening to compile a list of French stations and their telephone numbers, so as not to miss any more two-ways in future!

On the same evening, I heard my first ever QSO on 934MHz, so it is clear that

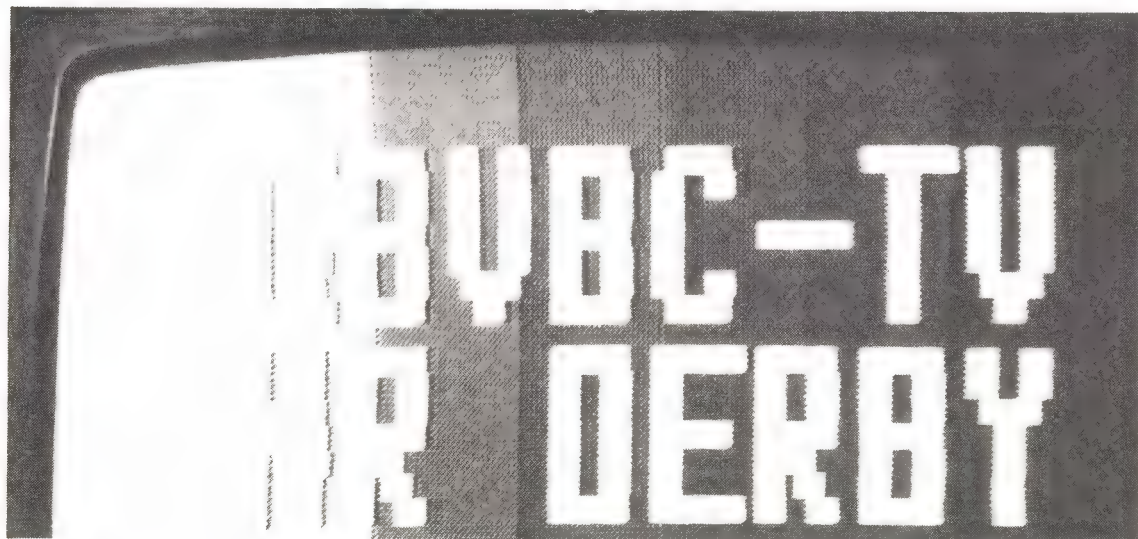*This is the test signal radiated by Rod G8VBC, from Woodville, south of Derby. Rod is very active on 24cm as well as 70cm*





## ATV ON THE AIR

ditions favoured the UHF's that thing and not VHF. I think I have marked before about a 70cm TV QSO a Dutch station; grade four pictures not a peep on two metres. We had to port to writing with felt pens on the k of test cards to pass over names and ports!

he safest means of catching UHF nings is, therefore, to monitor UHF. If have a scanning audio receiver it uld be worth putting a distant beacon uency into the memory bank. I tend monitor broadcast TV; if there is ceable patterning on a local or dium distance transmitter I know gs must be lively on 70cm. I live at rthampton and the Channel 4 trans- sions from Sandy Heath are regularly cked out by Antenne 2 from Lille en conditions are good. Another ication is multipath distortion and/or ep fading on a normally good but tant UHF transmitter, also 'freeze mes' on live TV broadcasts. What is ppening here is that the microwave dio-to-transmitter links (STLs) are pping out - e.g. grazing the ground e to bending - and a framstore makes od the instantaneous loss of picture. od fun for us but not for the oprofessionals...

### Video tapes

This column is called ATV on the Air, t I think that many ATVers are also

interested in video as well. So I have no apology to make if I include a bit of video technology now and again. One of the essentials of video is video tape and I was thinking to myself the other day how the price of this stuff has dropped. Remember when some shops charged £12 for a three hour tape? It wasn't so long ago, and in those days there were a lot more 'pirate' brands of blank tape too. Most were pretty poor, some really abominable, and a few were quite good. At least one of the good ones has now gone legitimate and obtained a licence from JVC. With the price of brandname tapes down to £6 for a three hour tape there is no excuse for buying cheap horrors now.

From time to time, though, there are shortages of blank tape and wholesalers are then forced to import tapes originally destined for the USA and Japanese home market. VHS tapes for 525-line countries are prefixed T instead of E (eg T-120) and play on our machines for almost a third longer. This is because our TV field rate is 50Hz rather than their 60Hz, and the tape moves past the record/playback heads at a more leisurely pace in European machines. So a T-120 plays for around 2 hours 40 minutes. These tapes are quite all right to use despite some silly scare stories you might have heard, though the picture quality may be marginally worse. One tends to find that HG or premium grade

T-series tapes are equivalent to our ordinary grade. If you look at some of the prerecorded tapes on sale or rental at your local shop you will discover that some have been put onto T-127 blanks, so they can't be that bad.

You often get more tape than you pay for, which is useful if a TV programme overruns or starts late (BBC-2!). Experience shows that Scotch tapes give you an extra minute, while JVC and Thorn can have up to 5 minutes to spare. The RCA VK-250 tapes are the most generous, offering an extra 10 minutes.

### Survey of video tape users

Not everybody uses the full length of their tape anyway; a survey commissioned by Scotch showed that 55% of users did not use all the time on a tape. A large number wasted 15 or 30 minutes of recording time per cassette. This is probably true; I know I do it myself; usually you can't help it - if a programme lasts 100 minutes you have little option but to use a two hour tape.

The same survey, which was directed at VHS users, purchased only the E-180 length but just 20% bought the E-120 size (film pirates?) and the remaining 15% purchased selectively according to their requirements. I must say that I tend to get only E-180s; they offer better scope for re-recording and cost little more than the E-120 size, often less in fact when they are on special offer.

# CORRECTIONS AND MODS

Whilst every effort is made to minimise errors in diagrams we will correct these as they come to our knowledge and we also appreciate the co-operation of our readers in notifying these.

We occasionally receive suggested modifications from readers who have constructed projects from **Radio & Electronics World** and we will publish those that would interest other readers.

For example, it may be possible to extend the use of a particular item by minor circuit changes or re-arrangement only. If this can be done for minimal cost and the idea has been proved in practice, others may benefit from the information. Write to Corrections and Mods, **Radio & Electronics World**, Sovereign House, Brentwood, Essex, CM14 4SE.

### Oscar-10 (March 1984 issue)

We regret that the computer printout (Figure 5) on the right was omitted from the article.

### 'Direct video interface' (Nov '82) and 'Direct RGB interface' (June '83) projects

We are advised by Mr Warne that the 80VA transformers used on these projects should be monitored for abnormally high working temperatures and replaced by a higher rated (120 VA) transformer if necessary.

Orbital elements for OSCAR 10  
Reference ID= NET 11 December 1983

U.T.C. MM:SS	AZ deg	EL deg	DOPPLER Hz	RANGE Km	HEIGHT Km	LAT deg	LONG deg	PHASE deg
0638:00	148	9	-1864	17258	12276	-13	339	22
0708:00	147	15	-1147	21585	17271	-4	329	33
0738:00	141	28	-1824	25294	21583	8	326	44
0808:00	138	25	-668	28586	25219	4	325	55
0838:00	137	28	-716	31154	28232	7	325	66
0908:00	137	32	-573	33276	38688	18	327	77
0938:00	137	35	-441	34989	32684	12	327	88
1008:00	141	37	-316	36888	34836	14	331	99
1038:00	143	42	-82	37114	35587	18	337	121
1108:00	146	44	32	36997	35567	19	348	132
1138:00	149	46	145	36459	35181	21	342	142
1208:00	153	48	261	35474	34342	22	345	153
1238:00	156	49	388	34888	33839	23	347	164
1308:00	159	49	585	32221	31258	24	348	175
1338:00	161	50	636	29866	28948	25	349	186
1408:00	162	50	777	26991	24891	26	349	197
1438:00	161	50	923	23573	22638	26	346	208
1508:00	156	49	1863	19639	18585	25	341	219
1538:00	148	46	1134	15443	13687	22	331	230
1608:00	136	37	871	12221	8378	13	318	241



EXT ISSUE • NEXT ISSUE • NEXT ISSUE • NEXT

**NEW IMPROVED**

# **Radio & Electronics**

The communications, electronics & computers magazine

## **World**

### **VHF/UHF FREQUENCY METER**

Stephen Ibbs describes the construction of a handy little digital frequency meter that covers a huge range and is very sensitive

### **SX-200N RELATIVE S-METER**

This article describes the construction of a relative signal strength indicator and shows how it can be fitted to the front panel of the SX-200N scanning receiver

### **UPDATE ON THE SPECTRUM ANALYSER**

Our spectrum analyser article (Nov/Dec 83) was very popular. Now we show how alternative components can be used in its construction

### **LOGIC PROBE SIGNAL GENERATOR**

One hours' work-and you have a probe with outputs ranging from 500kHz down to 30,518Hz

### **METEOR-SCATTER PROPAGATION**

A beginners' guide to this increasingly popular mode of operation

### **HAMEG MH203-4 D/T OSCILLOSCOPE**

After an extensive evaluation, this versatile dual trace oscilloscope is comprehensively reviewed by James Dick

**PLUS** all the usual features!

New Products • News • Reception Reports...


**DON'T MISS** the May issue – on sale **13th April**

To be sure of your copy of *Radio & Electronics world*, complete the newsagent order form in this issue or take out a subscription

EXT ISSUE • NEXT ISSUE • NEXT ISSUE • NEXT



## DOT MATRIX PRINTERS

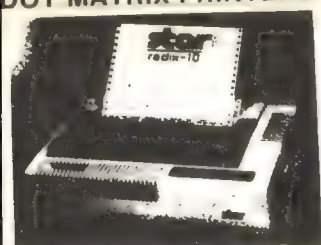

PRINTERS HAVE CENTRONIC PARALLEL INTERFACE UNLESS OTHERWISE STATED. ALL PRINTERS HAVE HI-RES. DOT MATRIX GRAPHIC MODE. PLEASE SEND SAE FOR DETAILS.

150 CPS 10" wide fric & pin feed	£344 - VAT	£395
180 CPS 15" wide fric & tract feed	£431 - VAT	£495
180 CPS 10" wide fric & tract feed	£261 - VAT	£299
100 CPS 10" wide tractor feed	£234 - VAT	£269

200 CPS Letter quality printer	£29 - VAT	£33
Interface for FX and RX printers	£60 - VAT	£69
RS232 interface with 2K buffer, xon/xoff	£7 - VAT	£7
Cartridge for RX80 FX80 & MX80	£12 - VAT	£13
Cartridge for FX100 & MX100		

10x120 CPS 10" wide fric & tract feed	£200 - VAT	£229
15x120 CPS 15" wide fric & tract feed	£295 - VAT	£339
10x160 CPS 10" wide fric & tract feed	£327 - VAT	£375
15x160 CPS 15" wide fric & tract feed	£414 - VAT	£475

10x200 CPS NLO 18K Buffer Par & interface downloadable characters	£431 - VAT	£495
table value at	£518 - VAT	£595

15x15" wide version of Radix-10		
15x50 CPS 10" wide tractor feed	£156 - VAT	£179
15x50 CPS 10" wide tractor feed -er & par	£196 - VAT	£225
15x50 CPS 10" wide tractor feed -er & par	£174 - VAT	£199
15x50 CPS 10" wide tractor feed	£187 - VAT	£215
15x50 CPS 10" wide tractor feed	£234 - VAT	£269
15x50 CPS 10" wide tractor feed	£174 - VAT	£199

180 CPS 10" wide friction & tract feed	£187 - VAT	£215
180 CPS 10" wide friction & tract feed	£6 - VAT	£8

180 CPS 10" wide friction & tract feed	£200 - VAT	£229
--	------------	------

180 CPS 10" wide friction & tract feed	£283 - VAT	£325
180 CPS 10" wide friction & tract feed	£347 - VAT	£399

180 CPS 10" wide friction & tract feed	£347 - VAT	£399
180 CPS 10" wide friction & tract feed	£181 - VAT	£215
180 CPS 10" wide friction & tract feed	£181 - VAT	£215

180 CPS 10" wide friction & tract feed	£347 - VAT	£399
180 CPS 10" wide friction & tract feed	£181 - VAT	£215
180 CPS 10" wide friction & tract feed	£181 - VAT	£215

180 CPS 10" wide friction & tract feed	£347 - VAT	£399
180 CPS 10" wide friction & tract feed	£181 - VAT	£215
180 CPS 10" wide friction & tract feed	£181 - VAT	£215

180 CPS 10" wide friction & tract feed	£347 - VAT	£399
180 CPS 10" wide friction & tract feed	£181 - VAT	£215
180 CPS 10" wide friction & tract feed	£181 - VAT	£215

## BBC MICROCOMPUTER SYSTEM

WE ARE AN OFFICIAL BBC COMPUTER DISTRIBUTOR  
DEALER ENQUIRIES ARE WELCOMED

Acorn Electron £199 INC VAT

WE SUPPLY FREE 30 HOUR BASIC BOOK AND A DUST COVER WITH EACH COMPUTER

This is the best microcomputer currently on the market. 32K RAM, 32K ROM, 8 modes of operation, full colour, full-size keyboard, internal expansions such as disc interface, speech synthesizer, Econet interface. In short it is a personal computer capable of expanding into a small business system.

BBC Microcomputer Model B	£348 - VAT	£399
BBC Mod B - disk interface	£409 - VAT	£469
BBC Mod B - Econet interface	£389 - VAT	£447
BBC Mod B - disk and Econet interfaces	£450 - VAT	£517
BBC 100K disk drive	£230 - VAT	£264
BBC 200K disk drive	£699 - VAT	£803

BBC dual 800K disk drive	£696 - VAT	£799
Torch 280 disk pack including Z80 2nd processor, 64K RAM and CPN operating system - Free Perfect Software	£196 - VAT	£225
BBC Teletext receiver (Aug)	£26 - VAT	£29
BBC cassette recorder and lead	£84 - VAT	£96
Disk interface kit (three fittings)	£70 - VAT	£80
Mod A to Mod B upgrade kit	£20 - VAT	£23
Filing charge for A to B upgrade kit	£30 - VAT	£34
16K memory upgrade kit	£11 - VAT	£12
Games paddles	£89 - VAT	£102
12 Monochrome monitor incl cable	£199 - VAT	£222
14 Colour monitor incl cable	£10 - VAT	£10
User guide	£60 - VAT	£69
Econet interface (three fittings)	£47 - VAT	£54
Speech interface (three fittings)	£30 - VAT	£34
BBC disk manual - formatting disk	£10 - VAT	£11
Parallel printer cable	£15 - VAT	£17
BBC word processor (view)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17
BBC Lsp language cassette	£15 - VAT	£17

BBC word processor (view)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17
BBC Lsp language cassette	£15 - VAT	£17

BBC word processor (view)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17
BBC Lsp language cassette	£15 - VAT	£17

BBC word processor (view)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17
BBC Lsp language cassette	£15 - VAT	£17

BBC word processor (view)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17</



# A GREAT MAGAZINE FOR COMMUNICATIONS, ELECTRONICS & COMPUTERS



Packed with more editorial features than any other magazine plus more pages of readers small ads

## ALSO . . .

. . . Product reviews . . .  
Communications & electronics news .  
Reception reports — shortwave, DX, ATV . . . Construction projects — what to build for your rig, your computer & your enjoyment . . . New technology . . . Educational articles . . . Coming events . . . Readers letters . . . Technical & practical questions answered . . .  
With special supplements in the December, January & February issue — The Radio & Electronics World Amateurs Handbook — A comprehensive collection of data for everyone using the airwaves.

## SUBSCRIBER BENEFITS

Take out a POST FREE (UK) S while offer lasts

- Delivery to your door publication date each month
- Inflation proof — price guaranteed for 12 months

On sale NOW at your newsagent and at equipment dealer

## RADIO & ELECTRONICS WORLD SUBSCRIPTION ORDER FORM

To: Subscription Department • Radio & Electronics World • 513 London Road • Thornton Heath • Surrey • CR4 6AR. Tel: 01-684 3157

NAME .....

ADDRESS .....

Postcode .....

PLEASE SUPPLY: (tick box) for 12 issues, all rates include P & P

Inland £10.20 ..... ☐ World-Surface £11.05 ..... ☐ Europe-Air £16.90 ..... ☐ World-Air £25.00 ..... ☐

PAYMENT ENCLOSED:

£ —

Cheques should be made payable to Radio & Electronics World. Overseas payment by International Money Order, or credit card.

CREDIT CARD PAYMENT



Signature .....

RE0484



# — CLUB NEWS —

## G celebrates Silver

1984, the British Amateur Radio Group (BARG) celebrates its Silver Anniversary. The Group has come a long way since those days in 1948 when a few pioneers got together to exchange ideas about what was then the new technique of amateur RTTY. Today, it caters for most forms of data transmission, ranging from RTTY, AMTOR, FAX, weather forecasting, satellite and telemetry, to the more advanced techniques of digital repeaters, packet radio, computer-to-computer communication, and so on. The BARG Newsletter is published quarterly, and consists of around 60 pages of technical, constructional and theoretical features, together with news and items of general interest. The Newsletter also carries a schedule of the RTTY News Bulletin service, which has recently been expanded. The bulletins are broadcast from stations all over the UK on Sundays on 10m, 2m and 20m. Test transmissions are also radiated regularly, to allow amateurs to check their receiving equipment. Bulletins are transmitted in RTTY at present, but AMTOR and ASCII will be added in the near future.

Another service offered by BARG is the sale of publications and specialist RTTY components. One of the most popular books available is 'RTTY The Easy Way' which describes the equipment required to operate RTTY with full details of terminal units, tone generators, and ancillary equipment, and has been responsible for many amateurs starting in this mode. The book is available from Mr Ian Brothwell, G4EAN, 56 Arnot Hill Road, Arnold, Nottingham, NG5 8LQ, at £1.15 including packing and UK postage.

Current membership is around 1300, and is expected to grow rapidly in the next year as interest in data transmission increases, particularly in the microcomputer field. Membership costs £5 per year, in return for which the member receives the Newsletters, and can take

advantage of discounted prices of publications and components. In addition, several trade suppliers offer discounts to BARG members. A SAE for membership details to: *John Beedie, G6MOK, 161 Tudor Road, Hayes, Middlesex, UB3 2QG. Tel: 01-561 0010*

## Chelmsford Amateur Radio Society

Future meetings planned are—March: Steve Oakman of Marconi Instruments Ltd. April: 'Microcomputers as applied to Amateur Radio' by Arthur G3KPJ. May: 'RF Power Transistors' by Dick G3WHR. June: Constructors Competition. Remember this year there is an extra prize for the first time winner. Details later.

The rally season is fast approaching and several members have enquired as to the possibility of running a coach/minibus to various events. We could run a trip to the RSGB National Amateur Radio Exhibition at the NEC, Birmingham, on 28th or 29th April or the National VHF Convention at Sandown Park Racecourse on 24th March if we have your support. I am starting a list of those interested, so please tell any of the Committee if you would like to go.

The long warm summer days seem a long way off but now is the time the Society must plan for our NFD entries. In addition to our customary HF activity on the 2-3rd June we would like to participate in the VHF activity on the 7-8th July, to give the class B licensees a chance to organise their own fun weekend. Two Committee members have volunteered to coordinate these events:—Dick Brooks G3WHR for HF NFD, and John Donnithorne G8MKX for VHF NFD. Names as soon as possible to these members for the planning groups to be formed.

## Biggin Hill Amateur Radio Club

The Club was founded at the beginning of 1982—one of the results of the Morse classes held in the winter of

1981/82 by Roger Jones (G3YMK) and Jim Burr (G3CTI). There are now over fifty members and we usually meet on the third Tuesday of each month for lectures or demonstrations of interest to licensed amateurs, SWLs, and all those concerned with the technicalities of radio and television. We also arrange sales of surplus equipment, which are always well attended.

To join, let me have a cheque for £5 payable to the BHARC with your name, address, phone number and callsign.

On March 20th we are planning to bring in some test equipment for you to check the performance of your rigs. For April 17th we've invited a Kent dealer to demonstrate his wares, and on May 15th we're planning a talk on ORP operation. Another junk sale is in the diary for June 19th.

The dates for the rest of the year are: July 17th, August 21st, September 18th, October 16th, November 20th and December 18th. Probable subjects include a construction competition, antennas, a live demonstration of RTTY, a DF hunt, and a visit from the leadership of the RSGB.

*Ian Mitchell, Greenway Cottage, Tatsfield, Westerham, TN16 2BT. Tel: 376*

## British Amateur Television Club

The BATC has installed a news 'Hotline' service controlled by a telephone 'answerphone' machine. The programme is updated at least every week or as often as necessary.

Up to the minute news and information will be included as well as essential details about the BATC.

The Hotline is located in Leicester so that it is as close as possible to everyone. The Hotline is open 24-hours a day. Tel: 0533 600108.

The Club is negotiating the acquisition of the use of a number of pages on the PRESTEL data service. As with the Hotline this will carry the very latest news concerned with amateur TV as well as details on the Club itself.

Further details on these services will be included in the next issue of CQ-TV magazine.

## The British Amateur Electronics Club

The BAEC started in Penarth, South Glam, in 1966, is the only national amateur electronics club in the UK. There are now many members from beginners to experts in all age groups all over the country, and also overseas.

The BAEC newsletter is the key to the club's success and is sent to members quarterly. It contains letters and articles covering all aspects of electronics, and the sections Help Wanted, Sales, Exchanges and Requirements are popular. A Members List is circulated so that members can contact other enthusiasts.

The Club has a special responsibility to assist all who are learning about electronics. Help is freely given, and important aids to practical work are available.

The library contains many technical books and electronics magazines, all available to members on loan. The selection includes British and American publications, some of which are difficult to obtain elsewhere. Except for postage, the library service is free for UK members, but special arrangements have to be made for members overseas.

Special concessions have been arranged with well-known suppliers of electronic components and equipment, and free BAEC labels help to obtain good service from these companies.

The BAEC Amateur Electronics Exhibition is held in Penarth annually, and members contribute their electronic projects and games for it.

The Membership fee for UK and Eire members is £5.50 sterling per year, and overseas fees are £7.00 sterling per year for Newsletters to be sent by surface mail, and £8.50 sterling for Newsletters to be sent by airmail outside Europe (£7.00 for Europe). All payments from overseas, including Eire, should be made in sterling. The BAEC year starts on January 1st, and all new members receive all the Newsletters for the year,



regardless of when they join.  
Mr J G Margetts, Hon Sec,  
BAEC, 113 South Road, Hor-  
dean, Hants PO8 0ER.

## Lough Erne Amateur Radio Club

Our club is holding its third Mobile Rally on Sunday 15th April, 1984, at the Killyhevlin Hotel, Enniskillen, starting at noon. The hotel is located on the shores of Lough Erne, hence the name of the club. We are having all the usual trade stands plus a large 'Bring and Buy', all items not sold will be auctioned at the end of the day (with owner's permission of course).

The Hotel is offering an attractive Mini Weekend from £30 per person. We welcome all those interested in radio communications and electronics to come along.

Admission will be £1.00 and full hotel facilities will be available. All the usual attractions - Boat Trips, Pony Rides for the kids, Jaunting Car Trips etc.

## Glenrothes & District Amateur Radio Club

Work on the alterations taking place in the clubrooms is slow due to lack of commitment by club members. Within the clubrooms the main tasks are joiner, electrical and paintwork, along with a general clean out and reorganisation of the facilities. Until all internal work is completed, it is unlikely that work will begin to re-instate the antenna installations on the roof of the clubrooms. If you can spare some time, notify either Jim GM4TNP or Drew GM3YOR, who are co-ordinating the work.

It is hoped to resume work on the 70cm Repeater GB3FE club project as soon as the internal work on the alterations to the clubrooms is completed. If you would like to assist in the work required to complete this project, notify Jim GM4TNP.

An article about the club was carried in both the Dundee Courier & Advertiser and the Glenrothes Gazette in January. Copies of both articles are available to members.

Les Hamilton, GM3ITN, has taken over as QSL manager for all GM series call signs. His address for sending self-addressed, stamped envelopes for the return of cards is

Halls Land, Hardgate,  
Clydebank, Glasgow G81  
6NR.

Dave, VP8AQA, brother of club chairman Jim GM4TNP, who is in Antarctica with the British Antarctic Survey Team, has ceased amateur radio operations prior to his return to Scotland.

Seven operators participated on the club's behalf in the 1984 Affiliated Societies Team Contest. Claimed scores were:

GM3YOR Drew, 1430 points, 143 contacts

GM3OLK Dave, 1290 points, 133 contacts

GM3ZSP Ken, 960 points, 96 contacts

GM4EJI Gavin, 880 points, 88 contacts

GM4SJJ Steve, 730 points, 73 contacts

GM3PFQ John, 550 points, 55 contacts

GM3YBQ Ken, 330 points, 33 contacts

The top five scores will be combined to give the club's score in the contest.

## ARTAC International

ARTAC (Amateur Radio Third Party Action Committee) International is a group of Australian Radio Amateurs who consider it time that a number of countries, especially Commonwealth countries, were encouraged to follow Australia's lead in allowing members of their Amateur Radio Service to use third-party operation, thereby removing a long standing, most unnecessary and highly 'political' strangle-hold on the Amateur Radio Service.

In some countries the third-party restrictions are so severe that it is illegal for members of the Amateur Radio Service who are operating within a legal radio network to relay messages, or even signal reports, to other amateur stations in the net who are having difficulties in receiving certain stations due to interference or poor conditions. It is therefore, illegal for stations under these rules to become involved in International 'DX' nets.

Authorities in many countries are so 'neurotic' about third-party, they insist that under no circumstances shall anyone's voice, except that of the licensed operator, be

# RSGB NATIONAL CONVENTION 1984 NEC, Birmingham PROVISIONAL PROGRAMME SATURDAY 28 APRIL

## ROOM 1

11am and 3.45pm

"An introduction to amateur radio" by the RSGB Education Committee.

2.15pm

Discussion with RAE tutors at which a representative of the C & GI will be present

## ROOM 2

11am-12 noon

A lecture by the RSGB EMC Committee

1pm-3pm

Raynet symposium by the RSGB Raynet Committee

3pm-4pm

"Patterns of hf propagation - or the shape of things to come" by Ray Flavell, G3LTP

## ROOM 3

1pm-2pm

"Introduction to the vhf bands" by the RSGB VHF Committee

2pm-3pm

"Getting the most from your vhf station" by the RSGB VHF Committee

3pm-4pm

"An introduction to microwaves" by Charlie Suckling, G3WDG

## HF CONVENTION (Pendigo Suite)

12 noon

"Operating as a dxpedition" by the RSGB HF Committee

1pm

"Linear amplifiers" by Peter Chadwick, G3RZP

2pm

Home-constructors forum. Talks by members of the G-QRP Club. Panel of experienced constructors and writers. Chaired by Rev George Dobbs, G3RJV

3.30pm

Presentation of hf awards and trophies

4pm

HF forum. Panel of members of the RSGB HF and HF Contests Committees, chaired by the Society's hf manager, John Allaway, G3FKM

## SUNDAY 29 APRIL

### ROOM 1

Two one-hour sessions commencing at 11.15am and 2.15pm for the beginner: "An introduction to amateur radio" by the RSGB Education Committee.

### ROOM 2

11am-12 noon

"Aspects of propagation studies as they affect the radio amateur" by Ray Cracknell, G2AHU

1pm-3pm

Raynet symposium by the RSGB Raynet Committee

3pm-4pm

A lecture by the RSGB EMC Committee

### ROOM 3

1pm-2pm

"Introduction to the vhf bands" by the RSGB VHF Committee

2pm-3pm

"Getting the most from your vhf station" by the RSGB VHF Committee

3pm-4pm

"An introduction to microwaves" by Charlie Suckling, G3WDG



## CLUB NEWS

ayed over the air. This action is so severe that licensee of the station expect to receive angement notification the authorities for hav- s microphone gain set a too high, thereby allow- unlicensed background s and voices to be mitted.

ese restrictions are necessary and insulting to Amateur Radio Service n is a responsible nisation. Members are ys ready and willing to de their skills and equip- free of charge for the fit of the community and, nationally, the Amateur o Service provides one of stabilizing factors for d peace, breaking down ical, racial and prejudi- barriers.

### BATH & DISTRICT AMATEUR RADIO CLUB

The Club will hold its AGM Wednesday, 18th April, at 7.30. The venue is The Englishcombe Inn, Englishcombe Lane, Bath.



For further details, please contact:-

Colin Ashley (PRO) on Frome 63939 or Mike Mason (Sec) on Bath 311046.  
**C D Ashley G4UMN (PRO)**

### MARCONI AMATEUR RADIO CLUB


The club will be participating in the 'D' Day Reunion 40th Anniversary in June and will operate three Stations for the first event on the

weekend of 3 - 4 June.

1. GBI MAR. operating from Southsea Common during the WWII Veteran Vehicle Display. VHF Station.
2. GB2 MAR. operating from Fort Widley HF Station.
3. F0???. operating from Normandy Beach-head with G6APD/G4RTT/G6IZN supported by F6FLB and local French amateurs. VHF station.
4. All these calls will count five points for Basic 'Mary Rose' award, the Basic requirement remaining the same. For those holding the award all count five points for 50/100 Endorsement Stickers. These stickers in silver or gold respectively, are in the form of a Tudor Rose.

The stations will be operating for the 28 day period, with the possible exception of the F0???. There will be special GSL's to commemorate the operation in tour modes, Army Navy & Airforce. A display of WWII communication equipment will be on show. Enquiries to:-  
**V G Scambell Cosham 373099**

# BURNS

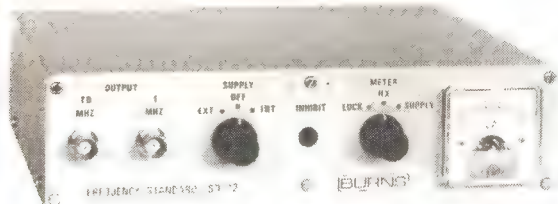

OUR NEW PORTABLE

### OFF-AIR FREQUENCY STANDARD SD-12 LOCKS TO A BBC TRANSMITTER CLOSELY CONTROLLED TO 200KHZ (DROITWICH, BURGHEAD, WESTERGLEN)

The BBC expect to change this Transmitter Frequency to 198 KHz. Conversion of SD-12 will be simple — necessary circuitry already built-in and replacement crystals supplied with original purchase. Output at 10MHz and 1MHz accuracy 0.1 Hz in 10 MHz

Suitable for calibration purposes (eg using internal battery) or continuous drive (with separate mains PSU) IE as a source of distribution within a laboratory-work shop.

Used by British Telecommunications and other authorities.

We still supply matching crystal calibrators CC-11 and Absorption wavemeters TC-101 as previously advertised.

Contact us at our new address:-

**BURNS ELECTRONICS**  
170a, Oval Rd, Croydon, Surrey CR0 6BN  
Telephone 01-680 1585

## HAVE YOU THOUGHT OF BECOMING AN AUTHOR?

We are always interested in receiving articles to be considered for publication and are particularly keen to hear from anyone who has something to say related to the amateur radio field. As mentioned before, projects for fellow readers to build are most welcome.

You don't need to be an expert writer. If you can get your ideas down on paper, preferably typed, with drawings that we can follow and photographs where relevant, we will sort out the style, grammar, spelling etc.

If you have an idea for an article, or have designed and built a project that you think others would be interested in, but still have doubts about becoming an author, why not write (giving brief details and your telephone number) or telephone Dennis Hayes... and of course you will be paid for your effort.



# FREE READERS SMALL ADS

## FOR SALE

- Complete 2 metre station. Ideal as a first rig or a portable station. Standard C146A, 2W handheld, 5 channels, 8 xstals, auto/manual toneburst, 1/4 wave and helical aerials, external miniature microphone, leather case, new nicads, base station unit and charger £90 ono for the complete station. G A Trickey (G4CDW), 11 Pheasant Way, Beeches Park, Cirencester, Glos GL7 1BJ. Tel: 0285 2036.
- Large office duplicator and postcard printer, complete with both red and black drums. Suit club £65. Tel: Horley 2210.
- Standard C8800 2mFM RX/TX rig, unmarked, with s/mount for mobile use, 10W output, LED signal meter, scan and memo for sale £200. Also FRG 7000 in very good condition, with handbook. Both can be seen working £200. Tel: Braintree, Essex 47631.
- 10GHz mixer diodes (1N4146) in original packing, 220pF NP0 ceramic chip capacitors, 5K sub-min pots, complete slow motion drive for Eddystone receiver, asstd RF power transistors, plus lots of other goodies. Contact G8URG, QTHR, or Tel: Canvey 682149 evenings, Phil Ridgeon.
- Barlow Wadley XCR30, XTAL controlled, general coverage communications receiver, as new £40 ono. Tandy TRS80 model 1, level 2, 16K, with monitor and cassette £150 ono. Tandy pocket TRS80 with cassette adaptor £50 ono. Mr M J Turner, 5 Robinson Rd, Hill Head, Fareham, Hants PO14 2DG. Tel: Stubbington 0329 664965.
- Oric 48K Micro, manuals, software etc. Wish to swap for oscilloscope, preferably dual beam but accuracy more important. Dave Churchward, 76 Medway, Crowborough, East Sussex TN6 2DW. Tel: Crowborough 63910.
- Clearout. Tons of new components - ICs, transistors, TV1 filters for TV's £2. Various general purpose loudspeakers, mains suppression filter £2. Various metal project boxes, large electrolytics, ferrite cores, assortment of valves, transformers. Telephone for details. Everything must go. No callers, please. Tel: 01 500 6022 or write, Phil Neville, 66 Oak Lodge Ave, Chigwell, Essex IG7 5HZ.
- Cavity wave meter to cover 2mts 70cms 23cm co-axial relay kit. Full instructions supplied. Twin and single paddle keys. For more information, write: P Sergeant, 6 Gurney Close, Costessey, Norwich. Tel: 0603 747782.
- 16 off MK4096P 4K Dynamic rams £7. 16 off 4116-2N 16K Dynamic rams £12. Thumbwheel decade switches with BCD outputs, one off 4-Bank £2.50. 8amp cut-out £1.50. Prices include postage. Mr Dixon, Kyrles Cross, Peterstow, Ross-on-Wye, Herefs. HR9 6LD.
- Belcom transceiver mobile 26.00MHz-29.99MHz multi-mode £188 no offers. Tel: 0734 883418 after 8pm.
- Belcom LS102L 10-11metres transceiver, multi-mode mobile £188. Tel: 0734 883418 after 8pm.
- Pye PF70 UHF Pocket-Fone, single channel with Ni-Cad, leather carrying case and crystals for RB6, unmodified 500mw output £40. TVI 27MHz RX filters £2. Tel: 0273 516801 (Newhaven).
- Yaesu 902DM, mint condition, original box, hardly used £600. Tel: 01 890 4666.
- CB Radio, Havard 420M, 40 channels FM, with power mike £38. Tel: 0734 883418 after 8pm.
- Spectrum beep £6, amplifier plus radio (MW+LW) plus better saving and loading. Spectrum Morse program. Tel: Kilbarchan 2288 David, or write JAVED, 2 Tandlehill Rd, Kilbarchan, Renfrewshire PA10 2DQ.
- Antique 2-way battery telephone, General Electric Co, Coventry. Brown bakelite hand pieces, with wooden box, bases and brass phone-hangers, also wiring instructions. Very old. Would consider exchange for UHF receiver covering marine bands, or ATU or WHY? Write with details for exchange only. All letters answered. Mr Marsden, 205 Moss Lane, Burscough, Ormskirk, Lancs L40 4AS.
- Shack clearout. Two metre, 70cm Air-band and test gear must go. Components and accessories, books and mags (1800 to present day). Very good prices. Phone for full lists. Steve Whitt. Tel: 0473 642635 (days), 0473 54405 (evenings).
- Creed 7B/RP and 6S6 tape recorder. Both perfect working order. Complete with full Creed maintenance manuals. Also details from Comput-

ing Today on using above as a computer printer. Offers please. Buyer collect or haggle on delivery. Tel: 0543 472054.

- Tandy DX302 general coverage receiver, 30 bands digital readout. As new condition. Original packing. Surplus to requirements. First sensible offer secures. Also have 8 element 2 metre Jaybeam and Araki 2 metre 3/4wave GP Co linear. Offers for any or all of above. SAE or phone for further details. J Peerless (G3JPJ), 157 Fairmead Crescent, Edgware, Middlesex. Tel: 01 958 6887.
- Stalker ST-9FDX-10W AM/FM 20W-USB ILSB-320FCC channels plus all 27MHz UK FM channels. Owner now licensed amateur. Boxed and in excellent condition £80. Also contra CP-163X HF Linear amplifier plus preamp input 0.5W/5W/10W. Output 20/50/100W. AM/FM, 40/100/200W SSB power supply 13 8Vdc. Suitable for mobile use. Frequency range 3-30MHz £80. Tel: 0789 295915.
- Pye 'International', 11 waveband. High performance receiver. 11m to 2000m. Perfect £30. Vidor battery eliminator 90V HT, 1.5V LT for valve portables £10. Pye Vanguard AM 25/B High band radio-telephone, mint £25. Admiralty wavemeter G56 (15KHz to 24MHz) with new calibration curves £20. VCR 131 Electrostatic CRT (12in version of VCR 97) £10. Collection of 1922-1939 wireless magazines. Send for list. K W Clark (G3WIF), 16 Goldney Rd, Clifton, Bristol. Tel: 0272 293738.
- Brazenose stereo h/phone/speaker or both, junction box £2.50. Three pairs plastic tweezers 50p. RAE manual by Benbow, 10th edition, 1982/85 syllabus £2. Electronics Digest, volumes 2 and 4, mint £1.50. Service manual for Phillips B & W video LDL1000/LDL1002 £3.50. Reel tape, spare spool for LDL1000/2 £1.50. P W Hall, 38 Old Hall Rd, Tingley, Nr Wakefield, West Yorks WF3 1QE. Tel: 0532 524108.
- Once used reel to reel computer tapes, 7 1/2ins. Will record over easily. About 30 in all. Most boxed. Good condition. Will sell separately. Offers to Kevin Gray, West Lodge, Carruth Estate, Bridge of Weir, Renfrewshire PA11 3SG. Tel: Kilmaccolm 050587 2169.
- York CB transceiver JCB863 complete with aerial PA, speaker instruction manual etc. Would swap for any home computer, any condition considered, with or without cash adjustment. Tel: Bourne 0778 424029.
- ZX81 with 16K RAM, full size keyboard, progs, books etc £45 ono. Yashica TL electro SLR camera with many extras, four lenses £150 ono. Full colour darkroom outfit, enlarger drums tanks etc £125 ono. SX200 Scanner £150 ono. Consider swap any of above for FT208 or any 70cm gear. Dave (GW6UGD). Tel: 0222 733885.
- Journals RSGB radio 'Com' good condition. 1978 and '79 to '83. 12 copies each. Offers please. Buyer collect. Tel: Southend 68254.
- Two Meter multi-palm II Transceiver, six channel. R0, R6, 14, 19, 20, 22, Ni-Cads and charger £50. Heathkit linear HA202 50W 12V £45. 10m linear, new, unused 140W SSB. 240V AC input £69. Maxcom 7E as new, in case, 4W including mag mount £45, as new. Tel: 0872 862575.
- 144MHz 2m linear amplifier, with integral PSU and coding £95. 2m 10-element Yagi £12. Tel: 0733 232769.
- Heathkit GR-78 receiver, R209 receiver, Windsor 30A oscilloscope, AVO signal generator type III 150KHz-220MHz, realistic PRO-20A 4-channel 68-88 144-174MHz pocket scanner, Antex precision de-soldering iron. Sensible offers. Tel: 06333 74227.
- Eddystone RX 840A. Very good order, very seldom used £60. Bargain. Mr A R Roxbee, 25 Toms Croft, Turners Hill, Hemel Hempstead, Herts HP2 4LL. Tel: 0442 66968.
- Swan Astro 200 digital broad band Transceiver. Complete ACPU manual 80-10 metres. Full scanning. Very good condition £250. PKW trap dipole 80-10 metres, complete, as new £20. Mrs D Haslam, 3 Meadow Crescent, Carlton, Blackpool. Tel: 0253 885234.
- CB TX/RX. Lafayette 1200FM. 120 channel. LSB USB FM AM PA switch. Instruction book, Circuit diagram. Good condition, in box £45. Buyer pays carriage. Tel: 051 355 9325.
- Two portable 'listening' cassette with headphones, talk-in button case, almost unused £24

- ono. Also soldering gun, Weller, with tips, Also 'unused' £16 ono. Mr Dave Evans, Summerhill Rd, Onchan, Isle of Man. Tel: 06 924 1111.
- New, unused DC lead for FT101 MK1 Tandy CB home base TRC 3000, 3 months new, boxed £55. Tandy 40ch portable, TRC 1 No offers. GM4DHJ QTHR. Tel: 041 889 90.
- Trio TR9130 multimode, PS30 20Amp PSU system base, very good condition £470 ono. Trio official service manual for TR9130 a SQY08 8-Elc Quagi £25 ono. Tel: 021 378 420 6pm.
- VHF 10-channel scanner crystalized repeaters and 145.800, 145.500 as in catalogue, cost £56, accept £30 ono. Also charger for above included. G4SZ1. Tel: V 7194 evenings.
- Trio 2300 including Ni-Cads and s purpose 5amp PSU and charger £145 ono. sell as separate items or consider part exc for FT 107 memory board. Write or phone Hazlewood, 16 Richmond Grove, Wollaston, bridge, West Mids DY8 4SF. Tel: 03843 (G4KZB).
- FT708R 70cm hand-held, in original box two Ni-Cads, NC9C charger £175. Pye F450L Base station on RB12 £25. 10metre FM Icon repeater shift and display modification G3XVL. Chris McCarthy. Tel: Chesham 0494 7.
- Three direct-drive record decks, su spares £5 lot. Micropeus floppy disk controller board £20. UK101 16K and extra ASC11 encoded keyboard £10. SEW VU m professional, 6in scales, brand new, ori packing, offers? 10Kg scrap electronic chass post paid. Microsecond chronometer, circa (massive case) £10, buyer collects. Hugh Br 363 Kennington Lane, Vauxhall, London SE11 Tel: 01 735 1862.
- Collector's item. Several early post war ra All cheap to clear. Space needed. P W H Gordon Rd, Chandlers Ford, Eastleigh, Hants, 1AN Tel: 04215 3920
- Teletype model 33 with stand, tape pu reader, dust cover, set manuals, £20. B collects. Chris Marshall Tel: Witney 4867
- Labgear aerial. AMP group C/D inc PSU (16 year old. Offers Tel: Dursley 0453 842238 (e ings)
- Murphy B40D communication receiver. Buyer collects. 16MM Filmosound projec excellent order £90. Would exchange for 2 m 100W linear MM with pre-amp. Tel: 0903 66329
- HB9CV 70cm antenna + clamp £4. MM 70 receive converter £15. Heathkit IG4505 sc calibrator and manual £10. TR10 MC50 desk m £15. Collect or could deliver North London are Van Walwyk, 11 Valette Court, 75 St James La London. N10 3RA
- Circa WWII private collection. All good con. TX/RX ZC1. TX.36 set with PSU RX BC34 Also CRT. Cossor 85K-15in CRT. 901GEC lifeb SOS-TX + auto keyer. Rees Mace retireme Limited space dictates disposal. Will accept £ the lot. Buyer collects. No splitting please. T 0543 490078
- Early television tubes, Mullard, Mazda A47, A CME 7 for £5. 12in CME1201 A31 Mazda, Gene Electric 10 1/2in TSD217, £2 each. Buyer collec Two old Garrard auto-record changers RC1 MK11. Offers. Tuning condensers, air spac mixed values spindles and preset, 500PF twin. Tel for £5. Edwards, 244 Ballards Lane, North Finchie London, N12 OEP Tel: 01-445 4321
- Sony VP-1000 low band U-matic player cor plete with handbook. New heads fitted recentl £250. Would exchange for 2mtr multi mode bas station TS700 or similar. Write Mr Bushnell, Grange Close, Fyfield, Andover, Hants. SP11 8DX Tel: Weyhill 3141
- Compucolor II computer. 8080 Processor, 16 BASIC and 32k memory, with integral 5.25ins dis and colour monitor. Plug-in 117 key keyboard Absolutely complete system. Looks like a attractive 13ins TV set. Lots of programs including amateur radio contest scoring/printing etc. With service and programming manual and many relevan books. £499 complete. Creed teleprinters, tape punches and readers, and spares. Mostly working Offers? Tel: Smallfield 3545.



# FREE READERS SMALL ADS

## FOR SALE

RAF Wop-Air 1944 wishes to consider your hobby and offers £300 of Trix OO gauge railway in best condition for beginner's type or transceiver and necessary instructional and assoc. equipment. Jack McMillan, Drumbrae Walk, Edinburgh. EH4 8DQ.

Like R4C/T4XC separates, AC4, M54, 6, 1.5, 0.5 filters, extra xtals, v.g.c. £550 ono. MFJ master memory keyer, 12 memories, auto, excellent contest keyer £65 ono. J Wayman (S), 190 Drove Road, Biggleswade, Beds. HP. Tel: Biggleswade 312609 (evenings)

Yaesu FT290, 2metre multimode rig with tuning case, nicads and battery charger. As new Microwave modules 30 watt linear amplifier will part exchange for solid state H.F. mobile or coverage receiver. Tel: Grimsby (0472)

ans fms isolation double wound. Ex ITT 240V in, 240V out - £10. 3kW ditto. £28. Can be S.E.8 only. Mr L Milton, Fairlight Cottage, Fairlight Rd, Fairlight, E/Sussex. TN35 4AG. Tel: 03392

Yaesu FRG 7700 receiver. FRA 7700 active antenna. Both boxed, hardly used, and in mint condition £230 ono. Or exch for RS232 Modem for £100 + cash. Phone Newport Pagnell 0908 01 (after 6 and weekends).

OW ATU for 160-10M. Unused £15. Electrolytics 100V, 25p. Ambit 25W linear £25 ono. Brand MM144/100LS 100W linear, unwanted gift £130. Westminster mid-band £15. Send SAE for list and back clearout. G8WXX QTHR. H M Field, 6 Wadbury Close, Winsford, Cheshire. CW7 1NA 06065 52834

Scope, Heath kit OS2 3in. Good working order ono. Tel: 06333 73048

Ultra small, high sensitivity, FM RX size 10 x 6 x 1cm. 0.9 Microvolts sensitivity. 100-120 MHz. Accurate tuning, professional monitor WBFM type. New Philips IC to give excellent performance. £54. G3PCN. Tel: 01-866-3300

Valves DA100. New, G.E.C. Boxed. Offers. 50W and 100W valve sets. 50W re-entry 25W speaker, new. Offers. 01-524-01

16K ZX81 DK Tronics keyboard, Qsave inverse code, over £70 software books and spares. Will sell swap for good SWR/PWR meter, WHY? Trio 130 hardly used. Will swap for VHF multi-mode sell. 10M FM 6W rig new £35. Log books £2 inc P. SAE with all queries. No sensible offers refused. Martyn Bolt, 112 Leeds Road, Mirfield, West Yorks. WF14 0JE Tel: 0924 495916

Motorola Design 5 IVE 68705 single chip micro-computer. Designer's kit. Contains nine special chips including 68705P3L micro-computer, A to D, timer, Ram etc. All data sheets, circuit diagrams and Motorola software. Unused competition prize but owner too busy to build kit. Cost £604. Asking £45 ono. Your only chance of your own powerful homebrew micro at such a low price. R Swale, 616 Reading Road, Winnersh, Berkshire. RG11 5HE Tel: (0734) 784035

11 meter linear amp. Ham intern. LA60 multimode, 100W, SSB £35. Mobile aerial 7 foot firestick with boot-mount £7.50. Mr Rolf, 282 Hyde End Rd, Spencers Wood. Tel: Reading 0734 883418 (after 6pm).

Eddystone 5 band midget communications receiver type S870A, 130KHz-24MHz perfect £38. Tel: 01-902 6437

Collaro Conquest 4-speed autochange unit. Collard 3-speed, 3 motor, tape deck. Mains XFR, C.R.T. for Solartron CD1014 oscilloscope. Various Cossor four inch D.B. CRT for 1045 etc. Marconi 600 OHM attenuator. Offers to C Cooper, 11 Radical Ride, Wokingham, Berks. Tel: 0734 734312

Drake R4B recently revalued, crystallised nine bands, all of 10M. T4X with top band Xtal. AC4 PSU rebuilt 1983. MS4 speaker, MN4 A.T.U. £295. 2m Trio TR7010, SSB/CW, with linked VFO700S giving coverage 144-145 MHz. R&EW pre-amp fitted £140. GM4IAO (ex GM8OVN). QTHR. Tel: (0466) 2673 evenings.

Icom IC-720A full gen. cov. TX/RX, used little, orig. packing, mint cond, (£949 new), £725 ono. Can deliver at half cost of petrol. Please write to S.

Langlois, GJ40DX, Merchant Navy College, Greenhithe, Kent DA9 9NY. All replies answered.

Goodman speakers, 15 OHM uncased stereo, bass AX10M 201 twelve inch twin cone, Midax, Trebax. All six speakers plus cross over units, XO5000 XO950, switch attenuator, wool packing, £25, will haggle. Voice operated transmit switch CBE-2003 Sirtel with mobile Electret boom mike. £30 or near offer. Buyer collects. Tel: Hertford 56164

Welson-Syntex Comp with FAL 500 watts 15in speakers, Bass, £300 ono or swap for H/F equipment, Yaesu FT101, FT902, FT707, FT7 or Cobra 148 GTL-DX, late version, with PLL MC145106 IC. Tel: Mr Thompson 01 575 1167 (after 12 noon)

MMT 432/144R transverter 2m input, 10W output on 70cm, 1.6 shift. Standard attenuator suits 10W 2m rigs plus 7dB attenuator to suit FT290R etc (£14.50 list). Lack of spare time forces sale, £140 ono. Also Packer WM7, 70cms wave meter with 70cm helical fitted, £15 ono or free with transverter. Both only six months old. Would exchange for anything interesting. Dino Bragoli, 12 Lynton Mead, Totteridge, London N20 8DJ Tel: 01-446 4932

Icom R70 receiver unused and boxed, £420. Tel: Richard (0223) 312624

AM SSB CB and 28MHz transceivers at keen prices. Also 2nd hand CB rigs and accessories. Contact Sean McAteer, 82 Woodlands, Gilford, Craigavon, Co. Armagh, BT63 6JP. Tel: 0762 831569

Icom IC-25E 144MHz FM 25Watts twin VFO, memory channels, orig. packing, handbook, mobile bracket etc. £210 ono. Also, 13.8V 5A/7A PSU £10. Or both for £215. Please write to Miss E Lawrence, G6TPD, 11 Mabel Road, Hextable, Swanley, Kent, BR8 7SH. Can deliver within 40 miles

Printer 101 Centronics matrix with CBM Pet interface £80. Modems 2200, Racal Milgo 1200 or 2400 B.P.S. B.T. approved £30ea or £50 pair. Keyboard enclosed alloy case. 76 Keys ideal for use with ZX81 or other micro/rtty uses £6. Tel: Ralph (G4PEY). Horsham (0403) 69835

VHF/UHF AM/FM 12 channel scanning receiver. Optiscan SBE. 12m 12V/240V covers 30-50, 68-88, 150-170, 450-470 MHz. SR9 VHF/FM, VFO tuning, 146-152 MHz plus 11 fixed channels. Ten marine bands fitted. £45 ono. I M Tasker. Tel: Grantham 0476 860421

Sir Douglas Hall offers modification or development details of 13 of his constructional designs appearing in volumes 27 onwards of Radio and Electronics Constructor for 25p and S.A.E. He will also reply free to requests for advice, not involving circuit modifications, about any of his designs published in that magazine, but please send S.A.E. Douglas Hall, Barnford, Ringmore, Kingsbridge, Devon

Elector teletext boards plus keypad. All full spec devices used. Cost £90. Bargain at £45. Also Pye teletext board similar to elector circuit, IC's alone would cost £45+. Bargain at £20. CCT board believed to be Prestel. No data. Hence £5. Mr Winwood (G4GPF), 132 Shakespear Crescent, Hallowes, Dronfield, Derbyshire S18 6ND Tel: 0246 410057

Sony ICF 2001 FM 76MHz 108MHz. AM 150kHz 29999kHz mains unit. Maker's packing. Offers or part exchange offers. Tel: Bradford 676556 (after 6pm)

Yaesu FT221R fitted with Mutek front end and complete with h/book and mike £275. Also for family of the late G8WXX MM144/100 (no preamp), MM144/432 transverter (unused). Offers please to G3CBW QTHR. Tel: 0228 39291

Yaesu FRV7700 Model F converter. Little used. Under guarantee £55 ono. Thompson Leitholm, Tunstead Rd, Hoveton, Norwich. Tel: Wroxham 2109

Nascom 2, 48K ram, NAS-SYS3 Zeap, NAS-DIS/Dee Bug graphics, parallel printer, cable, £250. Tel: Ian 08725 2121

Collins KWM 380 HF transceiver general coverage on receive. Extra CW filters £15 ono. Yaesu FT225 RD with Mutek Board - offers. Trio/Kenwood 2kW linear TL922 £450. Yaesu FT77 £375. Atlas 180/215. Tel: David Cole 01-594-3495

(office hours).

Exchange Icom IC-25E 25W 2m FM transceiver, mint condition, mobile mounting bracket etc. For good condition SX200W scanning receiver. Ian. Tel: Shephed (Leics) 0509 502989.

Racal RA17L communications receiver. 5-30MHz. Excellent condition with handbook £165. Bob. Tel: 0953 604019.

Eddystone 730/4 Gen. cov. receiver, good condition £80. Tel: 058 083 326 (evenings).

Tungar 50V 6amp Tapped charger. PSU rack mounting. Ex WD geiger counter. Obsolete valves new. Meters 0-50 microns. 0-10 microns. 0-20 amps M/iron. 0-1 M/iron 0.200V cased. Others. Large vintage round panel meters Volts amps. All very cheap. Blackburn, 57 Friern Watch Avenue, Nth Finchley, London N12 9NY.

Yaesu FC 102 Antenna tuner £130. TONO 9000E communications terminal RTTY ASCII CW Word processor etc. £500. Middleton, 49 Wolseley Road, Stafford, ST16 3XW.

Have Baker research microscope, Mechanical stage binocular eyepiece, camera, very complete outfit. Worth £350. Also Bronica 'C' camera and accessories. Exchange for CB base station complete, RTTY/CW reader terminal, VHF scanner, multi-system TV for DX-ing. Cash adjustment if necessary or will sell. Computer and VDU rig acceptable as RTTY/CW terminal. Tel: Trowbridge 61482 (Wiltshire).

Canon 110ED, flash, leather case £40. Minox B £45. Polaroid 350, portrait kit 581A, flash gun 268 £95. Audio/Visual IFR training course, FAA approved, manuals, projector, player £100 cost £400. SM-D100 stereo mic £15. Philips ultrasonic burglar alarm £10. Ameco (USA) tuneable pre-amp 1.8-54 MHz, 240V £15. FT101, unmodified £200. Woodpecker blanker AEA WB1A £40. SX200N scanner RX £175. FT101 Workshop manual £15. May, Upper Durford, Petersfield, Hants GU31 5AN. Tel: Liss 2143.

Tonna 17 element 2m new £33. Jaybeam 14 element parabeam new £45. Hameg 10MHz oscilloscope, hardly used £130. Icom IC2E modified USA £125. Halbar 6-element quad 70cms new, £10. Part built G4DHF transverter £25. Plus other bits and pieces from shack clearout. Ken. (GAUQN). Tel: 0945 61029.

New CR 2021 Uniden world radio. Offers or will consider part exchange Marine radio R1000 etc. Tel: 0274 676556 (after 6pm).

IC280E 2m mobile FM with remote mounting kit, 3 memory channels £120 ono. G4TAW. Tel: 0689 30334.

Yaesu FT227R 2m FM mobile, plus 3/4 whip, Magmount. 8ELE Yagi and download, SWR-25 Meter, base station colinear plus pole and download, RSGB VHF/UHF manual £150. Also Heathkit GR-64 HF receiver (valves), recently rebuilt and professionally realigned, £35. With original manual. Jim Cook, Jars Cottage, Charlton, Worcs WR10 3LE. Tel: Evesham 0386 860120.

Yaesu FT101Z, FM, 9-band, fan, desk mic. Spare (new) tubes, immaculate condition £400. SEM transmatch with top band and fitted easitune, as new £65. Scarab ZX81 RTTY cassette, plus built PCB £10. N M Lister, G4LVP, 42 Strathmore Avenue, Hitchin, Herts. Tel: Hitchin 58728.

Collectors' items, several early post-war radios, a few pre-war. All types. All cheap to clear, space needed. Pat Hill, 24 Gordon Road, Chandlers Ford, Hants SO5 1AN. Tel: 04215 3920.

Sony ICF2001 keyboard entry receiver, perfect condition, boxed as new, with full instruction book £99 ovno. A. Dermont (686GT), Burghfield Common, Berks. Tel: 073 529 2592 anytime.

Two RS C-jon rechargeable batteries, 2V 25 AH, almost new £7.50 each. For dismantling: emergency lamp units with transformer, rectifier and dropper resistor £1 each unit. Hawken. 0865 67907 (Oxford) after 6.30pm.

48K Lynx colour micro, as new, under guarantee, with compatible cassette recorder £190 ono. L Potts, Smithys Halt, Popes Hill, Newnham, Glos. GL14 1LD. Tel: Westbury-on-Severn 467.

Morse programme for VIC-20, sends random letters and numbers, speeds 1 wpm upwards, will get you your class A Licence £3. Roden, 126 High Street, Lye, Nr Stourbridge, West Midlands.



# FREE READERS SMALL ADS

## FOR SALE

● Early transistor car radio audio amplifiers, with AD140 or similar plus transformer, capacitors £1.50 each. Collins 20W modulation transformer £2. Mains transformer, output 215-0-215V, 100mA, ex-WD. Two 4V 6A 4V 2.75A, 11V 2.5A 2V-0-2V 1A £5. 'Belling' flex lead suppressor for vacuum cleaner fan £3. 'Belling' radio interference filter, cased, 2A £5. 'TCC' high pass television aerial filter £4. Transformer, 10Amp 3.5-40-0-40-3.5V, 240V £5. Alan (G3MBL), 244 Ballards Lane, London N12 0EP. Tel: 01 445 4321.

● 70301 brand new, but dusty because original packing missing. Complete with all cables and handbook. Prefer buyer collect, but could deliver 50 miles Slough, £120 ono. Teletype S52 scope identical X-Y amps, fitted orange filter for long persistence screen, ideal for slow scan TV, or change filter to blue for Standard scope DC, 3MHz complete with handbook £35 ono. (G4CRW), Slough. Tel: 0753 42301.

● Yaesu FT 200 SSB transceiver, with matching PSU and speaker, in superb condition £230. Tel: Wolverhampton 750497 (daytime).

● Maranz C-205 portable professional cassette recorder £60. Also realistic 5ch Stereo mixer with preface, plus mains PSU £25. All in good working condition. Will exchange both for 2mte or 70cms Synth hand hold, or 2m Synth rig 25W output Icom Yaesu or Trio. Mr V J Bobin, Flat 6, No 11 Hyde Road, Eastbourne, Sussex.

● Rascal R17L HF receiver £285. Eddystone 840C HF receiver £75. Redifon VHF radio telephone £110. Large desk radio console £100. All ono. Henry Howard, 108 Lindenthorpe Road, Broadstairs, Kent. Tel: 0843 601041.

● I have a full colour and sound home computer with brand new Sharp cassette recorder, and all books. Make is Mattel 'Aquarius'. Will swap for 2m or 70cm TX/RX with perhaps £10 offered on top. Will collect within 30 miles of Manchester. Martin. Tel: 061 795 5025.

● Large quantity of Electronic and Mechanical components - cheap. Send SAE for list to: M Black, 11 Moorland Avenue, Crumpsall, Manchester M8 6WT.

● B2 Spy set, mint condition, in original suitcase. All coils, crystals, key spares, in full working order. No mods of any sort. Also handbook. Best offer over £150, plus carriage. Tel: 0432 267876.

● Private station, has two 807 units, home brew, (PSU's fault), plus some 6/7MHz Xtals £35 ovno each. Have Phonic's five channel mixer model SM-3000 £15 ovno plus IT'S 9-Volt PSU. Calling Trio R-1000 owners - what offers for SP-100 speaker cost £26. Power problem 'Valradio' transverter 6Volt input, 20 watts, 240Volt output. Also National half track stereo open reel tpe/rec'der plus tapes, speeds 4.75 cm19. Mike Evans, 41 Great Auther House, London EC1. Tel: 01 251 4950.

● Disco lighting kit, still in box. 3-channel sound to light, professional model with auto level controls. 1Kw per channel with zero voltage switching. Similar to Pulsar zero 2250. Kit cost £40 will sell for £21. Also hy-gain five 480 channel CB, excellent condition £75 for quick sale. Brand new push button, American type phone, with last number redial facility. Cost £30 unwanted gift, will sell for £20. Steve. Tel: Sunderland 0783 282057.

● Ultrasonic cleaning machine by ICI. Costs new around £1,000, for sale at £175 ono. Tel: Abersoch 075 881 2845 (evenings).

● National Panasonic DR49 full communication receiver, LW MW FM SW, full coverage to 30MHz USB LSB CW, two speed drive giving fabulous bandspread. Mains/battery. Mint condition £195. Trio Kenwood R1000, fully synthesised 150kc-30MHz, built-in 24 hour clock timer, new condition, bargain £198. SX200N VHF UHF scanner 26-88, 108-180, 380-514, AM/FM throughout, new £185. Sony CRF 230 super portable LW to 30MHz plus FM. 61-108 AM, SSB, mains battery, mint £185. Joystick antenna and tuner £12. All plus carriage. Andrews, 12 Malton Way, Clifton, York YO3 6SG. Tel: 0904 59035.

● Electronics Today International, first issue April 1972 to December 1983. Complete £25. ASR33 Teletype Westrex with tape reader, punch and on pedestal £50. Tel: Slough 45939.

● Blank and assembled electronic music printed circuit boards. 2102 Rams. S Singh, 5 Llewellyn Road, Leamington Spa CV31 2BJ.

● Many synthesiser PCBs and guitar effects PCBs, for clearout. 2102 Rams. Send SAE for list and prices. R Sidhu, 94 Galloway Road, London W12 0PJ.

● GEC 26in colour TV, good condition, works OK £50 ono. Maxcom 4E CB rig, plus SWR meter and mag-mount aerial £25. Marconi TF801B AM Signal generator 12-485 MHz £50. Tel: Knockholt (Kent) 33296.

● Rascal RA17 MkII RX with case. Perfect £150. Tel: 0772 600239.

● 1000 Valves, Octal, UX, 4-pin, 5-pin, pre-war British and American types. SAE for lists. 150 240V 12V 2 amp Sec. screen Pri. Sec £1 each, plus postage 30p. Offers for all 150 Transformers. A E Jeffrey, 42 Dennis Road, Padstow, Cornwall PL28 8DF. Tel: Padstow 532723 (after 6.30pm).

● Realistic DX 302 Receiver, 10kHz to 30MHz, LED digital readout, six bands, tuneable preselector, as new £125. Serpent CB rig, legal FM, very good condition £20. Mr Barnett, 137 Ringinglow Road, Great Barr, Birmingham B44 9BN. Tel: 021 360 6510.

● 19, 31, 38 and 62 sets complete less batteries. Good condition. Various remote aerials, cables, leads for 88, 31, 19, 62 sets, mostly new condition. Sundry spare parts for these old sets. Need to dispose, due to lack of space. Sensible offers only please. Mike Buckley, 12 Ranmore Avenue, Croydon CRO 5QA. Tel: 01 654 2582.

● Atom 12k plus 12k, 6522 V1A, printer interface toolkit rom, wordpack rom £95 ono. Also 10-15-20m trapped vertical cushcraft, unused £30 ono. S Larson (GM4CLQ QTHR). Tel: Larkhall 883982.

● DX-TV equipment. Antiference XG14 Wideband UHF aerial £20. Maplin SP100 aerial rotator with control unit £25. Triax 45013 VHF plus UHF 22dB masthead amplifier with PSU £20. Elec mailorder B45HG UHF 20dB setback amp £5. All excellent condition and boxed, as new. D Bird, 5 Dean Road, Woodthorpe, Nottingham NG5 4FJ.

● Yaesu FRG 7000 receiver, 25-30MHz, 3 clocks, timer, LED readout, as new condition £140. Sommeritamp FT767 DX transceiver, 7M35 mike, fitted with CW and AM filters, spare Xtals for 10 meters, in very good condition £325. 160W linear 10/11 meters, solid state, 1 damaged RF device, hence £30. Ray Dann, 59 Meadow Road, Berkhamsted, Herts. Tel: 04427 4240.

● Following Manuals:- Trio KA2000A Stereo amplifier with service Manual £2. BCC mobile TX/RX 69 (DEFG) £2.50. Wilcox-Gay master oscillator, plus Xtal multiplier £2. Trio TR2200G £2. KW Viceroy TX MK2, plus large MK3 circuit £2.50. Yaesu FT200/250 instruction Manual £2.50. New Zealand wireless set ZC1 MkII, working instructions Part 1, 60 pages £2. Surplus radio conversion Manual, Vol 1 1948 BC-342, 348, SCR522 etc. Offers. Technical Manual 1943 BC312N, NX, BC342N, BC314G, BC344D, offers? Wanted, HRO Senior (or similar) Manual. Alan Edwards, G3MBL, 244 Ballards Lane, London N12. Tel: 01 445 4321.

● Icom 240 with scanner, SS-224 Manual, mag mounts antenna and power supply included, £150. Mint condition Apple II+ computer, with hi-res monitor, Manuals, software etc., £500 ono. Tel: 693 3875.

● Kenwood TR 2500 £175. Pioneer 5300 digital car radio cassette, 2 months old, as new, cost £189, sell for £89. Sharp MZ 80K basic, Pascal books, Progs., £189. Tel: 0277 354378 anytime (Essex).

● Eddystone 680X £100, Eddystone 880/2 £285, Hallicrafters S27 modified £50, Hallicrafters S72 £50, Pye PTZ 704 £15, Hudson with ZM synthesizer, £50. Tel: Wokingham 782236.

● Electronics course, Heathkit, plus ET 3100 trainer console. Current model, Mint condition £60, or split, (cost £120). Philips 2202 mono cassette recorder plus accessories £10. Tel: 01-794 5879 (evenings).

● Video recorder Akai VS-9700 £90, Q-Meter, Marconi TF 329G £30, AM/FM signal generator, Taylor 62A MkII £50, CRT Tektronix 21-9 £30 (new), Kodak Ektaflex processor £30, Sony H F receiver ICF 2001 £90, Sony S W Receiver ICF 5900W £30, Thandar frequency-counter, PFM200A £40 (new), Heathkit digital multimeter IM-102 £20, Sinclair

digital multimeter DM-2 £10 (not working Ruislip 75769).

● SX200-N Scanning Receiver for sale £16. Tel: 01-485 4251.

● Radio, Realistic DX 200 communication CB equipment, antenna G-P.A4 Coax, £14. power pack, 13.8V-3A, £10. S W R and indicator, £8. Power amplifier, B30W £10. T. 593 3159 Dagenham, Essex.

● LS102 Belcom 10-11 meter mobile trans with power supply, £185. Tel: 0734 883418, 4 pm.

● Philips G6 Hybrid, Thorn 3500, Bush A823 Hybrid, Philips G8, panels spares etc., che clear, or exchange for ultrasonic transducer books etc. on ultrasonics. Tel: Alan on She (0742) 311191 after 5 pm.

● Bearcat 220 scanner receiver, mains/12V -50, 118-136, 144-174, 421-512. MHz, £135.00 0273 516801 (Newhaven) G8RHU.

● Quad 22 control unit, two Quad II p amplifiers and Wharfedale FM tuner, in walnut cabinet with record storage and W/Dale W4 corner console speakers with 4 un each, excellent condition, £135. R Parker, Sherbourne Rd, Blackpool. Tel: Blackpool 25

● New, boxed valves: EB91, D77, 6AL5, CV4014, QZ77, EF91, 8D3, 6AM6, ECC91, CV2 OB2, 108C1, E88CC, 54pence each, inc. P & P Walker, 96 Sunnybank, Hull HU3 1LF, N Humberside.

● Colt Excalibur home base, Lo-Lo Lo, High H bands, USB, LSB, AM, FM. Zetagi 200W amp, Av 3 ELE. beam SWR meter, £300 the lot. Mr J Crai Clintpark, Ecclefechan, Dumfriesshire. Tel: 05 615.

● Clearing out packs of resistors/capacitors/transistors, mixed with some other devices, items £2.50 (2½p each). Miniature pots 22K, li for £1.00. Power pack 13A plug-type, output 100 at 8v DC £2.00. D. Martin, 29 St Johns Cl Leatherhead, Surrey.

● Swan 100 MX transceiver, 80m-10m, mobile base, 180 Watts, very good condition £190 o M.B.A. R.O. C/W. RTTY, as new, screen display decoder, £120 ono. K.W.E-Zee Match, £30, QRP V 7MHz, £5. G W Grieveson, 41 Donegal Park, Be Row, Bury St Edmunds, Suffolk, IP28 8 Tel: 717106 (Mildenhall).

● Yaesu FR 100B 80-10m, 100 KHz calibrat mechanical filter, R.F. antenuator, good con tion, handbook £65 ono, carriage extra. Tel: Bext 215619.

● Heath SB 101 transceiver plus P.S.U., go working order £100. Heath HW 101 used as extern V.F.O for SB101, requires attention for fo operation, with P.S.U. £35. Datong FL2 audio filt £50. R.F.C speech processor £25. Heath HD14 electronic keyer with Hi-mound paddle £15. C AMT, Trevescan, Sennen, Cornwall, Tel: 0736 560.

● Students, learn RAE in your home with hel from our low cost system at Dover YMCA amateur radio club. Information from P J Pennington, 14 Elms Vale Rd., Dover, Kent. CT17 9PN.

● Newnes 'Radio and TV Servicing' manuals in 1 vols 1953 to 1969. 'FM Servicing Handbook', G King 'TV Servicing Handbook', Price/Patchett. 'Practical Electrical Engineer' 5 Vols Newnes. Transisto Pocket Book. Heathkit OS1 Oscilloscope require attention. Sensible offers please. Tel: Birmingham 021 458 5374. (Evenings only).

● Complete 2 metre station. Belcom HC 1400 20 watts FM rig, P S U, A T U, S W R. meter. Tonna ELE Yagi, Butternut co-linear tons of UR 67 with al plugs sockets etc. Also mobile mounts, aerials, Home-brew mobile mike. Offers around £230. Ian, 45 Town Lane, Charlesworth, Sk14 6HQ. Tel: Glossop 62479.

● Broadcast transmitter VHF FM 88 to 108 MHz 80 watts output. Varactor modulation give Hi Fi audio reproduction, perfect for music and speech broadcasting. Will pass stereo if used with encoder. 240 volt mains operation. Fully transistorised, light and easily portable. Very simple to operate. As used by J.F.M. etc. Instructions, information and advice provided. Genuine bargain at £130. Tel: 01-672 8764 evenings (7.30-8.30pm only please).



# FREE READERS SMALL ADS

## WANTED

Wanted Philips Oscilloscope GM3152. Hunts Edge CRB3. Scrap Eddystone receiver 870A. Valves ELL80, PX4, PX25, DA60, and equivalents. Buy or swap large on valves 1930 onwards. P Taylor, 14 Willow Canewdon, Rochford, Essex. SS4 3QH. Tel: 098.

Wanted service manual for JVC colour video recorder, model HR 3330 EG, on loan or for sale. Also circuit diagram for UHF, VHF, TV. A S Murty, PO Box 2825, Safat, Kuwait (Arabian Gulf). Tel: 414572.

Wanted Yaesu FTV901R. Please call 01 958 for an instant deal (G6XGG). Martin Clayton, 17 Wick Ave, Edgeware, Middx.

Wanted service manual or circuit diagram for ferro-series seven, model 713H. Will buy or copy at your price. Robert Allen, 69 Callcott Kilburn, London NW6.

Wanted Philips R-390/A URR receiver, + TIMCO or SSB unit. Will buy or exchange Canoh F-1 5, 50, 135mm optics, case, filters, etc. Also wanted: receiver manuals, books, early Hi-Fi radios, (small), and other equipment of interest. Write offers, to Stig Lundstrom, Lapinkatu 27 E, 35 SF 00180, Helsinki 18, Finland.

Wanted: could anyone supply me with two audio ICs, type HA1389? These are replacements for Decca music centre, No CP100. Tried mail order companies, and Decca. I will pay all costs. Similar - appearance only - to TA7205AP. Mr A Hoyle, 109 Padstow House, Bodmin, Cornwall, Bransholme, Hull HU7 4HD.

Wanted: still required: USA 2 volt battery valves ID7 or ID5, IF5 and IF7. UX equivalents may be acceptable. Tel: Bath 891254.

Wanted: help! I have a Telequipment servicescope 532A with some parts missing. Can I borrow one? Tel: Steve (G8KUX) Odiham (025671) 3281. Disc drives for Nascom or Alome (bare drives). Ch Bridge, 363 Kennington Lane, Vauxhall, London SE11 5QY. Tel: 01 735 1862.

Wanted: 6K ram pack for ZX81. Also Morse tutor software, and any other amateur software. Also black and white portable TV. I have 2 vintage radios (Sh, Pye). VGC for exchange or sale. Patrick Atton, 4 Mansion Avenue, Whitefield, Greater Manchester. M25 7SS. Tel: 061 766 7012.

Wanted: Cushcraft R3 20/15/10 metre vertical antenna. Good ATV suitable HF TX. R T Capps, 309 Victoria Road, Lowestoft, Suffolk. NR33 9LR. Tel: westoft (0502) 65113.

Wanted: Copy of instructions for the Gilfer Mods to the G7. Also front perspex dust cover for FRG7. Any condition. Good price paid. George Tyler, 39 Plar Road, Hanham, Bristol, BS15 3BA. Tel: 0272 7987.

Wanted: IC R70 receiver or YAESU FRG 7700. Must be in very good order. K Edmund, 24 Pryde Ave, Pennyrigg, Midlothian. EH19 2BJ. Tel: 031 660 1679.

Wanted: 'Scope manuals/circuit diagrams for telequipment S32A and D43R oscilloscopes. Able to photocopy. Please ring Leeds (0532) 866897.

Wanted: Sphinx transmitter. Any condition. N J Birkett, The Moorings, Halvarras Rd, Playing Place, Truro. TR3 6HD. Tel: 862575.

Wanted: Computer, which I can expand to copy PROMS onto disk and vice versa, up to 2764, possibly Microtan or Nascom. Also technical advice wanted on above (I have Softy 2). Tel: Mark in 01 732 9165.

Wanted: Grundig or Phillips VCR, preferably working. Milton Keynes area or reasonable travelling distance. M Richardson, 77 North 7th Street, Milton Keynes, Bucks. MK9 2DP. Tel: 03664 602.

Wanted: Small short wave receiver, such as Codar T28 or similar. Marine amateur bands. I have 1948 Eddystone model 670 needs attention not working. Also have brand new Mullard valves for this receiver. Also have Syncrite projector and screen. Would consider exchange for these two items. A W Hyde, 54 The Causeway, Pagham, Bognor Regis, Sussex. PO21 4PG. Tel: Pagham 3256.

Wanted: 603kHz crystal, falling ball sound source, Admiralty wireless manuals 1912, 1920. 24GHz equipment for sale. Mann. Tel: 0223 860150.

Wanted: Mobile amateur radio. Just joined a club, so any basic equipment, transceiver wise, wants to swap

for FM CM 27MHz and ZX81 computer. Willing to pick up if local. Tel: St Helens 815320 anytime.

Any circuit diagrams for ZX Spectrum add-ons, interfaces, ports, joysticks etc. Prefer to photocopy and return, but will purchase. Robert MacDonald, 62 Balmoor Terrace, Peterhead, Grampian AB4 6ES.

For private collection. Old wireless sets made before 1930, complete or not, working or not. Also valves, parts, earphones, speakers etc for early sets, battery or mains. Please send full details with sketch or photo. Good prices offered. Mr Brand, 4 Temple Park Crescent, Edinburgh EH11 1HT. Tel: 031 228 1569.

Mullard QQV03/10 valves wanted for project. Rod McMillan. Tel: 01 445 25080.

TS 8305 CW filters. External VFO. J Wayman (G4DRS), 190 Drove Rd, Biggleswade, Beds SG18 0HP. Tel: Biggleswade 312609 (evenings).

Service manual for Tektronics 545A scope, to borrow, buy or copy. Also scope CRT wanted for Tektronics 502A. Any info on SIFAM 300 series OHM meter. David Dimelow, 1 Gateside Walk, Blackley, Manchester 9, Lancs.

Service manual for JVC model HR3330 eg colour video cassette recorder. At least printed circuit diagram would be appreciated. A S Murty, PO Box 2825, Safat, Kuwait, Arabian Gulf. Tel: 428712.

UHF and VHF converter. Latter to be compatible with FRG 7000. ATU also wanted. Can you help disabled pensioner equip at a reasonable price? Have got the bug. T W Foster, 5 Centre Parade, Kettering, Northants. Tel: 0536 516353.

Selective calling devices for CB. W Webber. Tel: Long Ashton 2811 (Mon-Fri, office hours).

YAESU FRG7 receiver in good condition. Would pay up to £120. Collect if within reasonable distance. Handbook required. May be interested in similar item. Tel: Tony Corbett, Wrexham 757435 (evenings or weekends). Or write to PO Box 97, Wrexham, Clwyd, N Wales.

Trio TS120V HF transceiver. Cash waiting. Accessories also considered for above. Chris Lorek (G4HCL), 11 Bevills Close, Doddington, March, Cambs. Tel: 0354 740672.

Dual beam scope. Also two PSVs 0-30V 1a. Must be in good working order. Also transistor tester. Mr Gagan, 127 Manygates Lane, Wakefield. Tel: 0924 258342.

FM board for FT101 ZD needed urgently. Will pay your price. Tel: 572 8168 (after 6pm).

Black and white portable TV. Must be cheap. Contact Sean McAteer, 82 Woodlands, Gilford, Craigavon, Co Armagh BT63 6JP. Tel: 0702 831569.

Philips AD8067 WMFB4 woofer with Piezo electrical transducer, 40W rms, 20cm diameter and Philips ADO 210/5Q8 5cm diameter midrange. Perhaps someone has these lying around. Price negotiable. Colin Waywood, No 2 Farm Cottages, Kitchen Hall Farm, Harlow, Essex CM17 9BU. Tel: 0279 29531 ext 2213 (9am-5pm).

Swan model 410 frequency control unit. Also Swan model 230-X AC power supply unit. Swan Mark 1 grounded grid linear amplifier. D R Owen, 12 Wolverley Ave, Wollaston, Stourbridge DY8 3PJ.

Service manual for model 8 Mark III avometer. About 12 years old. Contact Mr Dave Evans, 27 Summerhill Rd, Onchan, Isle of Man. Tel: 0624 3634.

I'm looking for CB sets, working but cheap, also TV tank battle game (not computer type). D Martin, 29 St John's Close, Leatherhead, Surrey.

Small oscilloscope, cheap, working or not working. Alan. Tel: (Sheffield) 0742 311191 after 5pm.

Tuning condenser for Wien 5 FM/AM receiver. Post and cost paid. Leslie Johnson, 31 Edward Avenue, Jacksdales, Notts NG16 5LB.

AM, FM broadcast band transmitters. Also TV transmitters, PSU's, modulators, aerials. Buy or exchange for similar, including stereo generator, keys, decks etc. Aleks. Tel: 01 250 0796 (days).

ZX81 printer for spares. Faulty or broken, one will do. A Jaques, 47 Newstead Road, Urmston, Manchester.

Service Manual or Circuit Diagram for Ferrograph series seven seven model 713H. Willing to buy at your price or photocopy. Also the same for breaking. Robert Allen, 69 Callcott Road, Kilburn, London NW6.

Wanted tech. Manual, circuit, info. for electronic organ, Rima orchestra. E Lind, 54 Cowper Close, Welling, Kent DA16 2JT. Tel: 01 304 1262.

Vintage wireless set, preferably with horn speaker, 1920's era, or vintage components to construct same. Also crystal set, same era required by retired radio amateur to refurbish as a project for subsequent shack adornment. Reasonable prices paid. (G3YJF QTHR) Tel: 061 437 7899.

Yaesu transverter modules for 4m and 70cms; type 70TV and 430TV, as used in FTV901R etc. John (G8KAX). Tel: Hornchurch 57782 (early evenings).

Sinclair Spectrum 48K. Three oscilloscopes offered in exchange plus Heathkit metal detector, all in working order. Possible cash adjustment. W H Davis, Gate House, Little Barford, St Neots, Cambs PE19 4YB. Tel: Huntingdon 72480.

Any information on Collins aircraft band RX 51X-2, TX 17L-7. B A Solomon, 43 Amberley Road, Macclesfield, Cheshire SK11 8LX. Tel: 0625 20782.

Single trace 15MHz Scope; also RE signal gen, and audio gen. Any age, any make, any cond, need not work, but must be repairable. Will collect Essex/Kent area. Gordon, 4 Lionel Oxley House, New Road, Grays, Essex RM17 6PP. Tel: 0375 79274 (after office hours).

1296-144MHz Receive converter (microwave modules, with bipolar frontend, or similar). Peter Jones (G8KJTJ). Tel: (Penn) 049481 2439 (evenings or weekends).

14MHz-30MHz Coilpack for National HRO. Must have bands spread. Reasonable price paid. Condition unimportant. A Dermont (G8BGT), Burghfield Common, Berks. Tel: 073 529 2592.

Collins 75A4 Receiver wanted, must be in nice condition. Also Yaesu YO-901 Multiscope. P Sullivan. Tel: Manningtree (Essex) 4336.

MFJ 1020 Active antenna. Details to Mr Roberts, 13 The Chase, Salford, Derby. Tel: Derby 761318.

Valve tester with data and RCA or Hallicrafters valve communication receiver. Condition must be reasonable and working or repairable. Details, price and condition to Leworthy, 147 Church Road, Burgess Hill, West Sussex. Tel: 04446 2544.

Small Marine band TX, cheap. Mike Evans, 41 Great Auther House, London EC1. Tel: 01 251 4950.

Sony ICF6800w or Grundig 3400, can exchange Sony 2000 with power unit, also 12-channel Scanner 2m RX. Findley, 27 Keyter Lane, Barford, Warwick CV35 8EP.

Yaesu FRG7 or Lowe SRX30 Receiver. R Miles, 59 Hungerford Road, Calne, Wilts. Tel: Calne 0249 813024.

Friends who will render assistance in purchase of components, books and journals. Kazeem Olayinka M, 33 Bank-Olemoh Street, Surulere, Lagos, Nigeria.

For Solartron CD513 Solarscope, Manual and/or Circuit Diagram or photostat copy of same. Will buy or pay postage and any costs incurred. Tel: 051 644 6028.

## FREE SMALL ADS

We are pleased to be able to offer readers this free Small Ad Service to enable you to sell unwanted equipment or advertise for your 'wants'.

Simply complete the order form overleaf, although we will accept ads not on our order form. Feel free to use an extra sheet of paper if there is not enough space on the order form. Send to: **Radio & Electronics World** Small Ads, Sovereign House, Brentwood, Essex CM14 4SE.

## DEADLINE

We will endeavour to include all ads received by 22 March 1984 in the May issue. Ads received after this date will be included in the next available issue.

## CONDITIONS

We will not accept trade advertisements. We reserve the right to exclude any ad.



# Radio & Electronics World

NEW IMPROVED

The communications, electronics & computers magazine

# SMALL ADS

## GREATER MANCHESTER

BETA COMM

231 Chorley Rd, Swinton  
Greater Manchester  
Tel: 061-793 1010  
Open: 7 days a week  
TRIO, YAESU, ICOM, GWHIP

## NORFOLK

SPANNER CITY CB CENTRE



Open 6 days  
9am-6pm

Parkside Garage  
Thursford  
Fakenham  
Tel: Thursford  
402

Grandstand  
LA83  
27 to 934 MHz  
TRANSVERTER

## KENT

Thanet  
Electronics



95 Mortimer St, Herne Bay  
Tel: 02273-69464  
Open: Mon, Tues, Wed 9-5  
Thurs 9-1, Fri, Sat 9-5.30

All mail order & service enquiries to head office, 143 Reculver Rd, Tel: 02273-63859

## NOTTS

R.A.S.(NOTTINGHAM)

P Owen G8UUS

3 FARNDON GREEN; WOLLATON PARK  
NOTTINGHAM: TEL: 0602 280267

Open: Tues-Fri 10-5.30, Sat 9-5

YAESU: FDK: ICOM: TONNA

HALBAR: WELZ: ANTENNAS & OWN GW5 H.F

# Radio & Electronics World

NEW IMPROVED

The communications, electronics & computers magazine

This method of advertising is available in multiples of a single column centimetre — (minimum 2cms). Copy can be changed every month.

### RATES

per single column centimetre:

1 insertion £9.65, 3 — £9.15, 6 — £8.65, 12 — £7.75.

# SMALL ADS

## RADIO & ELECTRONICS WORLD SMALL AD ORDER FORM

TO: Radio & Electronics World · Sovereign House  
Brentwood · Essex CM14 4SE · England · (0277) 219876

PLEASE RESERVE.....centimetres by.....columns

FOR A PERIOD OF 1 issue..... 3 issues..... 6 issues..... 12 issues.....

COPY enclosed..... to follow.....

PAYMENT ENCLOSED:.....

£ —

Cheques should be made payable to Radio & Electronics World. Overseas payments by International Money Order

CHARGE TO MY ACCOUNT.....

COMPANY .....

ADDRESS .....

SIGNATURE .....

TELEPHONE .....

For Publisher's Use—RE0484

Registered No 2307662 (England)

C P I

## MINIATURE TRANSISTORISED BFO

### MINIATURE TRANSISTORISED BFO

Enables you to receive CW and SSB TRANSMIS Fully transistorised (tunable). Very compact anywhere. Single hole Fixing. Brand new with instructions. £8.95. PP 50p. LIGHTWEIGHT HEAD (Govt. release). Brand new 600 ohms impedance bargain at £3.50. PP £1.50. 2 pairs for £7.50 pos

## THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK

Please allow at least 28 Days for delivery v reprinting

Gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment. Also suggested indication details improvements for surplus equipment. Incorporated is a Surplus/Commercial referenced valve and transistors guide. A standard reference work in this field. Only £5 p.p. £1.50. No VAT on books.

HALF-PRICE TRANSFORMER SALE. TYPE 1. M calmped type. Input 200/250v. 50 c/s. Output 250-0-60ma. 6.3v at 2 amps. Price £2.50. P&P £1.50. £7.00 post free. TYPE 2. Upright mounting, shrouded. 425-0-425v. 200ma. 6.3v. at 4a. C.T. plus 6.4a. Should be £25.00 each. OUR PRICE £7.50. £2.50. Ideal for valve amplifiers incl. RSC and LI TYPE 3. 450-0-450v. 200ma. 6.3v at 4a. C.T. Should be £25.00. OUR PRICE £8.00. P&P £2.50. Ideal for valve amplifiers and also for transmitters. ALL ARE TRANSFORMERS HAVE MAINS INPUT. ARE BRAND NEW AND FULLY GUARANTEED. Trade enquiries welcome.

PYE POCKET PHONE PFI DATA AND INSTRUCTIONS. Contains circuits, layouts, operating and modification details for amateur use etc. £1.50 post free.

VERSATILE POWER SUPPLY UNIT. 100/240V 50 c/s. Input. Output 20-0-20 Volts DC upto 5 amps. Incorporating one 20 volt DC output up to 5 a. Easily modified for 40V and 60V. Metal case size 7.4 with circuits. Usual price around £60.00. Our price £8.50 p.p. £3.00. 2 for £20 post free. These units make ideal variable voltage power supply.

CAPACITOR BARGAIN PACKS. Bulk purchase enables us to offer a pack containing 500 new standard polyester capacitors. 0.01 (MFD-0.47MFD). 100 to 1 working. PRICE £8 per 500 lot. PP. £1. 1000 lot £16 post free. Trade enquiries invited.

MINIATURE MAINS TRANSFORMER. Mains input. Output 6-0-6V. 250MA. 90p. P&P 35p. 2 for £2. Free. 10 for £8.75 Post free.

BULK BARGAIN TRANSISTOR RADIO/CASSETTE SERVICE PACK. Contains at least £25 worth of transistor radio and cassette spare. Loads of hard to obtain components and spares including hardware. Ideal for the radio service engineer. ON £6.50. P.P. £1.50. Double Pack £12.75 carr free.

GENUINE EX-GOVT COLLAPSIBLE AERIALS. A full adjustable highly efficient whip aerial in 5 sections. Length 1½ metres. Closed 300 mm. Copper plated sections. As used on Ex Govt Manpacks. Brand new makers boxes. £2.50 each, p.p. 75p. 2 for £5 post free. Aerial bases for same. £2.75, P&P £1.25.

HAVE YOU SEEN THE GREEN CAT? 1000's of new components, radio, electronic, audio at unbelievable low prices. Send 60p for catalogue.

GOVT SURPLUS LIST 60p. VALVE LIST. Valves from 1925 to 1960. Many obsolete types. Modern TV, radio and transmitting valves. Set 60p. Or £1 (Refundable on purchase) for all three.

WE SELL VALVES OF ALL TYPES. Please send SAE for your requirements.

Try a JUMBO PACK. Contains transistors, resistors, caps, pots, switches, radio and electronic devices. OVER £50 WORTH FOR £11.00. Carriage and packing £2.50.

Please add 15% VAT to all orders including carriage and PP.

## MYERS ELECTRONIC DEVICES

Dept. REW, 12/14 Harpers Street, Leeds LS2 7EA  
Tel: (0532) 452045. Retail premises at above address (opposite Corals) 9 to 5 Mon to Sat. Sunday 10 to 1 by appointment. GOVT. SURPLUS ITEMS ALWAYS IN STOCK.

## KITS & BUILT ELECTRONIC PRODUCTS

All high quality, novel design, and easy to make. All instructions included. 3 month warranty on all items. Examples: Brain wave analyser built: £19. Crystal calibrator-built: £20. ZX81 16K dialogue tape: £8.50. Many more exciting bargains. Send SAE for list to:

J Edwards, 17 Palace St, Norwich, Norfolk.

## Dummy Anti-Theft surveillance cameras £39.00.

Flashing red 'function' light for total realism and theft deterrence. Easy fixing. Phone your order on:

(0274) 871090 or write to: 'Churchill Cavendish Ltd', Blenheim Ridings, Timothy Lane, Batley, W Yorks



## TIGER LY9 70 Cms Antenna

from Ant Products, a superb addition to a range of renowned antenna, the Tiger LY9 70 cms. A light weight antenna with a heavy duty signal. Offering a high 11 db gain on a 70 inch boom length. Great for vertical or horizontal mounting. Supplied in matched pairs for the ultimate Oscar station complete with all hardware for mounting with elevation control. Precisely adjustable for angle in order to get the best performance. Also including matching unit for circular polarisation. Right or left hand can be chosen for equal efficiency. Last but not least our two year guarantee and full back up service.

Write now for full details enclosing SAE plus 25p in stamps

Ant Products, All Saints Industrial Estate  
Baghill Lane, Pontefract, West Yorkshire  
Tel: 0977 700949

**VALUABLE  
SPACE FOR  
SALE!**

Telephone:  
0277 219876  
for details

## MORSE CODE TRAINER

for unexpanded VIC 20

demonstrates, tests sending & receiving, also uses your recorded messages. SAE for sample instructions, or £5 on cassette inc vat, P&P from:

### STAFFSOFT SERVICES LTD

2 Prospect Place, Cemetery Rd  
Holmfirth, Huddersfield HD7 1RH

## RTTY

### THE COMPLETE SERVICE

PLI Terminal unit system modules from:-  
£13.50 (Kit) £18.50 (Built)  
Software for:-

Dragon 32 Acorn Atom  
Commodore 64 Vic 20

For a full catalogue of hardware & software send large (A4) SASE to:-

### PNP COMMUNICATIONS (REW)

62 Lawes Avenue, Newhaven  
East Sussex BN9 9SB

● Micro-mini transmitters, all supplied ex-stock, return post delivery, no special equipment required, built tested, with instructions.

**CT10H**, with up to 4 mile range and broadcast quality speech pick-up, even at fifty feet, no bigger than a PP3 battery, £13.98; the **CT10M**, professional grade, with extra high power, tunable frequency, 70-120MHz and variable microphone sensitivity, £19.48; the **CT10MB**, as above but employing unique dual microphones to eliminate echos, noise, etc., £21.40, we can also cater for specialised requirements, even radio stations. Please enquire: 061-905 1040. All prices are inclusive. **SAT Electronics, 164 Washway Road, Sale, Cheshire M33 1RH. LRCT**

Complete, full-size sets, any published service sheets £2 - large SAE - except CTV's/Music Centres from £3 - large SAE.  
Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications, for large SAE.  
Repair data/circs almost any named TV/CVR, £9.50 by return.

### TISREW

76 Church Street, Larkhall, Lanarkshire ML9 1HE  
Phone: 0698 883334

## B & T ELECTRONICS

Super packs all £5.00 p&p £1.90p  
**FT1** 80 assorted fuses 15-20mm & 1 1/4in  
**SP2** 100 transistor diodes mixed full spec  
**SP3** 50 Leds green  
**SP4** 50 Leds orange  
**SP5** 5000 resistors various  
**SP6** 200 wire wound resistors  
**SP7** 1 kilo Nuts, Bolts, Washers & tags  
**SP8** 1 kilo, vero and similar plated pins various  
**SP9** 10 green Leds Displays common cathode  
**SP10** 100 Germanium diodes  
**SP11** 2 Xenon - strobe lamps  
**SP12** 100 mixed Electrolytic copasitors  
**SP13** 10 small DC Brush Motors 6-12 volts  
**SP14** 100 mixed pre-sets various  
**SP15** 30 mixed potentiometers  
**SP16** 30 precision precepts

13 Tanner Hill, Deptford, London SE8  
Tel: 01-692 1441

Retail & Trade (official order accepted)

## AERIAL BOOSTERS

Next to the set fitting  
**B45H/G-UHF TV**, gain about 20db, Tunable over the complete UHF TV band. **PRICE £8.70**  
**B11-VHF FM RADIO**, gain about 14db, when on the off position connects the aerial direct to the radio. **£7.70**.  
All Boosters we make work off a PP3/006p/6F22 type battery of 8v to 18v DC. **P&P 30p PER ORDER.**

### ELECTRONIC MAILORDER LTD,

62 Bridge St, Ramsbottom,  
Lancs BL0 9AG. Tel (070682) 3036  
Access/Visa Cards Welcome SAE Leaflets

## THE NEXT ISSUE OF

*Radio &  
Electronics*  
World


ON SALE  
13 APRIL 1984

## THE VINTAGE WIRELESS COMPANY

1914 - 1960

Radios, amplifiers, service sheets, valves, vintage components, books new & used, repairs & restorations, mail order only.

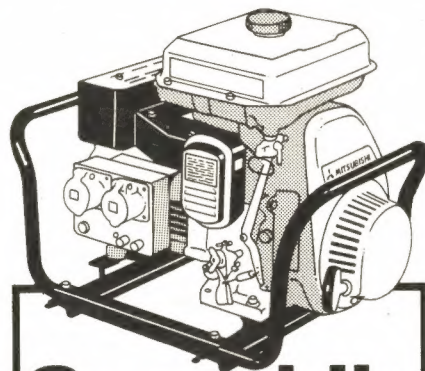**Tudor House**  
Cosham Street, Mangotsfield,  
Bristol BS17 3EN  
0272-565472



## Go mobile with Mitsubishi

There's no doubt that more and more operators enjoy the benefits of transmitting on location...

The Mitsubishi Portable Generators are compact, easy to move, have an auto voltage regulator, 110/240 volt AC or 12 volt DC (8.3 amps) output, speed control, frequency meter, circuit breaker and recoil starter.

Mr. Reeves of Waterlooville, Hampshire (Call Sign G8VOI) is one of our many satisfied users. His order to us included the following comment:

“Thank you very much for the information supplied today on Mitsubishi Generators by your representative at the Sussex Mobile Radio Rally at Brighton.

Having considered the specifications of these compared to both Honda and Yamaha types, this is by far the best for my needs in operating portable radio equipment.

Please supply: 1 x off  
Mitsubishi Portable Generator  
1.5kVA.99

**LIMITED OFFER ONLY**

1.5kVA Model @ £235 + VAT  
2.0 kVA Model @ £275 + VAT

... So if you want reliable mobile transmitting take a close look at the 1.5 and 2.0kVA Mitsubishi Portable Generators and fill in the coupon now.



**Ray-Lift Limited,**  
114 Kingston Avenue,  
Bilford Road,  
Worcester. WR3 8PP.  
Tel: (0905) 56671

Name: \_\_\_\_\_

Address: \_\_\_\_\_

Tel No: \_\_\_\_\_



# ADVERTISERS INDEX

Akhter Instruments.....91	Charlton Electrical.....78	Hart Electronics.....6	R.T.V.C.....
Alytronics.....32	P.M. Components.....78.79	Hately Antennas.....15	Radio Shack.....Outside Back
Amateur Electronics UK.....70,71	Comtech..... Inside Back cover	Hemmings.....15	Random Electronics.....
Amateur Radio Exchange.....52,53	Crimson Elektric.....48	Henrys Audio.....44	Reltech Instruments.....
Ambit International.....5		C.M Howes	
Ambit International.....50	Data Publications.....54	Communications.....17	Scarab Systems.....
Amtronics.....Inside Front Cover	Dau UK.....54		S.E.M.....
Ant Products.....14	Display Electronics.....33	Keytronics.....23	South Midlands
Armstrong Kirkwood			Communications.....
Developments.....40	East Cornwall Components.....60	Lascar Electronics.....6	Special Products Distributors
Autronics.....35	Edwardschild Ltd.....26	Lecmar Electronics.....22	Stewarts of Reading.....
Avcomm.....35	AD Electronics.....26	Les Wallen.....35	C.R Supply Co.....
	B.N.O.S. Electronics.....65		
Bi-Pak.....47	G4OGP Electronics.....48	Microwave Modules.....73	C-Tec Security.....
Black Star.....46	Electro-tech.....26	Mutek Ltd.....30	Thanet Electronics.....
Brian Reed.....54			
J. Bull Electrical.....36	Gamma Aerials.....44	New Ideas Ltd.....28	R Withers.....
Burns Electronics.....95	Garex.....26	Northern Amateur R.S.A.....32	Wood & Douglas.....

## Radio & Electronics World

The communications, electronics & computers magazine

## ADVERTISING RATES & INFORMATION

ABC membership approved pending first audit Jan-Dec 1984

DISPLAY AD RATES		series rates for consecutive insertions			
depth mm x width mm	ad space	1 issue	3 issues	6 issues	12 issues
61 x 90	1/8 page	£91.00	£86.00	£82.00	£73.00
128 x 90 or 61 x 186	1/4 page	£160.00	£150.00	£145.00	£125.00
128 x 186 or 263 x 90	1/2 page	£305.00	£290.00	£275.00	£245.00
263 x 186	1 page	£590.00	£560.00	£530.00	£475.00
263 x 394	double page	£1140.00	£1070.00	£1020.00	£910.00

COLOUR AD RATES		colour rates exclude cost of separations	series rates for consecutive insertions			
depth mm x width mm	ad space	1 issue	3 issues	6 issues	12 issues	
128 x 186 or 263 x 90	1/2 page	£420.00	£395.00	£375.00	£335.00	
297 x 210	1 page	£810.00	£760.00	£730.00	£650.00	

SPECIAL POSITIONS	
Covers:	Outside back cover 20% extra, inside covers 10% extra
Bleed:	10% extra [Bleed area - 307 x 220]
Facing Matter:	15% extra

DEADLINES

\*Dates affected by public holidays

issue	colour & mono display ad	small ad	mono artwork	on sale
May 84.....	15 Mar 84.....	21 Mar 84.....	23 Mar 84.....	13 Apr 84.....
June 84.....	9 Apr 84*.....	16 Apr 84*.....	18 Apr 84*.....	11 May 84.....
Jul 84.....	10 May 84.....	16 May 84.....	18 May 84.....	8 Jun 84.....
Aug 84.....	14 Jun 84.....	20 Jun 84.....	22 Jun 84.....	13 Jul 84.....

CONDITIONS & INFORMATION	
<b>SERIES RATES</b> Series rates also apply when larger or additional space to that initially booked is taken. An ad of at least the minimum space must appear in consecutive issues to qualify for series rates. Previous copy will automatically be repeated if no further copy is received. A 'hold ad' is acceptable for maintaining your series rate contract. This will automatically be inserted if no further copy is received. Display Ad and Small Ad series rate contracts are not interchangeable.	If series rate contract is cancelled, the advertiser will be liable to pay the unearned series discount already taken.  <b>COPY</b> Except for County Guides copy may be changed monthly. No additional charges for typesetting or illustrations (except for colour separations). For illustrations just send photograph or artwork. Colour Ad rates do not include the cost of separations.
Printed — web-offset.  <b>PAYMENT</b> All single insertion ads are accepted on a pre-payment basis only, unless an account is held. Accounts will be opened for series rate advertisers subject to satisfactory credit references. Accounts are strictly net and must be settled by the 15th of the month following invoice date.	Overseas payments by International Money Order. Commission to approved advertising agencies is 10%.  <b>CONDITIONS</b> A voucher copy will be sent to Display and Colour advertisers only. Ads accepted subject to our standard conditions, available on request.
<b>FOR FURTHER INFORMATION CONTACT</b> Radio & Electronics World, Sovereign House, Brentwood, Essex CM14 4SE. (0277) 219876	



# NEW YEAR SALE

DISCOUNT DOES NOT APPLY TO 741 & 555

## STORES

8	12p	BC415C	10p	BD243A	55p	MJ2955	90p	TIP3055	70p	2N4033	30p
C	10p	BC416C	10p	BD243C	68p	MJ3000	210p	TIS44	20p	2N4037	40p
4	16p	BC477	25p	BD244A	64p	MJ3001	225p	TIS90	20p	2N4058	10p
6	17p	BC478	23p	BD244C	78p	MJE340	48p	TIS92	20p	2N4059	10p
	28p	BC479	24p	BF180	30p	MJE350	70p	2N1613	30p	2N4060	10p
	32p	BC546	10p	BF181	30p	MJE370	80p	2N1711	30p	2N4061	10p
	29p	BC546B	9p	BF182	30p	MJE371	84p	2N1893	30p	2N4062	10p
	27p	BC547B	9p	BF183	30p	MJE521	68p	2N2218	24p	2N4400	15p
	30p	BC548B	9p	BF184	30p	MJE2955	80p	2N2219	25p	2N4401	15p
	32p	BC549C	9p	BF185	30p	MJE3055	68p	2N221A	25p	2N4402	15p
	32p	BC550C	10p	BF192	12p	MSPA05	20p	2N221A	18p	2N4403	15p
	8p	BC556B	10p	BF196	12p	MSPA06	20p	2N222A	10p	2N4404	15p
1B	9p	BC557B	9p	BF197	12p	MSPA12	22p	2N2368	23p	2N4405	15p
2C	9p	BC558B	9p	BF198	10p	MSPA13	22p	2N2369A	15p	2N4406	15p
3C	15p	BC559B	9p	BF199	12p	MSPA14	23p	2N2482	24p	2N4407	15p
7B	15p	BC559C	9p	BF200	40p	MSPA15	23p	2N2646	48p	2N4408	15p
8C	15p	BC560C	10p	BF224	15p	MSPA16	23p	2N2904	22p	2N4409	15p
9C	15p	BC560C	10p	BF244C	22p	MSPA17	23p	2N2904A	23p	2N4410	15p
12B	9p	BC637	20p	BF245	25p	MSPA18	23p	2N2905	22p	2N4411	15p
13B	9p	BC638	20p	BF256C	32p	MSPA19	23p	2N2906A	22p	2N4412	15p
14B	9p	BC639	22p	BF256LC	35p	MSPA20	23p	2N2907	23p	2N4413	15p
15B	9p	BC640	24p	BF257	32p	MSPA21	23p	2N2907A	23p	2N4414	15p
16B	9p	BCY70	18p	BF258	35p	MSPA22	23p	2N3053	23p	2N4415	15p
17B	9p	BCY71	18p	BF336	36p	MSPA23	23p	2N3054	23p	2N4416	15p
18B	9p	BCY72	17p	BF337	39p	MSPA24	23p	2N3055	50p	2N4417	15p
19B	9p	BD115	50p	BF338	40p	MSPA25	23p	2N3055H	75p	2N4418	15p
20B	9p	BD131	45p	BF339	40p	MSPA26	23p	2N2440	58p	2N4419	15p
21B	9p	BD132	48p	BF340	40p	MSPA27	23p	2N3441	120p	2N4420	15p
22B	9p	BD133	30p	BF341	37p	MSPA28	23p	2N3442	120p	2N4421	15p
23B	9p	BD134	30p	BF342	37p	MSPA29	23p	2N3443	120p	2N4422	15p
24B	9p	BD135	30p	BF343	37p	MSPA30	23p	2N3444	120p	2N4423	15p
25B	9p	BD136	30p	BF344	37p	MSPA31	23p	2N3445	120p	2N4424	15p
26B	9p	BD137	30p	BF345	37p	MSPA32	23p	2N3446	120p	2N4425	15p
27B	9p	BD138	35p	BF346	37p	MSPA33	23p	2N3447	120p	2N4426	15p
28B	9p	BD139	35p	BF347	37p	MSPA34	23p	2N3448	120p	2N4427	15p
29B	9p	BD140	35p	BF348	37p	MSPA35	23p	2N3449	120p	2N4428	15p
30B	9p	BD203	70p	BF349	37p	MSPA36	23p	2N3450	120p	2N4429	15p
31B	9p	BD204	70p	BF350	37p	MSPA37	23p	2N3451	120p	2N4430	15p
32B	9p	BD205	70p	BF351	37p	MSPA38	23p	2N3452	120p	2N4431	15p
100B	9p	BD273	70p	BF419	37p	MSPA106	23p	2N3520	120p	2N4499	15p

## BRIDGE RECTIFIERS

W005	18p
W01	20p
W02	22p
W04	24p
W05	28p
W08	32p
3A/50V	40p
3A/100V	42p
3A/200V	44p
3A/400V	46p
6A/50V	75p
6A/100V	80p
6A/200V	88p
6A/400V	94p
25A/100V	185p
25A/200V	198p



# BEARCAT 200FB — LIMITED NUMBER

## AVAILABLE AT THE OLD PRICE

### £184.95

#### SPECIFICATIONS

**Frequency range:**  
66-88 MHz Low Band  
138-144 MHz Extended VHF Range  
144-148 MHz 2-Meter Amateur  
148-174 MHz High Band  
406-420 MHz Extended UHF Range  
420-450 MHz 70-cm Amateur  
450-470 MHz UHF Band  
470-512 MHz UHF "T" Band

**Size:** 9"W x 3"H x 9 1/2"D

**Weight:** 3 lbs.

**Power Requirements:** 240 Vac, 50 Hz  
(using external wall outlet power supply, included)

**Audio Output:** 800 milliwatts RMS

**Antenna:** Telescoping (supplied)

**Sensitivity:** 1.0µV for 12 dB SINAD

**Scan Rate:** Selectable, 5 or 15 channels per second

**Connectors:** External speaker card edge connector (optional accessory Model No. WH-1)

**Wall outlet power supply.** Plug-in power supply converts standard household current to safe voltages used by radio.

**16 channels.** Program 16 frequencies for automatic scanning in any combination of bands and frequencies.

**Patented Track Tuning.** Extra-patented feature allows scanner to peak on each transmission automatically for optimum reception.

**2 banks.** Activate or lockout groups of channels quickly. Scan channels 1-10, 11-16, or both.

**Priority.** Lets you sample a designated frequency, on Channel 1, every two seconds to prevent missing important calls.

**On/Off Volume.** Power switch and continuously variable volume.

**Automatic squelch control.** Factory set for easier operation or manually adjust to block out unwanted noise.

**Dual scan speed.** Scan at either 5 or 15 channels each second.

**▼ /Limit key.** Sets lower and upper frequency limits for Automatic Search. Also used to "step down" through frequencies in Manual Search.

**Automatic lockout.** By-pass any channel not of current interest for faster scanning cycle.

**Single Antenna.** Single telescopic antenna provides optimized reception without the need for long low band antenna.

**Crystal-free.** Program thousands of frequencies with pushbutton ease... and without a single crystal needed.


**Decimal display.** Bright vacuum fluorescent display shows frequency being received.

**One piece keyboard.** Sealed keyboard with "key locator" ridges for positive, easy operation.

**8 band coverage.** Includes Low, High, UHF and UHF-"T" bands, 2-meter and 70-centimeter Amateur ("ham") bands, extended Land-Mobile bands.

**Direct channel access.** Go directly to any channel, without stepping through other channels.

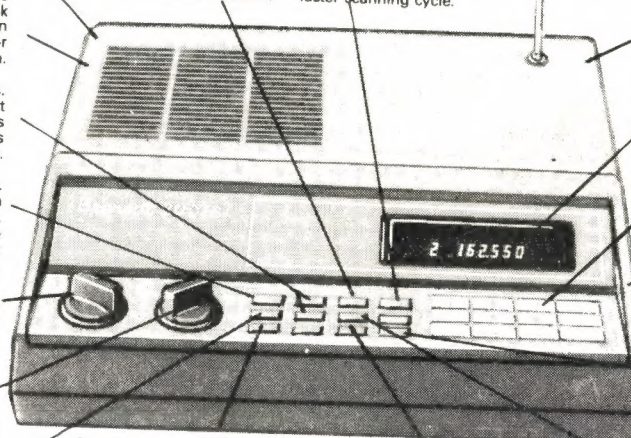**Automatic search.** Seek and find new active frequencies automatically between frequency limits you select.




**Patented Selective Scan Delay.** Adds a two-second delay on desired channels to prevent missing transmissions when "calls" and "answers" are on the same frequency.

**▲ /Hold key.** Stops searching action to hold on frequency of interest. Also used to "step up" through frequencies in Manual Search.

## Performance and Value. Bearcat® 200FB

### Direct-Access Keyboard Tuning of 22,884 Frequencies

#### £229.95

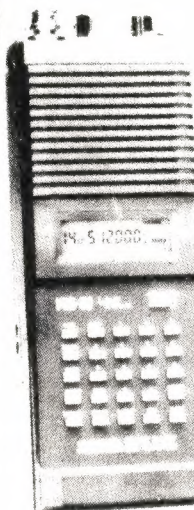

Available 15th January, 1984  
Covers 66-88 MHz VHF-Low, 144-148 MHz Ham,  
108-136 MHz AM Aircraft, 138-144 MHz,  
148-174 MHz VHF Hi, 380-450 MHz Ham,  
450-470 MHz UHF-Low, 470-512 MHz UHF-Hi

**Realistic PRO-30.** A full-feature, micro-processor-controlled scanner with extended frequency coverage — in a compact size you can carry wherever you go! Scan up to 16 of your favourite channels continuously, or search a selected frequency range for new or unpublished channels. Scan and Search in two speeds. Two-second Scan Delay, selectable for each channel prevents missed replies. Lockout feature temporarily bypasses unwanted channels. Big LCD display shows channels and frequencies being monitored or programmed as well as the status of the channels. Priority function monitors your favourite frequency while you listen to others. Frequency-tracking front end assures top sensitivity on all bands. Squelch control eliminates noise between messages. Has jacks for external antenna and earphones. With flexible antenna. 7 1/2 x 2 1/8 x 1 1/8". Requires six "AA" batteries or mains or DC adapter. Memory backup requires four silver-oxide batteries. **£229.95**  
Mains Adapter ..... **£6.99**  
DC Adapter ..... **£4.49**

### COLLINS KWM-380 Transceiver



**For the discerning...**  
One of the worlds greatest transceivers  
Listed in U.S.A. at over \$6000.00.  
Talk to us for the bargain of a lifetime, for the transceiver of a lifetime!

**TRS-80 COMPUTERS BY RADIO SHACK**  
DRAKE — TRIO — YAESU — ICOM — FDK — KDK —  
DATONG — HUSTLER — SHURE — ASTATIC — Hy-  
GAIN — TANDY — TELEX — MICROWAVE  
MODULES — HAL — DAVTREND — AVANTI and  
**EVERYTHING ELSE IN AMATEUR RADIO**



## RADIO SHACK LTD

(Just around the corner from West Hampstead Station on the Jubilee Line)  
Giro Account No. 588 7151 Telephone 01-624 7174 Telex: 23718

188 BROADHURST GARDENS,  
LONDON NW6 3AY

